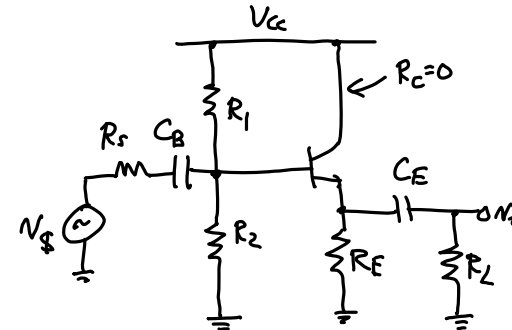


Lecture 29: Generally Loaded Transistor


- **Announcements:**
- HW#9 online and due Friday via Gradescope
- Extend Lab#5 due date by one week
 - ↳ Now due Tuesday, Nov. 6, 5 p.m.
- Midterm 2 coming up in about 2 weeks
 - ↳ Friday next week, Nov. 9, @ 5 p.m., in 277 Cory (just like last time)
 - ↳ More info this coming Friday
-
- **Lecture Topics:**
 - ↳ Other Amplifier Configurations
 - ↳ Generally-Loaded Transistor
-
- **Last Time:**
- Introduced inspection analysis and Miller effect
- Now provide the knowledge needed to properly inspect analyze general circuits



Other Popular Amplifier Configurations

- By merely altering the placements of input/output signals and bypass/coupling capacitors, one can realize other amplifier configurations
- Some examples:



↓ S.S. Ckt.

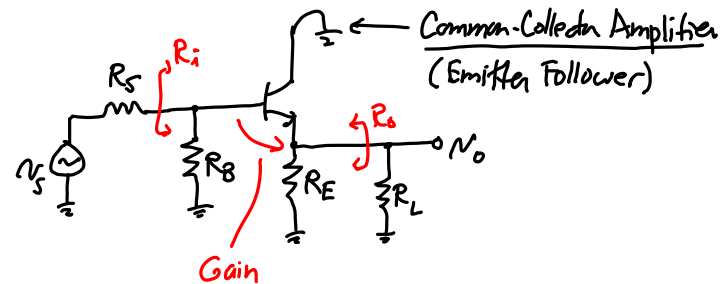

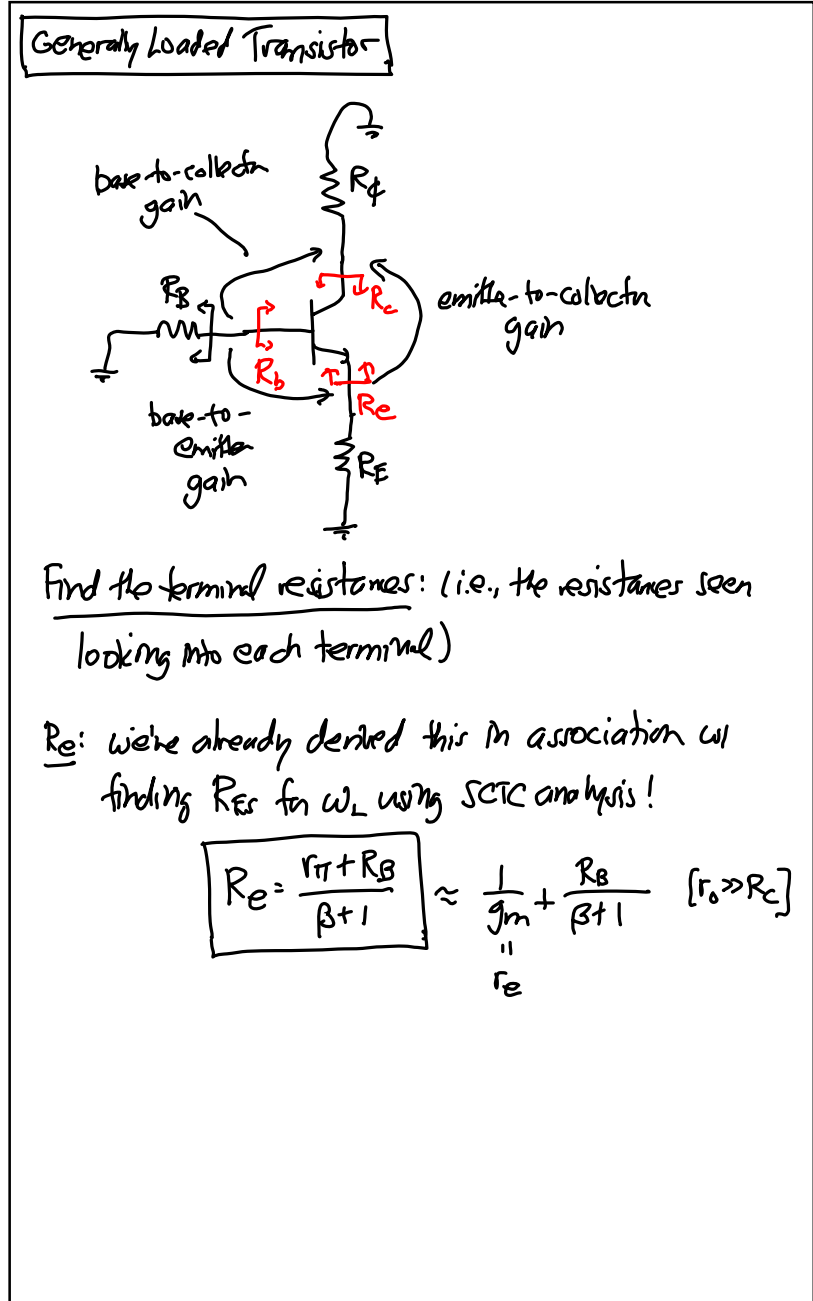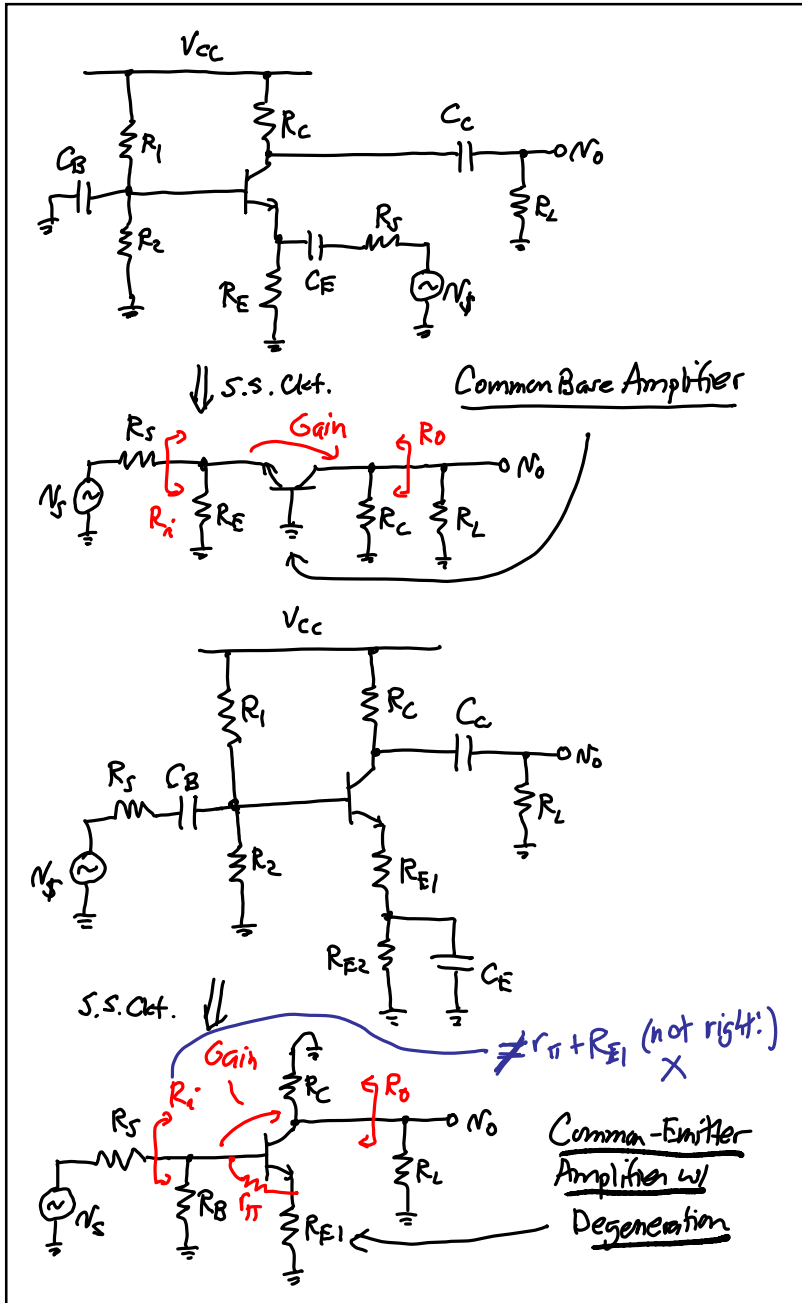

$R_b: i_x$

neglect $r_o = \text{large}$

KVL: $V_x = V_{be} + V_e$

$V_{be} = i_x r_{\pi}$

$V_e = (i_x + g_m V_{be}) R_E = i_x (1 + g_m r_{\pi}) R_E$

$V_x = i_x r_{\pi} + i_x (1 + g_m r_{\pi}) R_E$

$= i_x (r_{\pi} + (\beta + 1) R_E)$ *will be a big R !*

$R_b = \frac{V_x}{i_x} = r_{\pi} + (\beta + 1) R_E \approx r_{\pi} (1 + g_m R_E)$ *good for a $V \rightarrow V$ amplifier*

$[\beta = g_m r_{\pi} \gg 1]$

$V_x = i_x r_{\pi} + (\beta + 1) i_x R_E$

$R_b = \frac{V_x}{i_x} = r_{\pi} + (\beta + 1) R_E$

this comes about due to amplification of i_b

following the current

T-Model:

$V_x = (\beta + 1) i_x (r_e + R_E)$

$R_b = \frac{V_x}{i_x} = (\beta + 1) (r_e + R_E)$

$= (\beta + 1) (\frac{1}{g_m} + R_E)$

yet another form of the same thing...

Find R_c : (note that R_B can influence, so include in our analysis)

KVL: $V_x = r_o (i_x - g_m V_{be}) + V_e$

[Usually, for cases that matter, $R_E \ll R_B + r_{\pi}$]

\therefore most of i_x flows thru R_E :

for this class $\therefore v_e \approx i_x R_E$

$i_{\pi} = -\frac{v_e}{r_{\pi} R_B} = -\frac{i_x R_E}{r_{\pi} + R_B}$

$\therefore v_{be} = \frac{i_x r_{\pi} R_E}{r_{\pi} + R_B}$


* $\rightarrow v_x = i_x \left(1 + \frac{g_m r_{\pi} R_E}{r_{\pi} + R_B}\right) r_o + i_x R_E$

$\therefore R_x = \frac{v_x}{i_x} = r_o \left(1 + \frac{g_m R_E}{1 + (R_B/r_{\pi})}\right) + R_E$

$\therefore R_x \approx r_o \left(1 + \frac{g_m R_E}{1 + (R_B/r_{\pi})}\right) \approx r_o (1 + g_m R_E)$

[for $r_{\pi} \gg R_B$]

even bigger than r_o !

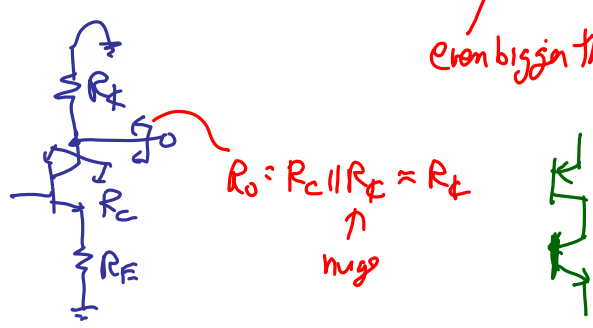

$R_o = R_C \parallel R_L \approx R_C$

↑
huge