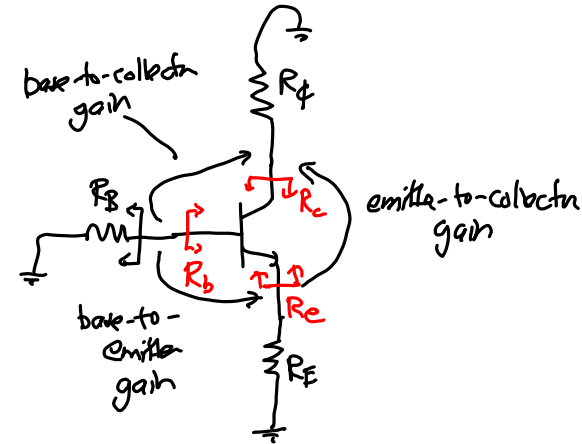


**Lecture 30: Transistor Terminal Gains**

- Announcements:
- HW#9 online and due Friday via Gradescope
- Lab#5 due Tuesday, Nov. 6, 5 p.m.
  - ↳ If you are using excel or matlab to compute equations for Lab#5 → you will regret doing this when taking midterm 2
  - ↳ You need to design by hand at least 3 times before going to a computer
  - ↳ This is the only way to get familiar with the process
  - ↳ You cannot see the trade-offs without analyzing by hand
  - ↳ You need to put the work in to be able to recognize things
- Midterm coming up
  - ↳ Friday next week, Nov. 9, @ 5 p.m., in 277 Cory (just like last time)
  - ↳ More info this coming Friday
- 
- Lecture Topics:
  - ↳ **Generally-Loaded Transistor**
    - Terminal Resistances
    - Terminal-to-Terminal Gains
    - Inspection Analysis Sheet
    - Examples
- 
- Last Time:
- Derived inspection analysis terminal resistances
- Now proceed to terminal-to-terminal gains

**Generally Loaded Transistor**



Find the terminal resistances: (i.e., the resistances seen looking into each terminal)

$R_e$ : we've already derived this in association w/ finding  $R_{in}$  for  $w_L$  using SDC analysis!

$$R_e = \frac{r_{\pi} + R_B}{\beta + 1} \approx \frac{1}{g_m} + \frac{R_B}{\beta + 1} \quad [r_o \gg R_C]$$

||  
re

$R_b: i_x$

*neglect  $r_o = \text{large}$*

KVL:  $v_x = v_{be} + v_e$

$v_{be} = i_x r_{\pi}$

$v_e = (i_x + g_m v_{be}) R_E = i_x (1 + g_m r_{\pi}) R_E$

$v_x = i_x r_{\pi} + i_x (1 + g_m r_{\pi}) R_E$

$= i_x (r_{\pi} + (\beta + 1) R_E)$  *will be a big  $R$ !*

$R_b = \frac{v_x}{i_x} = r_{\pi} + (\beta + 1) R_E \approx r_{\pi} (1 + g_m R_E)$  *good for a  $V \rightarrow V$  amplifier*

$[\beta = g_m r_{\pi} \gg 1]$

$v_x = i_x r_{\pi} + (\beta + 1) i_x R_E$

$R_b = \frac{v_x}{i_x} = r_{\pi} + (\beta + 1) R_E$

*this comes about due to amplification of  $i_b$*

*following the currents*

T-Model:

$v_x = (\beta + 1) i_x (r_e + R_E)$

$R_b = \frac{v_x}{i_x} = (\beta + 1) (r_e + R_E) = (\beta + 1) (\frac{1}{g_m} + R_E)$

*yet another form of the same thing...*

Find  $R_c$ : (note that  $R_B$  can influence, so include in our analysis)

KVL:  $v_x = r_o (i_x - g_m v_{be}) + v_e$

[Usually, for cases that matter,  $R_E \ll R_B + r_{\pi}$ ]

$\therefore$  most of  $i_x$  flows thru  $R_E$ :

for this case  $\therefore V_e \approx i_x R_E$

$i_{\pi} = -\frac{V_e}{r_{\pi} R_B} = -\frac{i_x R_E}{r_{\pi} + R_B}$

$\therefore N_{be} = \frac{i_x r_{\pi} R_E}{r_{\pi} + R_B}$

\*  $N_x = i_x \left(1 + \frac{g_m r_{\pi} R_E}{r_{\pi} + R_B}\right) r_o + i_x R_E$

$\therefore R_x = \frac{N_x}{i_x} = r_o \left(1 + \frac{g_m R_E}{1 + (R_B/r_{\pi})}\right) + R_E$

$\therefore R_x \approx r_o \left(1 + \frac{g_m R_E}{1 + (R_B/r_{\pi})}\right) \approx r_o (1 + g_m R_E)$

[for  $r_{\pi} \gg R_B$ ]

even bigger than  $r_o$ !

$R_o = R_C || R_E = R_x$   
↑  
huge


- Remarks:
- $R_c \sim (1 + (0.04)(1k))(100k\Omega) \sim 4.1M\Omega$  (this is huge)
- Rarely use  $R_c$  in discrete circuits, since it is generally much larger than  $R_c$
- In integrated circuits, however, the loading can be very large, especially if it comes from another transistor
- For example:

Base-to-Collector Gain


$R_o = r_o \left(1 + \frac{g_m R_E}{1 + \frac{R_B}{r_{\pi}}}\right) || R_C \approx R_C$

$\frac{v_c}{v_b} = -g_m R_o$   
 $= -\left(\frac{g_m}{1 + g_m R_E}\right) (R_C || R_E)$

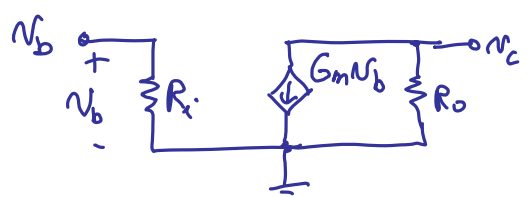Convert to an 'equivalent circuit' y-parameter model



All we need is  $G_m \triangleq$  short-circuit transconductance
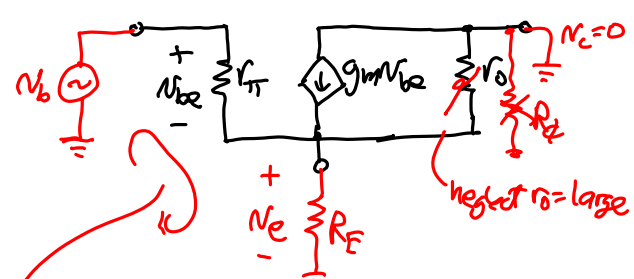
$$G_m = \frac{i_c}{v_b} \Big|_{v_c=0}$$


neglect  $r_o = \text{large}$

$$v_{be} = \left( \frac{v_b}{r_{\pi}} + g_m v_{be} \right) R_E = v_b \left( \frac{1}{r_{\pi}} + g_m \right) R_E$$

$$v_b = v_{be} + v_{RE} = v_{be} \left( 1 + \left( \frac{1}{r_{\pi}} + g_m \right) R_E \right)$$

$i_c = g_m v_{be}$


$$G_m = \frac{i_c}{v_b} \Big|_{v_c=0} = \frac{g_m v_{be}}{v_b \left( 1 + \left( \frac{1}{r_{\pi}} + g_m \right) R_E \right)} = \frac{g_m}{1 + g_m R_E} = G_{gm}$$

$\frac{1}{r_{\pi}} \ll g_m$

Gain =  $\frac{v_c}{v_b} = -G_m R_o$

$$G_m = \frac{g_m}{1 + g_m R_E} = \frac{g_m}{1 + \frac{R_E}{r_e}}$$

Base-to-Emitter Gain

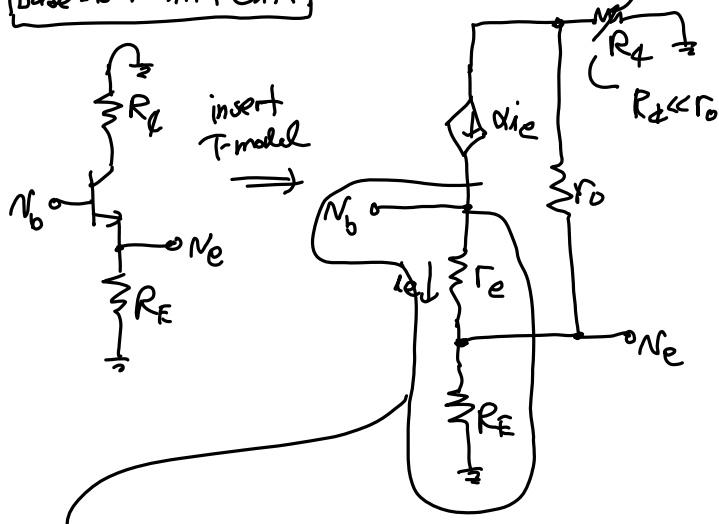

insert T-model

Voltage Divider!  $[r_o \gg R_E]$

$$\frac{v_{be}}{v_b} \approx \frac{R_E \parallel r_o}{r_e + R_E \parallel r_o} \approx \frac{R_E}{r_e + R_E} = \frac{g_m R_E}{1 + g_m R_E} \approx 1$$

$\frac{\alpha}{g_m} \approx \frac{1}{g_m} \approx 25 \Omega$   
 $\uparrow$   
 $I_C = 1 \text{mA}$

**Emitter-to-Collector Gain**

$R_o = R_C \parallel r_o \left(1 + \frac{g_m R_E}{1 + \frac{R_E}{r_o}}\right)$

$R_i = \frac{r_{\pi} + R_B}{\beta + 1}$

Again, all we need is  $G_m = \frac{i_c}{V_{be}} \Big|_{V_{ce}=0} \triangleq$  short-ckt transconductance

$V_{be} = -\frac{V_e r_{\pi}}{r_{\pi} + R_B}$

$\therefore i_c = g_m V_{be} = -\frac{g_m r_{\pi}}{r_{\pi} + R_B} V_e$

$G_m = \frac{i_c}{V_e} \Big|_{V_{ce}=0} = -g_m \left(\frac{r_{\pi}}{r_{\pi} + R_B}\right)$  if  $R_B = 0$ ,  $G_m = -g_m$

Thus,  $\frac{V_c}{V_e} = -G_m R_o \underset{\text{for the initial det}}{\approx} g_m \left(\frac{r_{\pi}}{r_{\pi} + R_B}\right) R_C = g_m R_C$

- Now go through the Inspection Analysis Handout