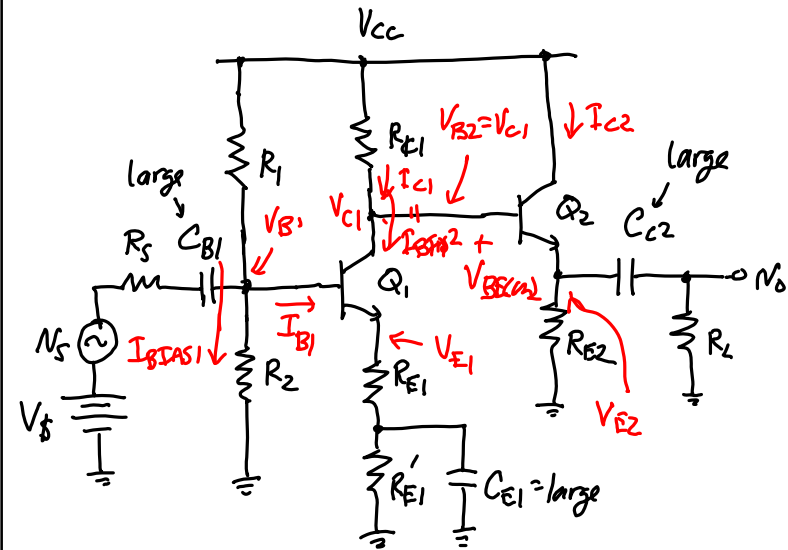


Lecture 32: Multi-Transistor High Frequency

- Announcements:
- HW#10 online soon and due Friday Nov. 16 via Gradescope
- Lab#5 due Tuesday, Nov. 6, 5 p.m.
- Midterm coming up
 - ↳ Friday this week, Nov. 9, @ 5 p.m., in 277 Cory (just like last time)
 - ↳ Midterm Info Sheet online
-
- Lecture Topics:
 - ↳ Multi-Transistor Example (Inspection Analysis)
 - Input/Output Resistances
 - Gain
 - High Frequency
 - ↳ MOS Inspection Analysis
-
- Last Time:
- Got the gain of the amplifier
- Now, get the high frequency cut-off

Example. Multi-Transistor Amplifier Inspection Analysis

(C.E. w/ Degeneration, C.C. Cascade)



Find R_i , R_o , $a_w = \frac{V_o}{V_s}$, and f_H .

First, find the DC operating pt:

Good Design: $I_{B1AS1} > 10I_{B1}$

$$V_{B1} = \frac{R_2}{R_1 + R_2} V_{CC} \rightarrow V_{E1} = V_{B1} - \underbrace{V_{BE(ON)}}_{0.7V}$$

$$I_{Q1} \approx I_{E1} = \frac{V_{E1}}{R_{E1} + R_{E1}'} = \frac{V_{B1} - V_{BE(ON)}}{R_{E1} + R_{E1}'}$$

$$V_{Q1} = V_{CC} - I_{Q1} R_{C1} = V_{B2} \rightarrow V_{E2} = V_{B2} - V_{BE(ON)}$$

$$I_{E2} = I_{E1} = \frac{V_{E2}}{R_{E2}}$$


Remarks.

- ① Look for the V_{BE} (or V_{CE})'s. \rightarrow well-defined voltages.
- ② Currents usually be determined by $\frac{V_E}{R_E}$'s.

For Bias Stability:

$$I_{B1} > 10 I_{B2} \quad \text{also} \quad I_{E1} = I_{B2} \approx 10 I_{B2}$$

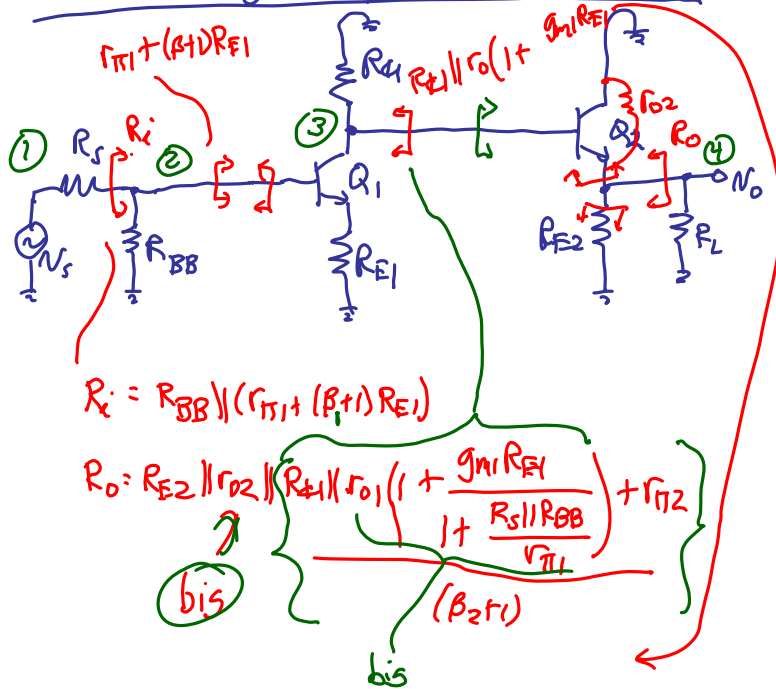Midband Small-Signal Analysis for G_m , R_i , and R_o :



$$R_o = R_{E2} \parallel \left(\frac{r_{\pi 2} + R_{C1}}{\beta + 1} \right)$$

Get gain $\frac{V_o}{V_s}$: (gain from ① to ④)

$$\frac{V_{\text{④}}}{V_{\text{①}}} = \frac{V_{\text{④}}}{V_s} = \frac{R_i}{R_s + R_i} = \frac{R_{BB} \parallel (r_{\pi 1} + (\beta + 1) R_{E1})}{R_s + R_{BB} \parallel (r_{\pi 1} + (\beta + 1) R_{E1})}$$

(voltage divider)

$$\frac{V_{\text{③}}}{V_{\text{②}}} = -G_{m1} R_{\text{③}}$$

$$= - \frac{g_{m1}}{1 + g_{m1} R_{E1}} \left\{ R_{C1} \parallel r_{o1} \left(1 + \frac{g_{m1} R_{E1}}{1 + \frac{R_{S1} \parallel R_{BB}}{r_{\pi 1}}} \right) \right\}$$

large

$$\left[r_{\pi 2} + (\beta + 1) (R_{E2} \parallel R_L \parallel r_{o2}) \right]$$

large

$$\frac{V_{\text{③}}}{V_{\text{②}}} = - \frac{g_{m1} R_{C1}}{1 + g_{m1} R_{E1}}$$

$$\frac{V_{\text{④}}}{V_{\text{③}}} = \frac{R_{E2} \parallel R_L \parallel r_{o2}}{r_{e2} + R_{E2} \parallel R_L \parallel r_{o2}} \approx 1$$

\uparrow
 $\frac{1}{g_{m2}}$

$$\therefore \frac{V_0}{V_S} = \frac{V_2}{V_1} \cdot \frac{V_3}{V_2} \cdot \frac{V_4}{V_3} = \frac{V_4}{V_1}$$

$$= - \frac{R_{FB} \parallel (r_{\pi} + (\beta_1 + 1) R_{E1})}{R_S + R_{FB} \parallel (r_{\pi} + (\beta_1 + 1) R_{E1})} \frac{g_{m1} R_{L1}}{1 + g_{m1} R_{E1}} = \frac{V_0}{V_S}$$


Procedure for Midband Gain Inspection Analysis:



- Identify and label all signal path nodes
- Get stage gain from node to node
 - ↪ For each stage, be sure to account for loading by the next stage, specifically load resistance to ground
 - ↪ For transistor terminal-to-terminal gains, will likely need to determine output node resistance to ground
 - including loading by the next stage, and
 - even the influence of loading by the previous stage, e.g., when determining R_c
- Take the product of all node-to-node gains to get the total gain
- Can do all of this by inspection if
 - ↪ There is no feedback
 - ↪ You know all the terminal-to-terminal gain equations or can "see" or "derive" them quickly
 - ↪ You know all the equations for resistances looking into the transistor terminals (to ground) or can "see" or "derive" them quickly
 - ↪ "see" or "derive" quickly can often be done by following the currents

Procedure for High Frequency Inspection Analysis:


- Identify and label all signal path nodes
- Draw in the small transistor capacitors
- Use the Miller transform to turn the base-to-collector or gate-to-drain capacitor into shunt capacitors to ground
- For the base-to-emitter or gate-to-source capacitor you will need to know the equation for driving point resistance, i.e., resistance in parallel
- Get the time constant for each node by
 - ↪ Determining the total capacitance C_{node} from that node to ground
 - ↪ Determining the total resistance R_{node} from that node to ground
 - ↪ Time constant = $R_{node} * C_{node}$
- Handle each feedback capacitor separately using knowledge of its driving point R equation (or derive the equation from scratch using the hybrid- π model)
- Add up all the time constants and take the reciprocal to get the ω_H

High Freq. Analysis

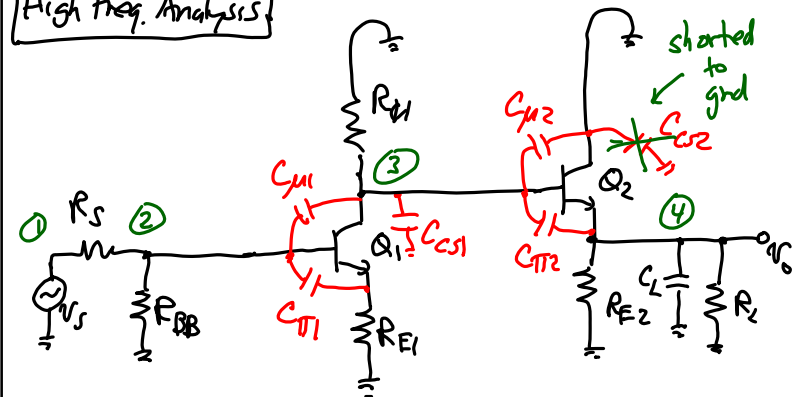


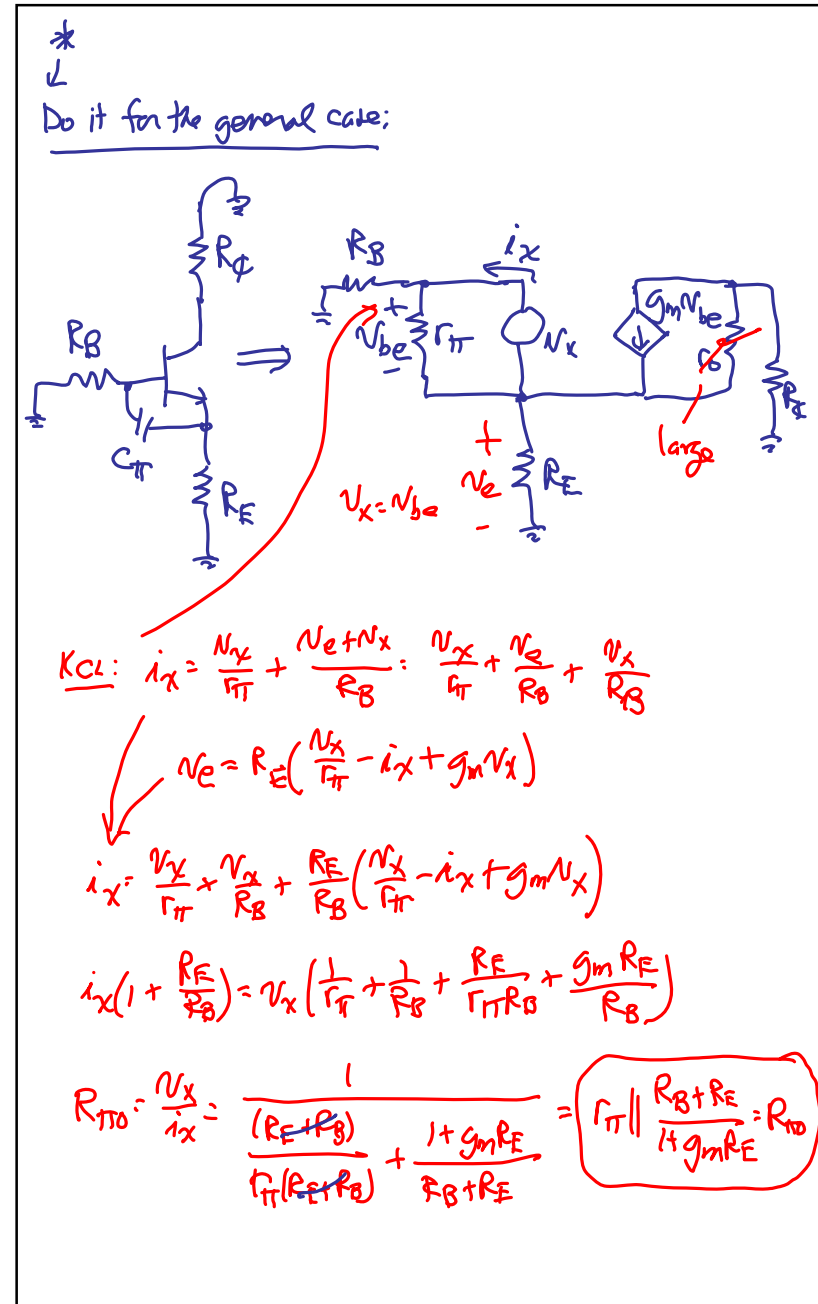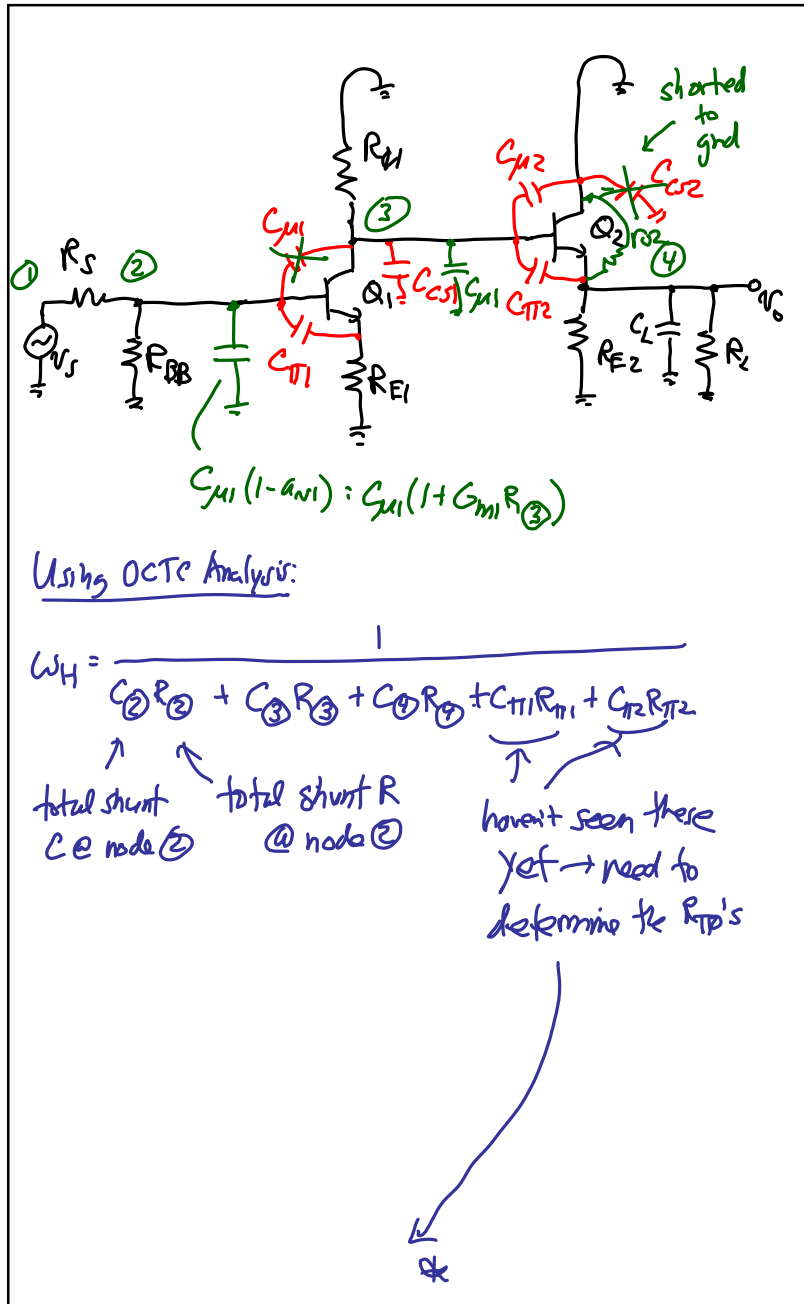

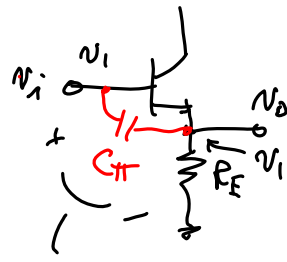$R_{TD} = r_{\pi} \parallel \frac{R_B R_E}{1 + g_m R_E}$
 $R_E = \text{large}$
 $r_{\pi} \parallel \frac{1}{g_m} = \text{small} \rightarrow \text{effortless can be neglected}$



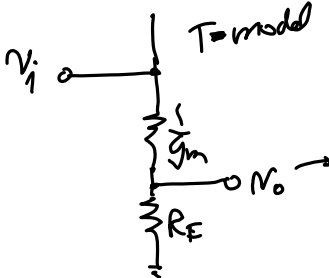$\frac{v_o}{v_i} \approx \frac{R_E \cdot 1k\Omega}{\frac{1}{g_m} + R_E} \approx 1$
 25Ω
 $v_i - v_i = 0 \rightarrow C_{\pi}$ is effective, not floo!



$\frac{v_o}{v_i} = \frac{R_E}{\frac{1}{g_m} + R_E}$

Now, get the τ 's to get ω_H :

$C_{C1} = C_{\pi 1} (1 + G_{m1} R_{C1})$
 $= C_{\pi 1} \left(1 + \frac{g_{m1}}{1 + g_{m1} R_E} \left\{ R_{C1} \parallel r_{o1} \left(1 + \frac{g_{m1} R_{E1}}{1 + \frac{R_{C1} R_E}{r_{\pi}}} \right) \parallel (r_{\pi 2} + (\beta_2 + 1) R_{E2} \parallel R_L \parallel R_{C2}) \right\} \right)$
 $= C_{\pi 1} \left(1 + \frac{g_{m1} R_{C1}}{1 + g_{m1} R_E} \right)$

$R_{C2} = R_S \parallel R_{B2} \parallel (r_{\pi 2} + (\beta_2 + 1) R_{E2}) \approx R_S \parallel R_{B2} \approx R_S$
 \downarrow
 $\tau_{C2} = C_{\mu 1} \left(1 + \frac{g_{m1} R_{C1}}{1 + g_{m1} R_E} \right) R_S$

$C_{C3} = C_{C1} + C_{\mu 1} + C_{\mu 2}$
 $R_{C3} = R_{C1} \parallel r_{o1} \left(1 + \frac{g_{m1} R_{E1}}{1 + \frac{R_{C1} R_E}{r_{\pi}}} \right) \parallel (r_{\pi 2} + (\beta_2 + 1) R_{E2} \parallel R_L \parallel R_{C2})$
 $\approx R_{C1}$
 $\tau_{C3} = (C_{C1} + C_{\mu 1} + C_{\mu 2}) R_{C1}$

$C_{C4} = C_L$
 $R_{C4} = R_{E2} \parallel R_L \parallel r_{o2} \parallel \frac{r_{\pi 2} + R_{C1} \parallel r_{o1} \left(1 + \frac{g_{m1} R_{E1}}{1 + \frac{R_{C1} R_E}{r_{\pi}}} \right)}{\beta_2 + 1}$
 $\approx R_{E2} \parallel R_L \parallel \left(\frac{r_{\pi 2} + R_{C1}}{\beta_2 + 1} \right)$
 $\tau_{C4} = C_L (R_{E2} \parallel R_L \parallel \frac{r_{\pi 2} + R_{C1}}{\beta_2 + 1})$