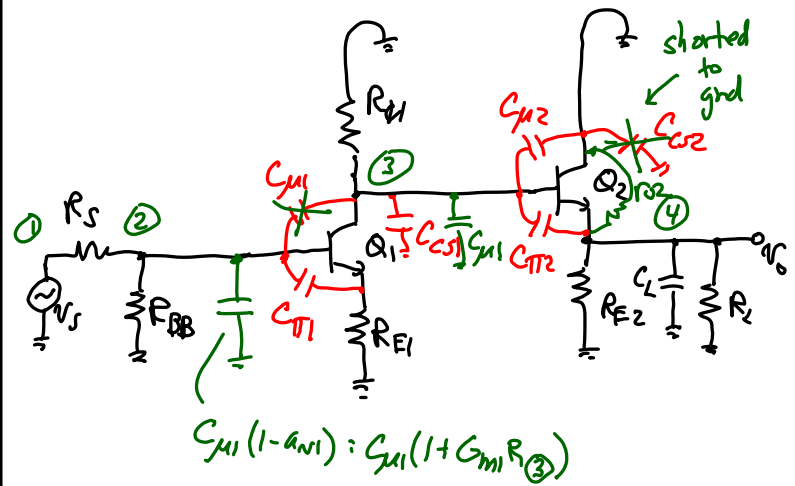


**Lecture 33: MOS Inspection Analysis**

- **Announcements:**
- HW#10 online and due Friday Nov. 16
- Midterm Friday this week, Nov. 9, @ 5 p.m., in 277 Cory (just like last time)
  - ↳ We will have 2 hours for this exam
  - ↳ Midterm Info Sheet online
- Lab 6 online and due 5 p.m., Friday, Dec. 7
- 
- **Lecture Topics:**
  - ↳ Multi-Transistor Example (Inspection Analysis)
    - Input/Output Resistances
    - Gain
    - High Frequency
  - ↳ MOS Inspection Analysis
- 
- **Last Time:**
- Practically finished high frequency cut-off
- Finish it off, then move to MOS inspection analysis



Using OCTC Analysis:

$$\omega_H = \frac{1}{C_2 R_2 + C_3 R_3 + C_4 R_4 + C_{T1} R_{T1} + C_{T2} R_{T2}}$$

Annotations:
 


- ↑ total shunt C @ node 2
- ↑ total shunt R @ node 2
- C<sub>T</sub>'s in FB ∴ determined their driving pts R<sub>no</sub>'s via hybrid-π model

Incorporating Results f/ Last Time

$$\omega_H = \frac{1}{\left\{ C_{M1} \left( 1 + \frac{g_{m1} R_C}{1 + g_{m1} R_{E1}} \right) (R_S || R_B) + (C_{C1} + C_{M1} + C_{M2}) R_{C1} \right.}$$


$$\left. + C_L (R_{E2} || R_L || \frac{r_{\pi 2} + R_{E1}}{\beta_2 + 1}) + C_{T1} \left( r_{\pi 1} || \left( \frac{R_B || R_S + R_{E1}}{1 + g_{m1} R_{E1}} \right) \right) \right\}}$$

$$+ C_{T2} \left( r_{\pi 2} || \left( \frac{R_C + R_{E2}}{1 + g_{m2} R_{E2}} \right) \right)$$

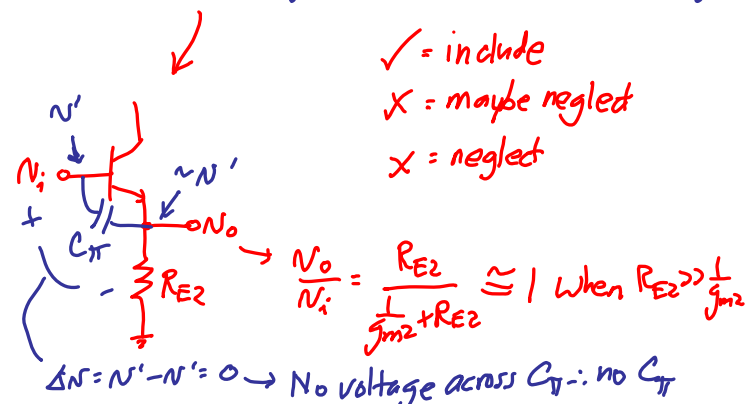

MOS Xinput Ckfr.

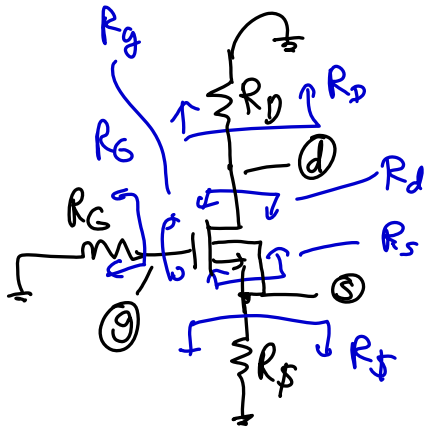⇒ for now, ignore Body effect (i.e., ignore  $g_{mb}$ )  
 ↪ use the same inspection formulas as bipolar,  
 but use  $\beta \rightarrow \infty$ ,  $r_{\pi} = \frac{\beta}{g_m} \rightarrow \infty$



⇒ referring to the bipolar "Inspection Formula Sheet?"

Bipolar		MOS
$R_b = (\frac{1}{g_m} + R_E)(\beta + 1)$	$\xrightarrow{\beta \rightarrow \infty}$	$R_g = \infty$
$R_e = \frac{1}{g_m} + \frac{R_b}{\beta + 1}$	$\xrightarrow{\beta \rightarrow \infty}$	$R_s = \frac{1}{g_m}$
$R_c = r_o \left[ 1 + \frac{g_m R_E}{1 + R_b / r_{\pi}} \right]$	$\xrightarrow{\beta \rightarrow \infty}$	$R_d = r_o (1 + g_m R_S)$


$$\frac{v_o}{v_g} = -G_m R_D, \quad G_m = \frac{g_m}{1 + g_m R_S}$$

$$\frac{v_o}{v_s} = -G_m R_D, \quad G_m = g_m$$

$$\frac{v_o}{v_g} = \frac{g_m R_S}{1 + g_m R_S} = \frac{R_S}{\frac{1}{g_m} + R_S}$$

MOS Inspection Analysis

Ex. Common-Source Common-Drain Cascade

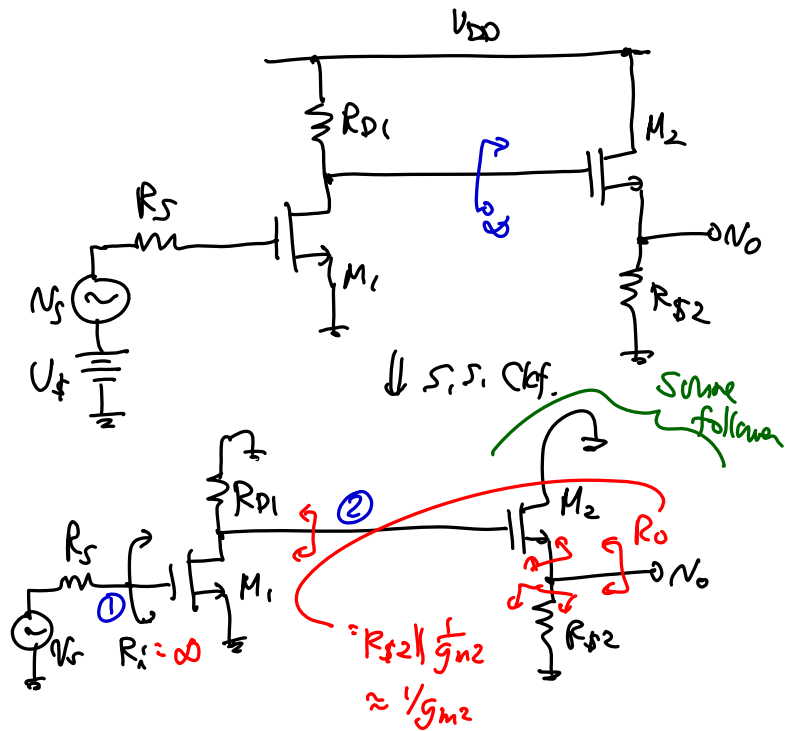

$$\frac{V_o}{V_s} = \frac{V_o}{V_s} \cdot \frac{V_o}{V_o} \cdot \frac{V_o}{V_o}$$

$$= (1)(-g_m R_{D1}) \left( \frac{R_{S2}}{\frac{1}{g_{m2}} + R_{S2}} \right) = \frac{V_o}{V_s}$$

Problem: Simulate via SPICE → the gain will be 80-90% of what is calculated using the problem is w/  $g_{mb}$  in the source follower

↑ This is the difference between bipolar & MOS hybrid- $\pi$  models!

Source Follower: (w/ substrate grounded)

$V_{GS} = V_i - N_o$   
 $V_{BS} = -N_o$

$$g_m(V_i - N_o) = N_o(g_{ds} + G_S + g_{mb})$$

$$\Rightarrow A_v = \frac{V_o}{V_i} = \frac{g_m}{g_m + g_{mb} + g_{ds} + G_S}$$

$\left[ \begin{array}{l} R_S \rightarrow \infty \rightarrow G_S = 0 \\ g_{ds} \ll g_m + g_{mb} \end{array} \right]$  Body factor

$$A_v \approx \frac{g_m}{g_m + g_{mb}} = \frac{1}{1 + \eta}, \quad \eta = \frac{\gamma}{2\sqrt{V_{SB} + 2\phi_f}}$$

$\neq 1$

To make it '1', do this:

**Effect of  $g_{mb}$  on Impedance**

$$\left[ \begin{matrix} V_{gs} = -V_x = V_{bs} \\ V_{ds} = -V_x \end{matrix} \right]$$

$$R_s = \frac{1}{g_m + g_{mb} + g_{ds}} = \frac{1}{g_m} \parallel \frac{1}{g_{mb}} \parallel R_o$$

$$R_s \approx \frac{1}{g_m + g_{mb}}$$

$\Rightarrow$  more extensive analysis shows that other inspection formulas change to accommodate a grounded body by replacing "gm" in the numerators w/ "gm+gmb"

$\Rightarrow$  end up w/ the following:  $\curvearrowright$  over

**Mos Inspection Formulas w/ Substrate Grounded**

$\hookrightarrow$  only difference from "substrate tied to source" case is that gm is replaced by gm+gmb in some of the formulas particularly over where the source is involved!

$R_g = \infty$   
 $R_s = \frac{1}{g_m + g_{mb}}$   
 $R_d = r_o [1 + (g_m + g_{mb}) R_b]$   
 $\frac{V_d}{V_g} = -G_m R_d$ ,  $G_m = \frac{g_m}{1 + (g_m + g_{mb}) R_b}$   
 $\frac{V_d}{V_s} = -G_m R_d$ ,  $G_m = -(g_m + g_{mb})$   
 $\frac{V_s}{V_g} = \frac{g_m R_b}{1 + (g_m + g_{mb}) R_b}$

Remark: When the substrate is tied to the source,  $g_{mb} = 0$ .

MOS High Frequency Inspection Analysis

$C_u = C_{gd1}(1 + g_{m1}R_{D1})$   
 $\tau_1 = [C_{gs1} + C_{gd1}(1 + g_{m1}R_{D1})] R_S$   
 $\tau_2 = [C_{gd1} + C_{db1} + C_{gs2}] (R_{D1} || R_{D2})$   
 $\tau_3 = C_{sb2} \left( \frac{1}{g_{m2} + g_{mb2}} || R_{S2} \right)$   
 ~~$\tau_{gs2} = C_{gs2} \left( \frac{R_{D1} + R_{S2}}{1 + (g_{m2} + g_{mb2})R_{S2}} \right)$~~

*because no signal across  $C_{gs2}$  w/ 2nd stage gain  $\approx 1$*

$\omega_H = \frac{1}{\tau_1 + \tau_2 + \tau_3 + \tau_{gs2}}$

*$N_x \approx 0$*