

EE 105: Microelectronic Devices & Circuits

Lecture 38w: Propagation Delay

Lecture 38: Propagation Delay I

- Announcements:
- HW#11 online and due during RRR week
- Lab 6 online and due 5 p.m., Friday, Dec. 7
- We're finally back from the smoke
- Z-scores at end of lecture today
- **If fixed a couple of things in this**
 - ↳ First, the fact that C_{db} goes from the drain to V_{DD} for the PMOS in an inverter
 - ↳ Second, the t_p equation, where $t_p = t_{p1} = t_{p2} = t_{p3}$, for the ring oscillator

Lecture Topics: (over the next few days)

Static CMOS Inverter Behavior

- V_{OL} and V_{OH}
- V_{IL} and V_{IH}

Dynamic CMOS Inverter Behavior

- Propagation Delay
- Capacitance

Astable Ring Oscillator



CMOS Inverter Propagation Delay

Last Time:

- Ended up defining propagation delay

Dynamic Behavior of the CMOS Inverter

Propagation Delay -

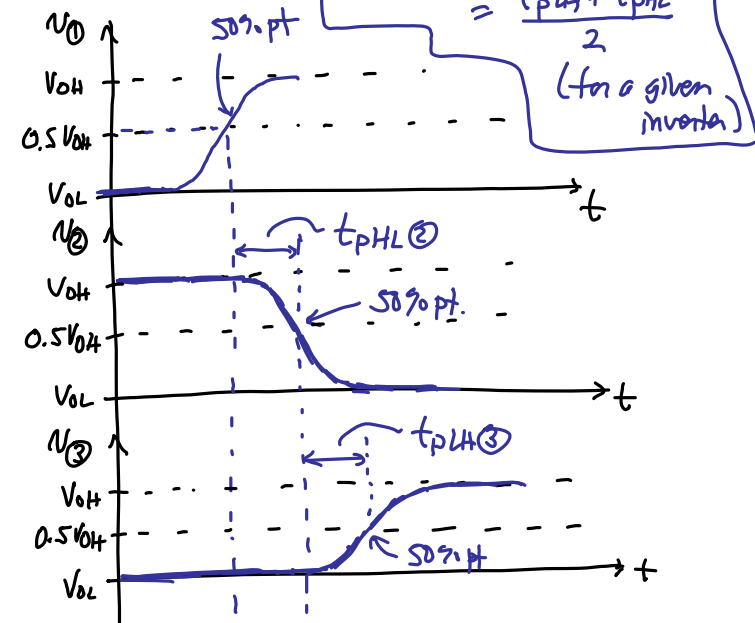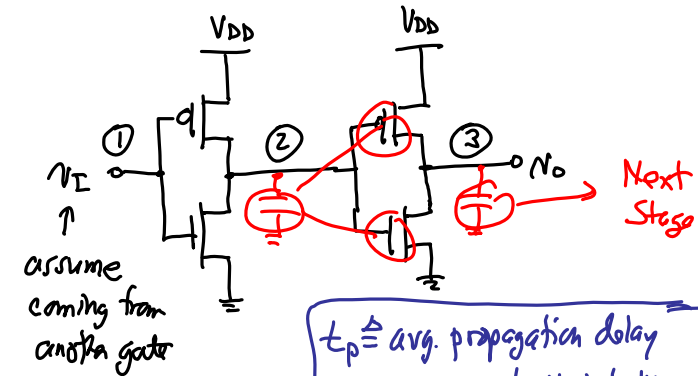


$t_{pHL(2)} + t_{pHL(3)}$ gives a value for the delay across this two-stage inverter chain

EE 105: Microelectronic Devices & Circuits
Lecture 38w: Propagation Delay


- **Remarks**
- Propagation delay is the delay experienced by a signal passing through a gate as measured between the 50% transition points between input and output waveforms
- In general, a gate displays different response times for rising and falling input waveforms
- Thus, define:
 - ↳ t_{pLH} : response time of a gate making a low \rightarrow high output transition
 - ↳ t_{pHL} : response time of a gate making a high \rightarrow low output transition
- Propagation delay then defined as the average of t_{pLH} and t_{pHL}
- What causes switching delay?
 - ↳ Finite current transistor current drive (i.e., finite on resistance R_{on})
 - ↳ Output node capacitance

Capacitance
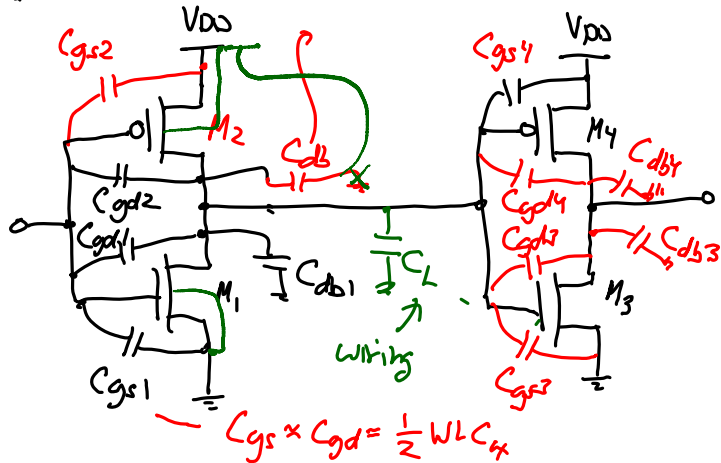
$$C_{db} = \frac{C_{db0}}{\sqrt{f(V_{DD})}} = \frac{C_{db0}}{(H \frac{V_{DD}}{\phi_J})^m}$$



Actual CMOS (old) (an inventor)

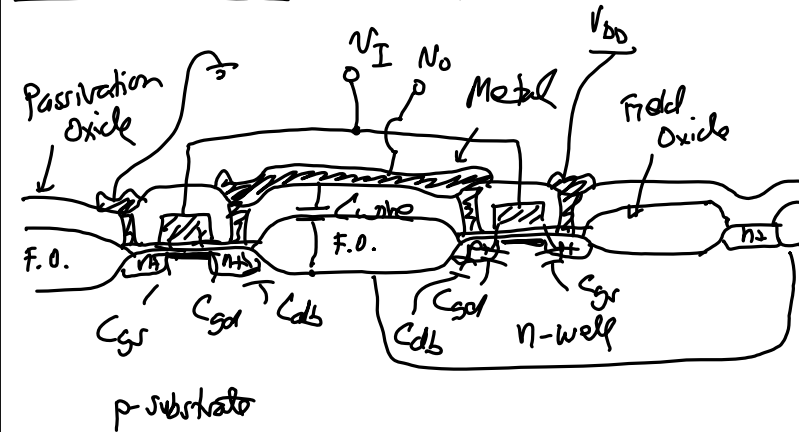

\Rightarrow take EE143 to learn MORE!!!

Astable Ring Oscillator

\Rightarrow what is an oscillator? \rightarrow a device that puts out a stable frequency!

