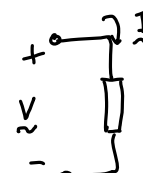


Lecture 3: Frequency Response

- Announcements:
- HW#1 online and due this Friday
- Discussions this week
- Labs start next week
 - ↳ Monday, Sept. 3 is a holiday, so the Monday lab will start one week later
 - ↳ The Tuesday lab starts Sept. 4
- Lab#1 will be online soon after lecture today
- Will let in concurrent enrollments end of this week
- -----
- Lecture Topics:
 - ↳ Finish Digital Communications Example
 - ↳ Review Impedance
 - ↳ Frequency Response
 - ↳ Bode Plots
- -----
- Last Time:
- Going through an example digital communication transmitter as motivation
- Now, continue with this ...

- Review of Analog Circuit Concepts:
- We assume you understand the following concepts from previous courses:
 - ↳ Transfer functions
 - ↳ Gain (voltage, current, power)
 - ↳ Input resistance
 - ↳ Output resistance
 - ↳ Two-port models for amplifiers
 - ↳ Bode plots
 - ↳ Ideal op am ckt design and analysis
- We'll review some of these now to jog your memory

Review of Impedance


 where \tilde{v} and \tilde{i} are phasor variables:

$$v(t) = V' \cos(\omega t + \phi) \iff \tilde{v} = V' e^{j\phi}$$

$$V'(\cos\phi + j\sin\phi)$$

$$i(t) = I' \cos(\omega t + \phi) \iff \tilde{i} = I' e^{j\phi}$$

and Impedance:
$$z = \frac{\tilde{v}}{\tilde{i}}$$

Resistor - $R = \frac{v(t)}{i(t)}$ $\xleftrightarrow{\text{phasor}}$ $R = \frac{\tilde{v}}{\tilde{i}}$

Capacitor - $i(t) = C \frac{dv}{dt} \iff \tilde{i} = C j\omega \tilde{v}$

$$\tilde{v} = z \tilde{i} \implies \frac{\tilde{v}}{\tilde{i}} = z = \frac{1}{j\omega C}$$
 (substitute $s = j\omega$)

Inductor $v = L \frac{di}{dt} \iff \underline{v} = L j\omega \underline{i}$
 $\frac{\underline{v}}{\underline{i}} = j\omega L = sL$

Example. Determine a transfer function

Recognize a voltage divider:
 $Z_1 = R$
 $Z_2 = \frac{1}{sC}$
 $\therefore N_o = \frac{Z_2}{Z_1 + Z_2} N_i \Rightarrow \frac{N_o}{N_i}(s) = \frac{1}{R + \frac{1}{sC}}$

$\frac{N_o}{N_i}(s) = \frac{1}{1 + sRC} = \frac{1}{1 + s\tau_p} = \frac{1}{1 + \frac{s}{\omega_p}}$
 $[\tau_p = RC] \quad [\omega_p = \frac{1}{RC}]$


- Frequency Response:
- To measure the frequency response of a given network:
 - ↪ Excite the network with a variable-frequency, sinusoidal, constant amplitude source
 - ↪ Measure the magnitude and phase of the output signal for different values of input frequency

Where
 $|N_o(j\omega)| = V_o = \text{magnitude}$
 $\angle N_o(j\omega) = \phi = \text{phase}$

- The frequency response of a given network is commonly described by a plot of magnitude and phase versus frequency. Usually, such a plot is of the transfer function of a given network:

$H(j\omega) = \frac{N_o(j\omega)}{N_i(j\omega)}$

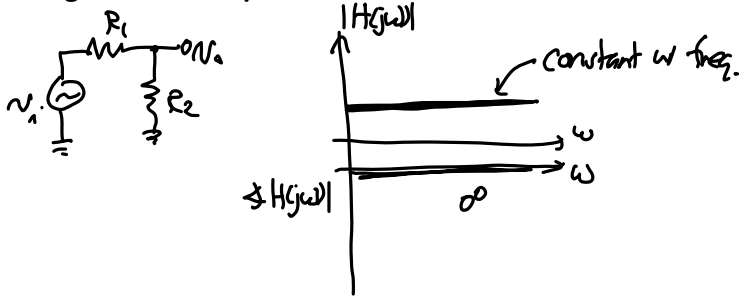- For a purely resistive network, the frequency response is constant (i.e., a straight line), both magnitude and phase



- The addition of reactive (energy storage) components, e.g., capacitors, inductors
 - Shapes the frequency response
 - Adds singularities, i.e., poles and zeros
 - Yields the general transfer function:

$$H(s) = \frac{V_o(s)}{V_i(s)} = H_0 \frac{(s-z_1)(s-z_2)\dots(s-z_m)}{(s-p_1)(s-p_2)\dots(s-p_n)} = H_0 \frac{\prod_{j=1}^m (s-z_j)}{\prod_{i=1}^n (s-p_i)}$$

resistive term

where

$$z_j = \sigma_{zj} + j\omega_{zj}; \quad \sigma_{zj} = \text{Re}(z_j), \quad \omega_{zj} = \text{Im}(z_j)$$

$$p_i = \sigma_{pi} + j\omega_{pi}; \quad \sigma_{pi} = \text{Re}(p_i), \quad \omega_{pi} = \text{Im}(p_i)$$

$V_i(s)$ ≡ input variable (not necessarily a voltage)

V - variable (" " ")

⇒ given this, you should be able to plot the Bode plot!

Bode Plot

- Plot magnitude in decibels (dB) vs. log (freq.)

$$[H(s) = H(j\omega)] \Rightarrow |H(j\omega)| = H_0 \frac{\prod_{j=1}^m |j\omega - z_j|}{\prod_{i=1}^n |j\omega - p_i|}$$

$$\Rightarrow = H_0 \frac{\prod_{j=1}^m |j(\omega - \omega_{zj}) - \sigma_{zj}|}{\prod_{i=1}^n |j(\omega - \omega_{pi}) - \sigma_{pi}|} = H_0 \frac{\prod_{j=1}^m \sqrt{(\omega - \omega_{zj})^2 + \sigma_{zj}^2}}{\prod_{i=1}^n \sqrt{(\omega - \omega_{pi})^2 + \sigma_{pi}^2}}$$

convert to dB → allow combination by addition rather than products → easier to graph

$$20 \log |H(j\omega)| = 20 \log H_0 + \sum_{j=1}^m (20 \log |j\omega - z_j|) - \sum_{i=1}^n (20 \log |j\omega - p_i|)$$