

Lecture 40: Complex Gates

- Announcements:
- Last lecture!
- HW#11 online and due during RRR week
- Lab 6 online and due 5 p.m., Friday, Dec. 7
- Labs will run as usual next week
- We will keep all normal office hours during RRR Week and Finals Week up through the Wednesday before the Final Exam
- There will be extra office hours during Finals Week, as explained in the Final Exam Info Sheet




-----  
 • Lecture Topics: (over the next few days)

- ↳ Complex CMOS Gates
- ↳ Final Exam Info Sheet

-----  
 • Last Time:

- Finished the expression for CMOS inverter  $t_{pHL}$  propagation delay
- Now summarize this ...

Propagation Delay in CMOS Inverters

   

EE 105: Microelectronic Devices & Circuits  
Lecture 40w: Complex Gates

Case:  $V_0 \geq V_{DD} - V_{TN} \rightarrow M_1$  saturated

$$i_{D(sat)} = \frac{K_N}{2} (V_{GS} - V_{TN})^2 = -C_L \frac{dv_c}{dt}$$

$$dt = \frac{-2C_L dv_c}{K_N (V_{GS} - V_{TN})^2} = \frac{-2C_L dv_c}{K_N (V_{DD} - V_{TN})^2}$$


$$[V_{GS} = V_{OH} = V_{DD} = V_I]$$

$$\int_{t_0}^{t_1} dt = \int_{V_{DD}}^{V_{DD} - V_{TN}} \frac{2C_L}{K_N (V_{DD} - V_{TN})^2}$$

$$(t_1 - t_0) = - \frac{2C_L}{K_N (V_{DD} - V_{TN})^2} (V_{DD} - V_{TN} - V_{DD})$$

$$(t_1 - t_0) = \frac{2C_L}{K_N (V_{DD} - V_{TN})} \frac{V_{TN}}{V_{DD} - V_{TN}} = 2C_L R_{on} \frac{V_{TN}}{V_{DD} - V_{TN}}$$

 effective  
"on resistance"  
of the X resistor



Case:  $V_0 < V_{DD} - V_{TN} \rightarrow M_1$  linear

$$i_{D(lin)} = -C_L \frac{dv_c}{dt}$$

$$K_N (V_{GS} - V_{TN} - \frac{V_{DS}}{2}) V_{DS} = -C_L \frac{dv_c}{dt}$$

$$[V_{DS} = V_c, V_{GS} = V_{DD}] \Rightarrow \left\{ K_N (V_{DD} - V_{TN} - \frac{V_c}{2}) V_c = -C_L \frac{dv_c}{dt} \right\} \times 2$$

$$\int_{t_1}^{t_2} \frac{K_N}{2C_L} dt = - \int_{V_1}^{V_2} \frac{dv_c}{[2(V_{DD} - V_{TN}) - V_c] V_c}$$

$$\left[ \int \frac{dx}{(a-x)x} = \int \frac{dx}{a(a-x)} + \int \frac{dx}{ax} \right]$$

$$= \frac{1}{a} \int \left[ \frac{1}{a-x} + \frac{1}{x} \right] dx = \frac{1}{a} \ln \left( \frac{x}{a-x} \right)$$

$$[V_2 = \frac{V_{DD}}{2}, V_1 = V_{DD} - V_{TN}] \Rightarrow$$

$$\frac{K_N}{2C_L} (t_2 - t_1) = - \frac{1}{2(V_{DD} - V_{TN})} \ln \left[ \frac{V_c}{2(V_{DD} - V_{TN}) - V_c} \right] \Bigg|_{V_{DD} - V_{TN}}^{\frac{V_{DD}}{2}}$$

; algebra

$$= - \frac{1}{2(V_{DD} - V_{TN})} \ln \left[ \frac{V_{DD}}{4V_{DD} - 4V_{TN} - V_{DD}} \right]$$

EE 105: Microelectronic Devices & Circuits  
Lecture 40w: Complex Gates

$$(t_2 - t_1) = \frac{C_L}{K_N(V_{DD} - V_{TN})} \ln \left[ \frac{4(V_{DD} - V_{TN}) - V_{DD}}{V_{DD}} \right]$$

$$= \frac{C_L}{K_N(V_{DD} - V_{TN})} \ln \left[ \frac{4(V_{DD} - V_{TN})}{V_{DD}} - 1 \right]$$

$$(t_2 - t_1) = R_{on} C_L \ln \left[ \frac{4(V_{DD} - V_{TN})}{V_{DD}} - 1 \right]$$

$$t_{pHL} = (t_2 - t_1) + (t_1 - t_0) = (t_2 - t_0)$$


$$= R_{on} C_L \left\{ \ln \left[ \frac{4(V_{DD} - V_{TN})}{V_{DD}} - 1 \right] + \frac{2V_{TN}}{(V_{DD} - V_{TN})} \right\} = t_{pHL}$$

$$\text{where } R_{on} = \frac{1}{K_N(V_{DD} - V_{TN})}$$

$$t_{pHL} = R_{on} C_L \times f(V_{DD}, V_{TN})$$

$t_{pLH}$ : output: L  $\rightarrow$  H

 $\rightarrow$  connect  $C_L$  to  $V_{DD} \rightarrow$  PMOS on, NMOS off



Through a similar analysis:


$$t_{pLH} = R_{on} C_L \left\{ \ln \left[ \frac{4(V_{DD} - |V_{TP}|)}{V_{DD}} - 1 \right] + \frac{2|V_{TP}|}{(V_{DD} - |V_{TP}|)} \right\}$$

$$t_p = \frac{t_{pLH} + t_{pHL}}{2}$$

EE 105: Microelectronic Devices & Circuits  
Lecture 40w: Complex Gates

Complex CMOS Gate

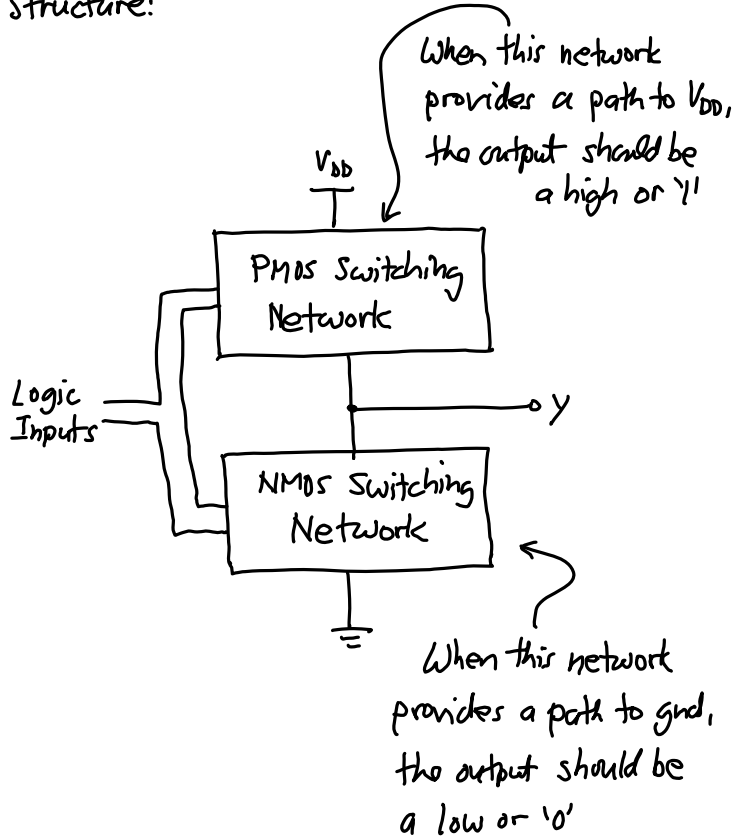To realize more complex gates, use the following structure:




- For CMOS, to save power consumption, must avoid a conductive path connecting  $V_{DD}$  and ground in steady-state
- Otherwise, too much current will flow and dissipate power
- Should also minimize this path during transitions

CMOS NOR Gate

A	B	$Y = \overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0


When both inputs are '0', there should be a path to  $V_{DD}$   $\hookrightarrow$  '1'

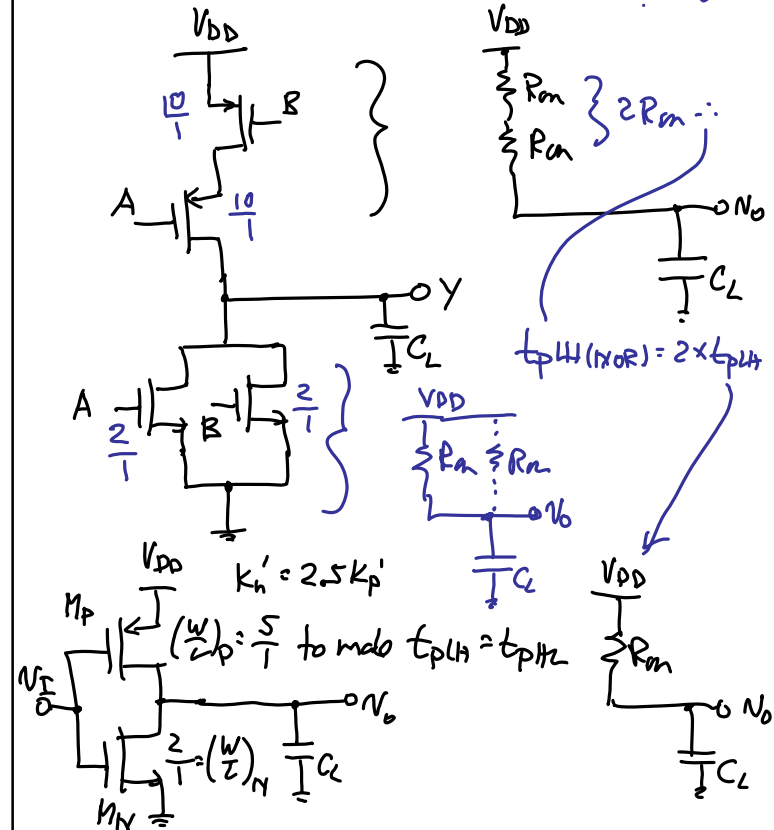Anytime there is a '1' in the input, need to pull down to gnd



How about 3 inputs (NOR)?

A	B	C	$Y = \overline{A+B+C}$
0	0	0	1
0	0	1	0
0	1	0	0
⋮	⋮	⋮	⋮

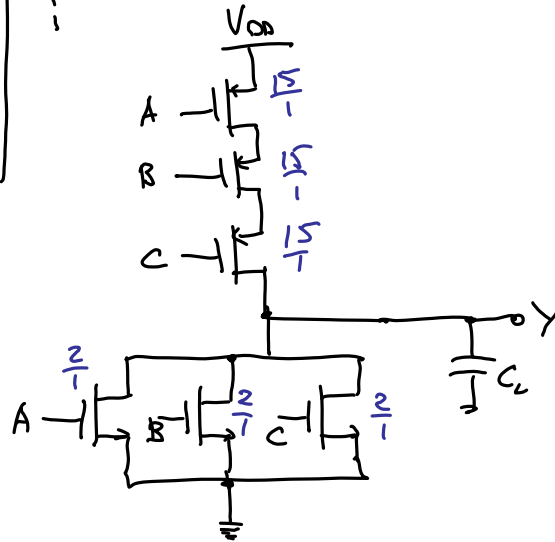

- What's Next?
- **EE130: Semiconductor Devices**
  - ↪ Did you like the physics parts? If so, then this is the course for you.
  - ↪ Will go much deeper and cover
    - Energy band diagrams
    - Short channel MOS
    - More accurate physical structure
    - Heterojunctions
    - Much more ...
- **EE143: Semiconductor Device Fabrication**
  - ↪ Planar wafer-level fabrication methods that make IC's possible
  - ↪ Tools and chemistry
  - ↪ Process flow design
  - ↪ Hands-on wafer fabrication
- **EE140: Analog Integrated Circuits**
  - ↪ Supply and temperature independent biasing
  - ↪ Much larger circuits
  - ↪ Deeper understanding of op amps
  - ↪ Stability compensation
  - ↪ Feedback methods (by inspection)
- **EECS151: Digital Integrated Circuits**
  - ↪ Build upon propagation delay concepts
    - Short channel devices
  - ↪ Logic gates, adders, etc.
  - ↪ System-level design
    - Interconnect issues
    - Programmable arrays

**EE 105: Microelectronic Devices & Circuits**  
**Lecture 40w: Complex Gates**

- **What's Next? (cont.)**
- **EE147: Microelectromechanical Systems (MEMS)**
  - ↳ **I'm biased, but ... this is the coolest stuff, period!**
  - ↳ **Mechanics and Materials**
  - ↳ **Methods for fabricating tiny mechanics**
  - ↳ **Mechanical circuit design**
  - ↳ **You'll learn that all of your EE math skills and circuit techniques can just as easily be applied to mechanical devices and systems**
  - ↳ **Applications to sensing and RF**