

Lecture 4: Amplifiers

• Announcements:

- HW#1 online and due this Friday
- Lab#1 online
- Labs start next week
 - ↳ Monday, Sept. 3 is a holiday, so the Monday lab will start one week later
 - ↳ The Tuesday lab starts Sept. 4
- Will let in concurrent enrollments end of this week


• Lecture Topics:

- ↳ Finish Bode Plots
- ↳ Amplifiers
- ↳ Amplifier Models (2-port networks)
- ↳ Input R_i
- ↳ Output R_o
- ↳ Ideal Voltage Amplifier

• Last Time:

- Going through procedure for doing a Bode plot
- Now, continue with this ...

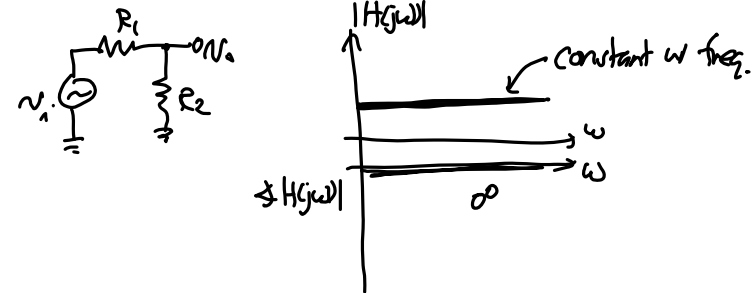- For a purely resistive network, the frequency response is constant (i.e., a straight line), both magnitude and phase



- The addition of reactive (energy storage) components, e.g., capacitors, inductors
 - ↳ Shapes the frequency response
 - ↳ Adds singularities, i.e., poles and zeros
 - ↳ Yields the general transfer function:

$$H(s) = \frac{V_o(s)}{V_i(s)} = H_0 \frac{(s-z_1)(s-z_2)\dots(s-z_m)}{(s-p_1)(s-p_2)\dots(s-p_n)} = H_0 \frac{\prod_{j=1}^m (s-z_j)}{\prod_{i=1}^n (s-p_i)}$$

resistive term

where

$$z_j = \sigma_{z_j} + j\omega_{z_j}; \quad \sigma_{z_j} = \text{Re}(z_j), \quad \omega_{z_j} = \text{Im}(z_j)$$

$$p_i = \sigma_{p_i} + j\omega_{p_i}; \quad \sigma_{p_i} = \text{Re}(p_i), \quad \omega_{p_i} = \text{Im}(p_i)$$

$V_i(s) \triangleq$ input variable (not necessarily a voltage)

V - variable (" " " ")

⇒ given this, you should be able to plot the Bode plot!

Bode Plot

① Plot magnitude in decibels (dB) vs. log (freq.)

$$H(s) = H(j\omega) \Rightarrow |H(j\omega)| = H_0 \frac{\prod_{j=1}^m |j\omega - z_j|}{\prod_{i=1}^n |j\omega - p_i|}$$

$$\Rightarrow = H_0 \frac{\prod_{j=1}^m |j(\omega - \omega_{zj}) - \sigma_{zj}|}{\prod_{i=1}^n |j(\omega - \omega_{pi}) - \sigma_{pi}|} = H_0 \frac{\prod_{j=1}^m \sqrt{(\omega - \omega_{zj})^2 + \sigma_{zj}^2}}{\prod_{i=1}^n \sqrt{(\omega - \omega_{pi})^2 + \sigma_{pi}^2}}$$

convert to dB \rightarrow allow combination by addition rather than products \rightarrow easier to graph

$$20 \log |H(j\omega)| = 20 \log H_0 + \sum_{j=1}^m (20 \log |j\omega - z_j|) - \sum_{i=1}^n (20 \log |j\omega - p_i|)$$

② Plot phase vs. log (freq.)

$$\angle H(j\omega) = \sum_{j=1}^m [\angle (j\omega - z_j)] - \sum_{i=1}^n [\angle (j\omega - p_i)]$$

where $\angle (j\omega - s) = \tan^{-1} \left(\frac{\omega - \omega_s}{-\sigma_s} \right)$
 $[s = \sigma_s + j\omega_s]$

- Because everything reduces to addition, one can determine the plot for each term then add/subtract them together
- Basically, can use superposition for both the magnitude and phase plots

Bode Plot Step-By-Step Procedure

- ① Get all factors into the form s or $(1 + \frac{s}{a})$
e.g., $s + b = b(1 + \frac{s}{b})$
- ② Plot the Bode plot for each factor, one factor at a time. (Note that there are only a few cases.)
- ③ Sum all decibel magnitude plots to obtain the total magnitude plot.
- ④ Sum all phase plots to obtain the total phase plot.



Example

$$H(s) = \frac{100s(s+10^5)}{(s+10)(s+10^3)} = \underbrace{100}_{10^2 = H_0} \frac{s(1 + \frac{s}{10^5})}{(1 + \frac{s}{10})(1 + \frac{s}{10^3})}$$


Factoring brings out the the gain term

Case: constant value

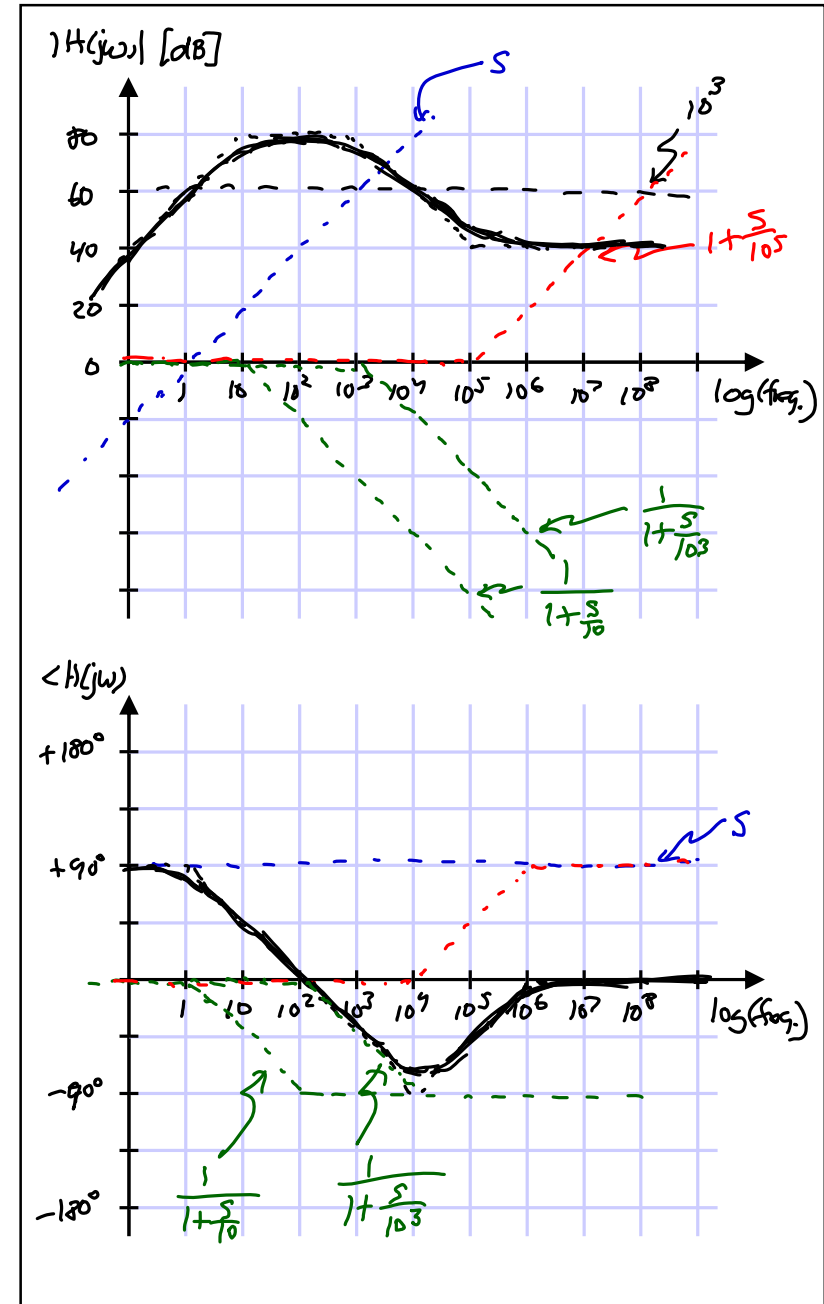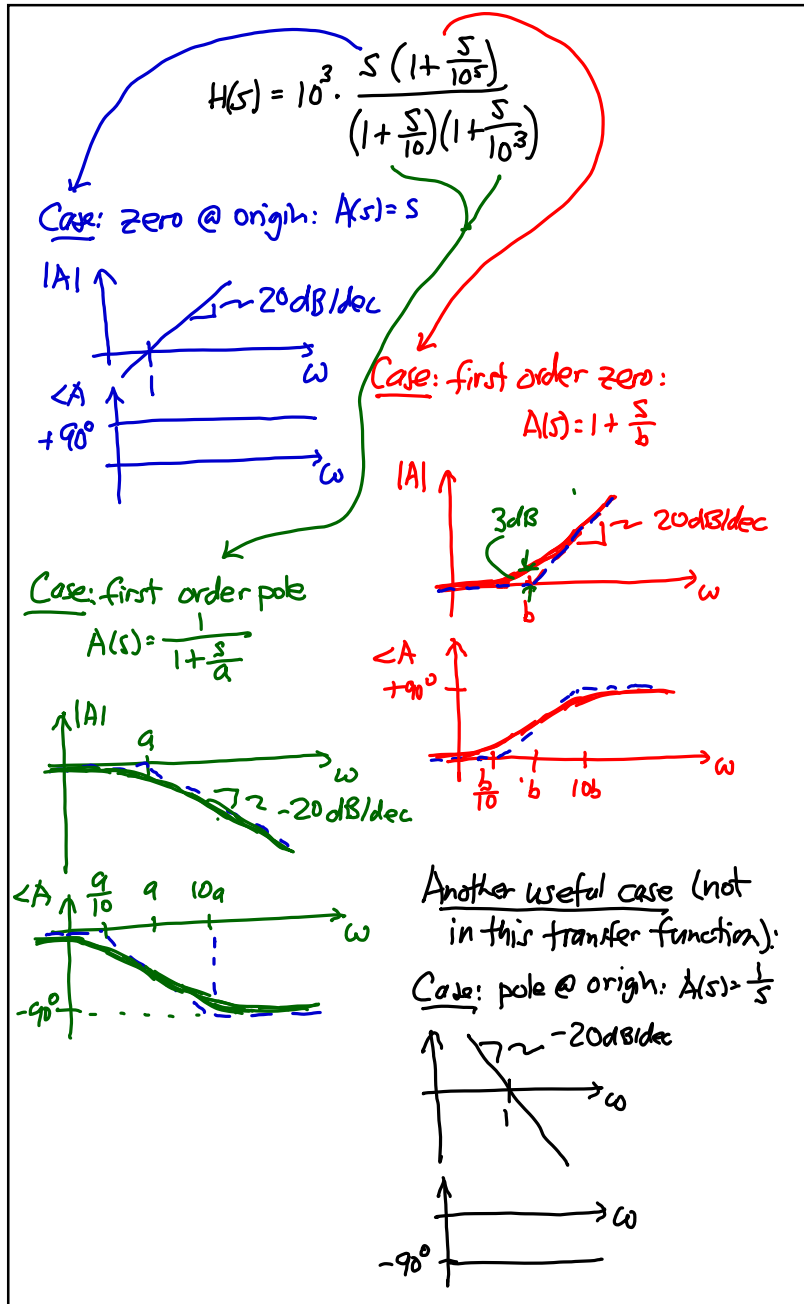- constant amplitude = $20 \log H_0$
- constant phase = 0°



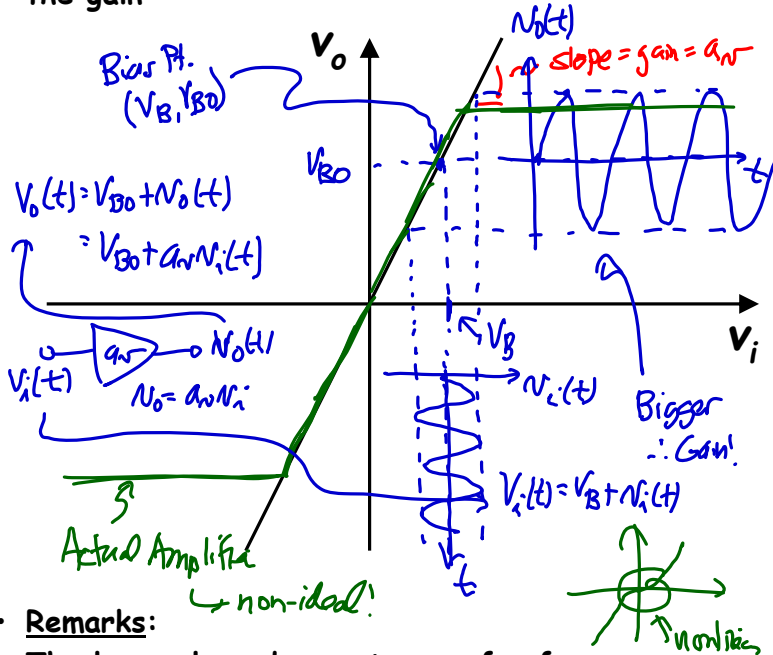
- **Amplification:**
- Really just boils down to creating a transfer function with a large slope, where the slope equals the gain



- **Remarks:**
- The large slope does not come for free
 - ↳ generally requires power if you want power gain
- Ideal amplifier generally has an infinite linear line transfer function
- Power and device non-ideality prevent a truly ideal amplifier
 - ↳ Power rails limit the acceptable input/output range
 - ↳ Device nonlinearity limits the linear range
 - ↳ Noise limits the minimum detectable signal
 - ↳ Parasitic elements, e.g., capacitors, limit the frequency range (i.e., the bandwidth)

Amplifier Models

⇒ generally given the symbol:

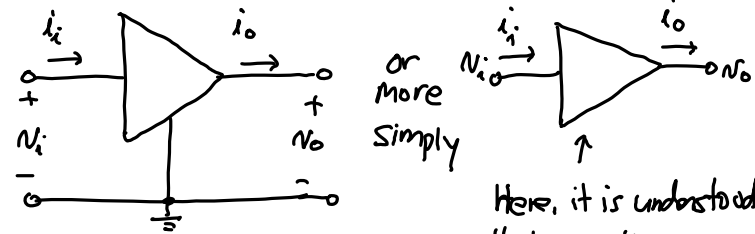

Here, it is understood that everything refers to the same ground

We can interpret a given amplifier as any of four types:

- ① Voltage Amplifier: $N_i \rightarrow N_o$
(g-parameter model fits best)
- ② Current Amplifier: $i_i \rightarrow i_o$
(h-parameter model fits best)
- ③ Transconductance Amplifier: $N_i \rightarrow i_o$
(y-parameter model fits best)
- ④ Transresistance Amplifier: $i_i \rightarrow N_o$
(z-parameter model fits best)

This class will mainly see there


- All of these are equivalent representations, each comprising a gain factor along with an input and output resistance that model the resistance seen looking into the amplifier terminals
- Take for example a voltage amplifier:

Voltage Amplifier



⇒ most appropriate general model is the

g-parameter model → Defining Equations:

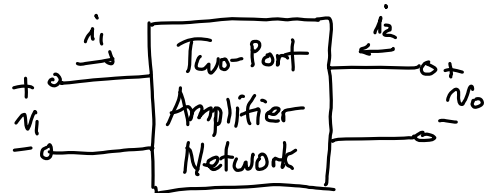Note the matrix form →
$$\begin{cases} i_1 = g_{11}v_1 + g_{12}i_2 \\ v_2 = g_{21}v_1 + g_{22}i_2 \end{cases}$$



|||

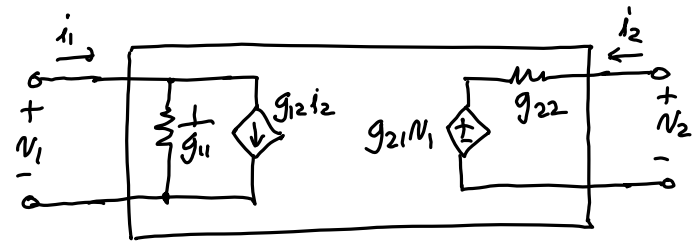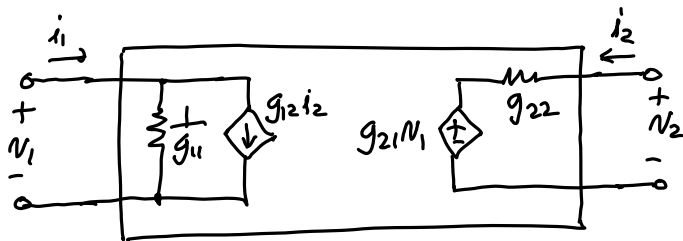

where:

$$g_{11} = \left. \frac{i_1}{v_1} \right|_{i_2=0} = \text{open-circuit input conductance}$$

$$g_{12} = \left. \frac{i_1}{i_2} \right|_{v_1=0} = \text{reverse short-circuit current gain}$$

$$g_{21} = \left. \frac{v_2}{v_1} \right|_{i_2=0} = \text{forward open-circuit voltage gain}$$

$$g_{22} = \left. \frac{v_2}{i_2} \right|_{v_1=0} = \text{short-circuit output resistance}$$

Assuming a design to amplify in the forward direction → neglect the current source $g_{12}i_2$ in the g-parameter model → the result:

