

Lecture 5: Ideal Op Amps

- Announcements:
- HW#2 online and due next Friday via Gradescope, which means you will submit pdf
- General Lab Instruction Manual online in the "Labs" link of the website
- Labs start next week
 - ↳ Monday, Sept. 3 is a holiday, so the Monday lab will start one week later
 - ↳ The Tuesday lab starts Sept. 4
- Will let in concurrent enrollments soon
- -----
- Lecture Topics:
 - ↳ Amplifier Models (2-port networks)
 - ↳ Input R_i
 - ↳ Output R_o
 - ↳ Ideal Voltage Amplifier
 - ↳ Ideal Op Amps
 - ↳ Negative Feedback
 - ↳ Op Amp Circuits
- -----
- Last Time:
- Going through amplifier models
- Now, continue with this ...


- All of these are equivalent representations, each comprising a gain factor along with an input and output resistance that model the resistance seen looking into the amplifier terminals
- Take for example a voltage amplifier:

Voltage Amplifier


⇒ most appropriate general model is the


g-parameter model → Defining Equations:

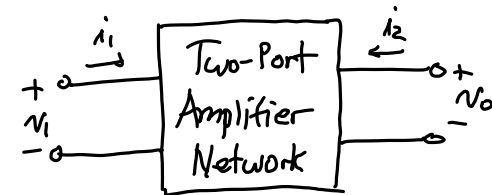Note the matrix form →
$$\begin{cases} i_1 = g_{11}v_1 + g_{12}i_2 \\ v_2 = g_{21}v_1 + g_{22}i_2 \end{cases}$$



|||

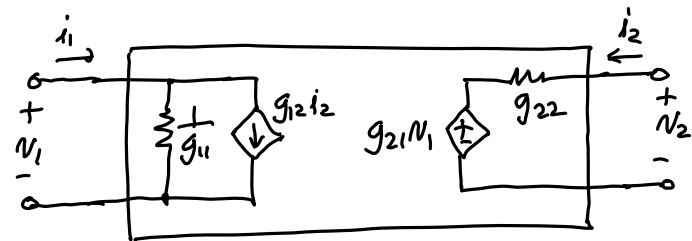

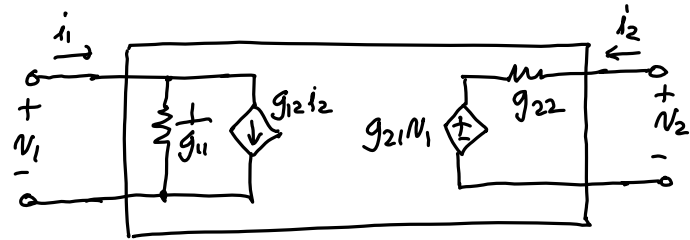

where:


$$g_{11} = \left. \frac{i_1}{v_1} \right|_{i_2=0} = \text{open-circuit input conductance}$$

$$g_{12} = \left. \frac{i_1}{i_2} \right|_{v_1=0} = \text{reverse short-circuit current gain}$$


$$g_{21} = \left. \frac{v_2}{v_1} \right|_{i_2=0} = \text{forward open-circuit voltage gain}$$

$$g_{22} = \left. \frac{v_2}{i_2} \right|_{v_1=0} = \text{short-circuit output resistance}$$

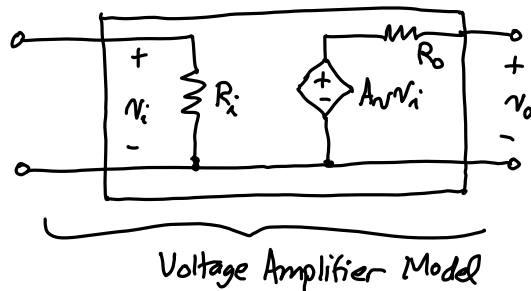Assuming a design to amplify in the forward direction \rightarrow neglect the current source $g_{12}i_2$ in the g -parameter model \rightarrow the result:



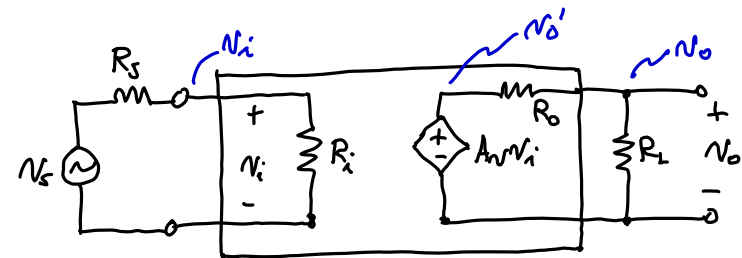$\Rightarrow R_i \neq R_o$ directly influence the total voltage gain via the input & output voltage dividers:



$$\frac{v_i}{v_s} = \frac{R_i}{R_i + R_s} \quad \frac{v_o'}{v_i} = A_v \quad \frac{v_o}{v_o'} = \frac{R_L}{R_L + R_o}$$


$$\therefore \frac{v_o}{v_s} = \frac{R_i}{R_i + R_s} A_v \frac{R_L}{R_L + R_o} = \text{total voltage gain} \neq A_v$$

$$\frac{v_o}{v_s} = \frac{v_i}{v_s} \cdot \frac{v_o'}{v_i} \cdot \frac{v_o}{v_o'}$$

these terms attenuate the intended gain!

\rightarrow get when $R_i = \infty \neq R_o = 0 \leftarrow$ These values define an ideal voltage amplifier!

To Determine R_i

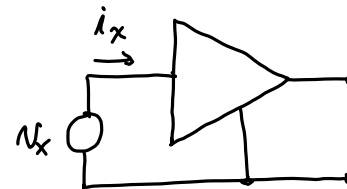


① Apply test voltage source, v_x .

② Measure resulting current, i_x .

③ $R_i = \frac{v_x}{i_x} \leftarrow$ same as $\frac{1}{g_{11}} = \left. \frac{v_1}{i_1} \right|_{i_2=0}$ from the g -parameter model

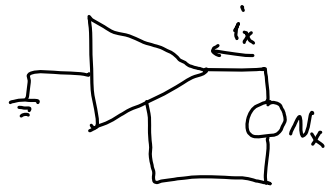To Determine R_o (for a voltage amplifier)



① Ground input. (Zero out all independent sources.)

② Apply test voltage source, V_x .


③ Measure resulting current, i_x .

④ $R_o = \frac{V_x}{i_x}$ ← same as $g_{22} = \frac{v_2}{i_2} |_{v_1=0}$ from the g-parameter model

Ideal Operational Amplifier (op amps)


⇒ the work horse of analog electronics
 ⇒ combinations of op amps w/ feedback components allow realization of analog computers, sampled-data systems, A/D converters, DAC's, instrumentation amplifiers, ...

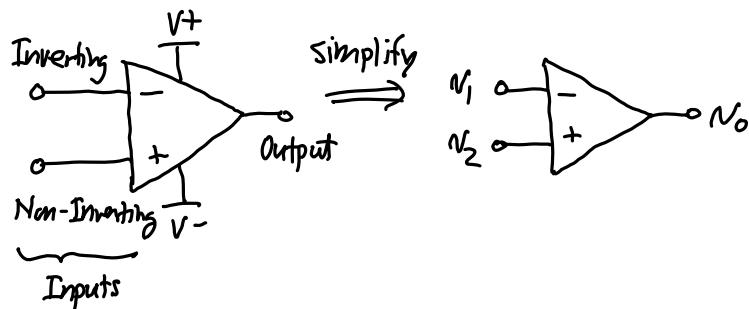⇒ in general, have a minimum of 5 terminals:




Why have 2 inputs?

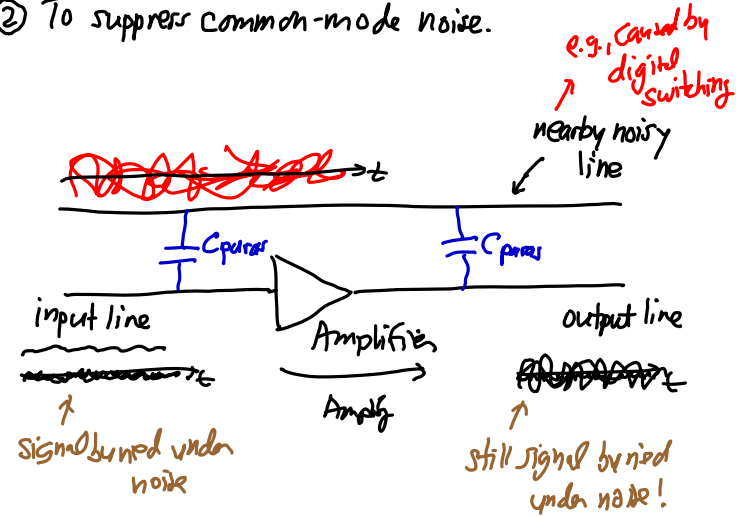- ① To get a virtual ground for op amp ckt's.
- ② To suppress common-mode noise.




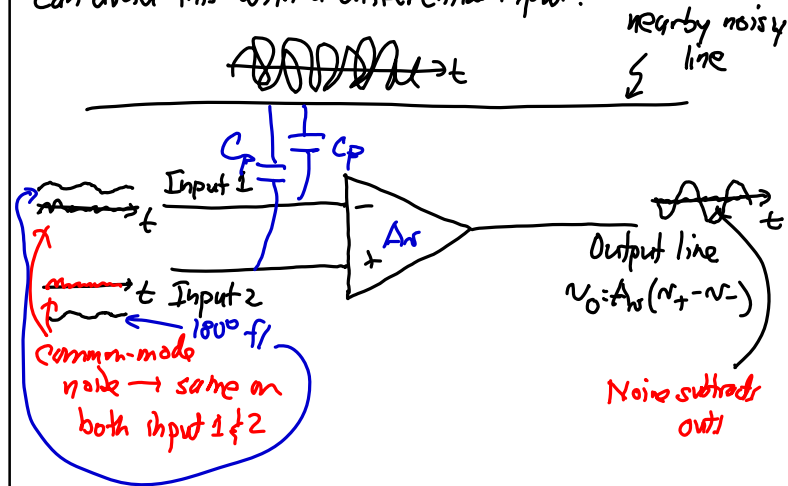Can avoid this with a differential input:



Perhaps the best way to define an op amp is via its equivalent ckt:

Op Amp Equivalent Ckt.

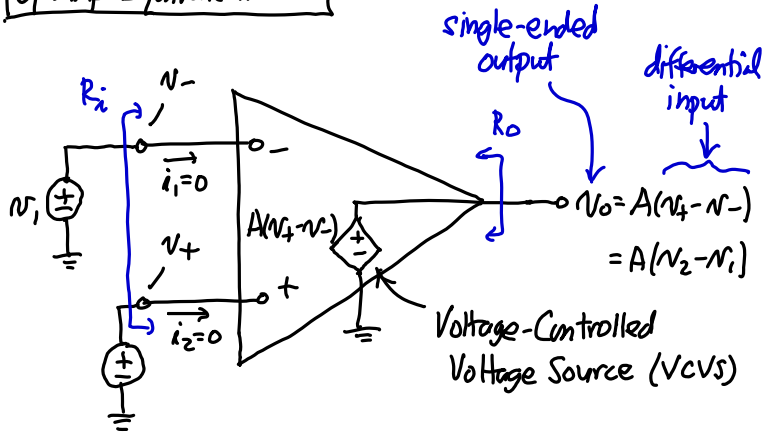


Properties of Ideal Op Amps:

- ① $R_i = \infty \rightarrow$ ④ $i_+ = i_- = 0$
- ② $R_o = 0$
- ③ $A = \infty \rightarrow$ ⑤ $v_+ = v_-$, assuming $v_o = \text{finite}$

Why? $\infty(v_+ - v_-) = v_o = \text{finite}$
 $\therefore v_+ - v_- = 0 \rightarrow v_+ = v_-$
 Source of "virtual ground"

Big Assumption!
 only holds when we have negative feedback!


Negative Feedback

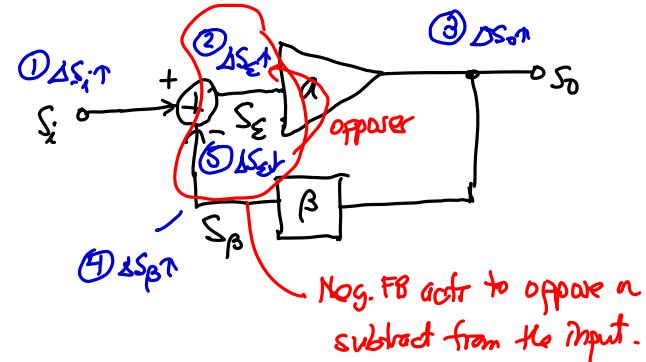

$$\begin{cases} S_o = a S_E \\ S_E = S_i - \beta S_o \end{cases} \Rightarrow \begin{cases} S_o = a(S_i - \beta S_o) \\ S_o(1 + a\beta) = a S_i \end{cases} \Rightarrow \boxed{\frac{S_o}{S_i} = \frac{a}{1 + a\beta}}$$

$$[a \rightarrow \infty] \Rightarrow \frac{S_o}{S_i} \approx \frac{a}{a\beta} = \frac{1}{\beta} = \text{finite!}$$

Contrast w/ Positive Feedback

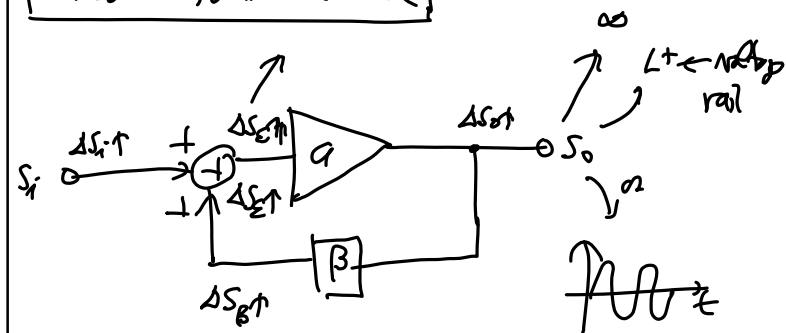

- Remarks: (on neg. FB)
- Neg. FB can insure $v_o = \text{finite}$ even with $a = \text{infinity}$
- Overall closed-loop gain (or transfer function) is dependent only on external components (e.g., β)
- Overall closed-loop gain S_o/S_i is independent of amplifier gain a
- This is very important, since it's easy to get large amplifier gain, but it's hard to get an exact value
 - ↳ If you're shooting for $a = 50,000$, you might get 47,000 or 60,000 instead
 - ↳ But it won't matter much in the feedback ckt.

Op Amp Ckts.

Example. Inverting Amplifier

