

Lecture 6: Finite Gain & Bandwidth


- Announcements:
- HW#2 online and due Friday via Gradescope
- Lab#2 online
- Lots of SPICE this week
- Approved all concurrent enrollments
- Next Wednesday, 9/12: I will be out of town.
 - ↳ So no ground lecture that day
 - ↳ Make up will probably need to be by video recording and put online

-
- Lecture Topics:
 - ↳ Ideal Op Amp Circuits
 - ↳ Non-Ideal Op Amp Bode Plot
 - ↳ Finite Gain & Bandwidth
 - ↳ Closed Loop Amplifier Freq. Response
 - Non-Inverting Amplifier
 - Inverting Amplifier

-
- Last Time:
 - Op amp circuit example
 - Now, continue with this ...

Perhaps the best way to define an op amp is via its equivalent ckt:

Op Amp Equivalent Ckt.

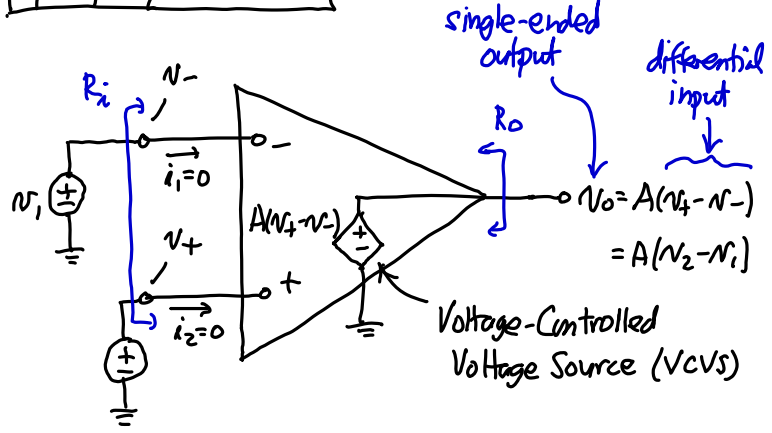

Properties of Ideal Op Amps:

- ① $R_i = \infty \rightarrow$ ④ $i_+ = i_- = 0$
- ② $R_o = 0$
- ③ $A = \infty \rightarrow$ ⑤ $v_+ = v_-$, assuming $v_o = \text{finite}$

Why? $\infty(v_+ - v_-) = v_o = \text{finite}$
 $\therefore v_+ - v_- = 0 \rightarrow v_+ = v_-$
 Source of "virtual ground"

↳ Big Assumption!
 ↳ only holds when we have negative feedback!

Negative Feedback

Neg. FB acts to oppose or subtract from the input.

$$\left. \begin{aligned} S_o &= a \Delta S_E \\ \Delta S_E &= S_i - \beta S_o \end{aligned} \right\} \begin{aligned} S_o &= a(S_i - \beta S_o) \\ S_o(1 + a\beta) &= a S_i \rightarrow \boxed{\frac{S_o}{S_i} = \frac{a}{1 + a\beta}} \end{aligned}$$

$[a \rightarrow \infty] \Rightarrow \frac{S_o}{S_i} \approx \frac{a}{a\beta} = \frac{1}{\beta} = \text{finite!}$

Contrast w/ Positive Feedback

L+ ← not opp real

- **Remarks:** (on neg. FB)
- Neg. FB can insure $v_o = \text{finite}$ even with $a = \text{infinity}$
- Overall closed-loop gain (or transfer function) is dependent only on external components (e.g., β)
- Overall closed-loop gain S_o/S_i is independent of amplifier gain a
- This is very important, since it's easy to get large amplifier gain, but it's hard to get an exact value
 - ↳ If you're shooting for $a=50,000$, you might get 47,000 or 60,000 instead
 - ↳ But it won't matter much in the feedback ckt.

Op Amp Ckts.

Example. Inverting Amplifier

Virtual ground = 0V

due to 0V across C parasitic

- ① Verify that there is neg. FB. \therefore ideal op amp rules apply.
- ② $\therefore N_o = \text{finite} \rightarrow N_+ = N_- \rightarrow \text{virtual ground}$
- ③ $i_- = 0, i_1 = i_2$

$$\left. \begin{aligned} i_1 &= \frac{N_i - 0}{R_1} \cdot \frac{N_i}{R_1} = i_2 \\ N_o &= -\left(\frac{N_i}{R_1}\right) R_2 = -\frac{R_2}{R_1} N_i \end{aligned} \right\} \therefore \boxed{\frac{N_o}{N_i} = -\frac{R_2}{R_1}}$$

Yarr Lab 11:

Example.

① verify neg. FB → X


∴ $V_o \neq \text{finite} \rightarrow V_+ \neq V_-$
⇒ this ckt. will rail out!

Non-Ideal Op Amps

Finite Op Amp Gain & Bandwidth

For an ideal op amp, $A = \infty$.

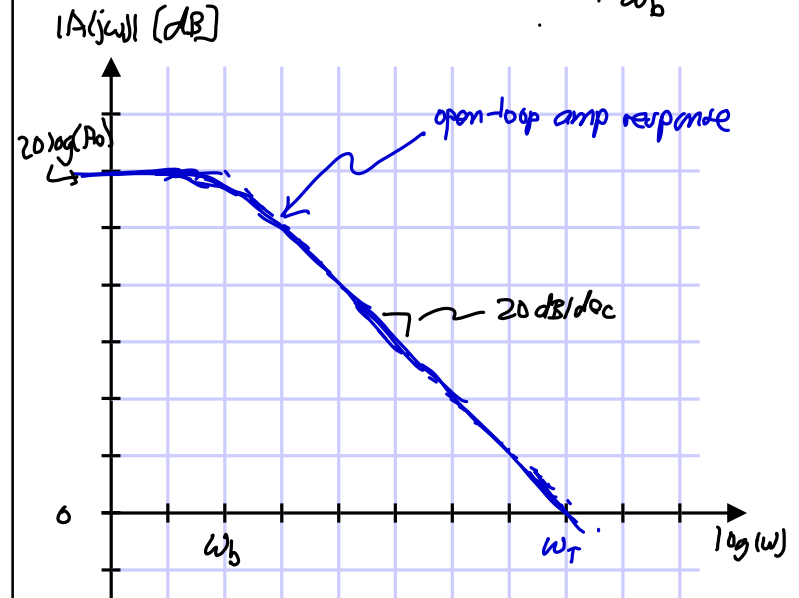In reality, the gain goes as: $A(s) = \frac{A_0}{1 + \frac{s}{\omega_b}}$



$\omega_T \triangleq$ unity gain frequency = freq. @ which $|A(j\omega)| = 1$
(= 0 dB)

$$\text{At } \omega_T, |A(j\omega_T)| = 1 = \frac{A_0}{\sqrt{1 + \left(\frac{\omega_T}{\omega_b}\right)^2}} \Rightarrow \frac{A_0}{\frac{\omega_T}{\omega_b}} = 1 \rightarrow \boxed{\omega_T = A_0 \omega_b}$$

[$\omega_T \gg \omega_b$]

↑ gain ↑ Bandwidth


(For $\omega \gg \omega_b$) $\Rightarrow A(s) = \frac{A_0}{s} : \frac{A_0 \omega_b}{s} = \frac{\omega_T}{s} \Rightarrow \frac{f_T}{f}$

ω_T in data sheets

(an op amp ultimately is an integrator w/ time constant $\tau = \frac{1}{\omega_T}$)

Frequency Response of Closed Loop Amplifier

Example. Non-Inverting Amplifier

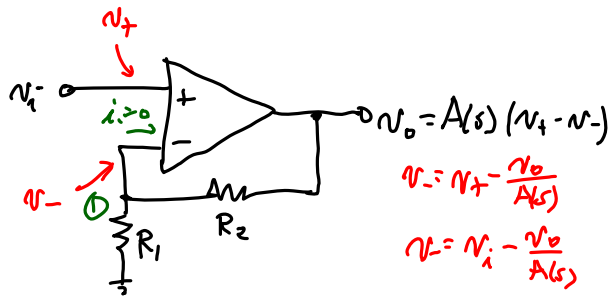

$v_+ = v_i - \frac{v_o}{A(s)}$
 $v_- = v_i - \frac{v_o}{A(s)}$

Find an expression for gain as a function of freq.

① Brute Force Determination:

KCL: $\frac{v_o - v_-}{R_2} = \frac{v_-}{R_1} \rightarrow \frac{v_o}{R_2} = v_- \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$

$\frac{v_o}{R_2} = \left(v_i - \frac{v_o}{A(s)} \right) \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \rightarrow \frac{v_o}{v_i}(s) = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{1}{A(s)} \left(1 + \frac{R_2}{R_1} \right)}$

$\left[A(s) \cdot \frac{A_0}{1 + \frac{s}{\omega_b}} \right] \rightarrow \frac{v_o}{v_i}(s) = \left(1 + \frac{R_2}{R_1} \right) \frac{1}{1 + \frac{s}{A_0 \omega_b \left(\frac{R_1}{R_1 + R_2} \right)}}$