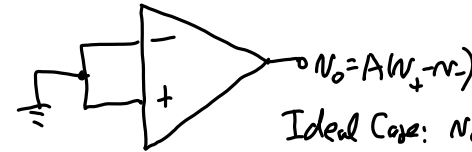


Lecture 9: Vos and Input Bias Current

- Announcements:
- HW#3 online and due Friday via Gradescope
- Lab#2 will be a two week lab
 - ↳ Prelab is due in the second week
 - ↳ But you should have proof of having started it when you go to lab this week
 - ↳ You will still do the lab this week and continue next week
- This Wednesday, 9/12: I will be out of town.
 - ↳ So no ground lecture that day
 - ↳ This is a video lecture
-
- Lecture Topics:
 - ↳ Input Offset Voltage
 - ↳ Input Bias Current
-
- Last Time:
- Started input offset voltage
- Now, continue with this ...


Input Offset Voltage, V_{os}



Ideal Case: $V_o = 0V$


Reality: $V_o \neq 0V$
 (usually, $V_o = I^+ \text{ or } I^-$;
 it rails out)

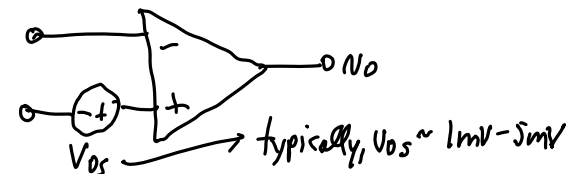Model this w/ equivalent
 input offset voltage, V_{os} :



Effect of V_{os} on Op Amp Ckt. -

Example. Non-Inverting Amplifier

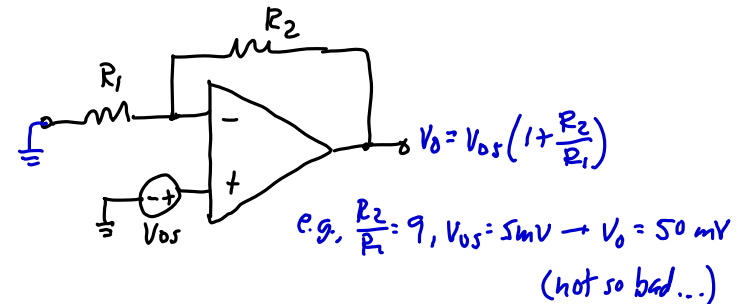

Example. Integrator

$$V_{os} = \frac{V_{os}}{R} R$$

$$i_i = \frac{V_{os}}{R}$$

$$V_o = V_{os} + \frac{1}{C} \int_0^t i_i dt$$

$$= V_{os} + \frac{1}{C} \int_0^t \frac{V_{os}}{R} dt$$

$$= V_{os} \left(1 + \frac{t}{RC} \right) + N_{cl} t = 0$$

$$V_o \uparrow$$

$$V_{os} + N_{cl} t = 0$$

continues to increase until op amp saturates!

Solution: place resistor R_f in shunt w/ C

then $V_o = V_{os} \left(1 + \frac{R_f}{R} \right)$ ← prevents N_o from going to the rail!

Input Bias Currents

⇒ many op amps require small currents into their input transistors that allow the transistors to function

⇒ currents are independent of R_{in}

over ↷

Schematically:

$$I_{B1} = I_B + \frac{I_{OS}}{2}$$

$$I_{B2} = I_B - \frac{I_{OS}}{2}$$

Average or Common-mode Value $\left. \vphantom{\begin{matrix} I_{B1} \\ I_{B2} \end{matrix}} \right\} = I_B = \frac{I_{B1} + I_{B2}}{2} \triangleq$ input bias current
 (typ.: 100 nA for bipolar op amps)

Difference or Differential Value $\left. \vphantom{\begin{matrix} I_{B1} \\ I_{B2} \end{matrix}} \right\} = I_{OS} = |I_{B1} - I_{B2}| \triangleq$ input offset current
 (typ.: 10 nA for a bipolar op amp)


Example. Non-Inverting Amplifier

$$V_o = I_{B1} R_2 = \left(I_B + \frac{I_{OS}}{2} \right) R_2$$

not zero!

"virtual ground" \therefore current cannot flow thru R_1

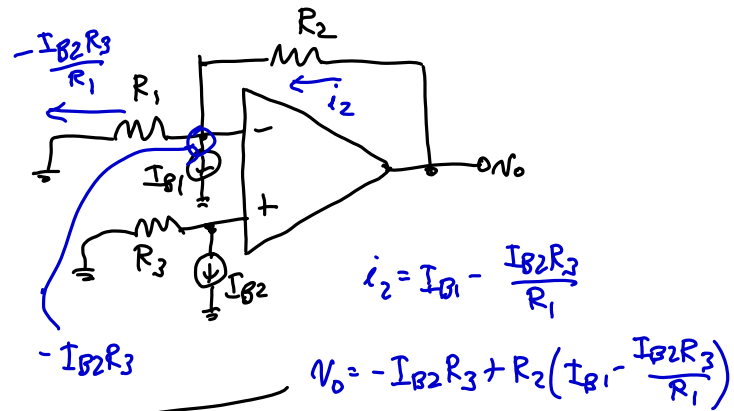To reduce this effect: add resistor to the (+) input



What value of R_3 makes $V_o \rightarrow 0$?

Case $I_{os} = 0$: (i.e., $I_{B1} = I_{B2} = I_B$)

$$V_o = I_B \left(R_2 - R_3 \left(1 + \frac{R_2}{R_1} \right) \right)$$

$$[\text{For } V_o = 0] \Rightarrow R_2 = R_3 \left(1 + \frac{R_2}{R_1} \right) \rightarrow R_3 = \frac{R_2}{1 + \frac{R_2}{R_1}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$\therefore R_3 = R_1 || R_2 \rightarrow V_o = 0 \text{ w/ } I_{os} = 0$$

Case $I_{os} \neq 0$: (i.e., $I_{B1} = I_B + \frac{I_{os}}{2}$, $I_{B2} = I_B - \frac{I_{os}}{2}$)

$$V_o = -I_{B2}R_3 + R_2 \left(I_{B1} - \frac{I_{B2}R_3}{R_1} \right)$$

$$V_o = -I_B R_3 + \frac{I_{os} R_3}{2} + R_2 \left(I_B + \frac{I_{os}}{2} - \frac{I_B R_3}{R_1} + \frac{I_{os} R_3}{2 R_1} \right)$$

$$[R_3 = R_1 || R_2] \Rightarrow$$

$$= I_B \left(R_2 - \frac{R_2 R_2}{R_1 + R_2} - \frac{R_1 R_2}{R_1 + R_2} \right) + \frac{I_{os}}{2} \left(\frac{R_1 R_2 + R_2 + \frac{R_2 R_2}{R_1 + R_2}}{R_1 + R_2} \right)$$

$$= \frac{I_{os} 2(R_2)(R_1 + R_2)}{2(R_1 + R_2)}$$

$$V_o = I_{os} R_2 \ll (I_B + \frac{I_{os}}{2}) R_2$$


\uparrow 10nA \uparrow 100nA ~ 5nA

setting $R_3 = R_1 || R_2$ still helps even if $I_{os} \neq 0$!


Generalized Circuit Elements

Resistor

Linear Resistor

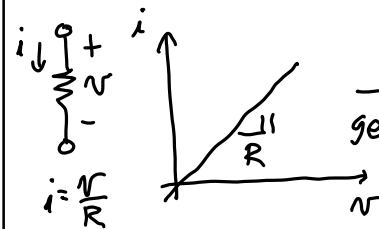

Nonlinear Resistor

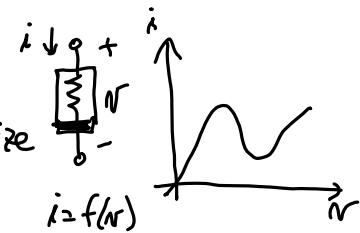

generalize

Capacitor

Linear Capacitor

$q = CV$

Nonlinear Capacitor

$q = f(v)$

⇒ there are also nonlinear inductors → generally not seen in low-to-mid frequency integrated ckt.

Example. Diode → several models, all of which represent nonlinear resistors

A. Ideal -

B. Constant V_D -

↳ diode "on" voltage → usually from 0.5 to 0.7V

C. Actual Diode -

$$i = I_S (e^{v/nV_T} - 1)$$

$I_S \triangleq$ saturation current

$V_T = 25\text{mV} = \frac{kT}{q} \triangleq$ thermal voltage

$n = 1 \text{ or } 2$
 ↗ discrete diodes
 ↘ IC diodes

Diode → not only a nonlinear resistor
 ↳ also includes nonlinear capacitance
 ↳ a more exact model for a diode would look like:

$i_D = f'(v) = I_S (e^{v/nV_T} - 1)$

$Q = f''(v) = q \left(\frac{N_A N_D}{N_A + N_D} \right) A W_{do} \sqrt{1 + \frac{vR}{\phi_j}}$
 [$vR = -v$]