

**UNIVERSITY OF CALIFORNIA**  
**College of Engineering**  
**Department of Electrical Engineering and Computer Sciences**  
**Costas J. Spanos**

**Problem Set #5**  
**Due Wednesday, September 30<sup>th</sup>, 1998**



**EECS105**

**FALL 1998**

Default values: unless the problem states otherwise, use  $\mu_n C_{ox} = 50 \mu A/V^2$ ,  $\mu_p C_{ox} = 25 \mu A/V^2$ ,  $V_{Tn} = 1 V$ ,  $V_{Tp} = -1 V$ ,  $\lambda_n = 0$ ,  $\lambda_p = 0$ .

1. Take a look at the gorgeous circuit your TA painstakingly designed in Adobe Photoshop (it's on the next page). It's relatively common in modern circuit design.
  - a. First we'll analyze the NMOS device. Here's a few important numbers for the calculation. The oxide thickness is 100 Angstroms for the whole device. The p-type doping is  $N_a = 10^{17} \text{ cm}^{-3}$ , while the source and drains are  $n^+$  with  $N_d \gg 10^{17} \text{ cm}^{-3}$ . Assume for the time being that  $V_{DS}$  and  $V_{GS}$  are 2 V. Finally  $C_{OV} = .5 \text{ fF}/\mu\text{m}$ . Find these small signal capacitances:  $C_{gs}$ ,  $C_{gd}$ ,  $C_{sb}$ , and  $C_{db}$ . Draw a quick sketch of the small signal model with these capacitances included. You don't need to calculate  $g_m$ ,  $g_{mb}$ , or  $r_0$ .
  - b. Use SPICE to draw the IV characteristics of the NMOS transistor. HINT: use a circuit similar to the one in the textbook, Figure 4.3a. Your graph should be much like 4.3b (without the  $V_{DS}$  line). But make sure to use the correct dimensions!
  - c. Sketch a schematic of the entire circuit, correctly labeling the PMOS and NMOS transistors (you don't need to draw their small signal models). What logic function does this circuit implement?
  - d. Use SPICE to simulate the voltage transfer characteristics --  $V_{out}$  vs.  $V_{in}$  -- of the circuit. Please turn in your \*.cir file and a plot of  $V_{out}$  vs.  $V_{in}$  for  $V_{in} = 0$  to 5 volts.
  - e. (Extra-credit) Maybe you noticed that the two transistors are sized differently. Can you come up with a theory on why the designer would have done this?
2. More MOSFET excitement. You are looking to analyze an NMOS transistor with the following characteristics:  $W/L = 20 \mu\text{m}/3 \mu\text{m}$ ,  $V_{GS} = 2 V$ ,  $V_{DS} = 3.5 V$ ,  $V_{BS} = 0 V$ .
  - a. Find the DC drain current  $I_D$ .
  - b. Now a small signal  $v_{gs}(t) = 20 \text{ mV} \cos(2\pi \cdot 1000 \cdot t)$  is added in series with  $V_{GS}$ . What is the small-signal drain current  $i_d(t)$ ? You can ignore  $g_{mb}$  and  $r_0$  for this calculation (assume they are zero).
  - c. Plot the total current  $i_D(t)$  vs. time (for  $t=0$  to 3 ms) from the answers in part (a) and (b).

  3. Occasionally analog circuits require large, voltage-controlled resistors. Design a NMOS transistor with a resistance of  $1\text{ M}\Omega$  for  $V_{GS} = 1.5\text{ V}$  (see Figure 3a). Your process parameters: the minimum feature size is  $2\text{ }\mu\text{m}$ , the substrate doping  $N_a = 10^{17}\text{ cm}^{-3}$ ,  $C_{ox} = 1.42\text{ fF}/\mu\text{m}^2$ ,  $C_{OV} = .5\text{ fF}/\mu\text{m}$ , and the poly gate is  $n^+$ .
- How would you size the NMOS, i.e. what should its width and length be?
  - Find the capacitance between the channel and the gate, and between the gate and the drain? What is the total capacitance due to these two caps? HINT: I know we haven't given you a formula for the first capacitance, but try to visualize what area it represents capacitance over...it's simple when you picture the transistor!
  - Now think of the transistor as a low-pass RC filter (see Figure 3b). Find the break (-3 dB) frequency using the resistance and the two capacitance's solved for above . HINT: For those who haven't taken EECS 120: the break frequency for this device will occur at  $\omega = 2\pi f = RC^{-1}$ . This should help **a lot!**



Please visit our web site: <http://www-inst.EECS.Berkeley.EDU/~ee105/>

Please post your questions on our newsgroup: [ucb.class.ee105](mailto:ucb.class.ee105)

Please return your homework in 558 Cory Hall, to Cheryl Craigwell ([cmc@eecs](mailto:cmc@eecs), 642-1237, fax 642-2739), by 11am of the due date. Late homeworks will not be graded.