

4. For the next stage in your education you will compare a bipolar and MOS voltage source. The two sources are shown in Figure 4. $I_{REF} = 100 \mu A$, and the device characteristics are as follows:
- BJT Characteristics: $I_S = 10^{-15} A$, $\beta_F = \beta_0 = 100$, $V_A = 20 V$.
- MOS Characteristics: $W/L = 20/2$, $V_{Th} = 0.7 V$, $\lambda_n = 0.03 V^{-1}$
- Find an expression for V_{OUT} as a function of I_{OUT} in the bipolar case, and find its explicit value for $I_{OUT} = 0$. This time do NOT neglect I_B .
 - Now solve for V_{OUT} in the MOS case.
 - Solve for the incremental source resistance in the BJT.
 - Solve for the incremental source resistance in the MOS.

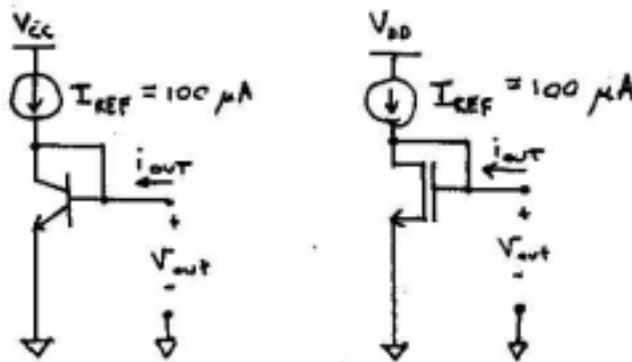


Figure 4.

5. Last but not least, inspect the cascode current source in Figure 5. For the questions, assume that the W/L ratio of all devices is 10 and that $I_{OUT} = 100 \mu A$. The PMOS device characteristics are as follows: $V_{Tp} = -0.7 V$ and $\lambda_p = 0.03 V^{-1}$. Assume that all bulk connections are tied to the source.
- Calculate the incremental source resistance of the current source.
 - If I_{OUT} is required to be $20 \mu A$, what is the new W/L of devices M_2 and M_{2B} assuming that I_{REF} remains at $100 \mu A$?
 - Assuming part (b) is implemented, what is the new incremental source resistance?

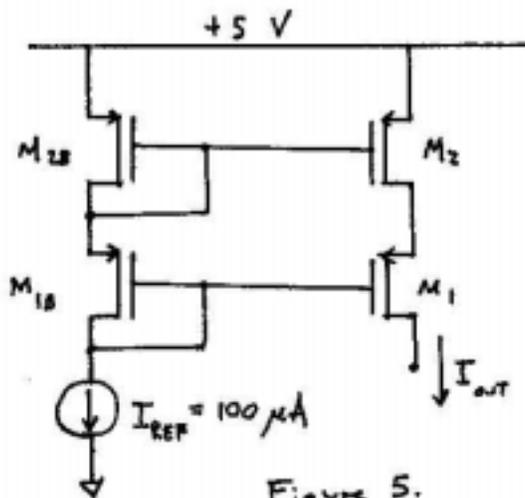


Figure 5.

Notice the new Date and Time for the 2nd Midterm: Friday 6-7:30pm, 20th of November in Sibley
For the latest news, visit our web site: <http://www-inst.EECS.Berkeley.EDU/~ee105/>
Please post your questions on our newsgroup: ucb.class.ee105
Please return your homework in 558 Cory Hall, to Cheryl Craigwell (cmc@eecs, 642-1237, fax 642-2739), or in class by 11:10am of the due date. Late homeworks will not be graded.