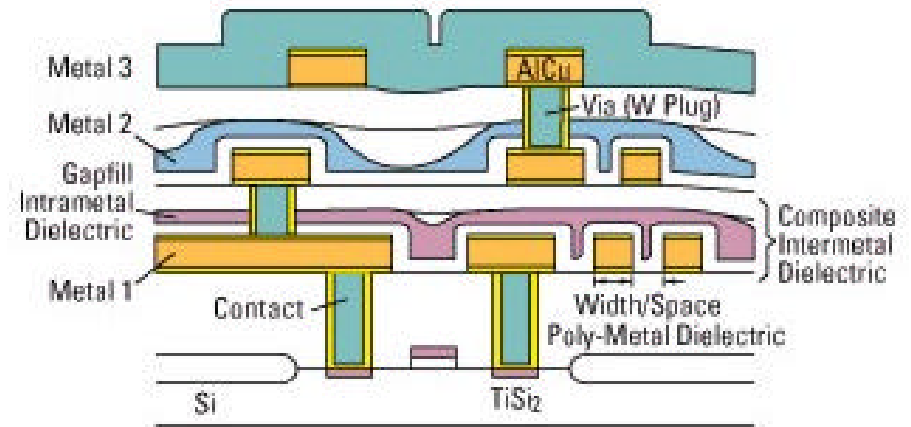


Lecture 2, February 19, 2001

EECS 105 Microelectronics Devices and Circuits, Spring 2001

Andrew R. Neureuther

Topics:
Value Added by Circuits



**Reading: (review of EE
40), HS 1, 8.2.2, 9.1**


How Does a Digital Camera Work?

- Physics (semiconductor junction)
 - » **Photons => charge => voltage**
- Analog Circuits
 - » **Amplify, gray level conversion**
- Digital Circuits
 - » **Encode, store, move, play**
- Analog Circuits
 - » **Display drivers**

Model for Photo Detector


- Film sensitivity $\sim 3 \times 10^4$ photons
 $\Delta Q_S = 3 \times 10^4$ electrons
- Junction capacitance $C_J \sim 30$ fF
- $\Delta V_S = \Delta Q / C_J = 3 \times 10^4 \times 1.6 \times 10^{-19} / 3 \times 10^{-14}$
 $\Delta V_S = 160$ mV
- Series resistance $R_S = 200$ Ohms
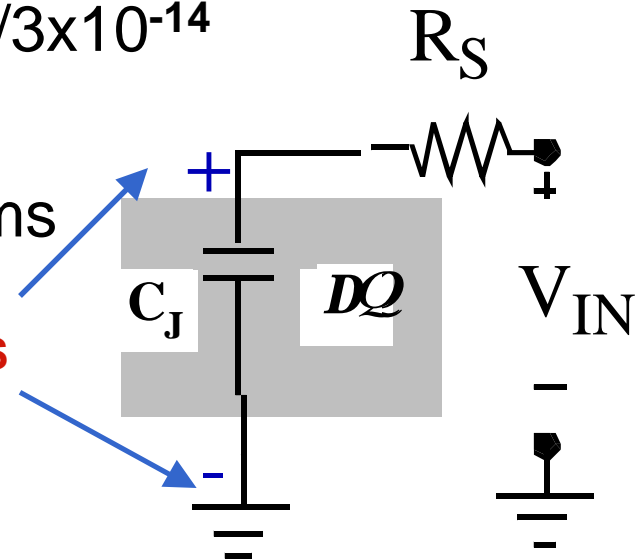
$$\begin{aligned} V_{\text{SOURCE}} &= V_{\text{BIAS}} + \Delta V_S \\ &= V_{\text{BIAS}} + \Delta Q / C_J \end{aligned}$$



Current to Voltage Conversion

● Op-Amp Circuit

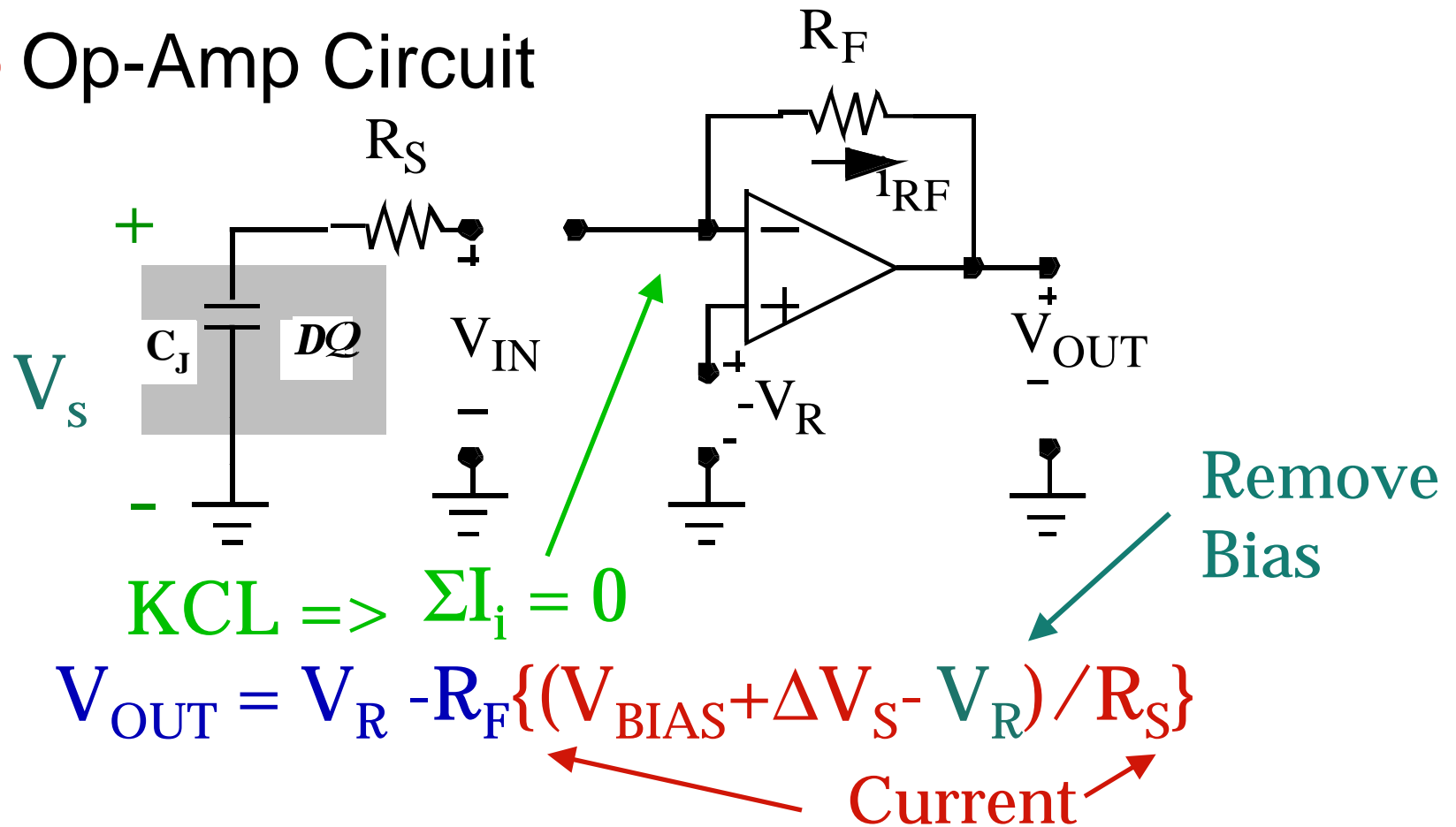

Op-Amps are Ideal but EE 105 is Not

- Ideal Op-Amp properties
 - » No input current (**Infinite R_{IN} !**)
 - » $V_- = V_+$ (**Infinite voltage gain!** With feedback) ← **Topic for EE 140**
- **Circuit configurations** give the leverage to build nearly ideal circuits from devices with less than ideal properties.

How do we get these?


Don't forget about Op-Amps from EE 40 as in EE 105 we will use Op-Amps to study circuit concepts like frequency-response.

Back to the Future

- 3 MegaPixels with 3 colors requires nearly 10M Op-Amps.
- If each draws 100 μA , the battery must supply 1000A. **A car battery would last only 3 minutes!**
- Solution: Analog switch array of 10 levels and 2^{10} – 1024 factor of sharing.

Resistance and Capacitance of 10 analog switches in series

**1024
Photodiodes**

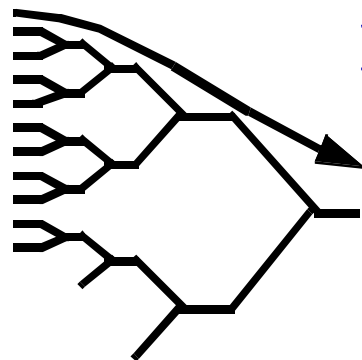


Amplifier

$$R_{SA} = 10 * 10 \text{ k}\Omega = 100 \text{ k}\Omega$$

$$C_{SA} = 10 * 30 \text{ fF} = 300 \text{ fF}$$

Model For Switching and Amplifier

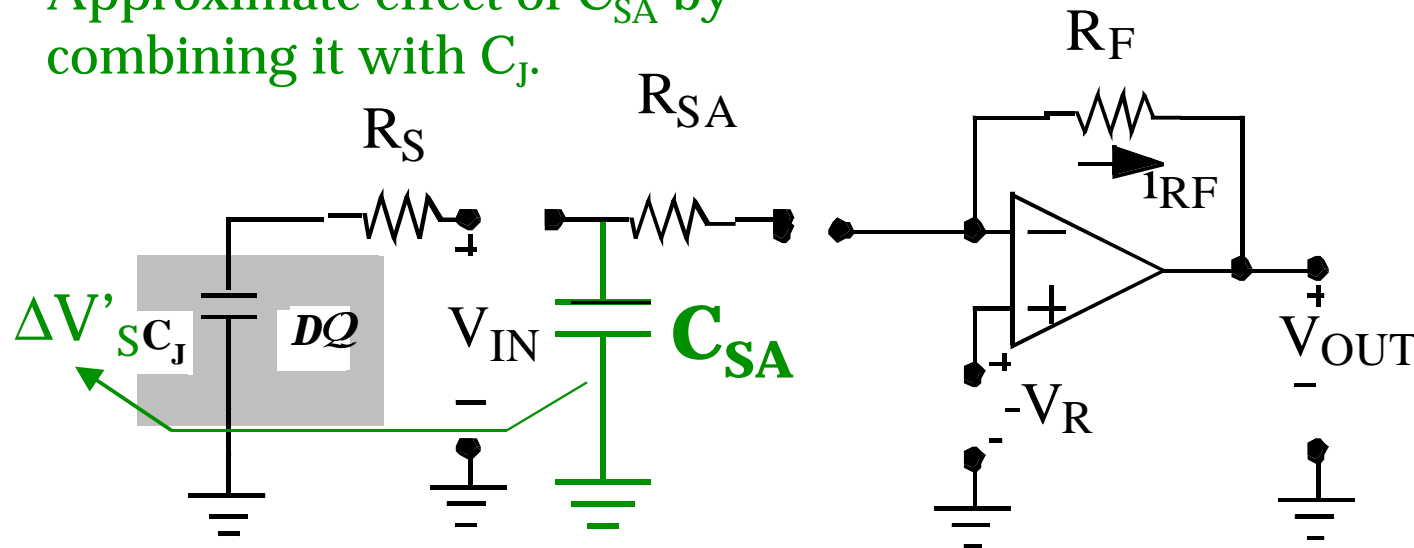Approximate effect of C_{SA} by combining it with C_J .




$$V_{OUT} = V_R - R_F \{ (V_{BIAS} + \Delta V'_S - V_R) / (R_S + R_{SA}) \}$$

$\Delta V'_S$ is 10 times smaller due to C_{SA} and is now about 15 mV

From 200 Ohms to 100,200 Ohms => 500X smaller signal!

Simple EE 105 Amplifier
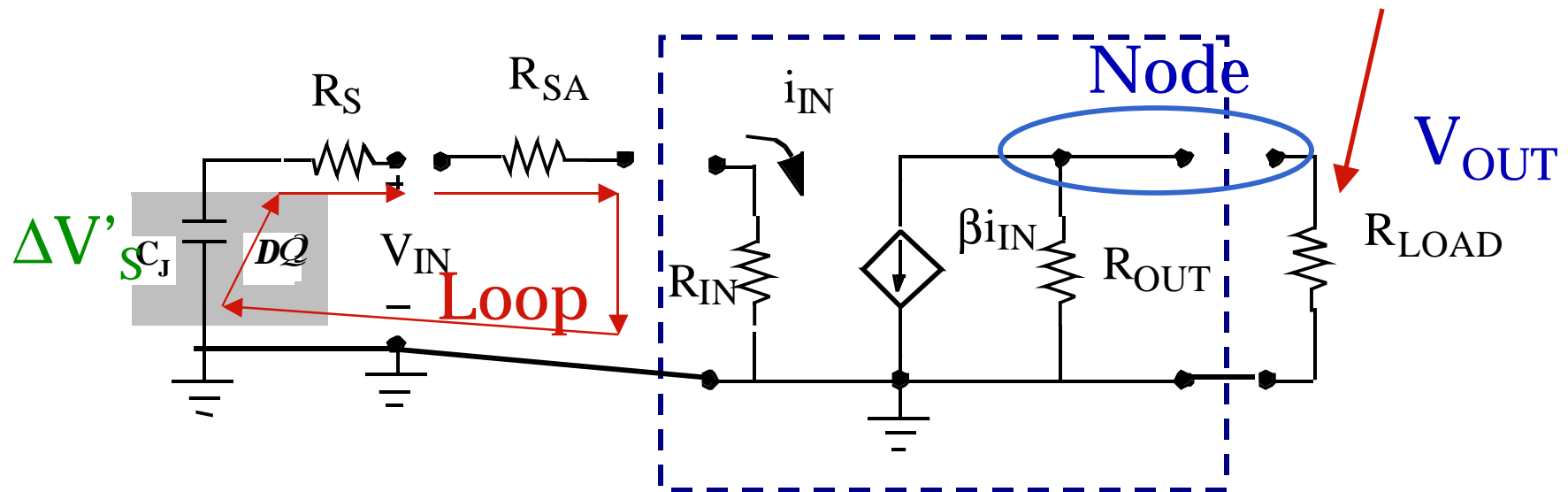
$$R_{IN} = 30 \text{ k}\Omega \quad \beta = 100 \quad R_{OUT} = \text{Infinite} \quad R_{LOAD} = 10 \text{ k}\Omega$$



$$V_{OUT} = \left[\Delta V'_s / (R_S + R_{SA} + R_{IN}) \right] (-\beta) R_{LOAD} = 115 \text{ mV}$$

$$\Sigma V_i = 0 \Rightarrow i_{IN} \quad \Delta V'_s = 15 \text{ mV}$$

Analog Integrated Circuits

Overview and Circuit Value Added

$$\Sigma I_i = 0 \text{ with } R_{OUT} = \text{Infinite} \Rightarrow$$

Circuit to Hold the Charge Longer

- Problem C_J Discharges Quickly


$$T = C_J * R_{SA} = 30\text{fF} * 100\text{k}\Omega = 3 * 10^{-10} \text{ Sec}$$

- Solution: Add Value Through Circuit
Design of High Input Resistance
Amplifier

High Input Impedance Circuit

$$R_E = 30 \text{ k}\Omega \quad R_{IN \text{ EQ}} = R_{IN} + (\beta + 1)R_E = 3.06 \text{ M}\Omega$$

23.5 times less current

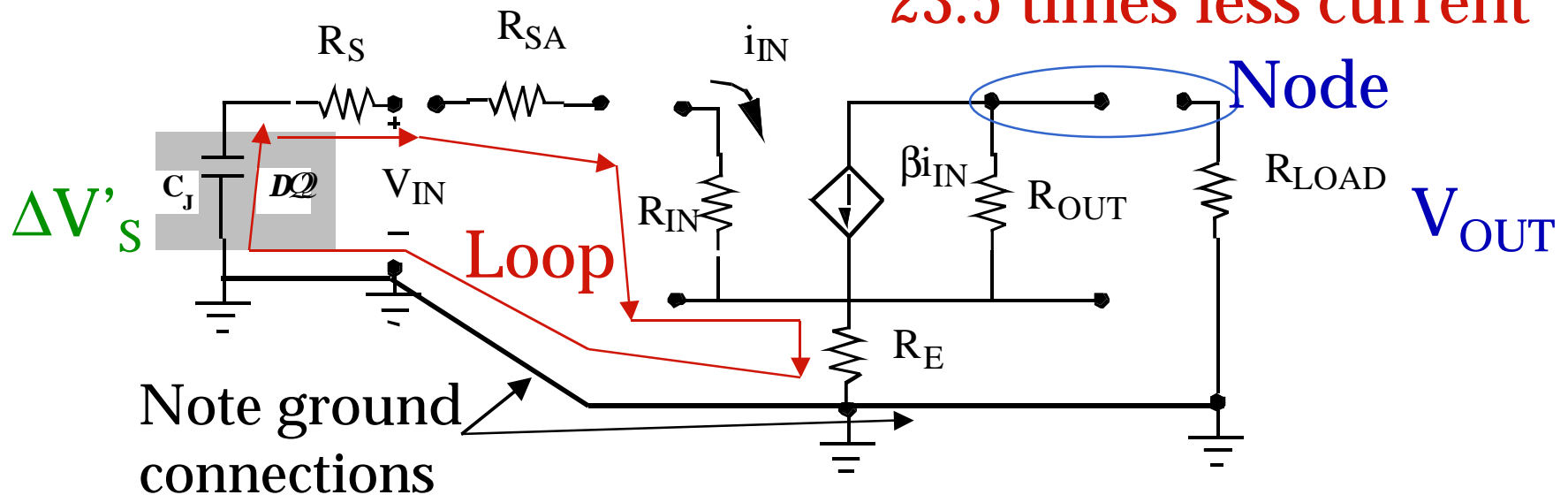


$$V_{OUT} = \left[\frac{\Delta V'_s}{(R_S + R_{SA} + R_{IN \text{ EQ}})} \right] (-\beta) R_{LOAD} = 5 \text{ mV}$$

$$\Sigma V_i = 0 \Rightarrow i_{IN}$$

23.5 times smaller gain

Adding a Second Stage

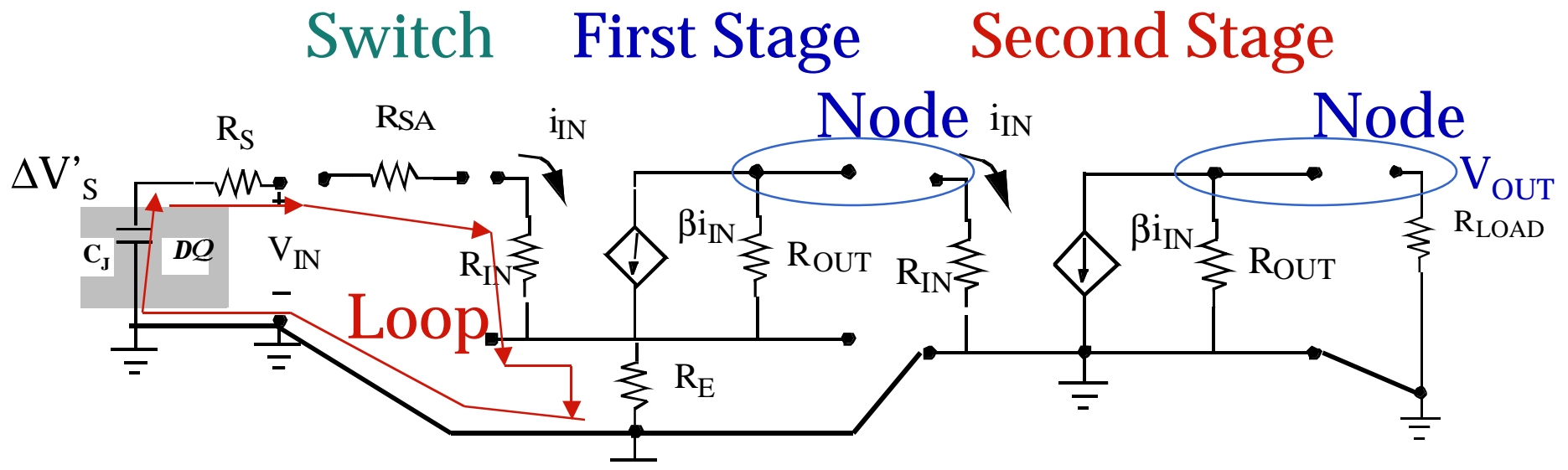


$$V_{OUT} = [\Delta V'_S / (R_S + R_{SA} + R_{IN\ EQ1})] (-\beta_1) R_{in2}$$

$$(1/R_{in2}) (-\beta_2) R_{OUT} = 490 \text{ mV}$$

Visualizing as a Multistage Amplifier

Error fixed 1/21/00

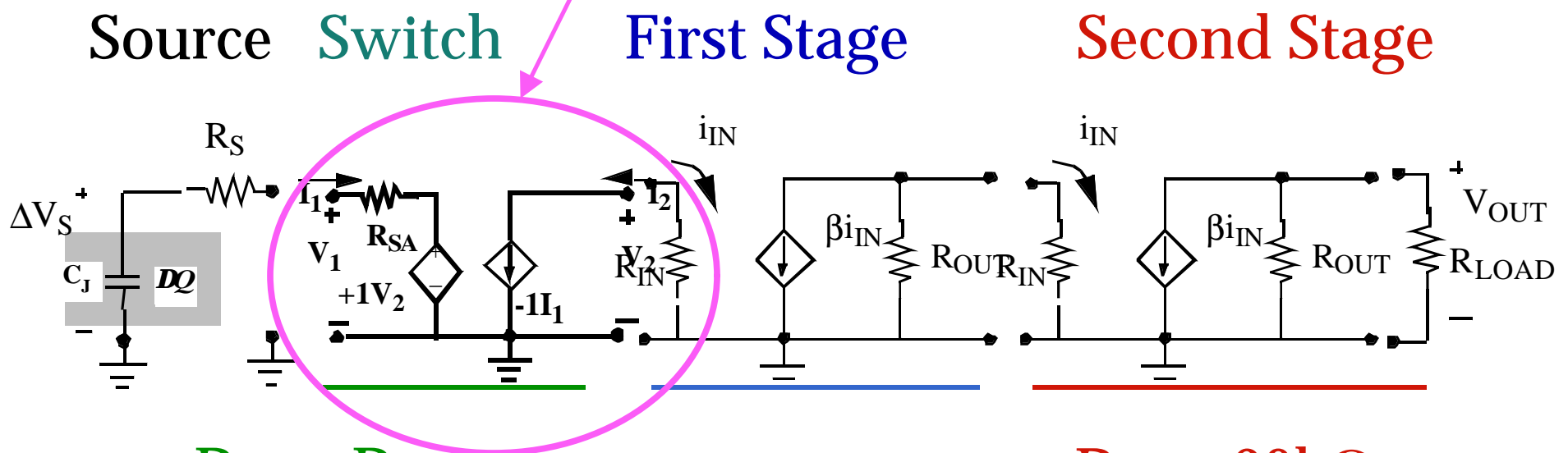

$$R_{IN} = R_{SA}$$

$$A_I = 1, A_O = 1$$

$$R_{OUT} = R_{SA}$$

$$R_{IN} = 3.06M\Omega$$

$$\beta = 100$$


$$R_{OUT} = \text{infinite}$$

$$R_{IN} = 30k\Omega$$

$$\beta = 100$$

$$R_{OUT} = \text{infinite}$$

Visualizing as an Equivalent Two-Port

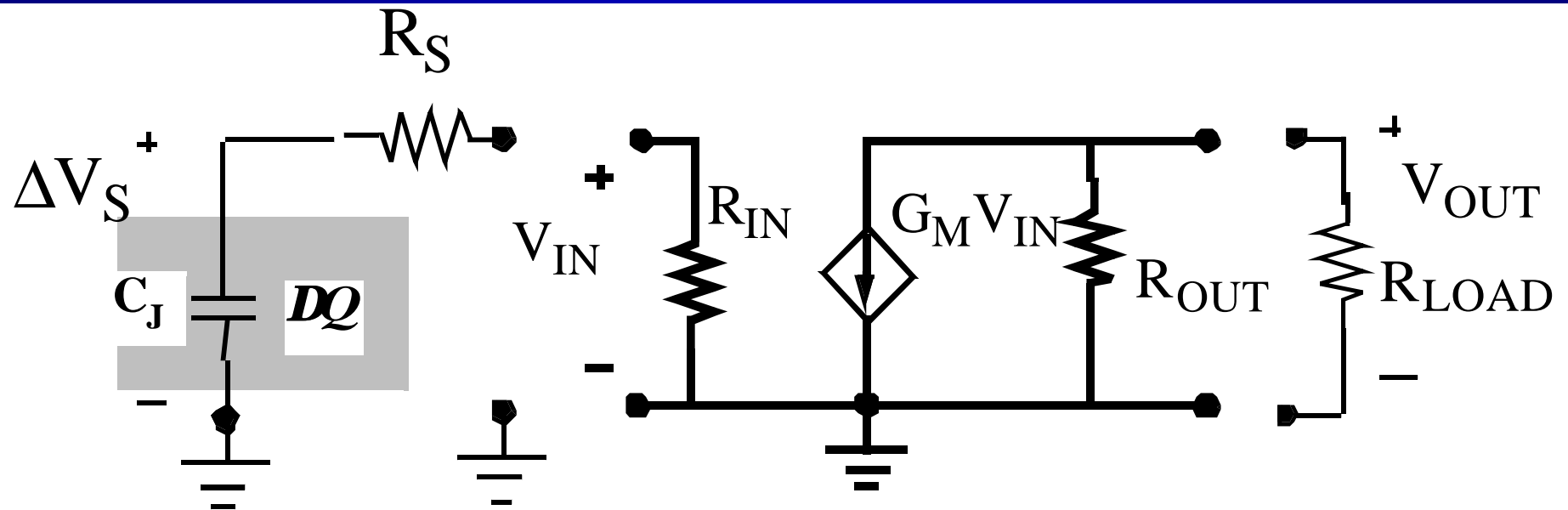


$$R_{IN} = R_{SA} + R_{IN\ EQ1}$$

$$G_M = [1 / (R_S + R_{SA} + R_{IN\ EQ1})] (-\beta_1) R_{in2} (1 / R_{in2}) (-\beta_2)$$

$$R_{OUT} = \text{Infinite (Assumed Initially)}$$


Multistage Amplifiers

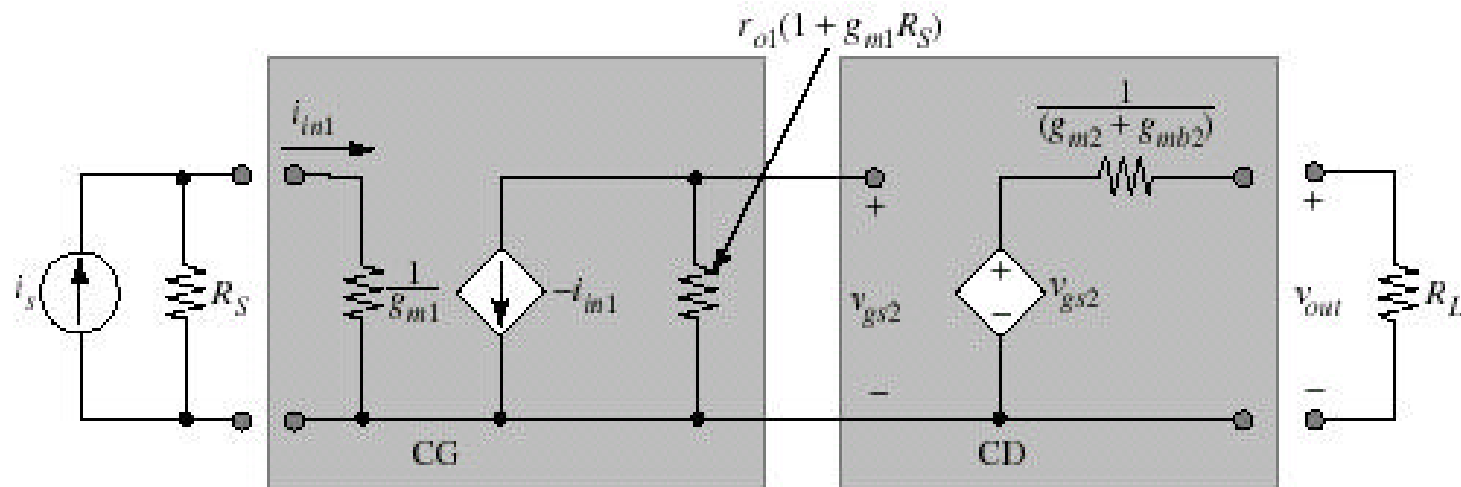

This example from the reading
in Chapter 8 this week.


Classification of Two-Port Amplifiers

Voltage Amplifier

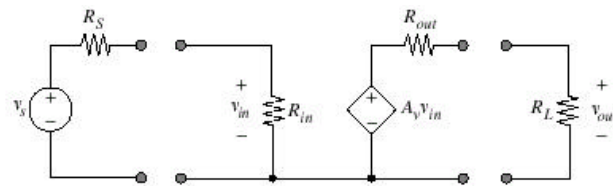


Voltage

Current Amplifier

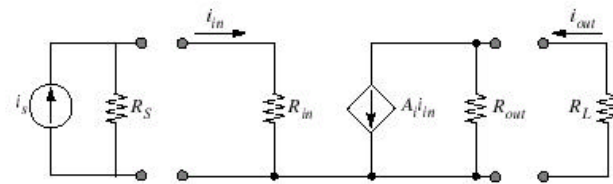


Current

Transconductance Amplifier

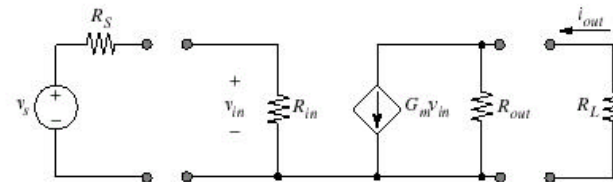


Transconductance

Transresistance Amplifier

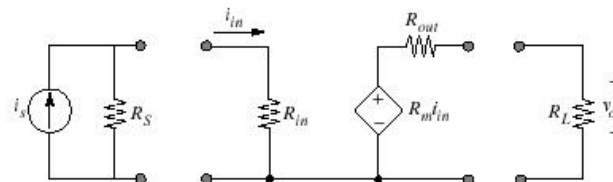


Transresistance

What Goes in the Amplifier Box

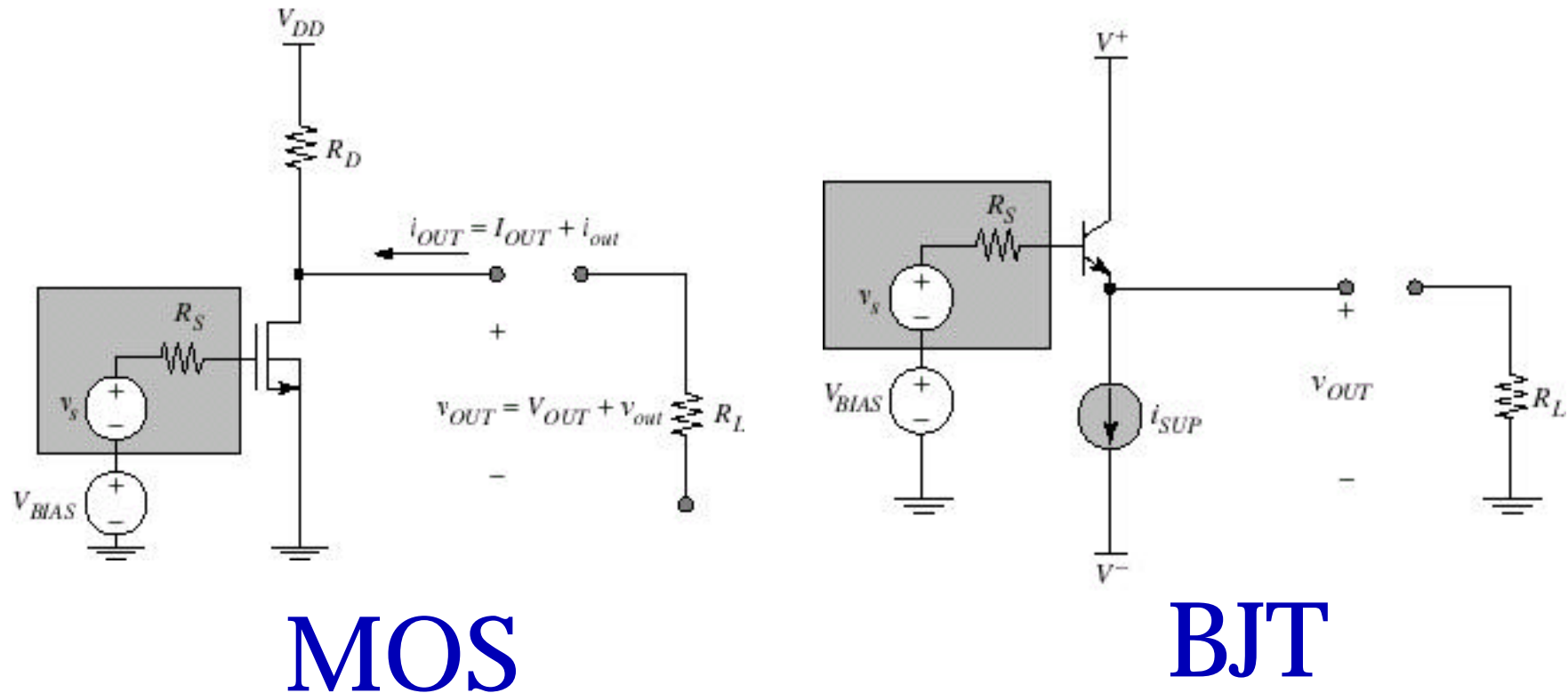


Material from Chapter 8 from week 11.

Small Signal Models for Transistors

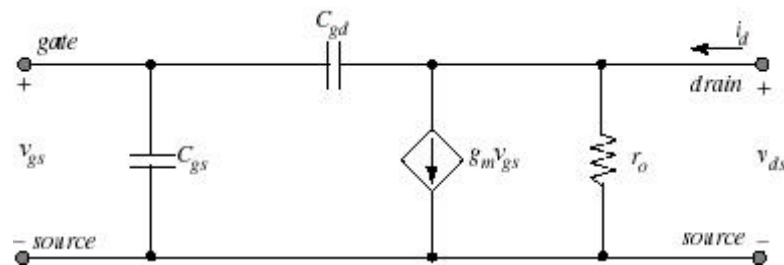

MOS


Week 5

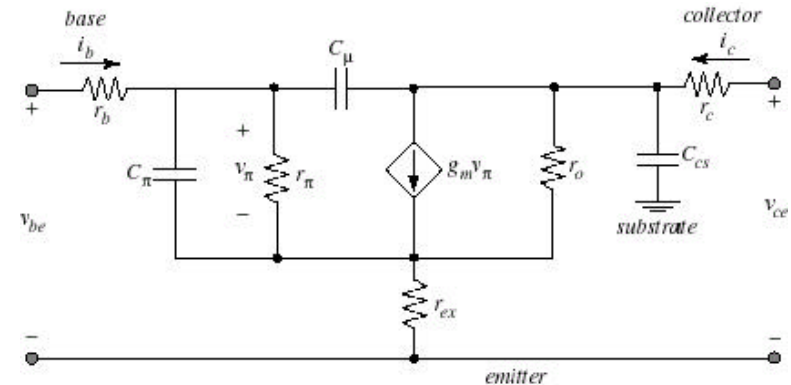

BJT


Week 8

Layout of Transistors

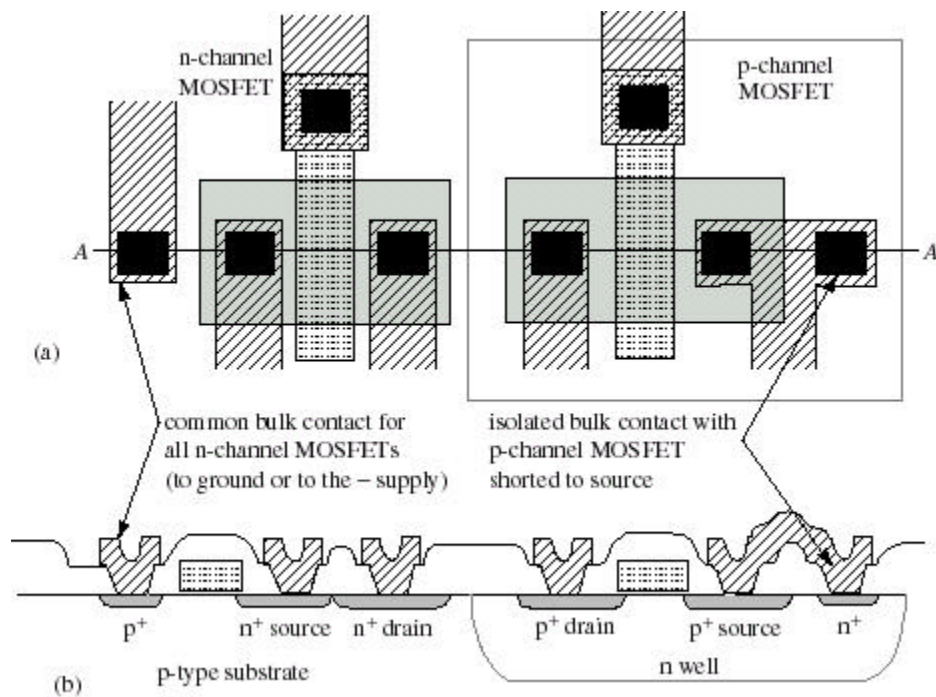

Week 2

Analog Integrated Circuits

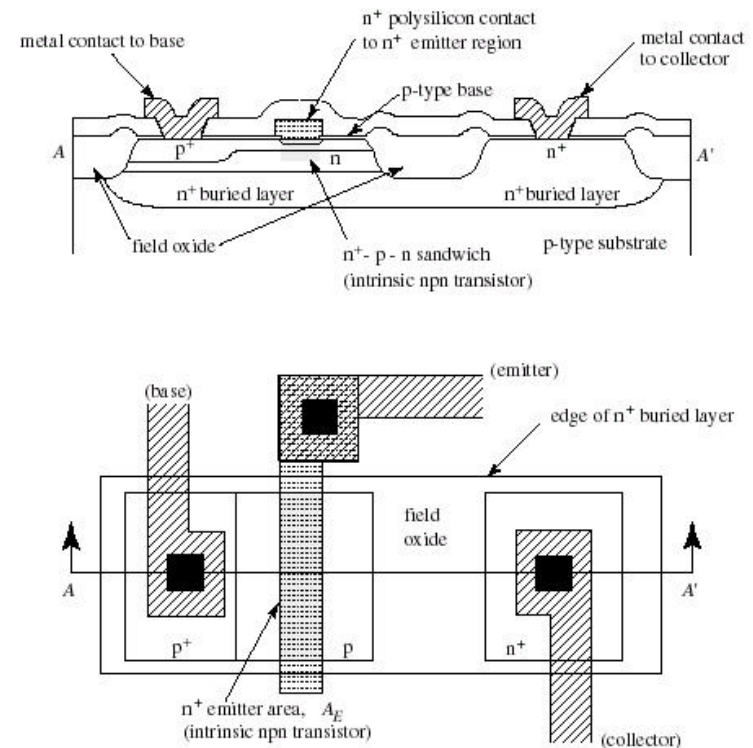

Week 8

Overview and Circuit Value Added