

# Course Overview

- EE 105 – new version
  - Prerequisite: EECS 40
  - *analog* integrated circuits + basic IC device models needed to design them
  - course incorporates a laboratory
- Related courses :
  - EE 130, 140, 141, 142

# Sinusoidal Function Review

$$v(t) = v \cos(\omega t + \phi)$$

amplitude  
(half of  
peak-to-peak)

frequency  
(radian) ...  $\omega = 2\pi f = 2\pi (1/T)$


phase (degrees  
or radians)

# Graphical Description

$$v_1(t) = v \cos(\omega t)$$

$$v_2(t) = v \cos(\omega t - 45)$$

$$\omega = \frac{2\pi}{T}$$

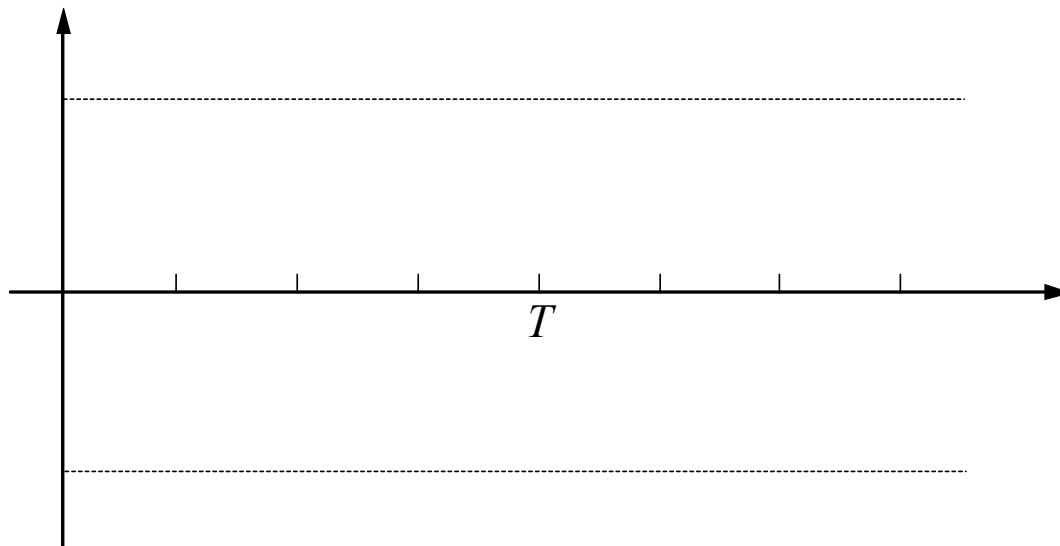


# Why are Sinusoids Important?

- *Any* periodic signal  $v(t)$  can be expressed as a sum of sinusoidal signals by a Fourier series expansion (EECS 20N, EE 120)
- The response of a linear circuit to a sinusoidal input, as a function of its frequency  $\omega$ , leads to insights into the behavior of the circuit.

# Linear Circuits

- *Theorem:* solutions for voltages and currents in a linear circuit (i.e., one consisting of  $R$ ,  $L$ ,  $C$  and dependent sources  $G_m$ ,  $R_m$ ,  $A_v$ , and  $A_i$ ) with a *sinusoidal* signal as the input are:

# RC Circuit with Sinusoidal Input

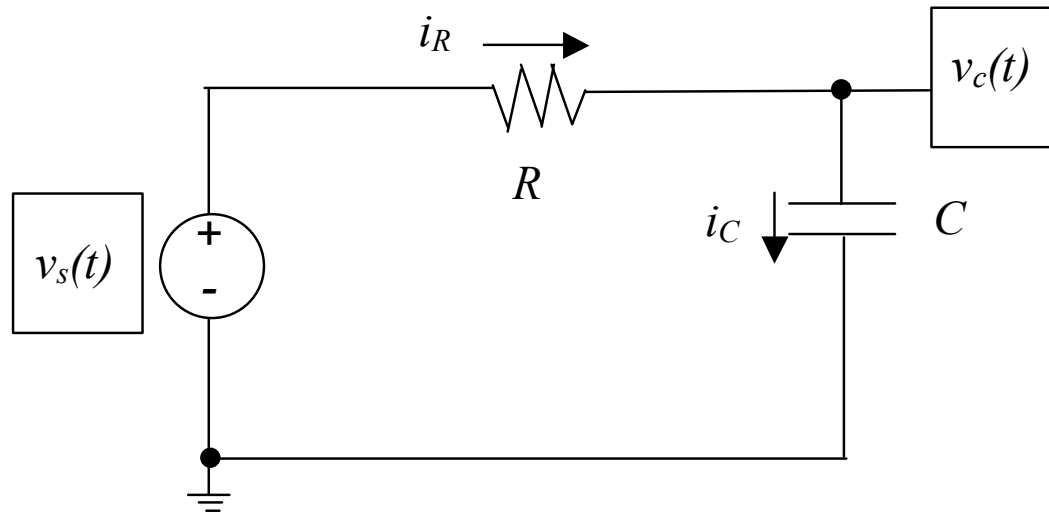

$v_s(t) = V_s \cos(\omega t)$  : set phase of source to zero (use as the reference)


$v_c(t) = V_c \cos(\omega t + \phi)$  : solution is a sinusoidal signal with the same frequency, but with a different amplitude and phase-shifted with respect to the source

# Circuit Analysis

# Circuit Analysis (Continued)



# Graphical Result for Phase $\phi$

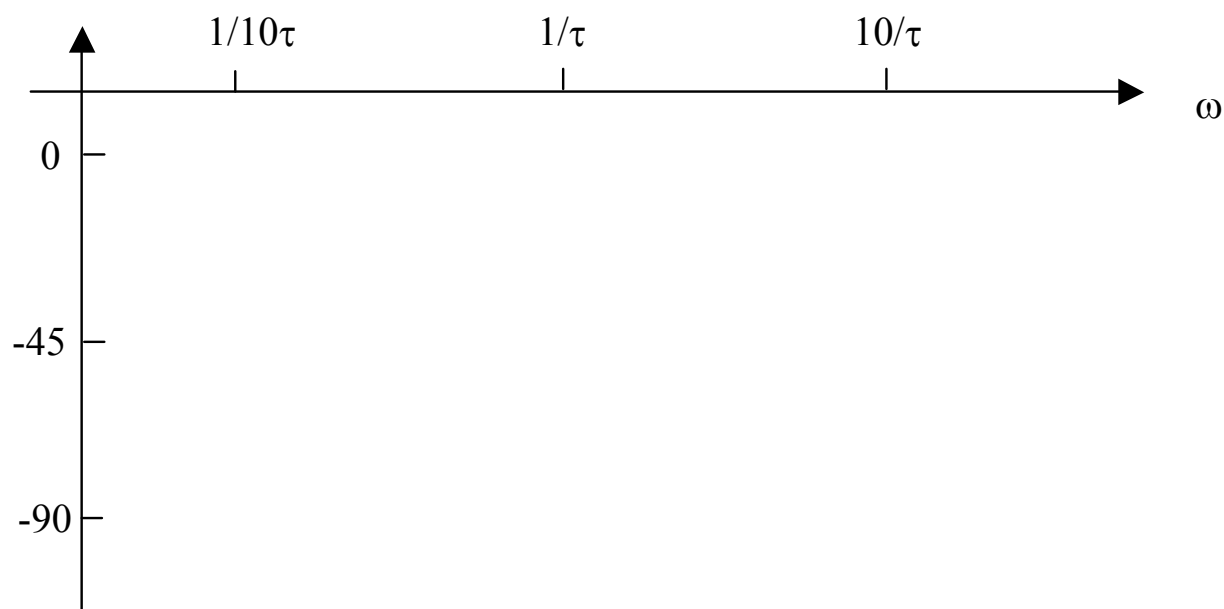

# Graphical Result for Amplitude Ratio

