

# Lecture 15

- Last time:
  - Square-law MOSFET model
  - Linear MOSFET model
- Today :
  - MOSFET small-signal model: three (four) terminal device → complicated!


# Why Find an Incremental Model?

- Signals of interest in analog ICs are often of the form:


$$v_{GS}(t) = V_{GS} + v_{gs}(t)$$

Direct substitution into  $i_D = f(v_{GS}, v_{DS})$  is tedious AND doesn't include charge-storage effects ... pretty rough approximation

# Which Operating Region?

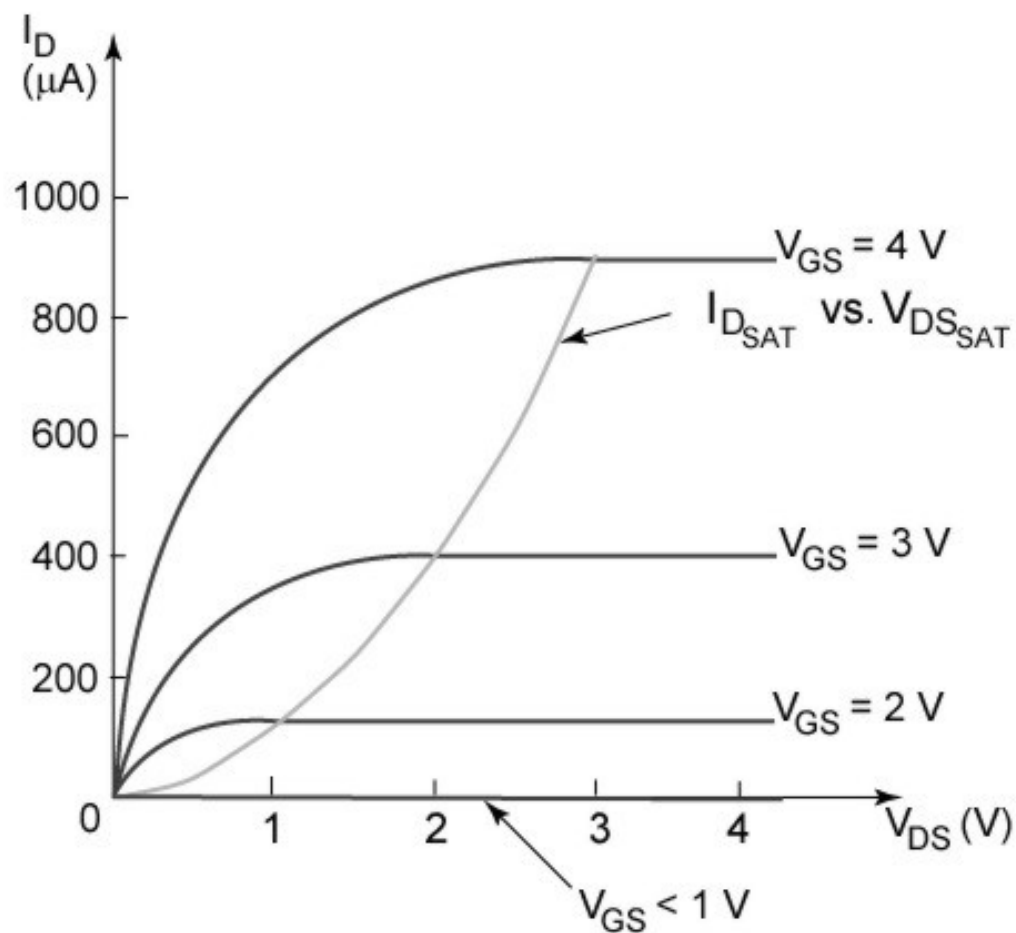

# Changing One Variable at a Time

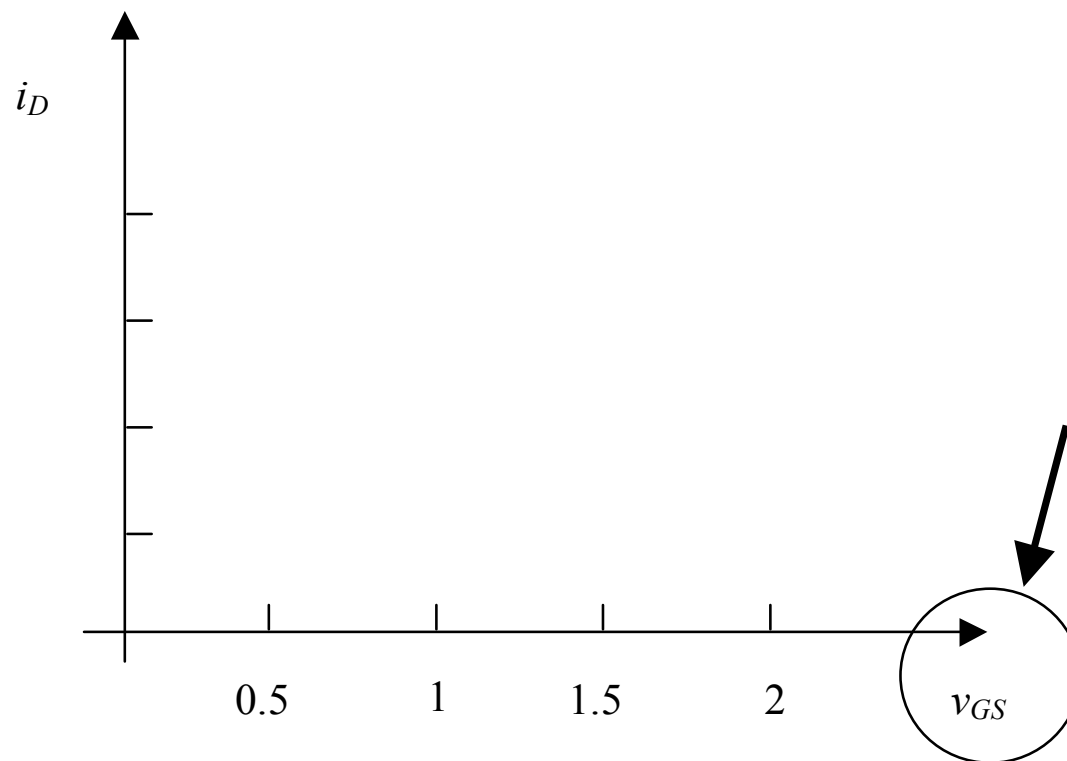

Assumption:  $V_{DS} > V_{DS,SAT} = V_{GS} - V_{Tn}$  (square law)

# The *Transconductance* $g_m$


Defined as the change in drain current due to a change in the *gate-source* voltage, with *everything else constant*

$$g_m = \left. \frac{\Delta i_D}{\Delta v_{GS}} \right|_{V_{GS}, V_{DS}} = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{V_{GS}, V_{DS}}$$

Square-law: MOSFET saturation region

$$i_D = (W / 2L) \mu_n C_{ox} (v_{GS} - V_{Tn})^2 (1 + \lambda_n v_{DS})$$

# Another Way to Find $g_m$

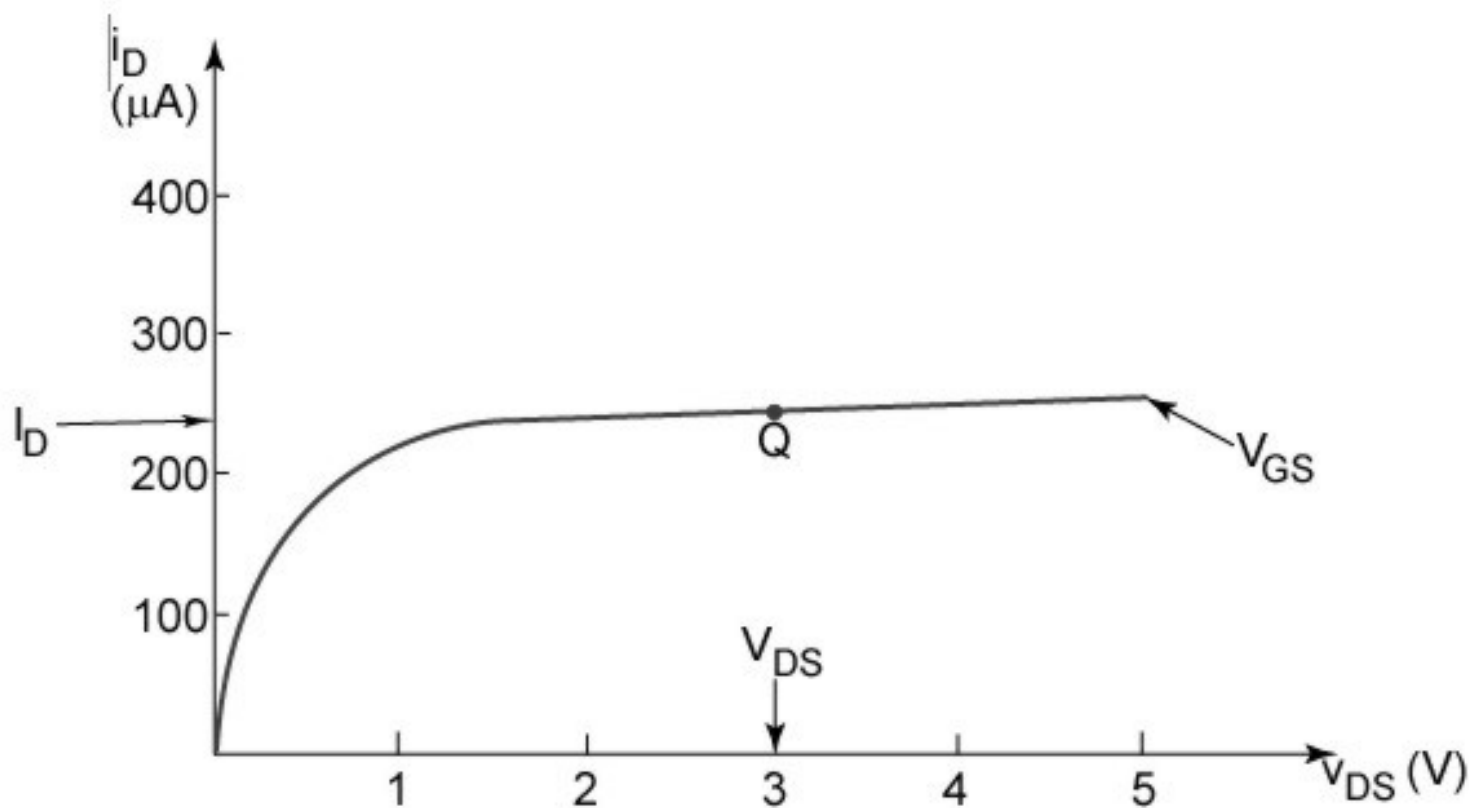

# Evaluating $g_m$

Square-law characteristic: H&S 1<sup>st</sup> Edition


$$g_m =$$

Linear characteristic: better for submicron CMOS

$$i_{D,SAT} = v_{sat} W C_{ox} (v_{GS} - V_{Tn}) (1 + \lambda_n v_{DS})$$
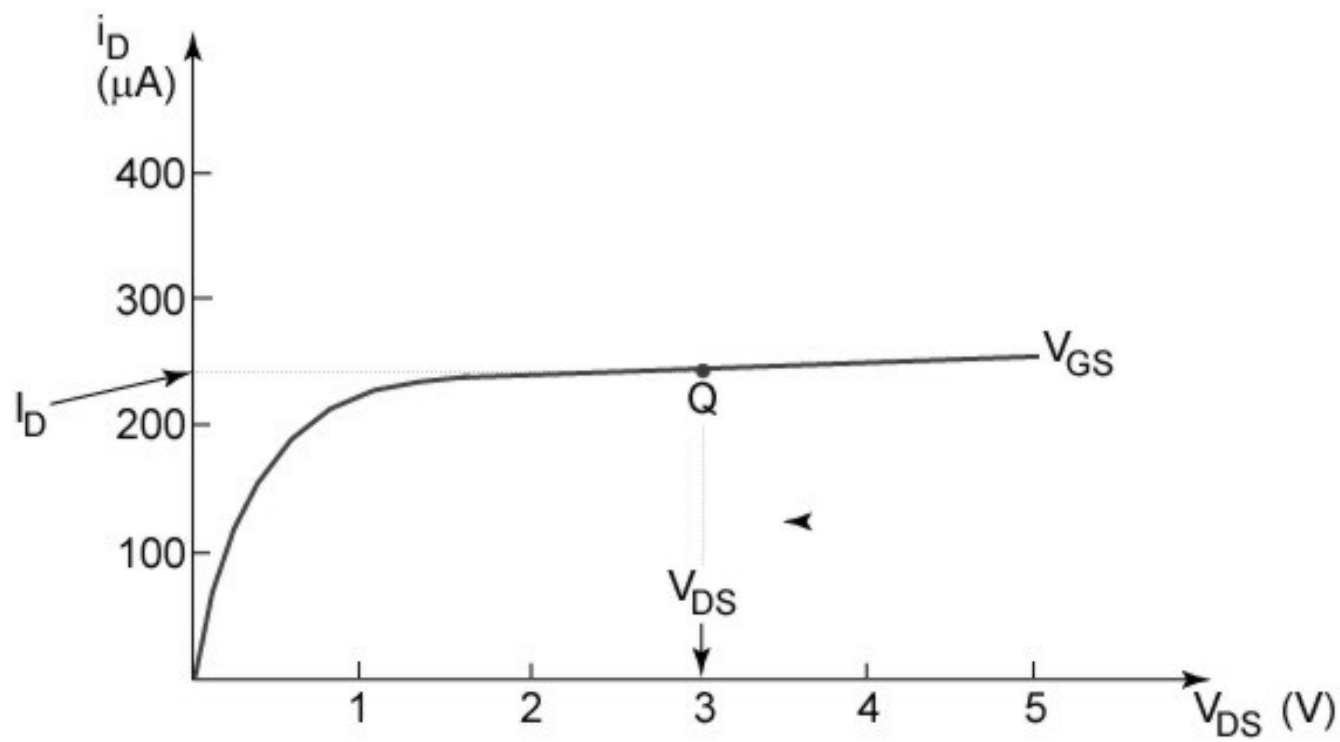
# Output Resistance $r_o$

Defined as the inverse of the change in drain current due to a change in the *drain-source* voltage, with *everything else constant*






# Evaluating $r_o$

$$r_o = \left( \frac{\partial i_D}{\partial v_{DS}} \bigg|_{V_{GS}, V_{DS}} \right)^{-1}$$

Typical value:

# Putting Together a Circuit Model

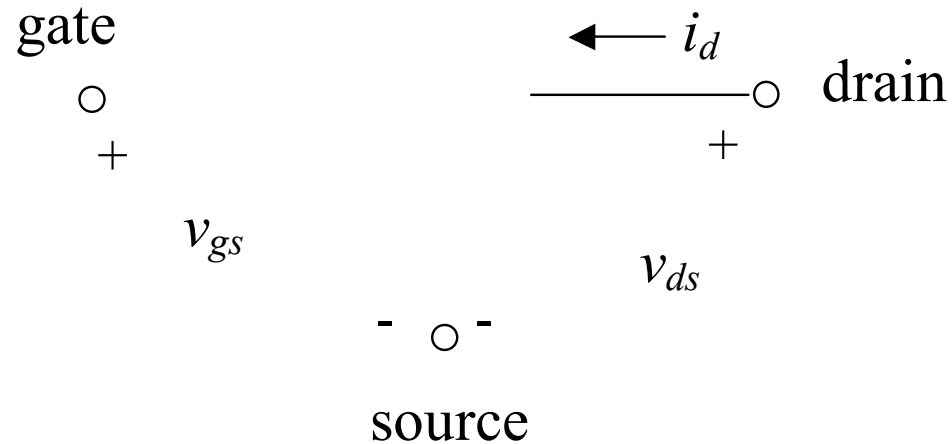

# Role of the Substrate Potential

Need not be the source potential, but  $V_B < V_S$

Effect: changes threshold voltage, which changes the drain current ... substrate acts like a “backgate”

$$g_{mb} = \left. \frac{\Delta i_D}{\Delta v_{BS}} \right|_Q = \left. \frac{\partial i_D}{\partial v_{BS}} \right|_Q$$

$$Q = (V_{GS}, V_{DS}, V_{BS})$$