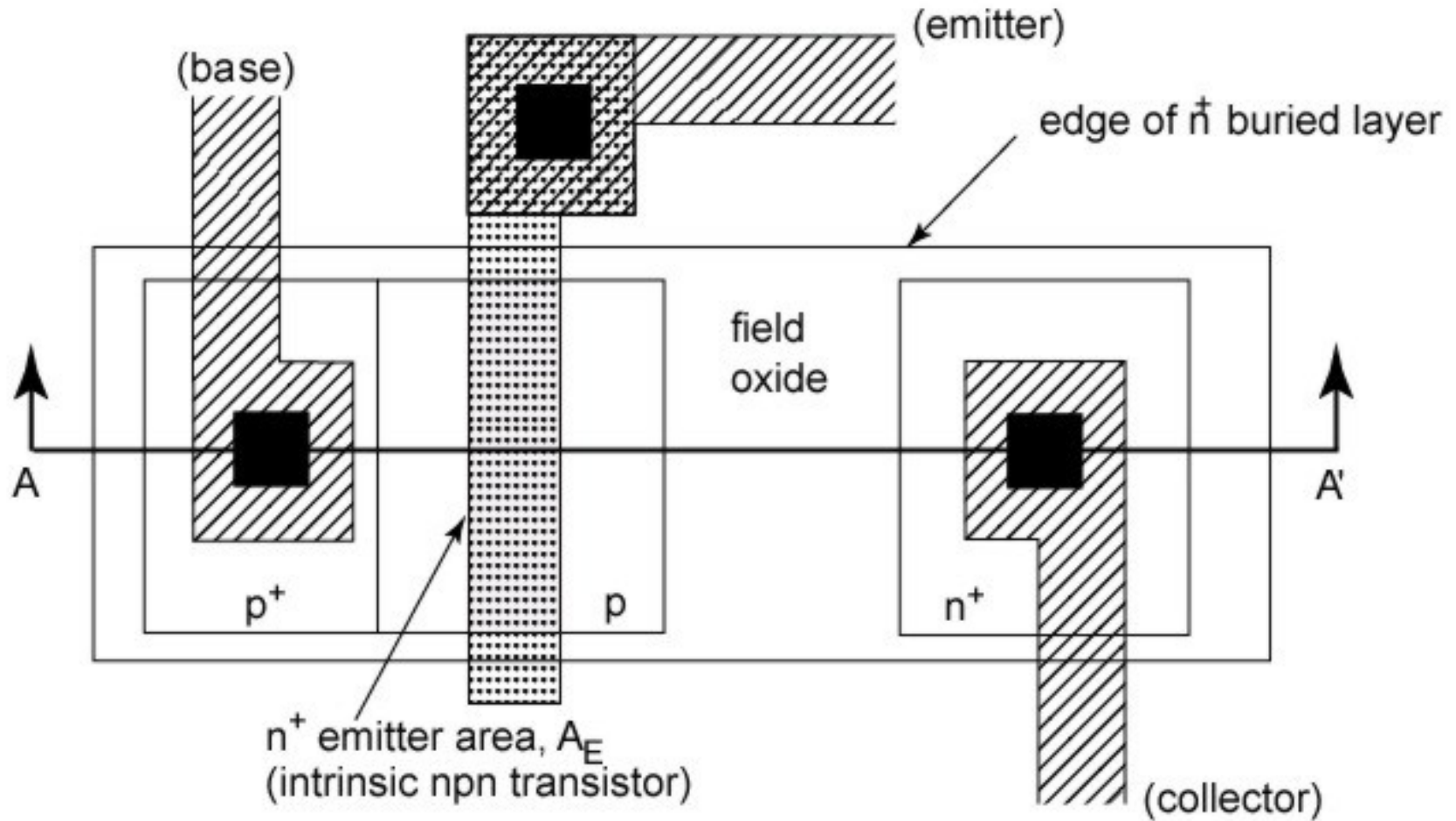



Lecture 19

- Last time:
 - DC and small-signal model of the forward-biased diode
- Today :
 - the npn bipolar junction transistor (BJT):
large-signal characteristics


nnp Bipolar Transistor Layout




BJT Symbol

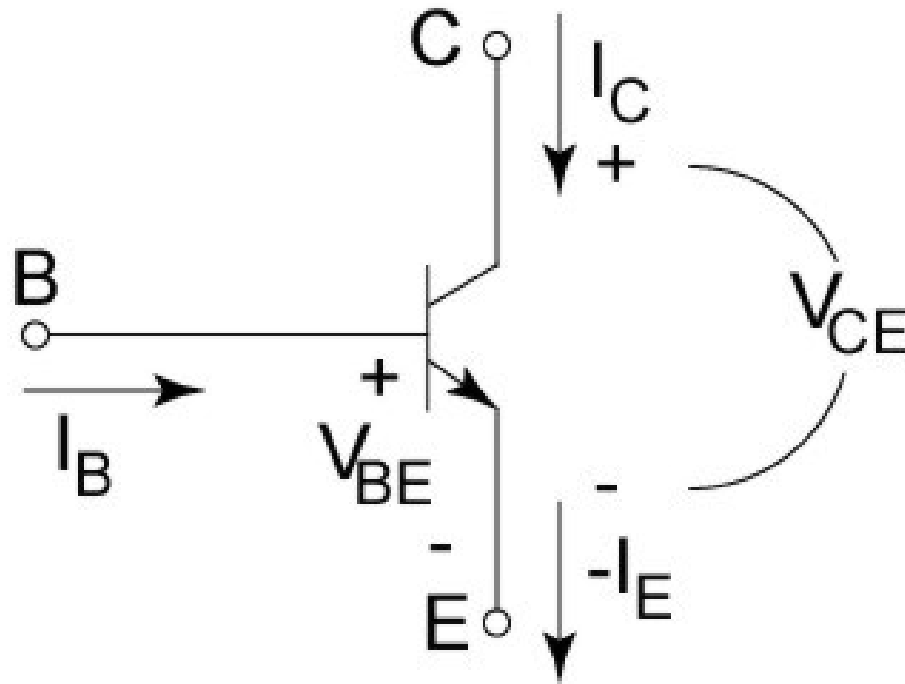

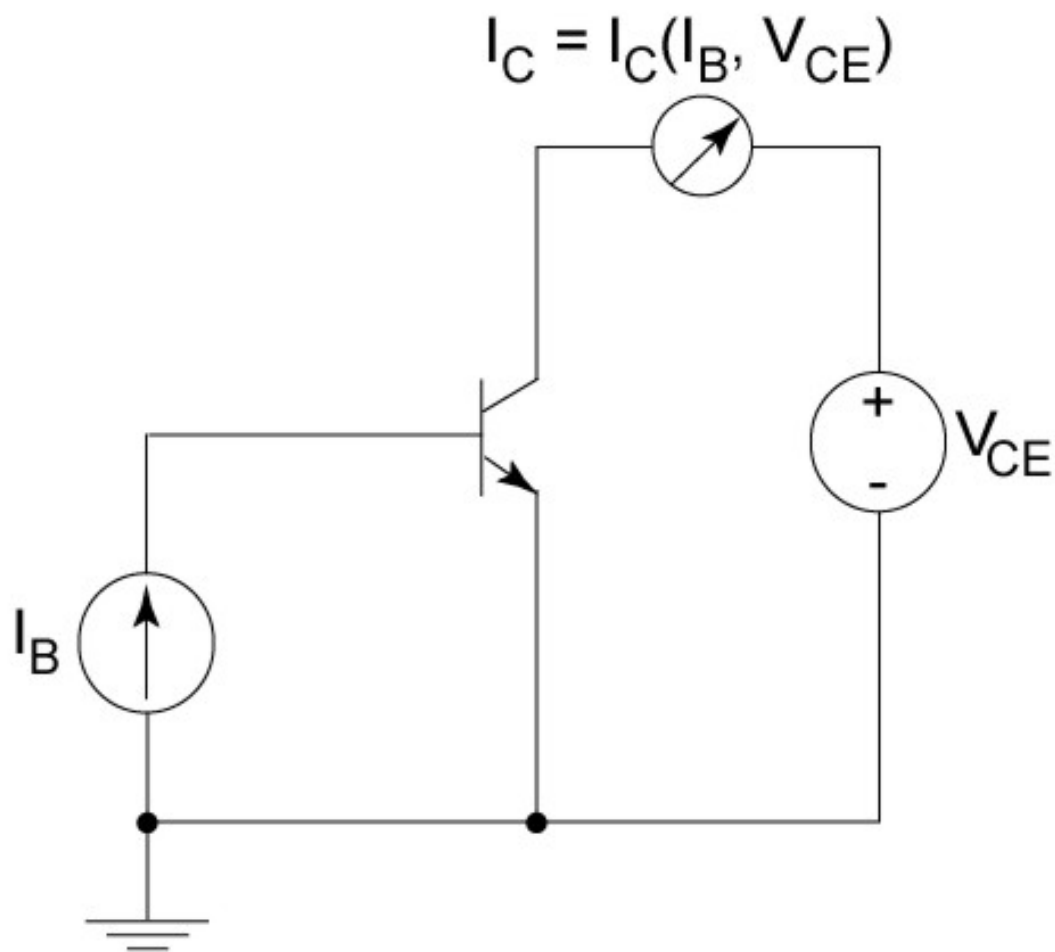
Measuring the BJT's Collector Characteristics




Collector Characteristics

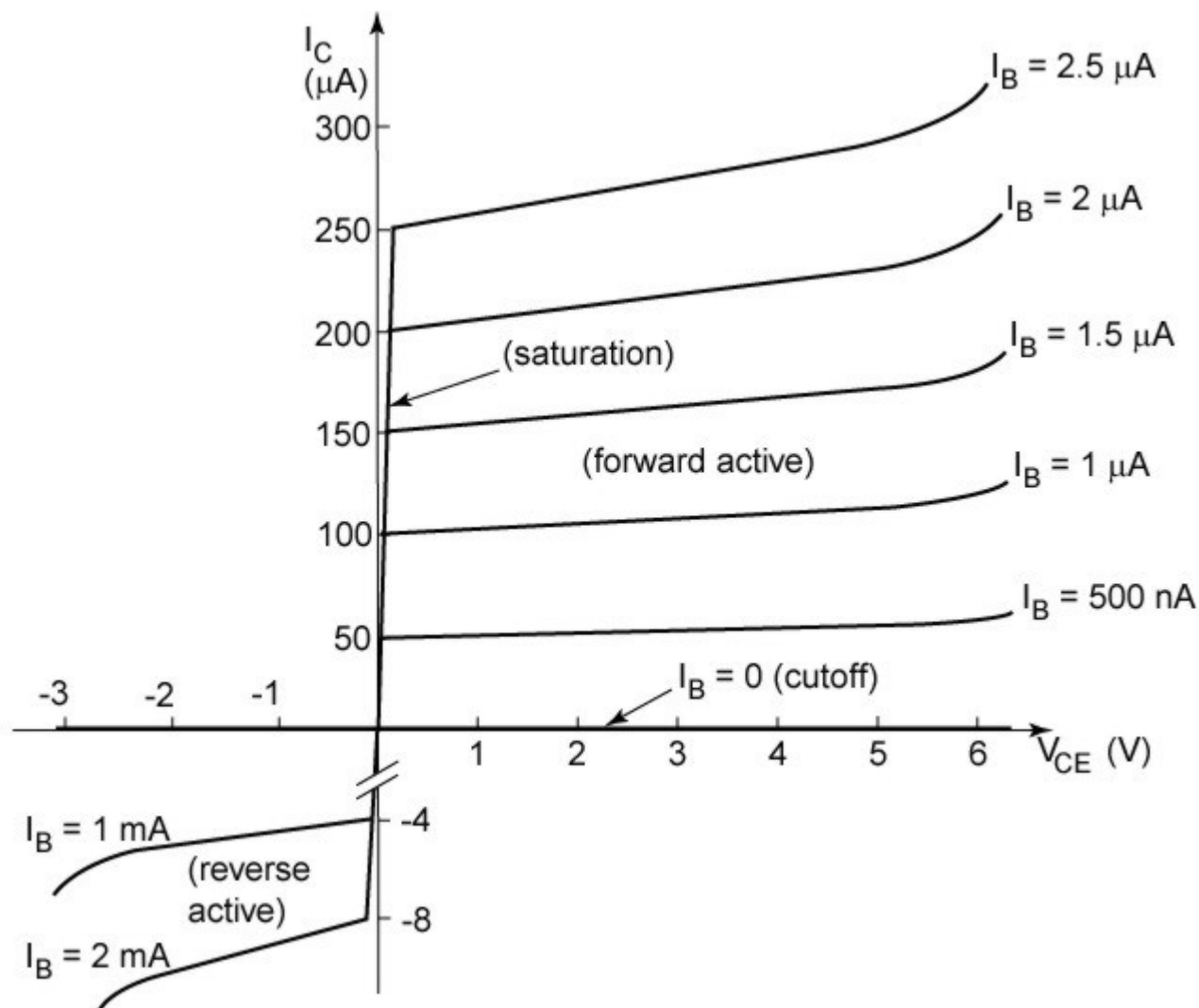


Base-Emitter Voltage Control

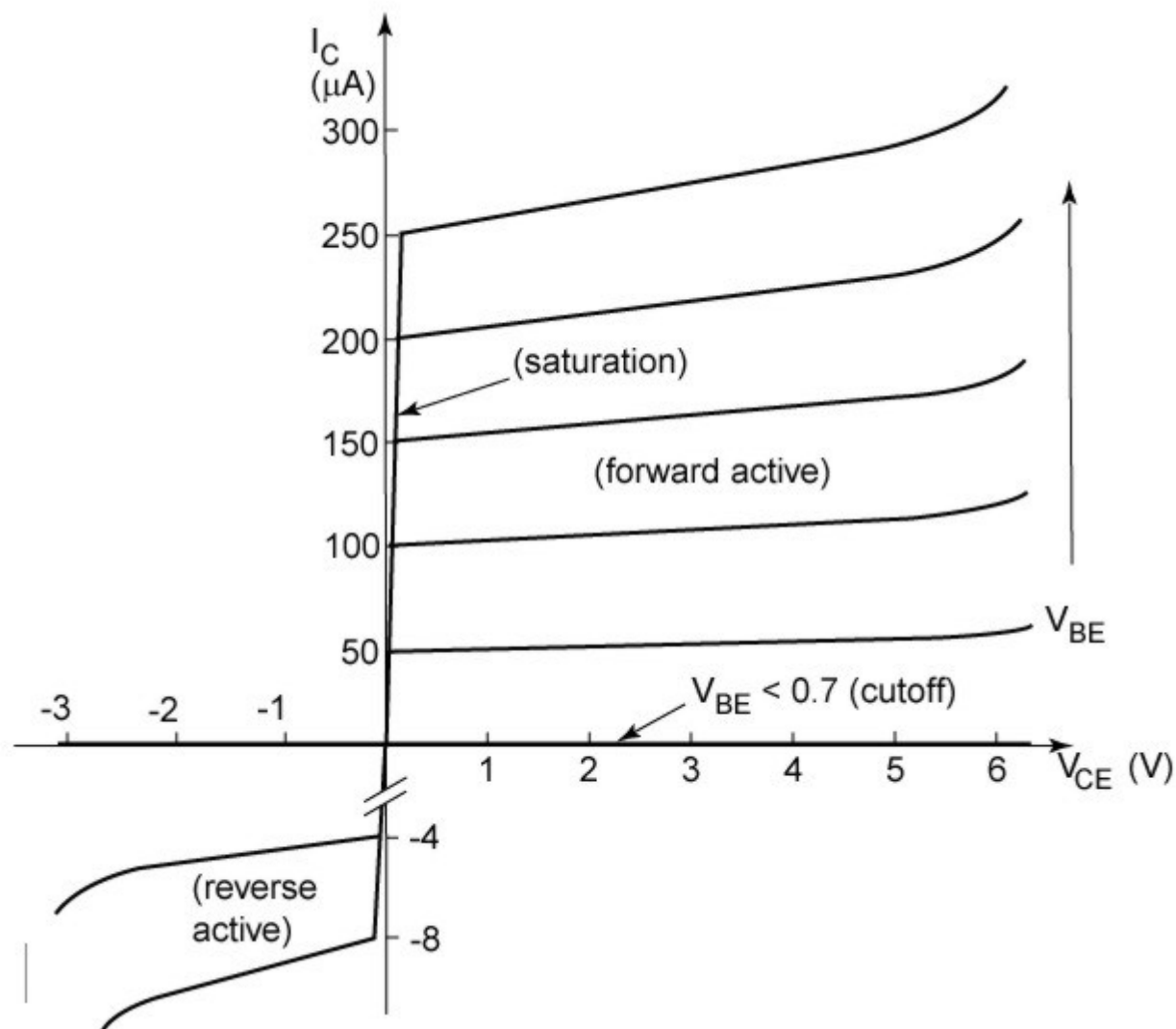

“Transistor Action”

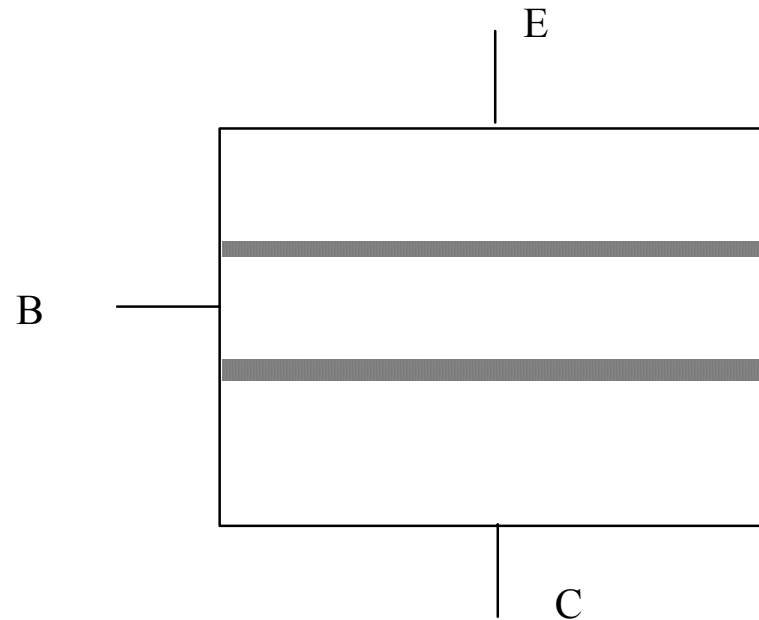

Diffusion Currents

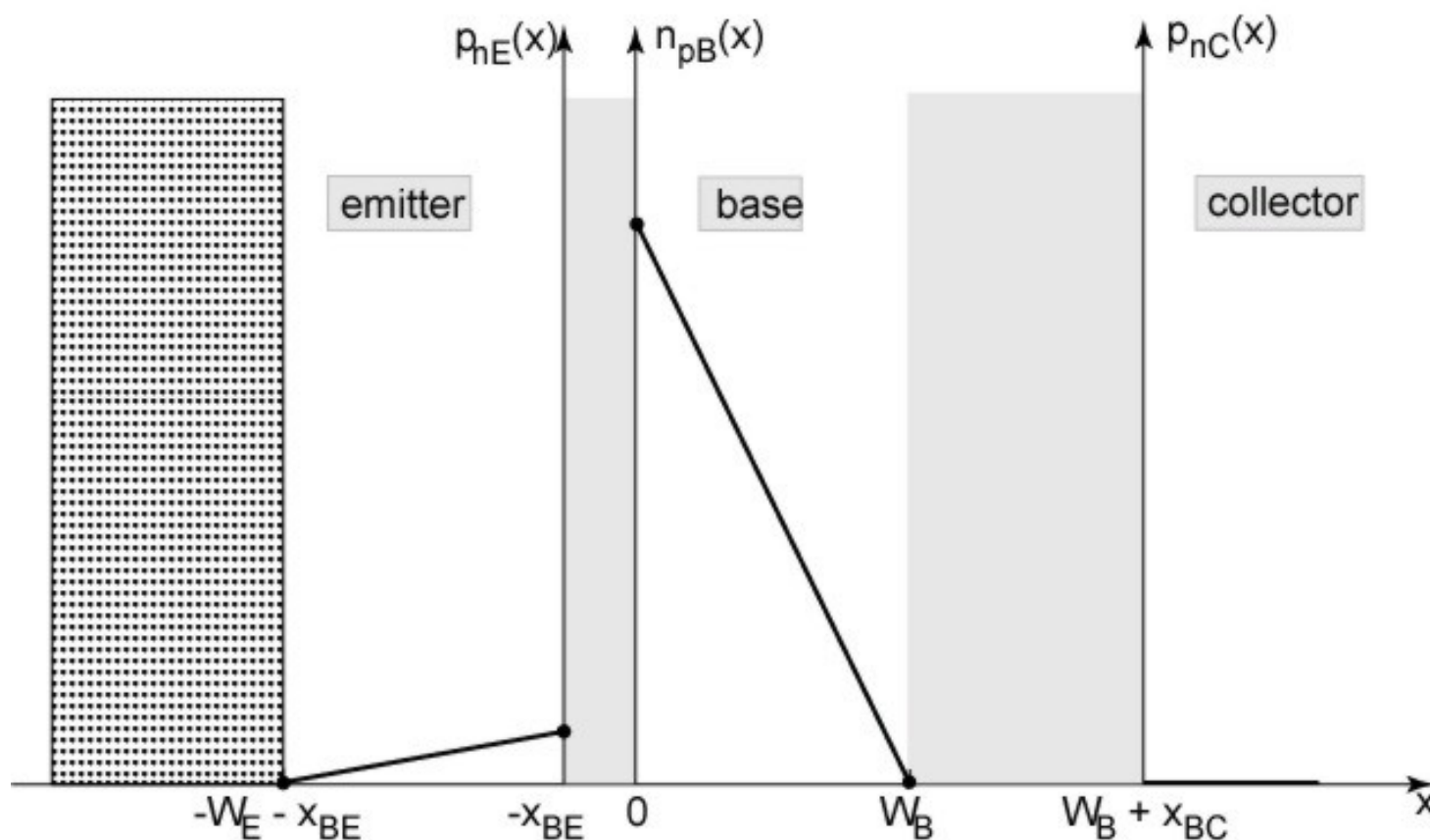

BJT Currents

Collector current is nearly identical to the (magnitude) of the emitter current ... define

$$I_C = -\alpha_F I_E$$


Kirchhoff:

$$-I_E = I_C + I_B$$

DC Current Gain:

Origin of α_F

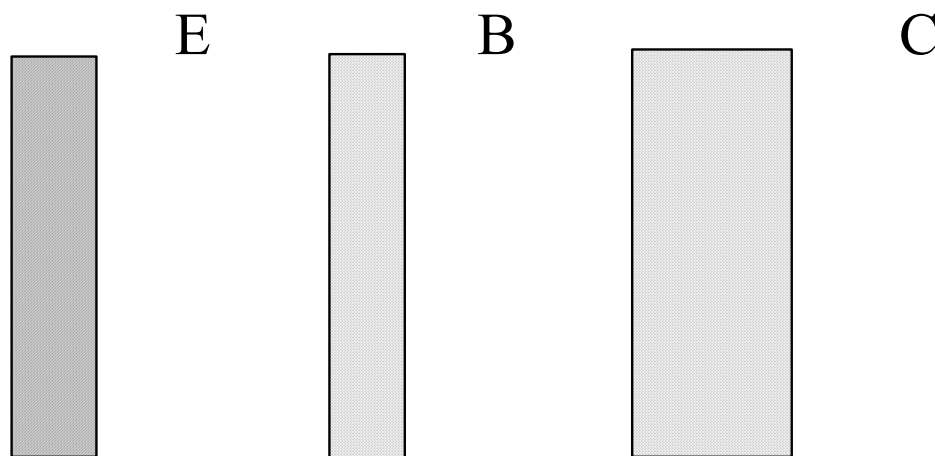Base-emitter junction: some reverse injection of holes into the emitter \rightarrow base current isn't zero



Typical α_F