

Lecture 21

- Last time:
 - Large-signal model under forward bias
 - Ebers-Moll model, start small signal model
- Today :
 - Small-signal model of the npn bipolar transistor

Transconductance (cont.)

- Forward-active large-signal current:

$$i_C = I_S e^{v_{BE}/V_{th}} (1 + v_{CE}/V_A)$$

- Differentiating and evaluating at $Q = (V_{BE}, V_{CE})$

Comparison with MOSFET g_m

- Bipolar transistor:
- MOSFET:
- Typical bias point: drain/coll. current = 100 μA ;
Select $(W/L) = 8/1$, $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$

What about the Base Current?


Unlike MOSFET, there is a DC current into the base terminal of a bipolar transistor:

$$I_B = I_C / \beta_F = (I_S / \beta_F) e^{V_{BE} / V_{th}} (1 + V_{CE} / V_{th})$$

To find the change in base current due to change in base-emitter voltage:

$$\frac{\partial i_B}{\partial v_{BE}} \Big|_Q = \underbrace{\frac{\partial i_B}{\partial i_C}}_Q \underbrace{\frac{\partial i_C}{\partial v_{BE}}}_Q =$$

Small-Signal Current Gain β_o

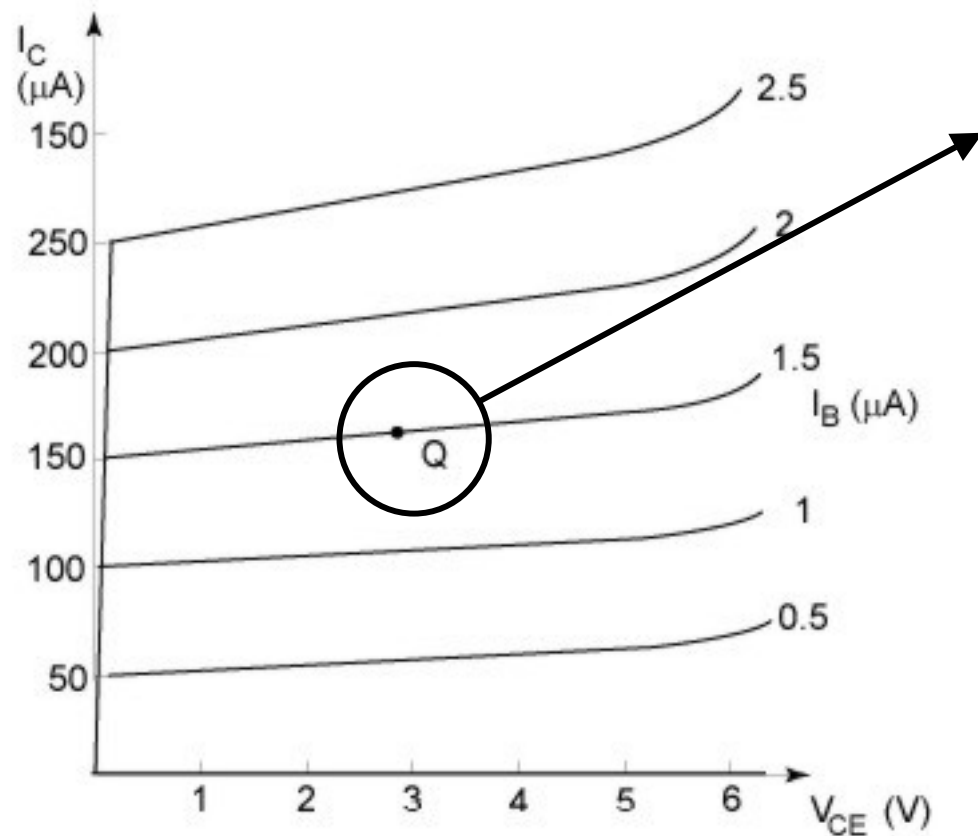

Input Resistance r_π

$$(r_\pi)^{-1} = \left. \frac{\partial i_B}{\partial v_{BE}} \right|_Q$$

In practice, the DC current gain β_F and the small-signal current gain β_o are both highly variable (+/- 25%)

Typical bias point: DC collector current = 100 μA


Output Resistance r_o

Why does current increase slightly with increasing v_{CE} ?

Model: math is a mess, so introduce the Early voltage


$$i_C = I_S e^{v_{BE}/V_{th}} (1 + v_{CE}/V_A)$$

Graphical Interpretation of r_o

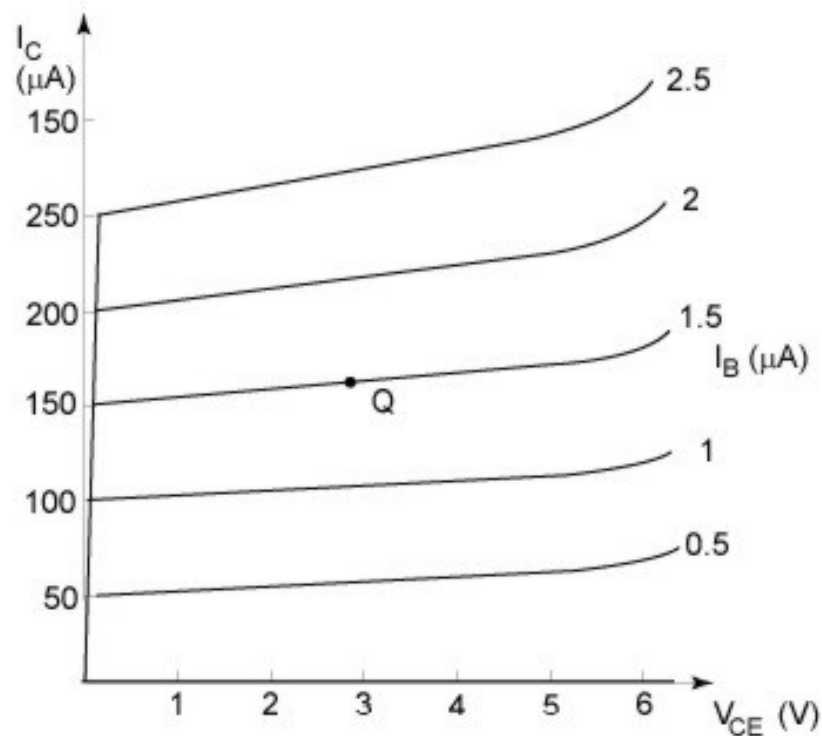

Typical value:

BJT Small-Signal Model

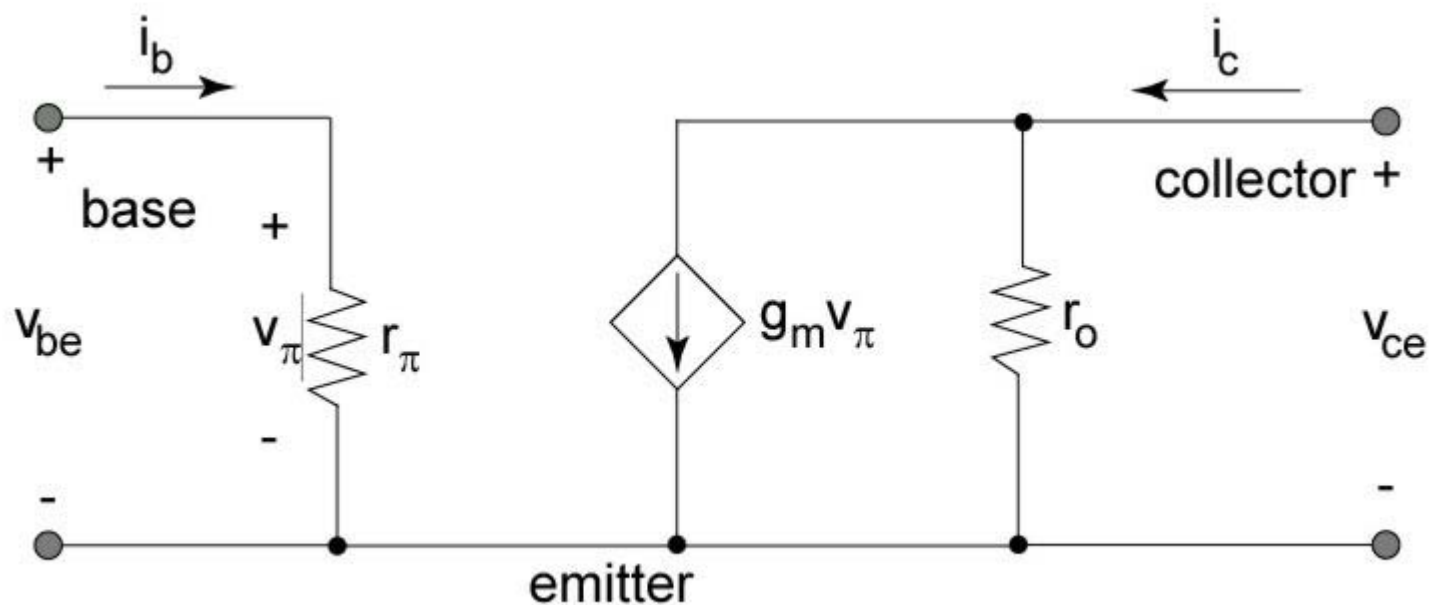

BJT Capacitances

Base-charging capacitance C_b : due to minority carrier charge storage (mostly electrons in the base)

$$C_b = g_m \tau_F$$

Base-emitter depletion capacitance: $C_{jE} = 1.4 C_{jE0}$

Total B-E capacitance: $C_\pi = C_{jE} + C_b$

Complete Small-Signal Model

