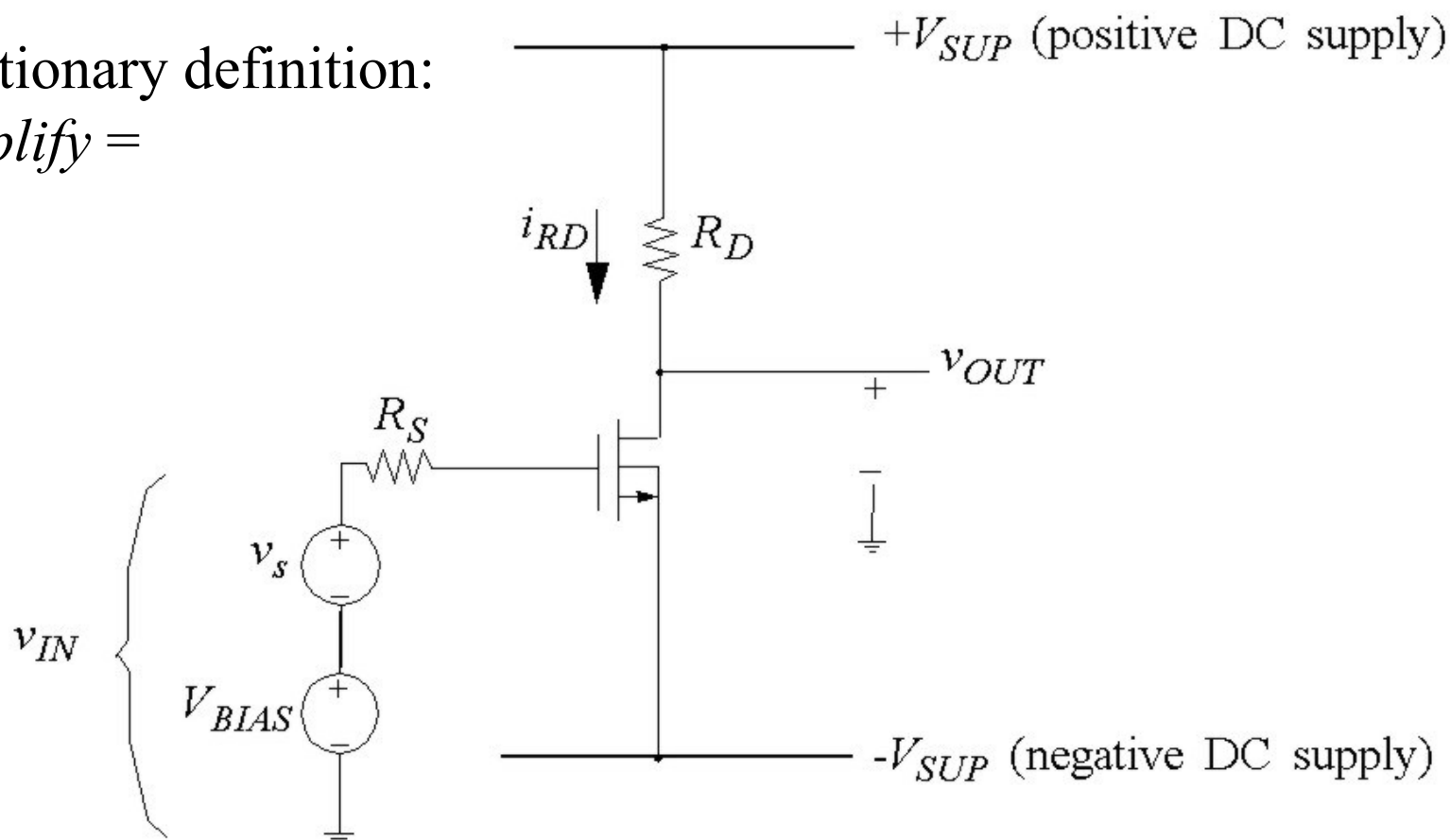


Lecture 22

- Last time:
 - Small-signal model of the npn bipolar transistor
- Today :
 - Introduction to amplifiers: a common-source MOS single-stage amplifier

An MOS Amplifier

Dictionary definition:
amplify =



Selecting the Output Bias Point

V_{BIAS} is selected so that V_{OUT} is centered between $+V_{SUP}$ and $-V_{SUP}$ (why?)

$$V_{OUT} = 0 \text{ V} \dots \textbf{NOT } v_{OUT} = 0 \text{ V!}$$

Constraint on the DC drain current:

$$I_{RD} = (V_{SUP} - V_{OUT}) / R_D = V_{SUP} / R_D$$

$I_{RD} = I_D = I_{D,SAT} \dots$ verify that MOSFET is saturated after finding V_{BIAS}

Finding the Input Bias Voltage

Hand calculation: neglect “fudge factor” in $I_{D,SAT}$

$$I_{D,SAT} = (W / 2L) \mu_n C_{ox} (V_{GS} - V_{Tn})^2$$

Typical numbers: $W = 40 \mu\text{m}$, $L = 2 \mu\text{m}$, $R_D = 25 \text{ k } \Omega$
 $\mu_n C_{ox} = 100 \mu\text{A/V}^2$, $V_{Tn} = 1 \text{ V}$,
 $V_{SUP} = 2.5 \text{ V}$

$$I_{RD} = \frac{V_{SUP}}{R_D} = I_{D,SAT} = 10 \cdot 100 \cdot (V_{GS} - 1)^2$$

Applying the Small-Signal Voltage

Approach 1. Just use v_{IN} in the equation for the total drain current i_D and find v_{OUT}

$$v_{IN} = V_{BIAS} + v_s \quad v_{GS} = v_{IN} - (-V_{SUP}) = [V_{BIAS} + v_s + V_{SUP}]$$

$$v_s(t) = \hat{v}_s \cos(\omega t)$$

Result:

$$v_{OUT} = V_{SUP} - R_D i_D \cong V_{SUP} - R_D (\mu_n C_{ox}) \left(\frac{W}{2L} \right) (V_{GS} + v_s - V_{Tn})^2$$

Solving for the Output Voltage v_{OUT}

$$v_{OUT} = V_{SUP} - \underbrace{R_D (\mu_n C_{ox}) \left(\frac{W}{2L}\right) (V_{GS} - V_{Tn})^2}_{I_D} \left(1 + \frac{v_s}{(V_{GS} - V_{Tn})}\right)^2$$

$$v_{OUT} = V_{SUP} - \underbrace{R_D I_D}_{V_{SUP}} \left(1 + \frac{v_s}{(V_{GS} - V_{Tn})}\right)^2$$

Small-Signal Case

Linearize the output voltage for the s.s. case

Expand $(1 + x)^2 = 1 + 2x + x^2 \dots$ last term can be dropped when $x \ll 1$

$$\left(1 + \frac{v_s}{V_{GS} - V_{Tn}}\right)^2 = 1 + \frac{2v_s}{V_{GS} - V_{Tn}} + \left(\frac{v_s}{V_{GS} - V_{Tn}}\right)^2$$

Linearized Output Voltage

For this case, the total output voltage is


$$v_{OUT} \cong V_{SUP} - R_D I_D \left(1 + \frac{2v_s}{(V_{GS} - V_{Tn})} \right) = \cancel{V_{SUP}} - \cancel{V_{SUP}} - \frac{2R_D I_D v_s}{(V_{GS} - V_{Tn})}$$

The average output voltage $V_{OUT} = 0$ V so the total output voltage is the small-signal voltage in this special case:

$$v_{OUT} = v_{out} = - \left[\frac{2R_D I_D}{(V_{GS} - V_{Tn})} \right] v_s = - \left[\frac{2R_D I_D}{(V_{GS} - V_{Tn})} \right] v_s = A_v v_s$$

Plot of Output Waveform

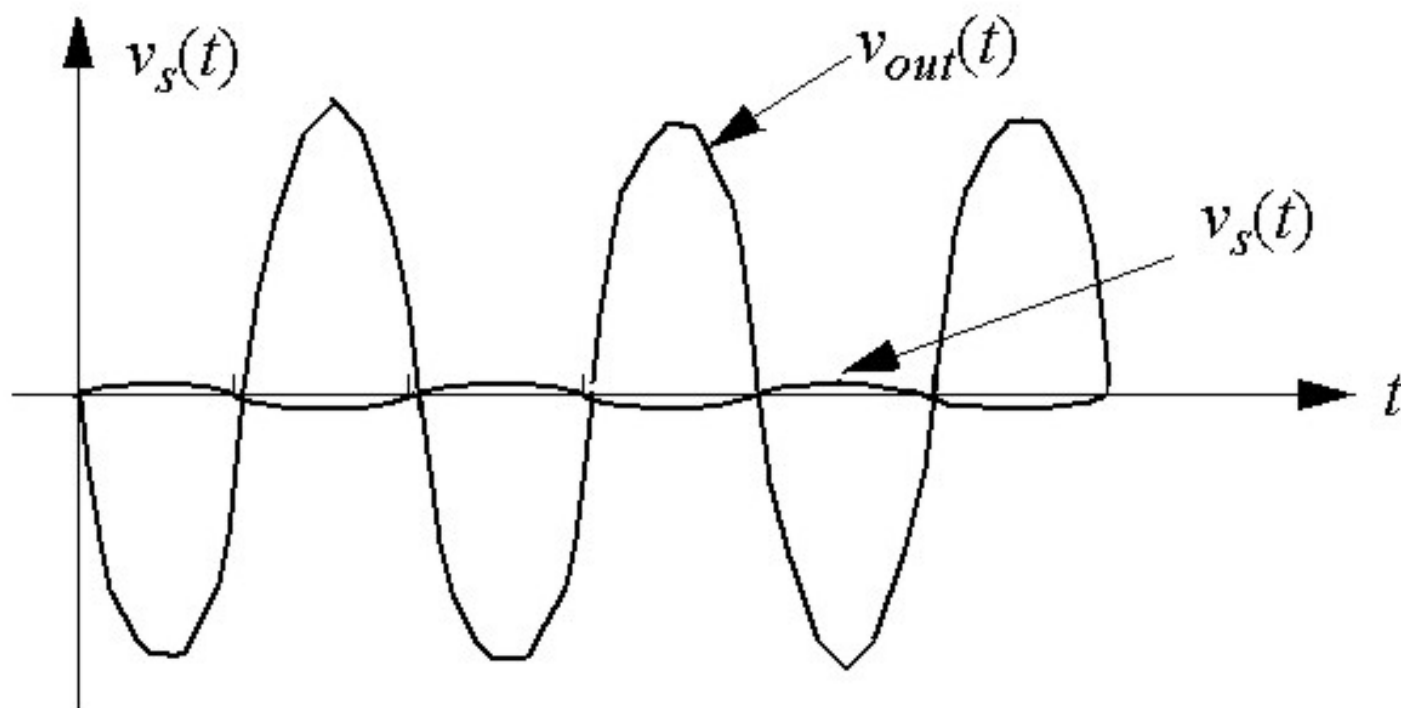Numbers: $2 I_D R_D / (V_{GS} - V_{Tn}) = (2 \times 2.5) / 0.31 = 16.1$



Is there a Better Way?

What's missing: no inclusion of fudge factor term or of charge storage effects

Approach 2. Do problem in two steps.

1. DC voltages and currents (ignore small signals sources): set bias point of the MOSFET ... we had to do this to pick V_{BIAS} already
2. Substitute the small-signal model of the MOSFET and the small-signal models of the other circuit elements ...