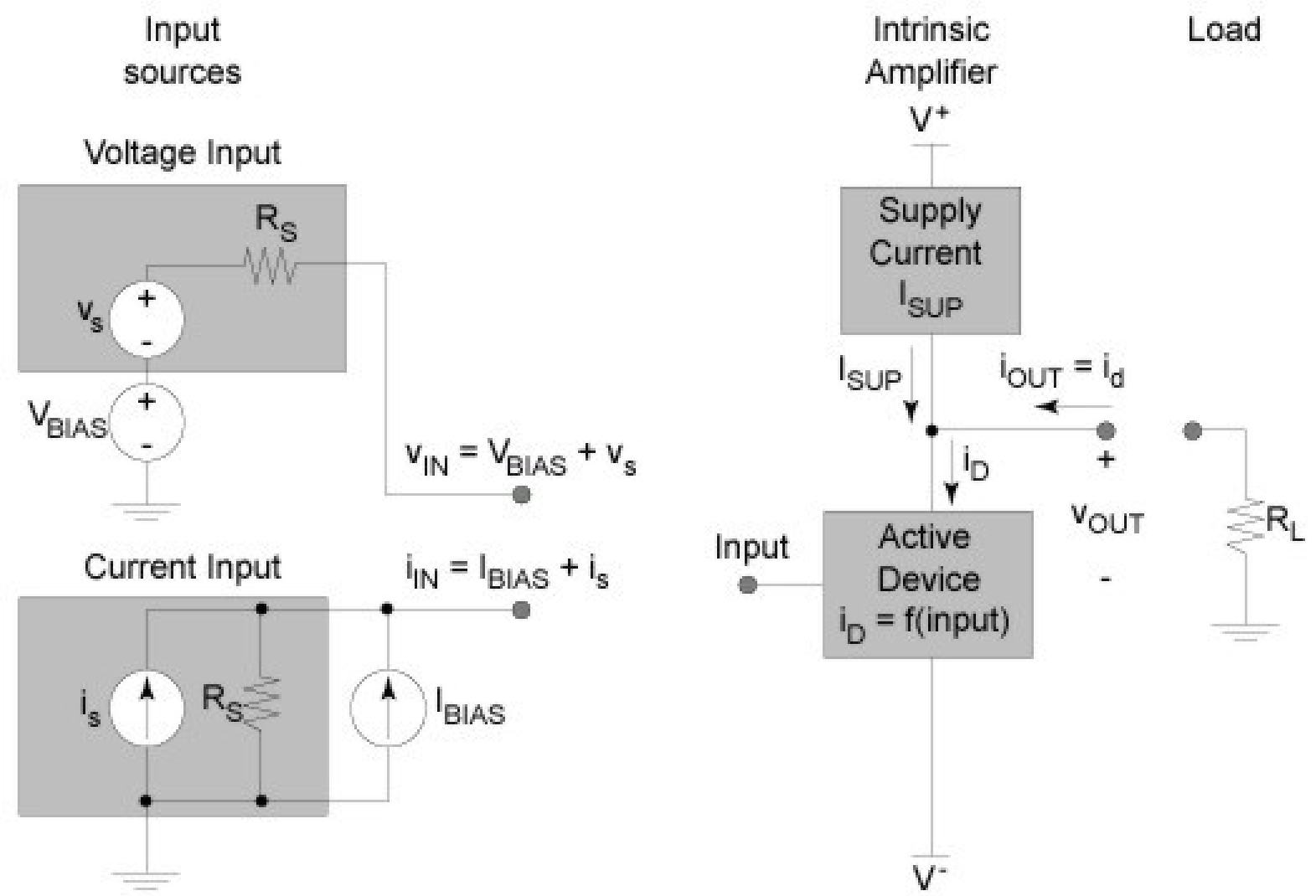


Lecture 24

- Last time:
 - Small-signal model for the entire common-source amplifier
 - Limits to model
- Today :
 - Two-port small-signal models of amplifiers

Generalized Amplifier



Amplifier Terminology

Sources: signal, its source resistance, and bias voltage or current

Load: use resistor in Chap. 8, but could be a general impedance

Port: a pair of terminals across which a voltage and an associated current are defined

source, load: “one port”

amplifier: “two port”

Amplifier Biasing

Select V_{IN} (or I_{IN}) to set the DC device current to equal the supply current I_{SUP} .




DC output current $I_{OUT} =$

DC output voltage $V_{OUT} =$


Small-signal source voltage or source current results in small-signal device current $i_d \rightarrow$

One-Port Models (EECS 40)

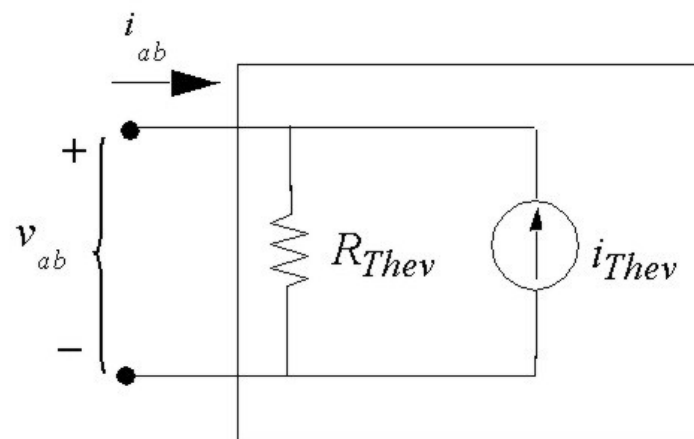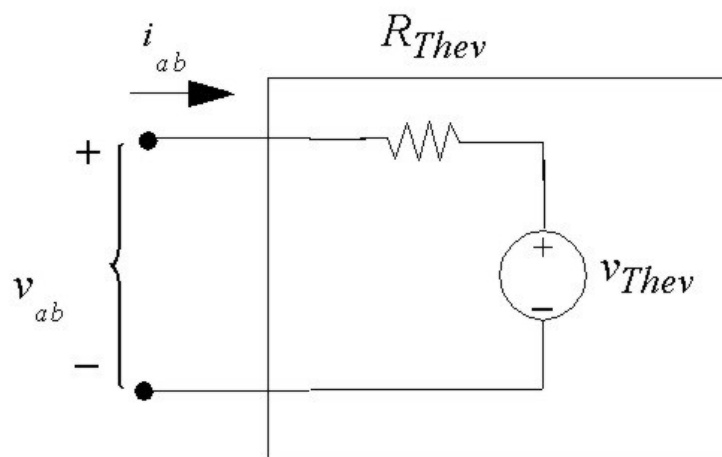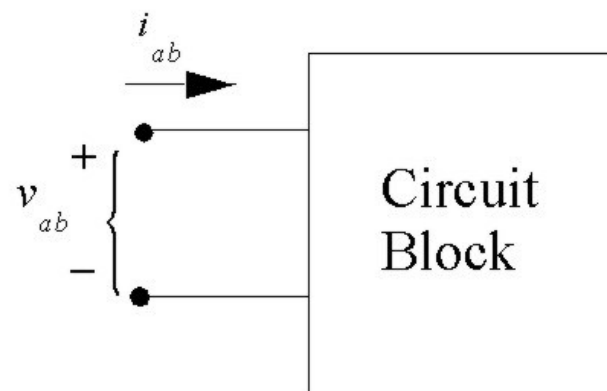a terminal pair
across which a
voltage and associated
current are defined



Small-Signal Two-Port Models

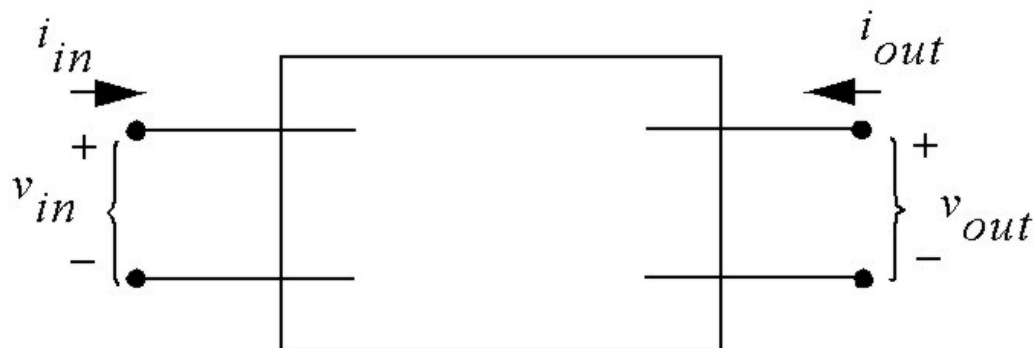

We assume that input port is linear and that the amplifier is *unilateral*:

The output port : depends linearly on the current and voltage at the input and output ports

Math 54 Perspective

Can write linear system of equations for either i_{out} or v_{out} in terms of two of i_{in} , v_{in} , i_{out} , or v_{out} : possibilities are

$$i_{out} = \alpha_1 v_{in} + \alpha_2 v_{out}$$

$$i_{out} = \alpha_3 i_{in} + \alpha_4 v_{out}$$

$$v_{out} = \alpha_5 v_{in} + \alpha_6 i_{out}$$

$$v_{out} = \alpha_7 i_{in} + \alpha_8 i_{out}$$

What is physical meaning of α_1 ? of α_6 ?

EE Perspective

Four amplifier types: determined by the output signal and the input signal ... both of which we select (usually obvious)

Voltage

Current


Transconductance

Transresistance


We need *methods* to find the 6 α_i parameters for the four models and equivalent circuits for unilateral two ports

Two-Port Small-Signal Amplifiers


Voltage Amplifier

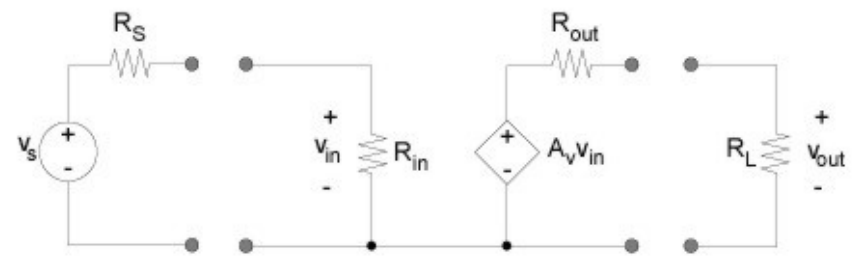


Current Amplifier

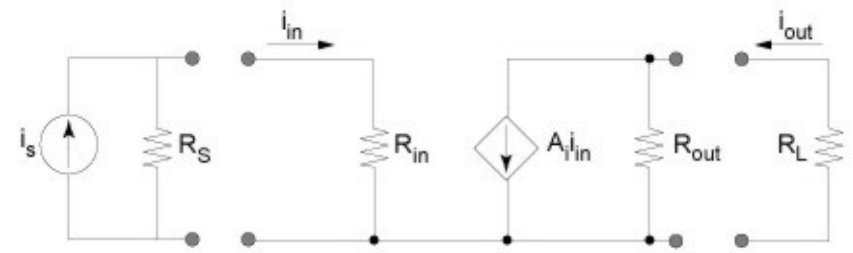

Transconductance Amplifier

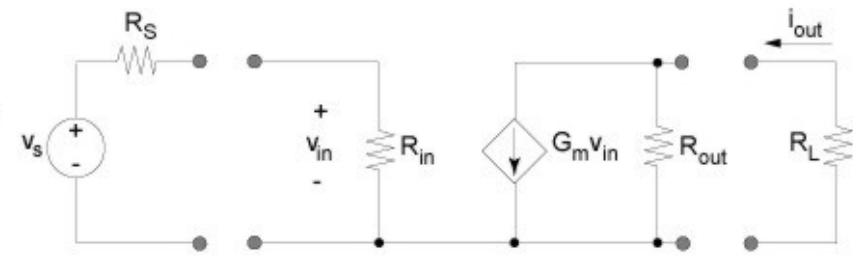


Transresistance Amplifier

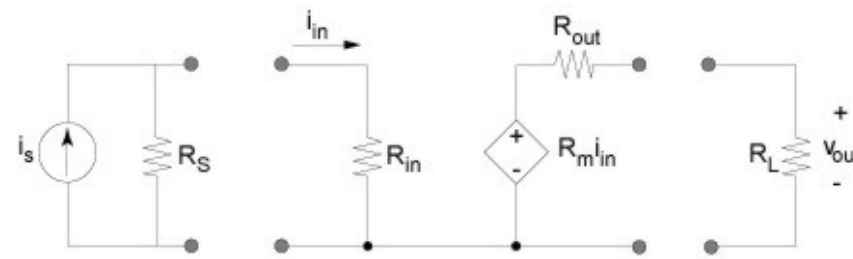

Input Resistance R_{in}

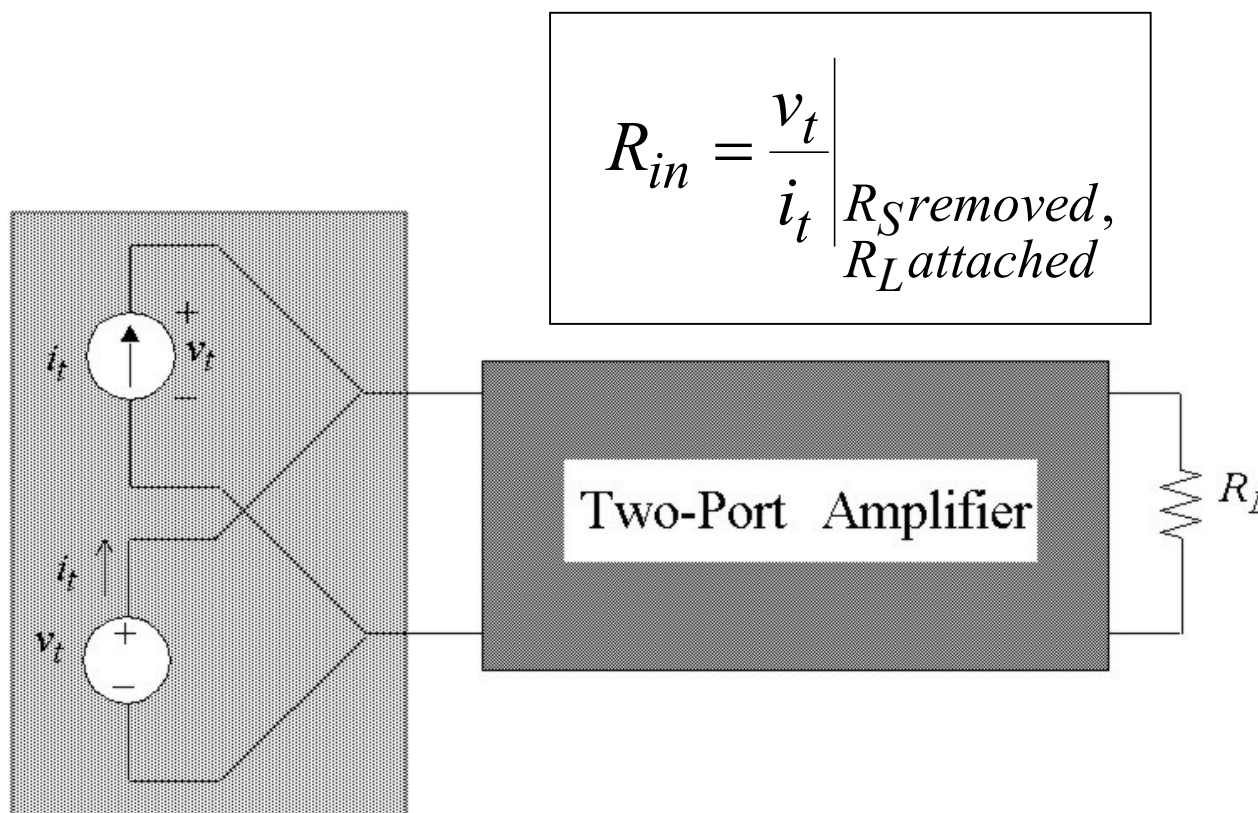Looks like a Thevenin resistance measurement, but note that the output port has the load resistance attached



Output Resistance R_{out}

Looks like a Thevenin resistance measurement, but note that the *input* port has the *source* resistance attached

$$R_{out} = \frac{v_t}{i_t} \left| \begin{array}{l} R_L \text{ removed,} \\ R_S \text{ attached} \end{array} \right.$$

