

# Lecture 29

- Last time:
  - Bipolar single-stage amplifiers: biasing, common-emitter, common-base, common-collector
- Today :
  - Overview of single-stage amplifiers
  - Frequency response of CS stage operated as a current amplifier


# Common-Collector Summary

- Typo in Fig. 8.47 in text ...  $R_{in}$  can't depend upon  $R_S$ !
- Input and output resistances depend on load and source resistances, respectively
- See Appendix to Chapter 8 for limits to using this model with very low values of  $R_L$

# Summary of Two-Port Parameters for CE/CS, CB/CG, CC/CD Amplifiers


Amplifier Type	Controlled Source	Input Resistance $R_{in}$	Output Resistance $R_{out}$
Common Emitter	$G_m = g_m$	$r_{\pi}$	$r_o \parallel r_{oc}$
Common Source	$G_m = g_m$	infinity	$r_o \parallel r_{oc}$
Common Base	$A_i = -1$	$1 / g_m$	$r_{oc} \parallel [(1 + g_m(r_{\pi} \parallel R_S)) r_o]$ , for $g_m r_o \gg 1$
Common Gate	$A_i = -1$	$1 / g_m, (v_{sb} = 0)$ -otherwise- $1 / (g_m + g_{mb})$	$r_{oc} \parallel [(1 + g_m R_S) r_o], (v_{sb} = 0)$ -otherwise- $r_{oc} \parallel [(1 + (g_m + g_{mb}) R_S) r_o]$ both for $r_o \gg R_S$
Common Collector	$A_v = 1$	$r_{\pi} + \beta_o(r_o \parallel r_{oc} \parallel R_L)$	$(1 / g_m) + R_S / \beta_o$
Common Drain	$A_v = 1$ if $v_{sb} = 0$ , -otherwise- $g_m / (g_m + g_{mb})$	infinity	$1 / g_m$ if $v_{sb} = 0$ , -otherwise- $1 / (g_m + g_{mb})$
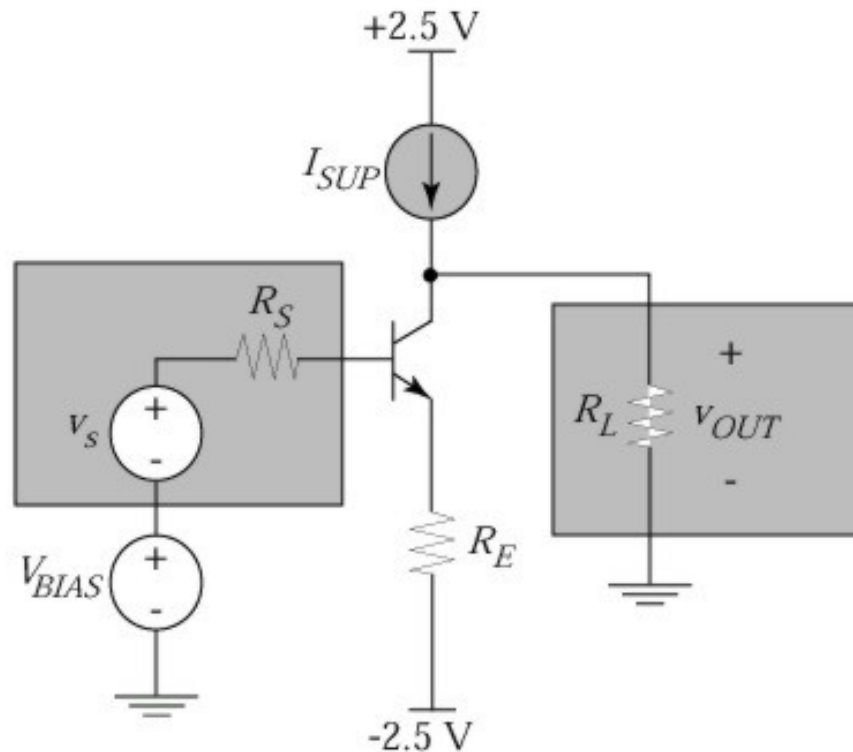
# The “Chapter 8” Method for Single-Stage Amplifier Analysis




1. What is it?
2. DC Bias
3. Small-signal 2-port model
4. Output swing

# DC Bias for $CE_{deg}$

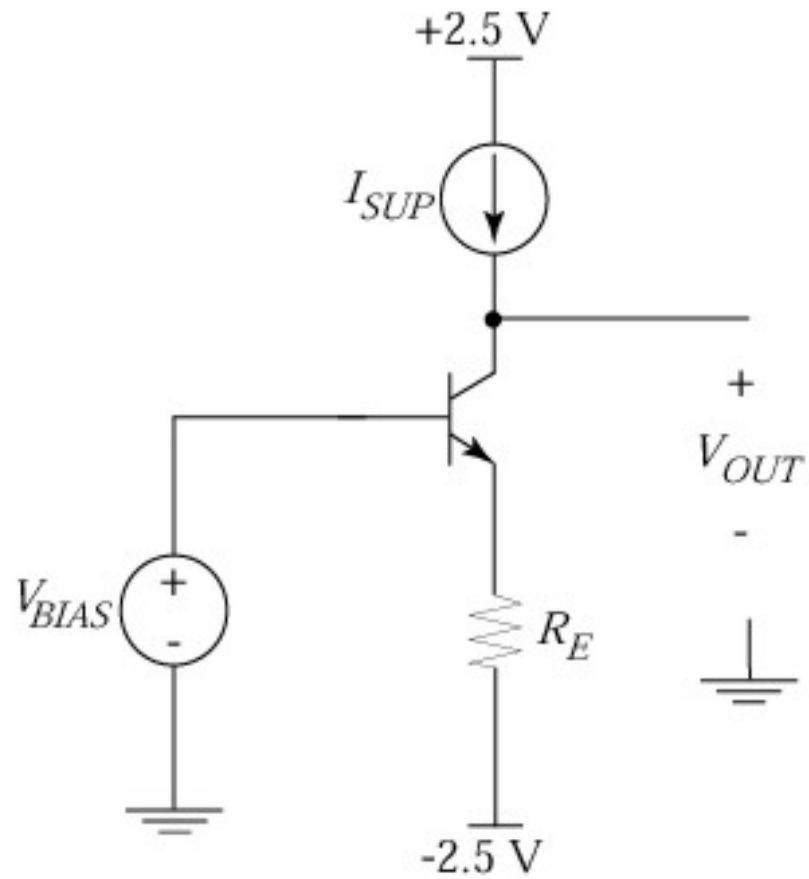
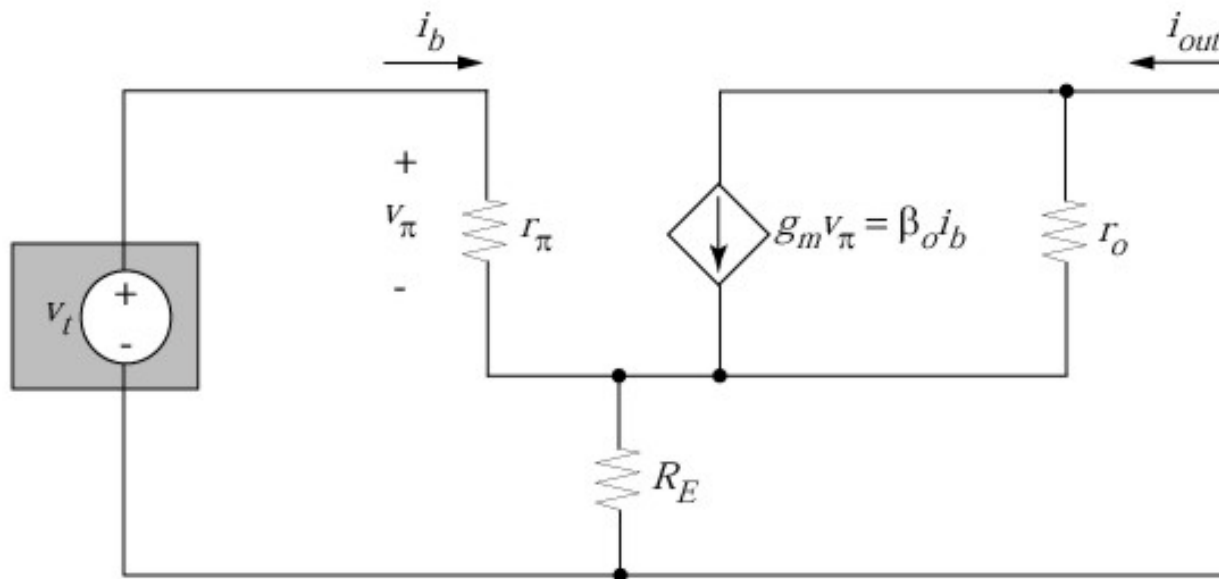
# Two-Port Model for $CE_{deg}$

- Input looks like CC  $\rightarrow R_{in} =$
- Output looks like CB (see p. 504 for details)  $\rightarrow R_{out} =$
- Transconductance:  $G_m =$



# Two-Port Model for $CE_{deg}$ (cont.)

- Find  $G_m$
- Voltage Gain:
- Is it a good voltage amplifier (vs. CE)?

# Output “Swing”

- Maximum  $v_{OUT} = V_{OUT} + v_{out} = v_{out}$
- Minimum  $v_{OUT}$