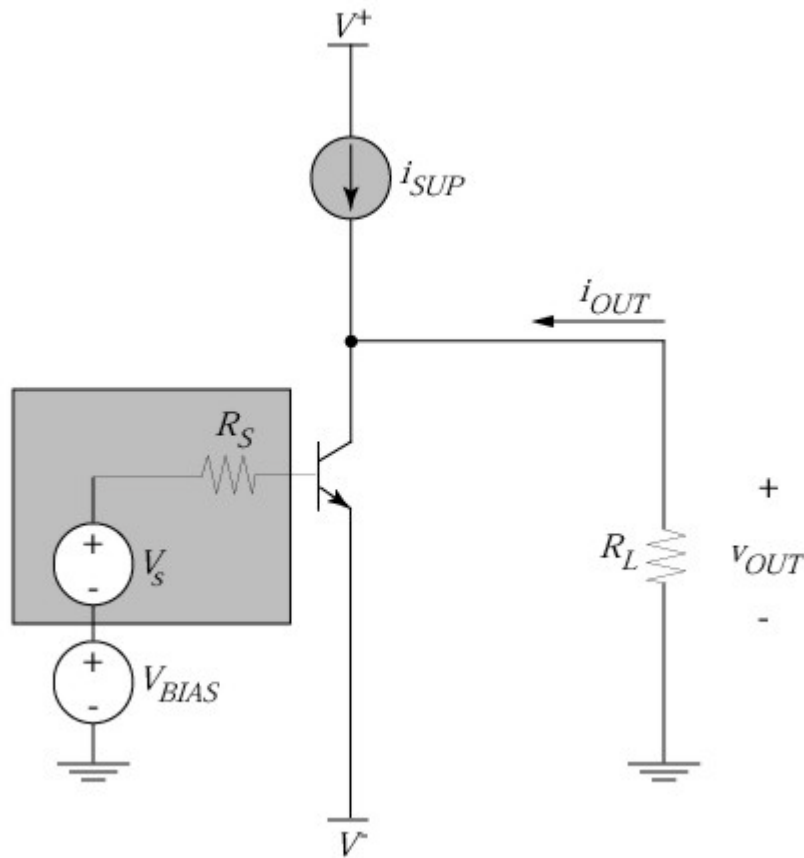


Lecture 31


- Last time:
 - Short-circuit current gain of CE and CS amps
 - Unity-gain frequency ω_T
- Today :
 - Frequency response of the CE as voltage amp
 - The Miller approximation

Common-Emitter Voltage Amplifier




Small-signal model:
omit C_{CS} due to avoid
complicated analysis

CE Voltage Amp Small-Signal Model

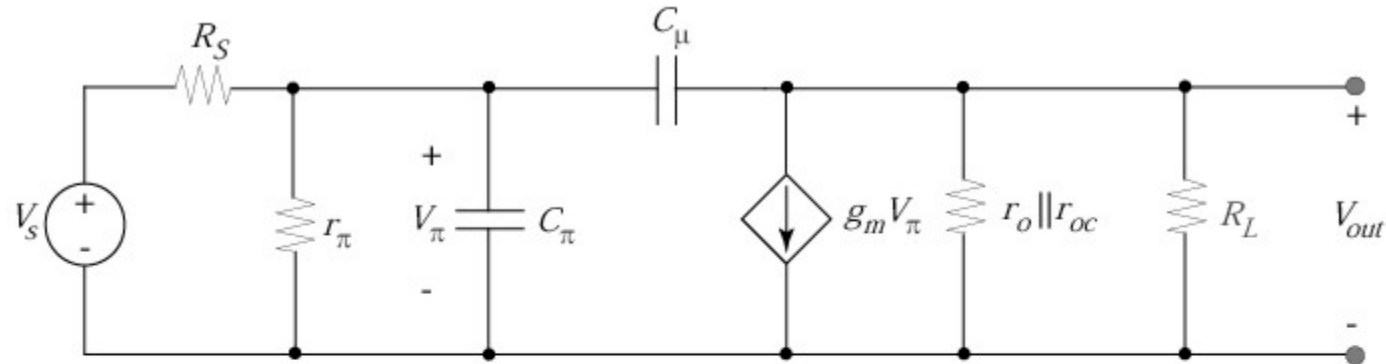

switch to Norton equivalent at input

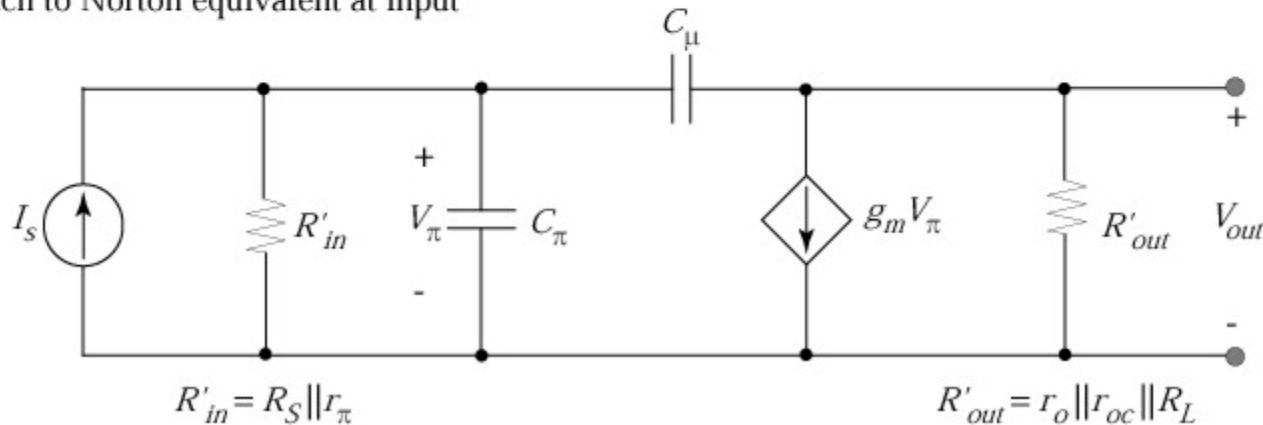

Frequency Response

KCL at input and output nodes; analysis is made complicated due to Z_μ branch \rightarrow see H&S pp. 639-640.

$$\frac{V_{out}}{V_{in}} = \frac{-g_m \left(\frac{r_\pi}{r_\pi + R_S} \right) [r_o \parallel r_{oc} \parallel R_L] (1 - j\omega / \omega_z)}{(1 + j\omega / \omega_{p1})(1 + j\omega / \omega_{p2})}$$

Low-frequency gain:

$$\text{Zero: } \omega_z > \omega_T = \frac{g_m}{C_\pi + C_\mu}$$

Poles


$$\omega_{p1} \approx \frac{1}{(R_S \parallel r_\pi) \{C_\pi + (1 + g_m R'_{out}) C_\mu\} + R'_{out} C_\mu}$$

$$\omega_{p2} \approx \frac{R'_{out} / (R_S \parallel r_\pi)}{(R_S \parallel r_\pi) \{C_\pi + (1 + g_m R'_{out}) C_\mu\} + R'_{out} C_\mu}$$

Decoupling Input and Output: the Miller Approximation

Results of complete analysis: not exact and little insight

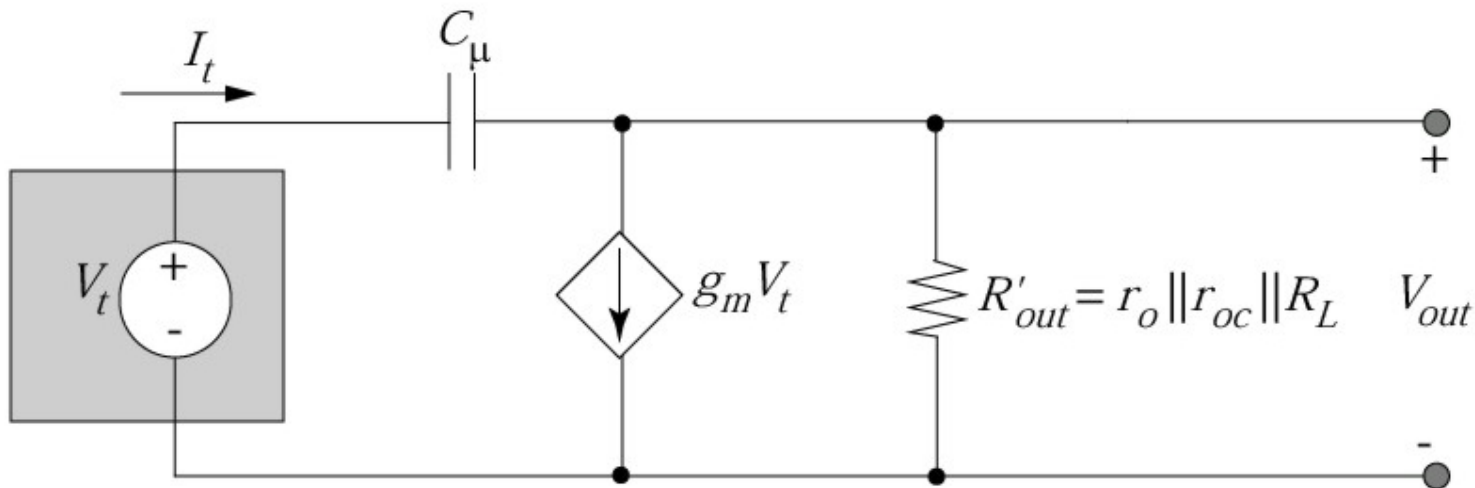Look at how Z_μ affects the transfer function: find Z_{in}



Input Impedance $Z_{in}(j\omega)$

$$I_t = (V_t - V_{out}) / Z_\mu$$

At output node:

$$V_{out} = (-g_m V_t - I_t) R'_{out} \approx -g_m V_t R'_{out} \quad \text{Why?}$$


$$I_t = (V_t - A_{vC_\mu} V_t) / Z_\mu$$

$$Z_{in} = V_t / I_t = \frac{Z_\mu}{1 - A_{vC_\mu}}$$

Miller Capacitance C_M

Effective input capacitance:
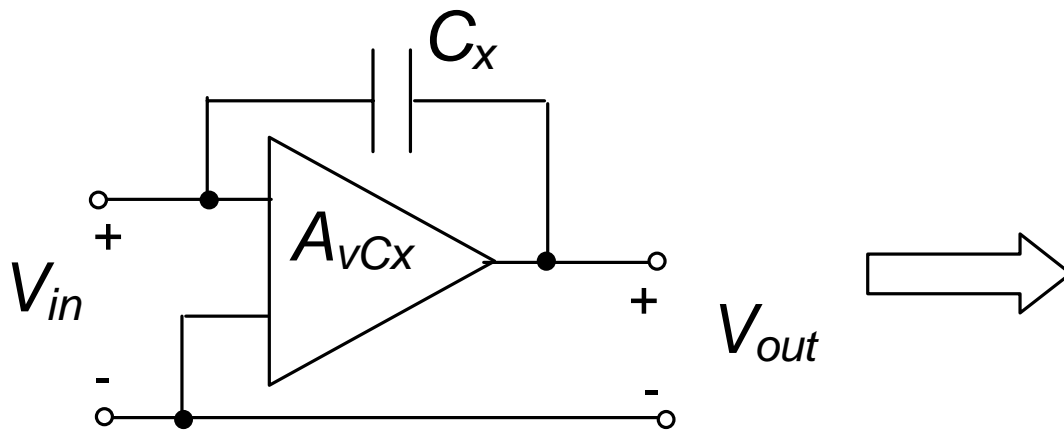
$$Z_{in} = \frac{1}{j\omega C_M} = \left(\frac{1}{1 - A_v C_\mu} \right) \left(\frac{1}{j\omega C_\mu} \right) = \frac{1}{j\omega [(1 - A_v C_\mu) C_\mu]}$$



What about the role of C_x when viewed from the output port?

Some Examples

Common emitter/source amplifier:


$$A_{vC_{\mu}} = \text{Negative, large number (-100)}$$

Common collector/drain amplifier:

$$A_{vC_{\pi}} = \text{Slightly less than 1}$$

CE Amplifier using Miller Approx.

Use Miller to transform C_μ

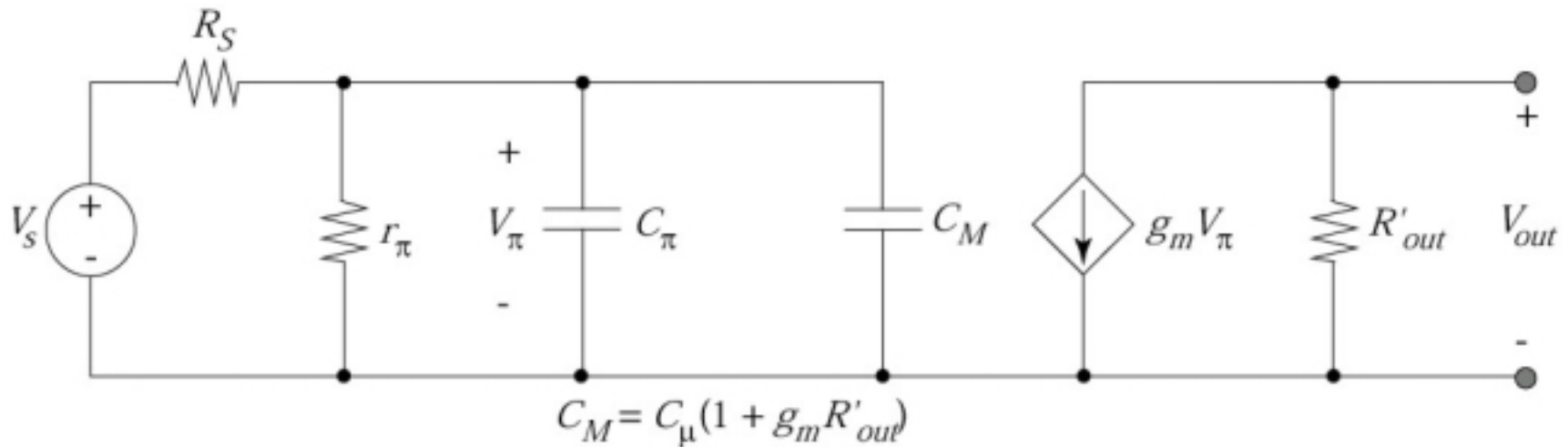

Analysis is straightforward now ... single pole!

Comparison with “Exact Analysis”

Miller result:

$$\omega_{p1}^{-1} =$$

Exact result:

$$\omega_{p1}^{-1} = (R_S \parallel r_\pi) \left\{ C_\pi + (1 + g_m R'_{out}) C_\mu \right\} + R'_{out} C_\mu$$