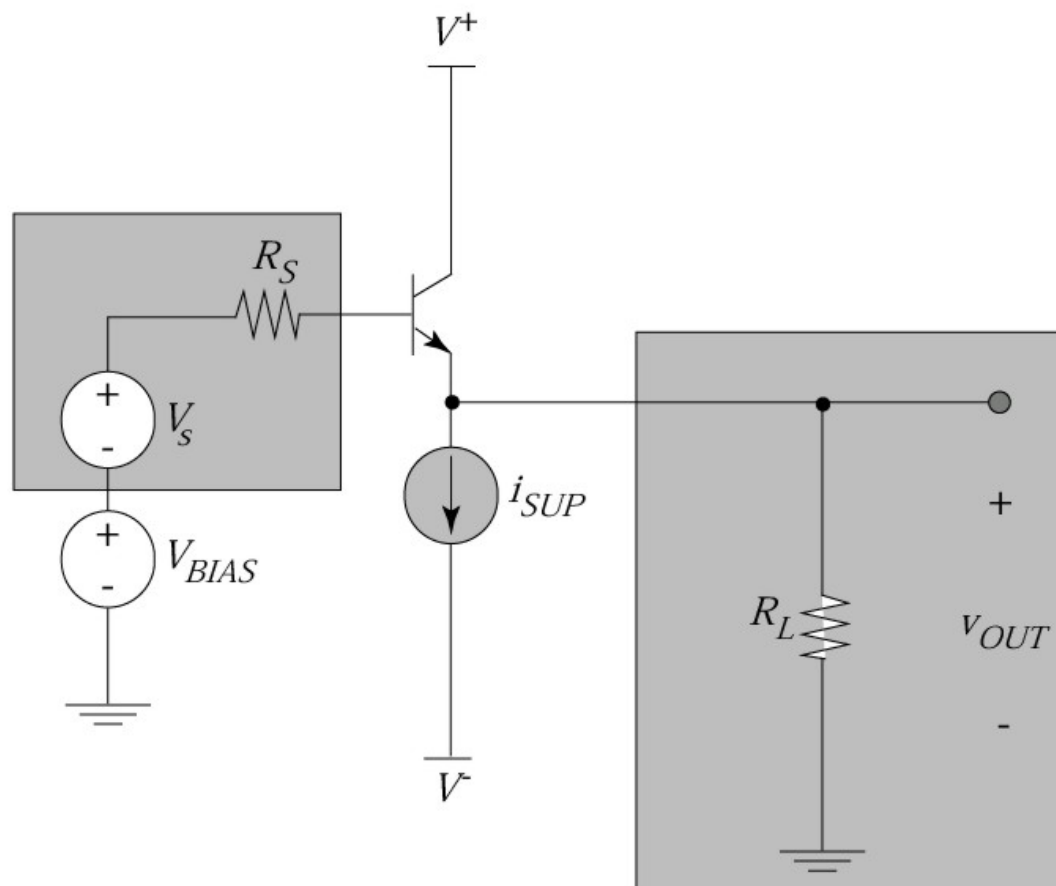


# Lecture 32

- Last time:
  - Frequency response of the CE as voltage amp
  - The Miller approximation
- Today :
  - Frequency response of voltage and current buffers
  - Start multi-stage amplifiers: Chapter 9


# Common-Collector Amplifier



Procedure:

1. Small-signal two-port model
2. Add device (and other) capacitors

# Two-Port CC Model with Capacitors

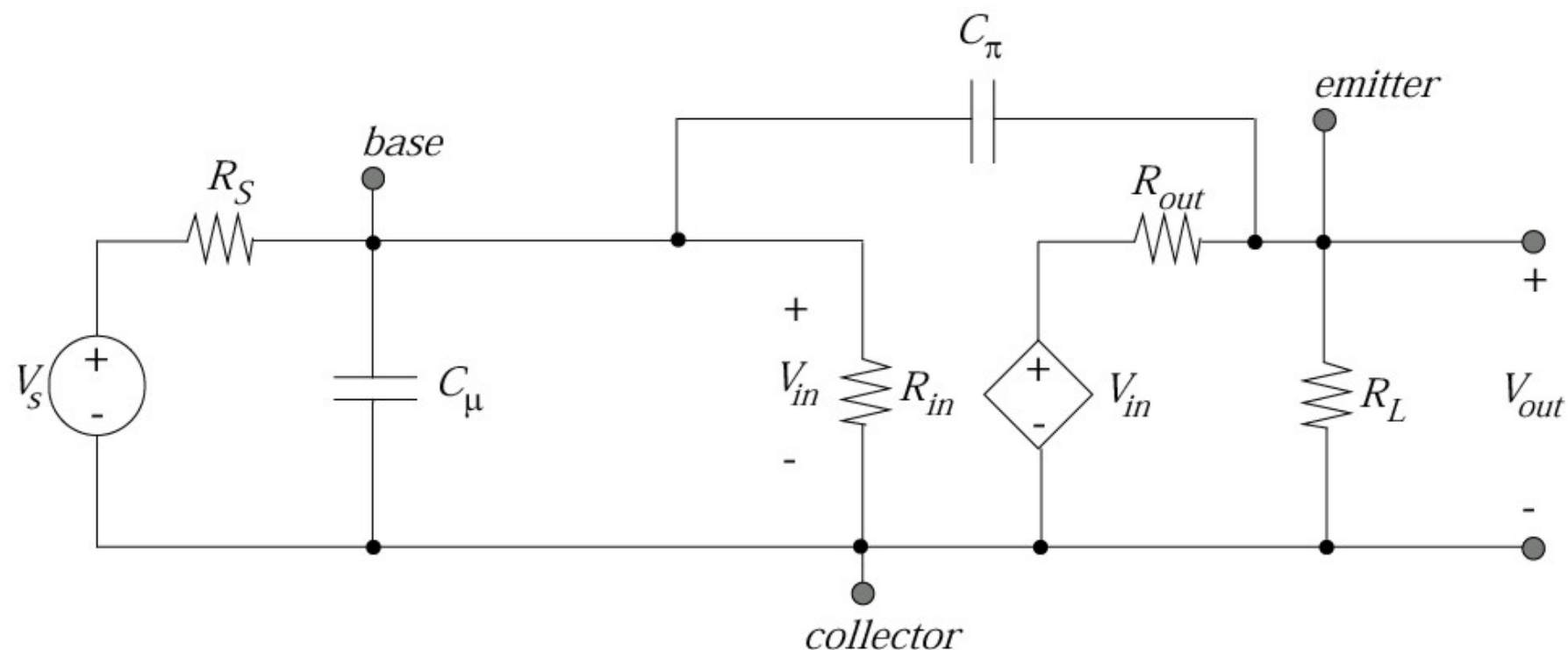

Find Miller capacitor for  $C_\pi$  -- note that the base-emitter capacitor is  
Between the input and output

# Voltage Gain $A_{vC_\pi}$ Across $C_\pi$

$$A_{vC_\pi} =$$

Note: this voltage gain is neither the two-port gain nor the “loaded” voltage gain

$$C_{in} = C_\mu + C_M = C_\mu + (1 - A_{vC_\pi})C_\pi$$

# Bandwidth of CC Amplifier

Input low-pass filter's  $-3$  dB frequency:


$$\omega_p^{-1} = (R_S \parallel R_{in}) \left( C_\mu + \frac{C_\pi}{1 + g_m R_L} \right)$$

Substitute favorable values of  $R_S$ ,  $R_L$ :

$$R_S \approx 1/g_m \quad R_L \gg 1/g_m$$


$$\omega_p^{-1} \approx (1/g_m) \left( C_\mu + \frac{C_\pi}{1 + \text{BIG}} \right) \approx C_\mu / g_m$$
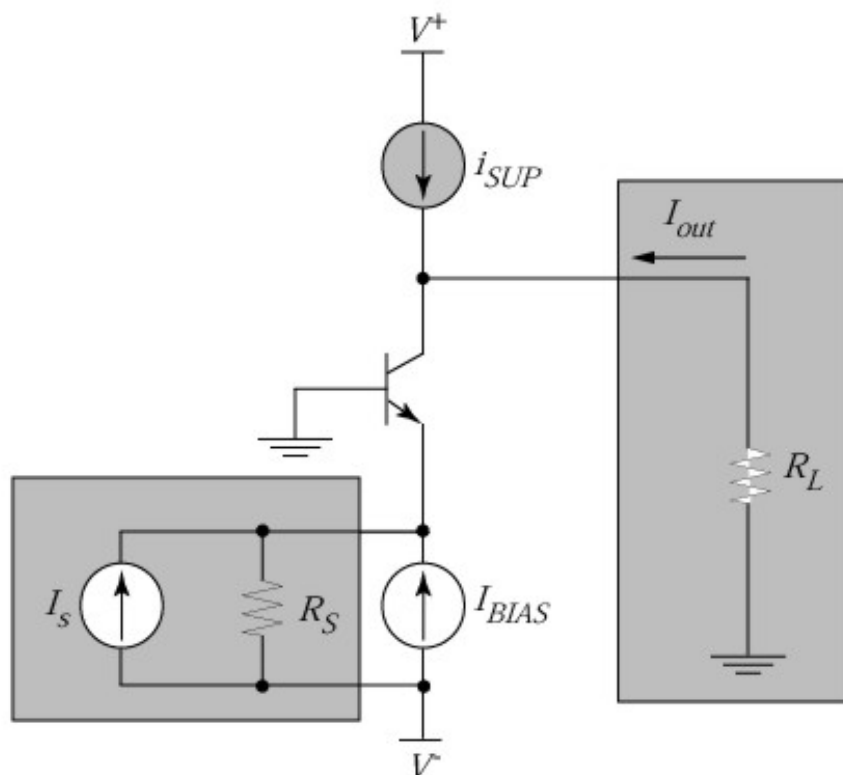
# Bandwidth of the Common-Base Current Buffer



Same procedure: start with two-port model and capacitors

# Two-Port CB Model with Capacitors

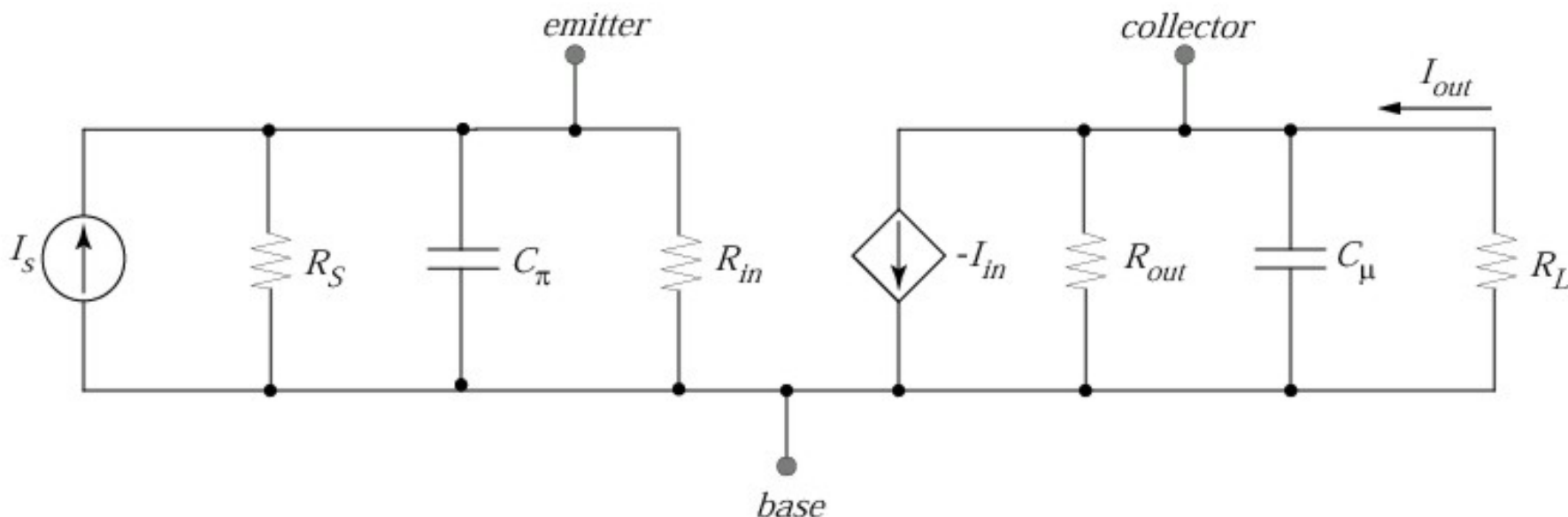

No Miller-transformed capacitor!

Unity-gain frequency is on the order of  $\omega_T$  for small  $R_L$


# Summary of Single-Stage Amplifier Frequency Response

- CE, CS: suffer from Miller-magnified capacitor for high-gain case
- CC, CD: Miller transformation  $\rightarrow$  nulled capacitor  $\rightarrow$  “wideband stage”
- CB, CG: no Millerized capacitor  $\rightarrow$  wideband stage (for low load resistance)



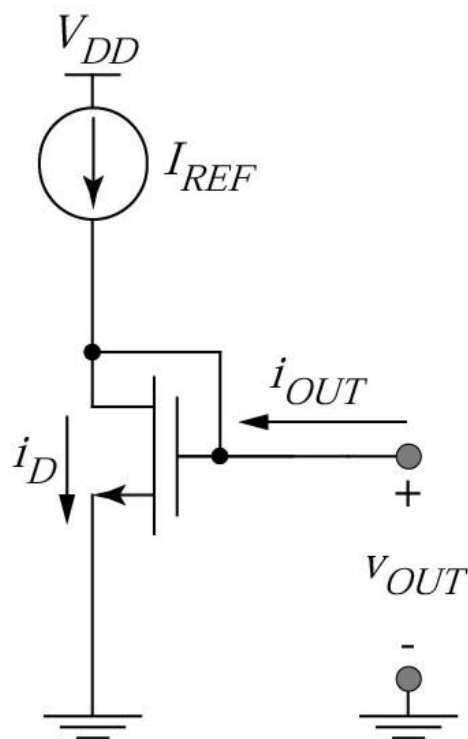
# Multi-Stage Amplifiers: Chap. 9

- First topic: voltage and current sources (9.4)
- Generating a voltage: use a current source to set  $V_{GS}$  (or  $V_{BE}$ )



# Modeling the Voltage Source

Find  $i_{OUT}$  versus  $v_{OUT}$  MOSFET is off or saturated: why?

$$i_{OUT} = i_{D,SAT} - I_{REF} = \mu_n C_{ox} \left( \frac{W}{2L} \right) (v_{GS} - V_{Tn})^2 (1 + \lambda_n v_{DS}) - I_{REF}$$


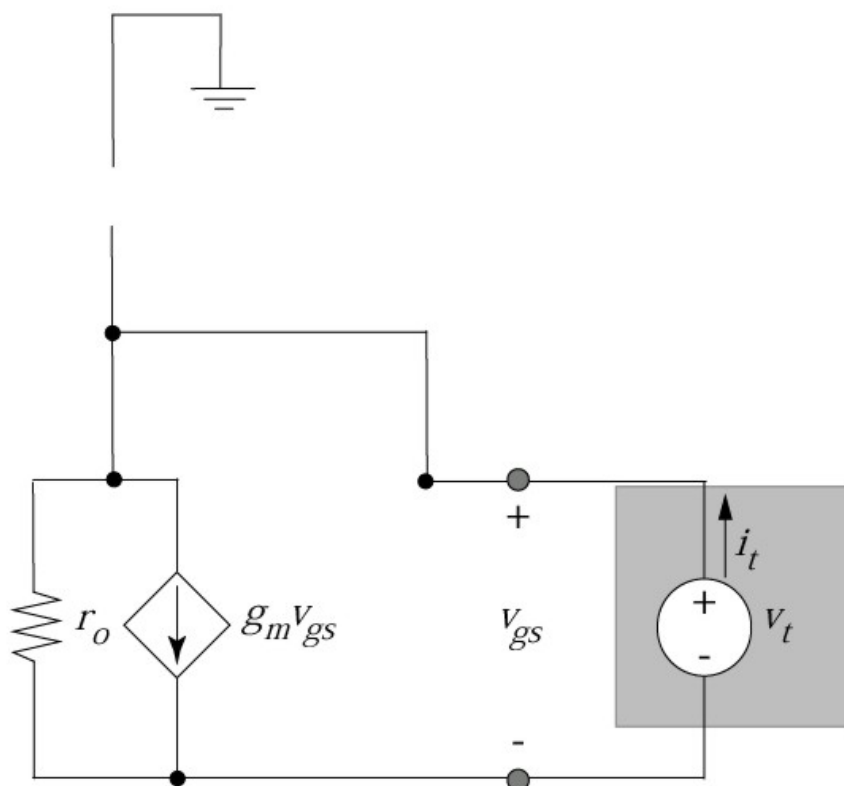


Typical operating point:


$$i_{OUT} = 0 \text{ A}$$

# Small-Signal Source Resistance

$$R_S = \left( \frac{di_{OUT}}{dv_{OUT}} \Big|_{I_{OUT}=0} \right)^{-1} = \frac{v_t}{i_t}$$



Equivalent Circuit:

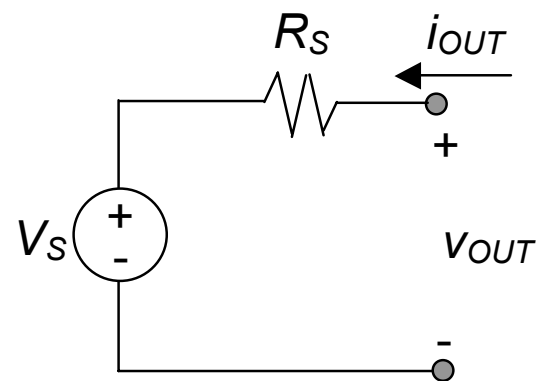

# Using a Voltage Source to Make a Current Source

