

Lecture 33


- Last time:
 - Frequency response of voltage and current buffers
 - Voltage/Current sources using MOS transistors
- Today :
 - Improved current sources
 - Current mirrors

Equivalent Circuit for I -Source

Find the DC current for “gray circle” equivalent circuit

$$I_{OUT} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right)_2 (V_{REF} - V_{Tn})^2 \quad \text{Substitute for } V_{REF}$$


Small-Signal Resistance of I -Source

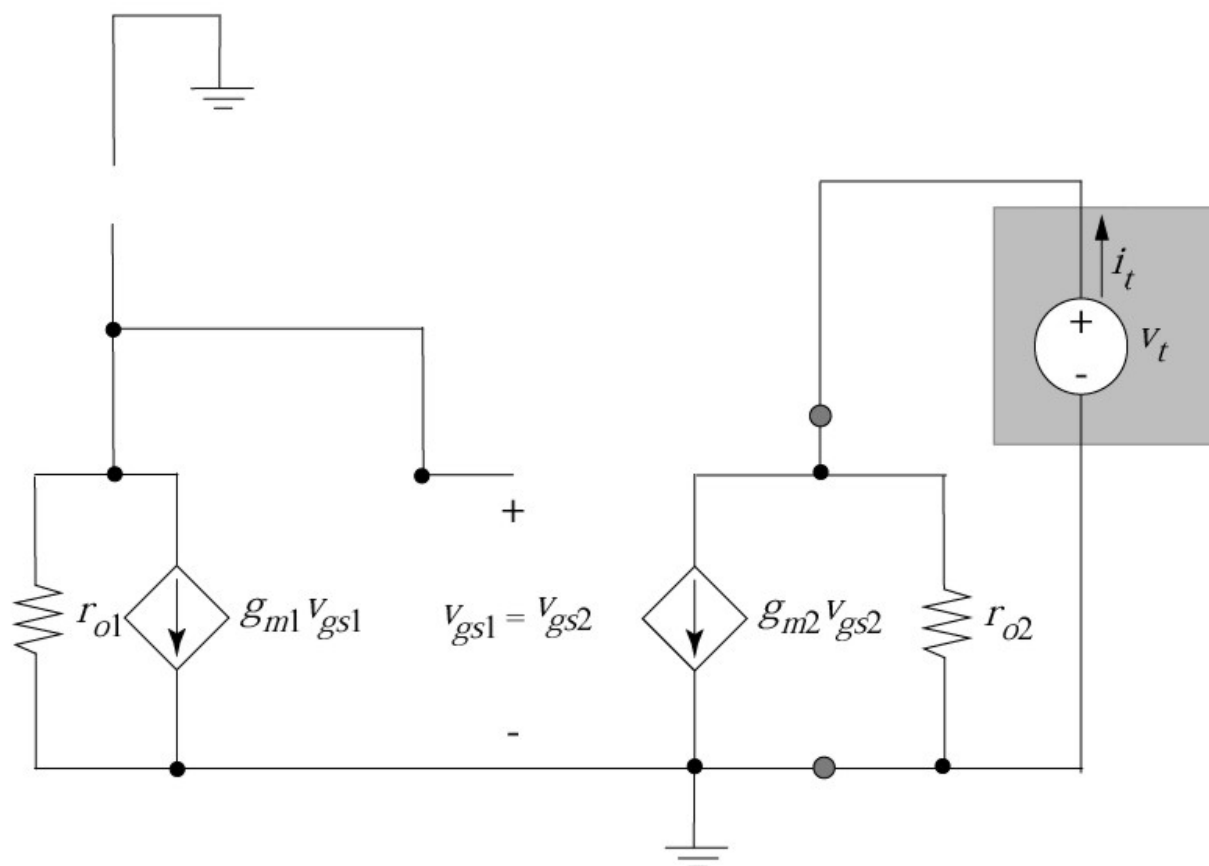


Improved Current Sources

Goal: increase r_{oc}

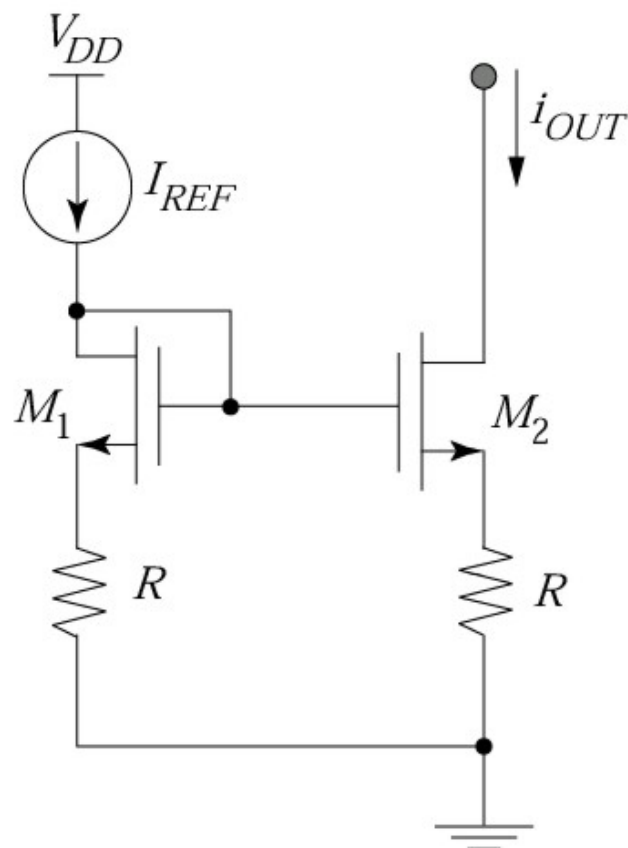Approach: look at *amplifier* (?) output resistance results
... to see topologies that boost resistance



Cascode (or Stacked) Current Source

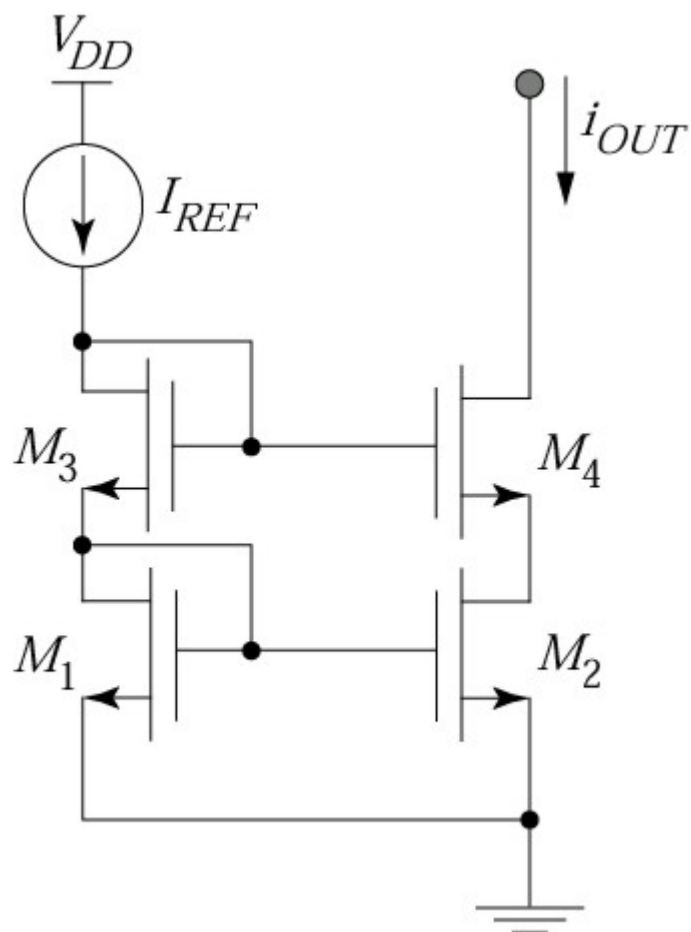

Insight: $V_{GS2} = \text{constant}$ AND
 $V_{DS2} = \text{constant}$

Small-Signal Resistance r_{oc} :

Drawback of Cascode I -Source

Minimum output voltage for all transistors saturated:



$$V_{OUT,MIN} = V_{DS4,SAT} + V_{S4} = V_{DS4,SAT} + V_{GS2}$$



Current Sinks and Sources


Sink: output current goes to ground

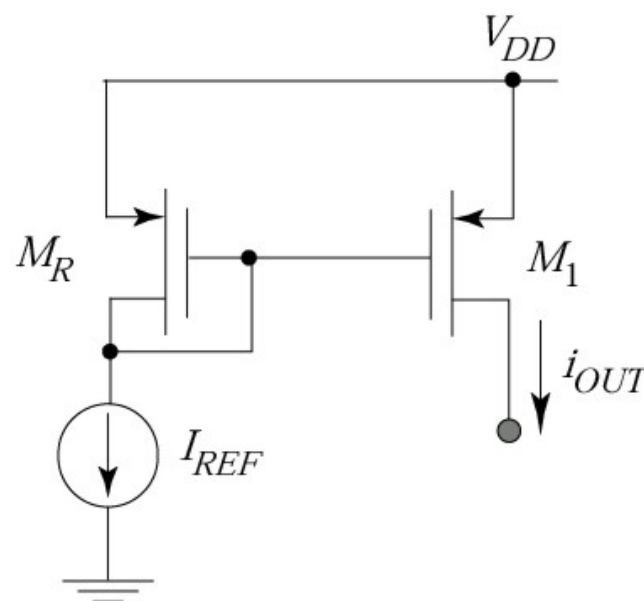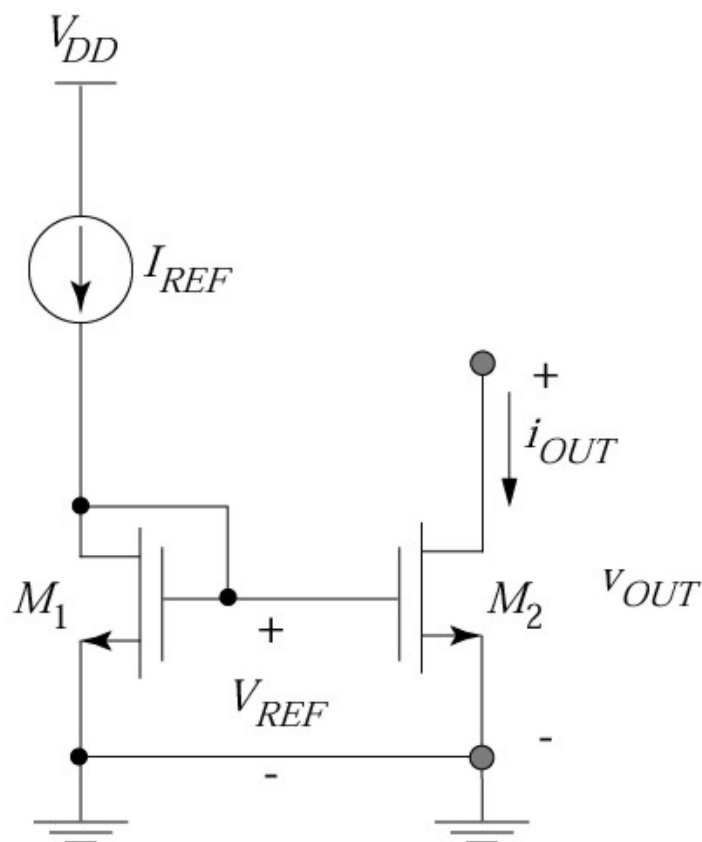Source: output current comes from voltage supply



Current Mirrors

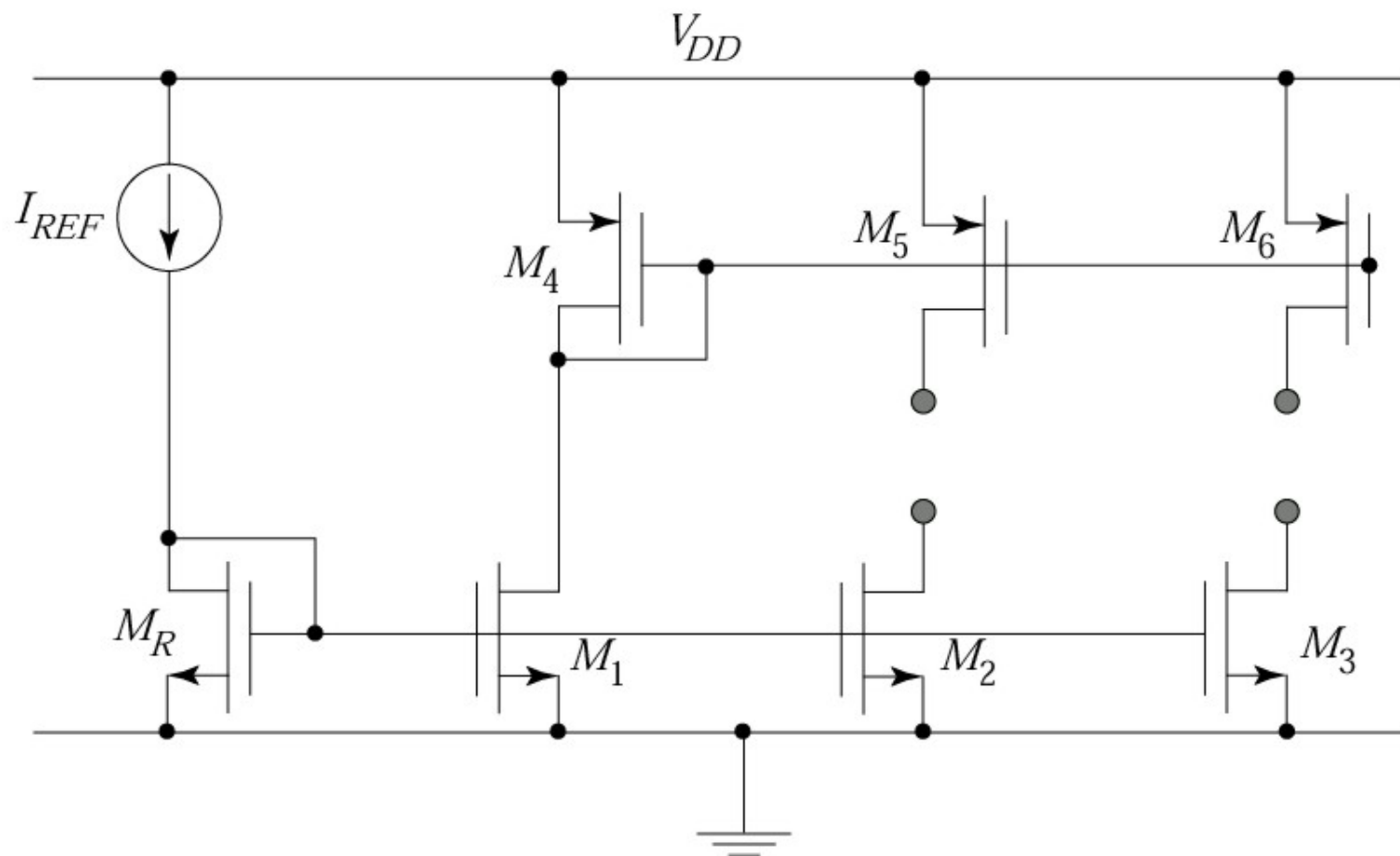Idea: we only need one reference current to set up all the current sources and sinks needed for a multistage amplifier.



Multistage Amplifiers

Necessary to meet typical specifications for any of the 4 types


We have 2 flavors (NMOS, PMOS) of CS, CG, and CD and the npn versions of CE, CB, and CC (for a BiCMOS process)

What are the constraints?

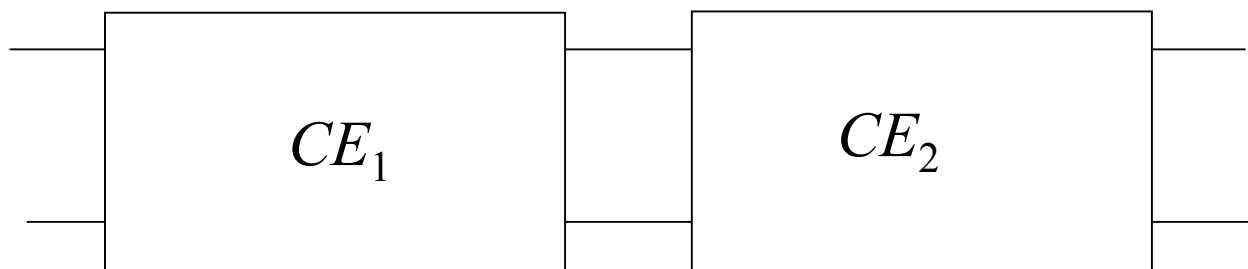1. Input/output resistance matching
2. DC coupling (no passive elements to block the signal)

Start: Two-Stage Voltage Amplifier


- Use two-port models to explore whether the combination “works”



Results: $R_{in} = R_{in1}$, $R_{out} = R_{out2}$, $A_v =$


Add a Third Stage: CC

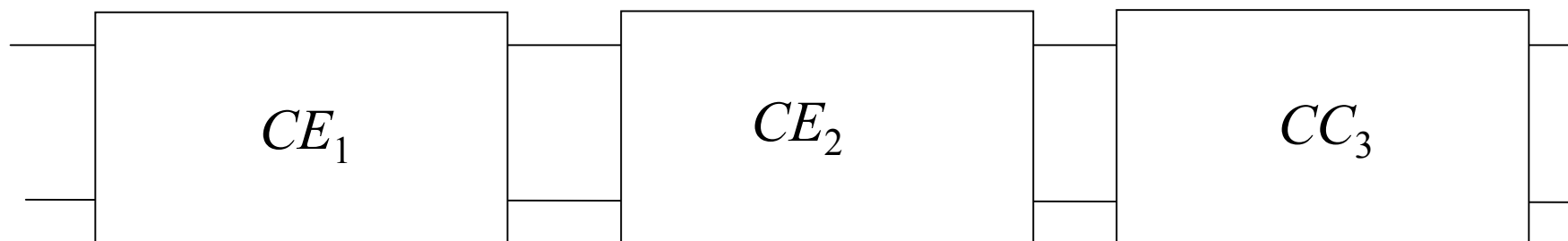Goal: reduce the output resistance
(important spec. for a voltage amp)



Output resistance:

Using CMOS Stages

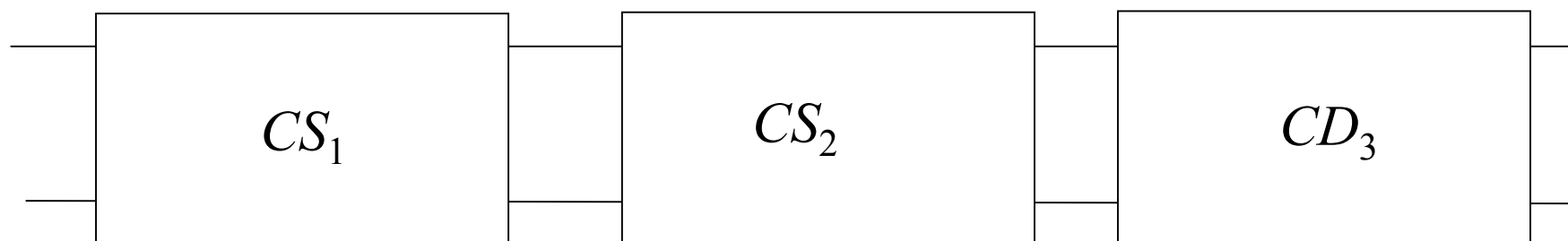

Input resistance:

Voltage gain (2-port parameter):

Output resistance: