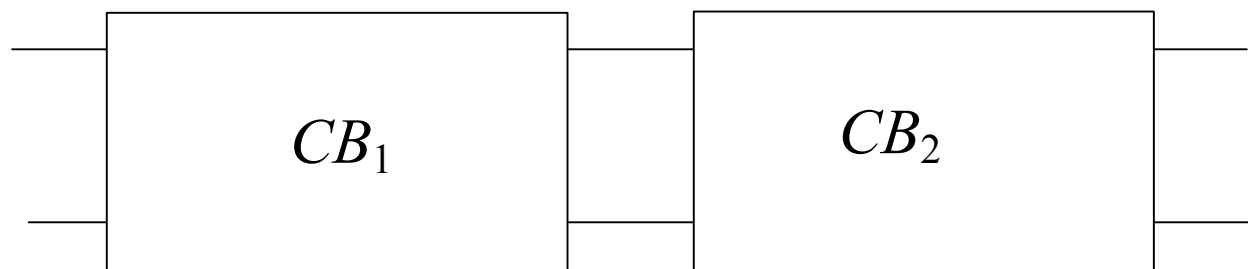


Lecture 34

- Last time:
 - Improved current sources and current mirrors
 - Start multistage amplifiers
- Today :
 - More examples of cascades
 - DC coupling issues


Multistage Current Buffers

Are two cascaded common-base stages better than one?




Input resistance: $R_{in} = R_{in1}$

Two-Port Models

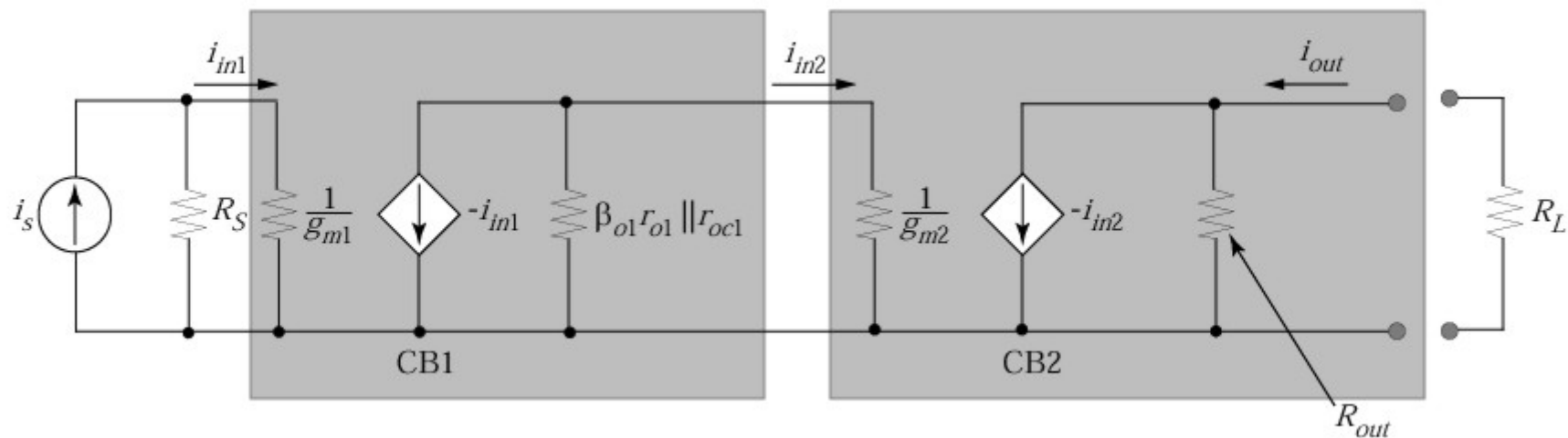

$$R_{out} = R_{out2} \cong r_{o2} \left(1 + g_{m2} r_{\pi 2} \parallel R_{S2} \right) \parallel r_{oc2}$$

Common-Gate 2nd Stage

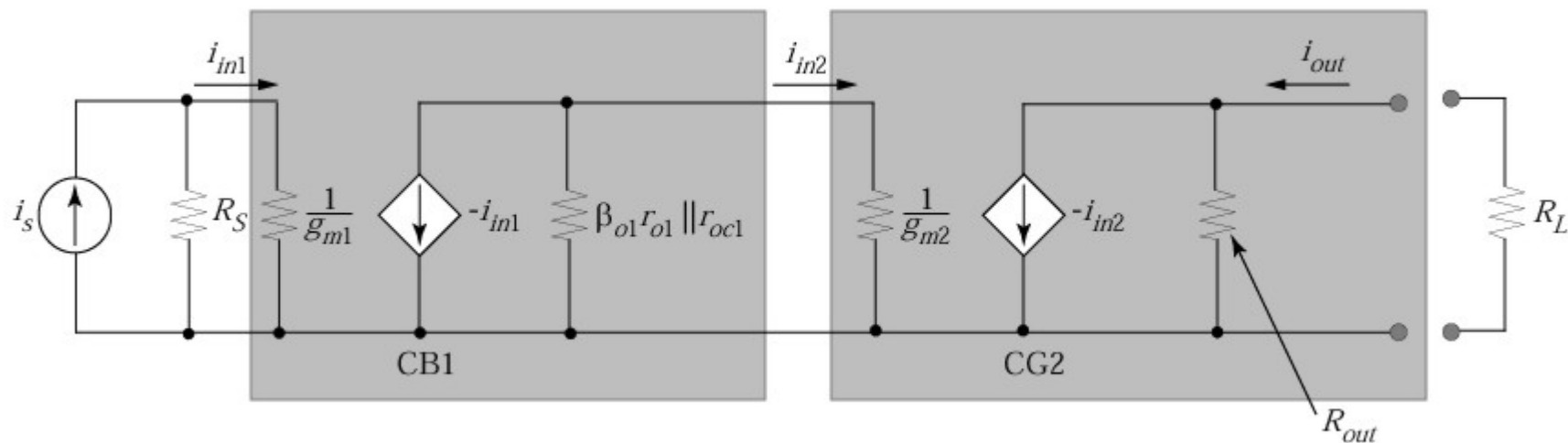

$$R_{out} = R_{out2} \cong r_{o2} (1 + g_{m2} R_{S2}) \parallel r_{oc2}$$

Summary of Cascaded Amplifiers

General goals:

1. Boost the gain parameter (except for buffers)
2. Optimize the input and output resistances

 R_{in} R_{out}

Voltage:

Current:


Transconductance:

Transresistance:

Second Design Issue: DC Coupling


Constraint: large inductors and capacitors are not available

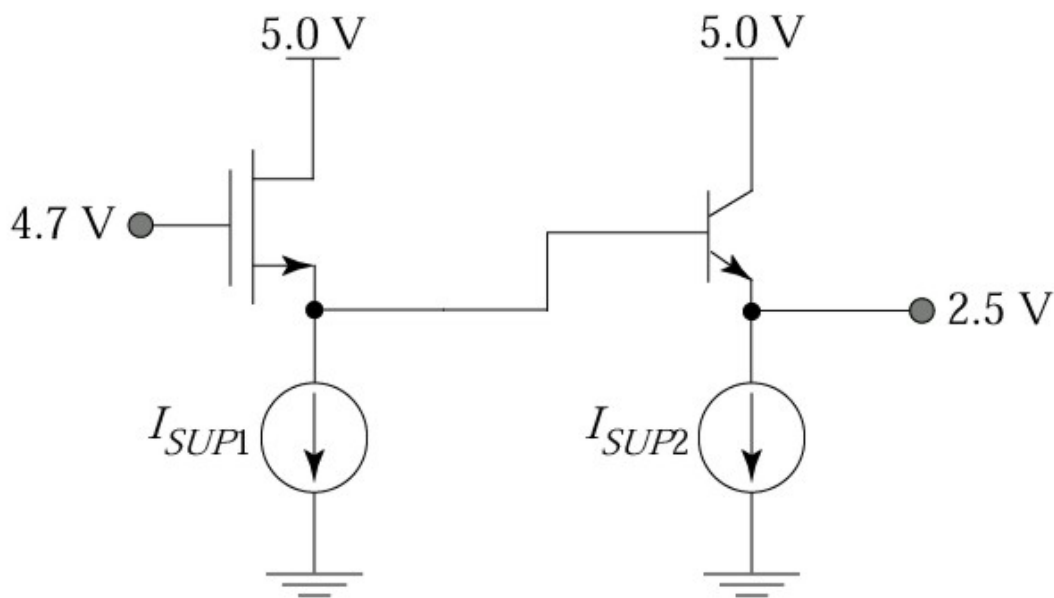Output of one stage is directly connected to the input of the next stage → must consider DC levels ... why?




Alternative CG-CC Cascade

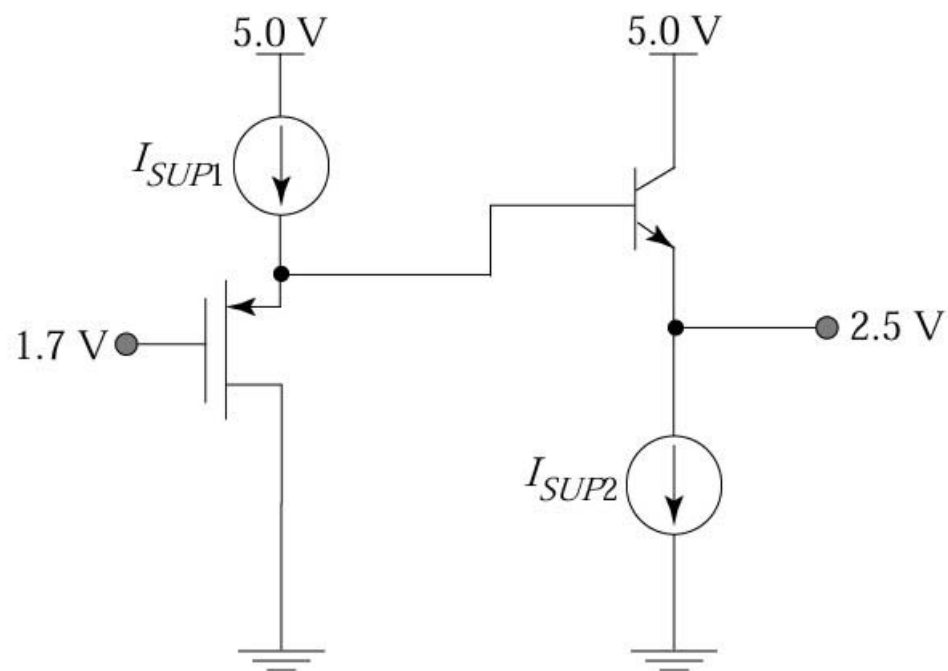Use a PMOS CD Stage: DC level shifts upward



CG Cascade: DC Biasing

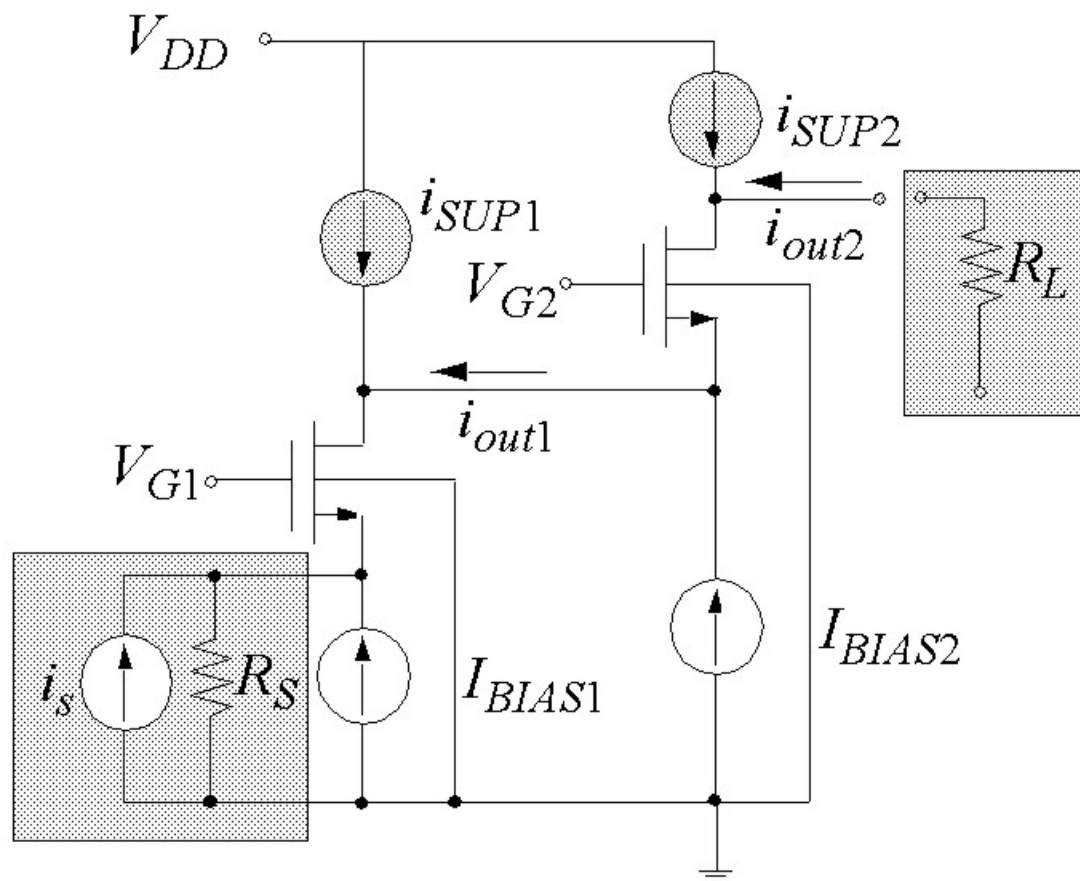
Two stages can have different supply currents



Extreme case:
 $I_{BIAS2} = 0$ A

CG Cascade: Sharing a Supply

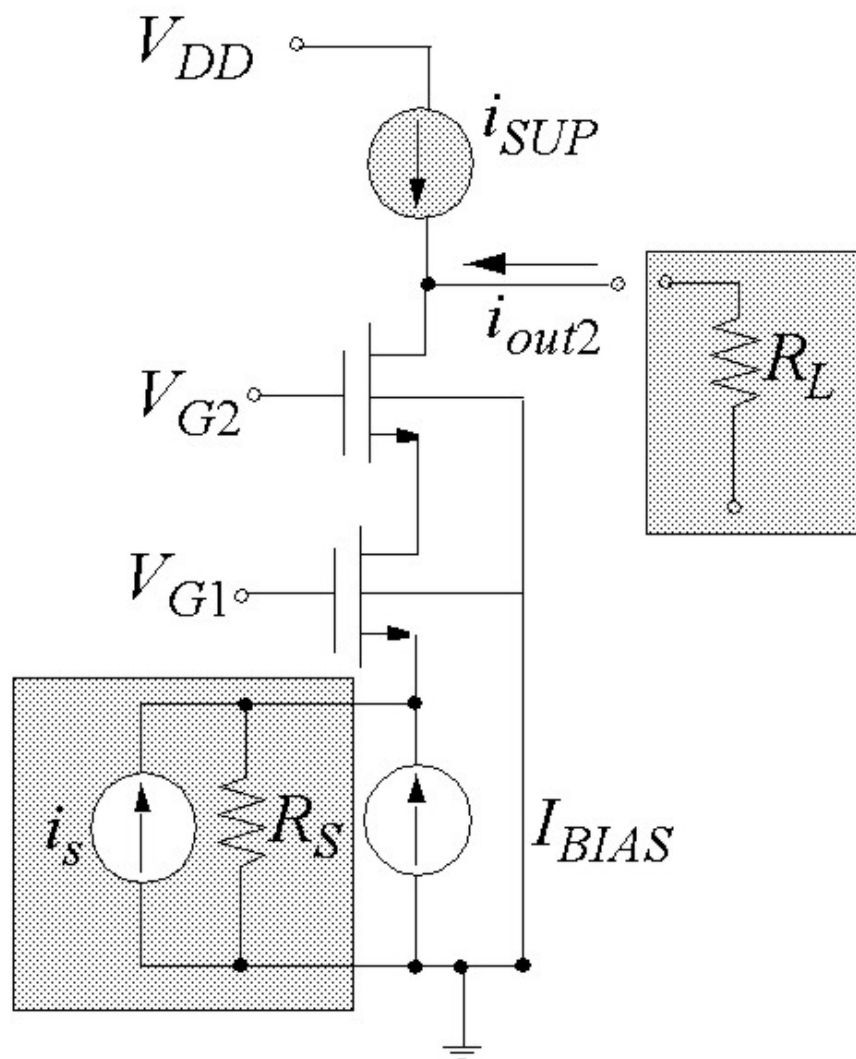First stage has no current supply of its own \rightarrow its output resistance is modified



Two-Port Model of Common-Gate Cascade with Shared Current Supply

