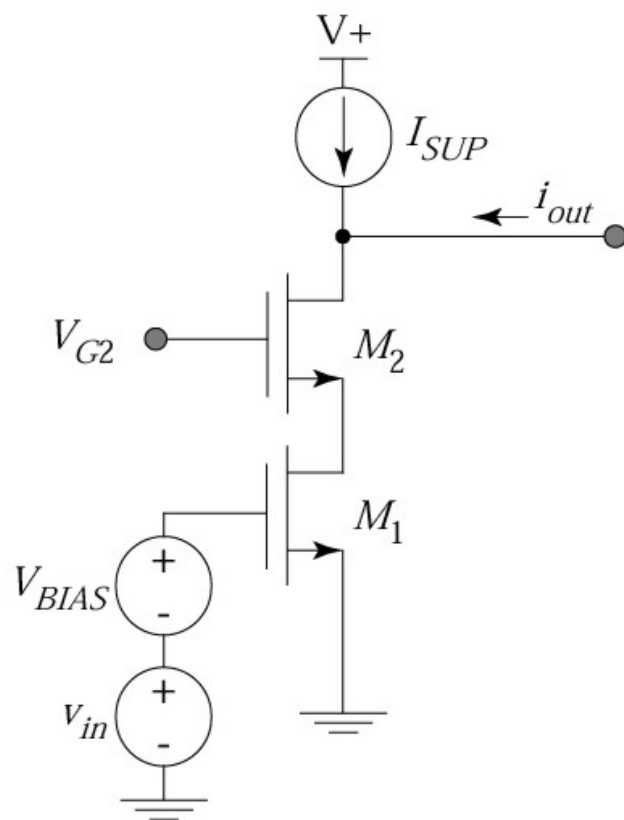


Lecture 35

- Last time:
 - More examples of cascades
 - DC coupling issues
- Today :
 - Cascode amplifiers
 - Totem pole voltage supplies
 - Start: multistage amplifier design examples

The Cascode Configuration




Common source / common gate cascade is one version of a *cascode* (all have shared supplies)

DC bias:

Two-port model: first stage has no current supply of its own

Cascode Two-Port Model

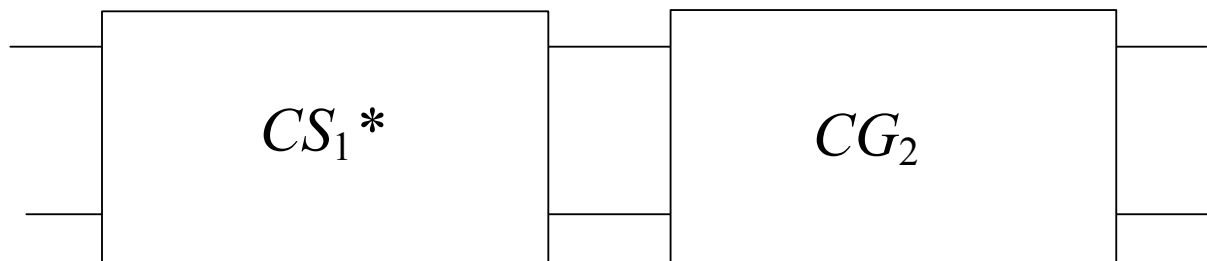


Output resistance of first stage = $R_{out,CS^*} = R_{down,CS} = r_{o1}$

Why is the cascode such an important configuration?


Miller Capacitance of Input Stage

Find the Miller capacitance for C_{gd1}

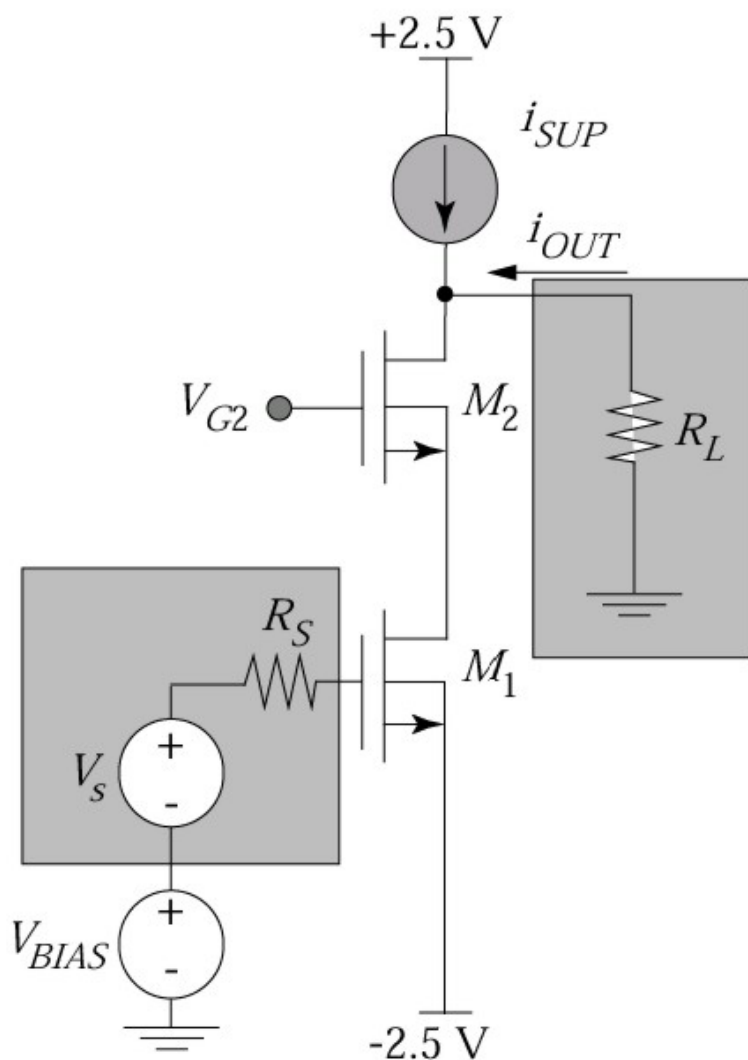

Input resistance to common-gate second stage is low \rightarrow gain across C_{gd1} is small.

Two-Port Model with Capacitors

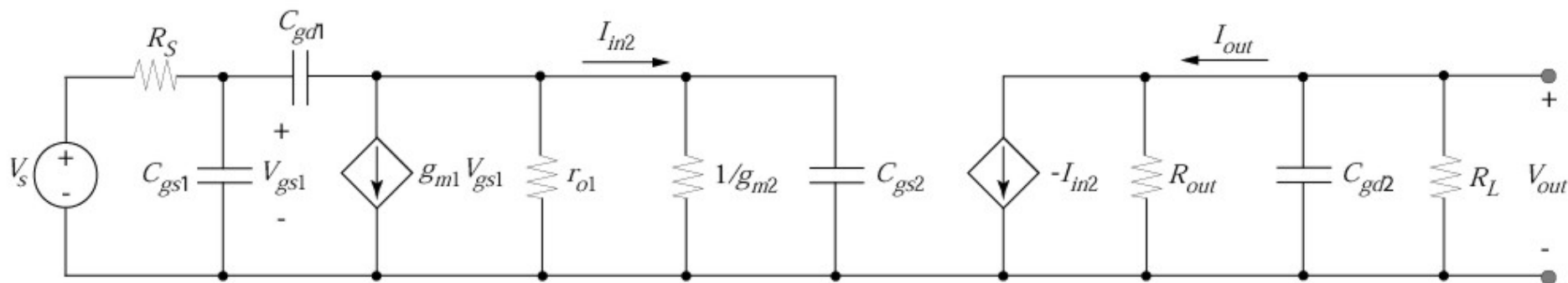

Miller capacitance:
$$C_M = (1 - A_v C_{gs1}) C_{gs1}$$

Other Cascode Configurations

Basic configuration: transconductance stage
followed by current buffer


$$CE_n - CG_n$$

$$CS_n - CB$$

$$CS_p - CG_n$$


Generating Multiple DC Voltages

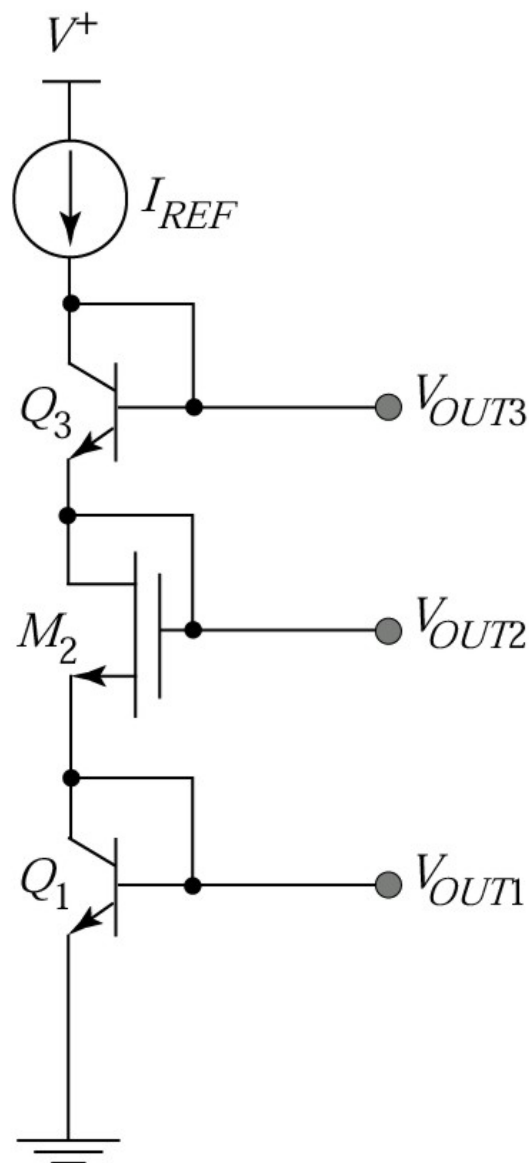Stack-up diode-connected MOSFETs or BJTs and run a reference current through them → pick off voltages from gates or bases as references



Multistage Amplifier Design Examples

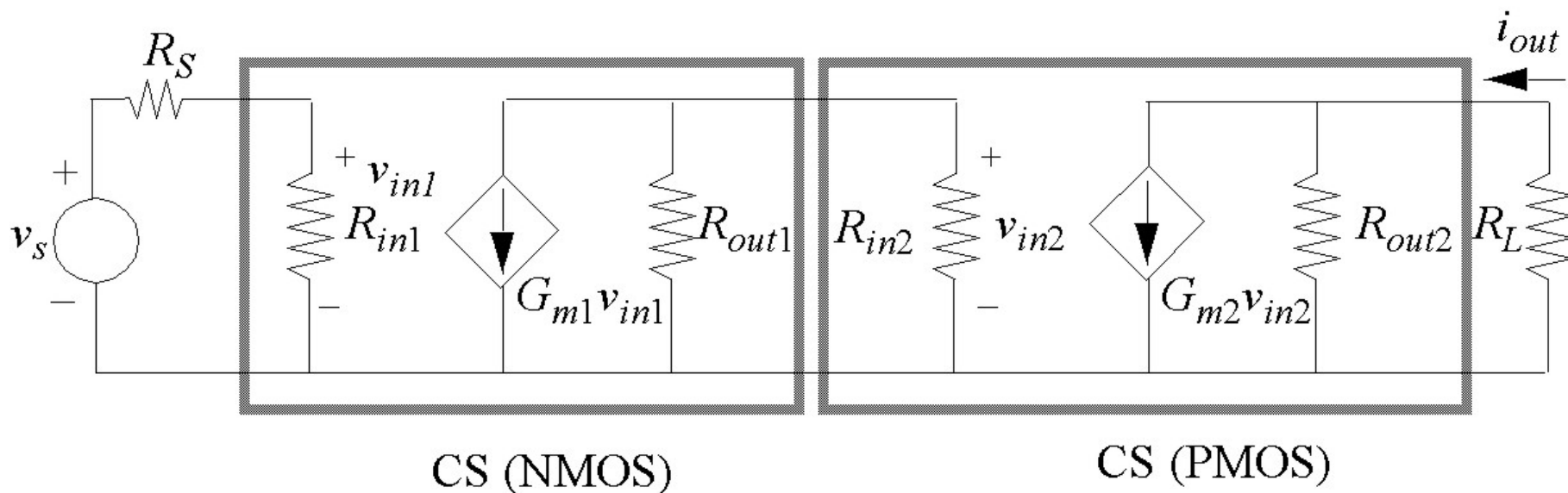
Start with basic two-stage transconductance amplifier:



Why do this combination?

Two-Stage Amplifier Topology


Direct DC connection: use NMOS then PMOS

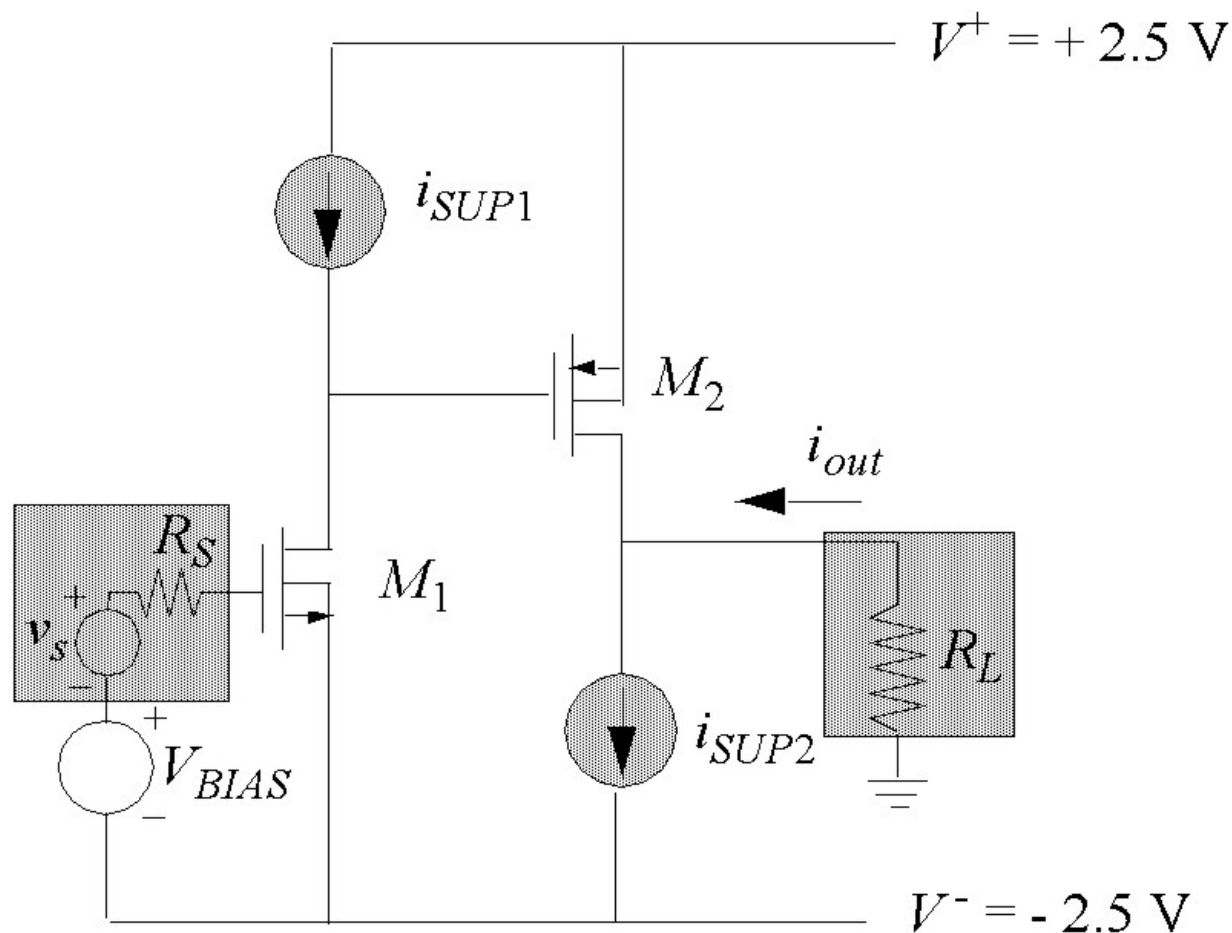


Current Supply Design

Assume that the reference is a “sink” set by a resistor

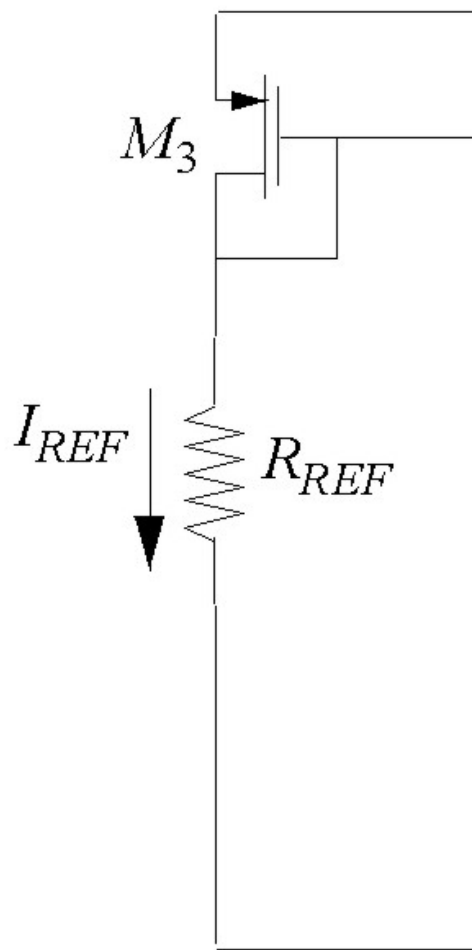
Must mirror the reference current and generate a sink for $i_{SUP 2}$



Use Basic Current Supplies

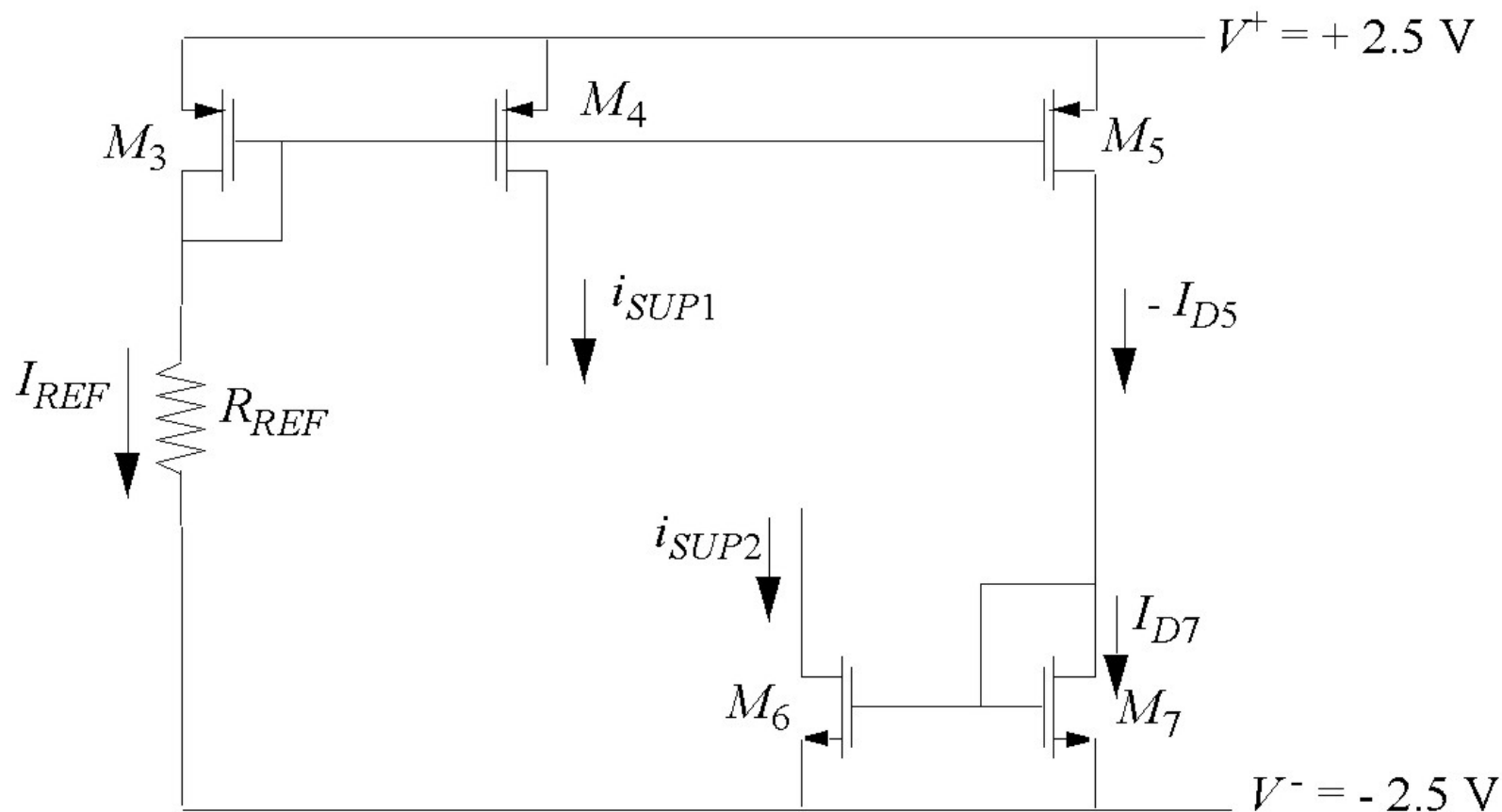

Complete Amplifier Topology

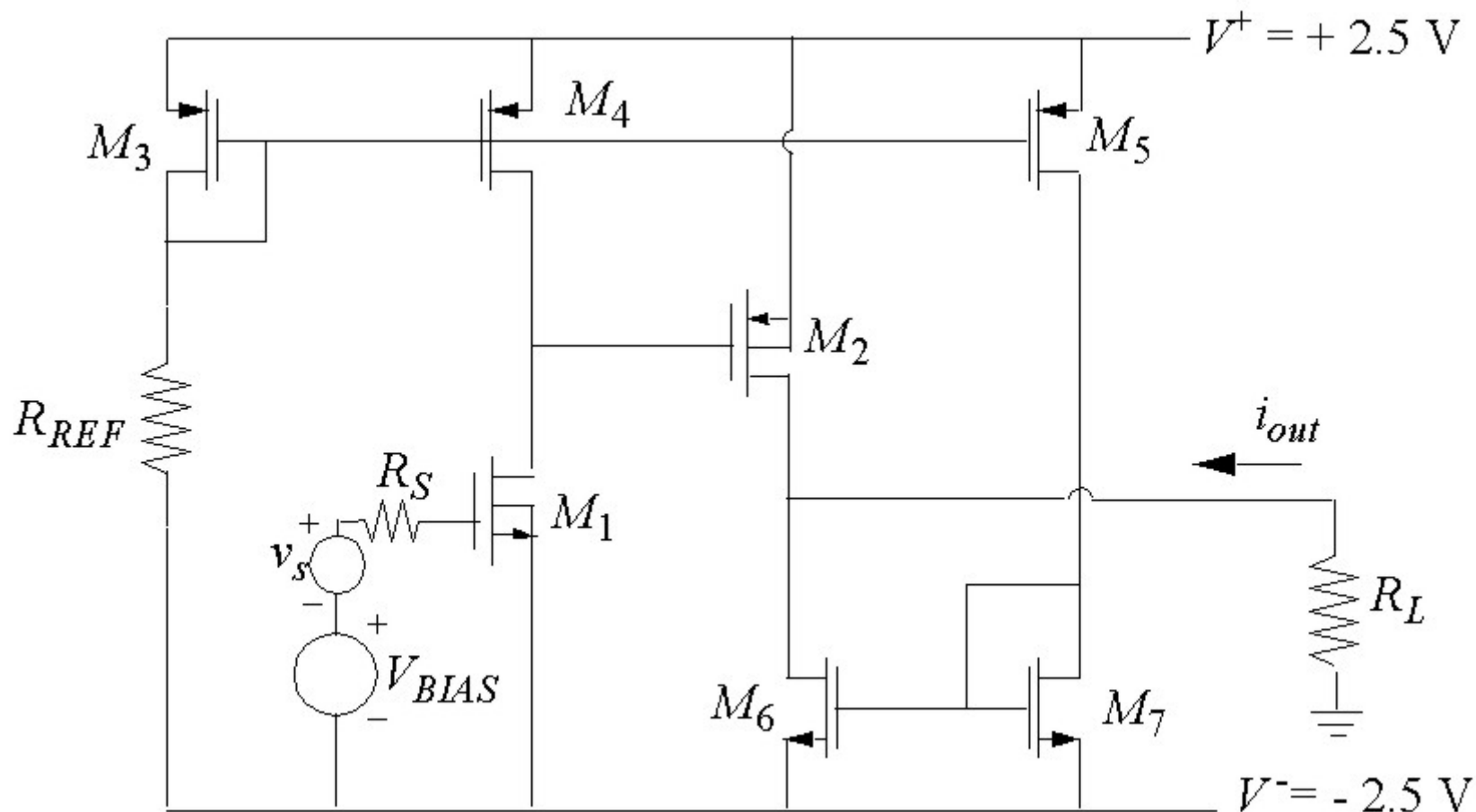

What's missing? The device dimensions and the bias voltage and reference resistor