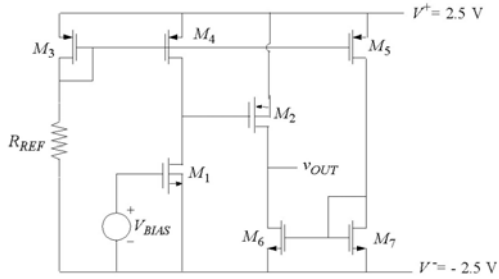


## Output Voltage Swing



Transistors  $M_2$  and  $M_6$  will limit the output swing

## Limits to Output Voltage

$M_6$  will leave saturation when  $v_{OUT}$  drops to:

$$v_{OUT,MIN} = V^- + V_{DS6,sat} = -2.5 + \sqrt{\frac{2I_{D6}}{\mu_n C_{ox} (W/L)_6}}$$

$$v_{OUT,MIN} = -2.5 + 0.28 = -2.22 \text{ V}$$

$M_2$  will leave saturation when  $v_{OUT}$  rises to:

$$v_{OUT,MAX} = V^+ - V_{SD2,sat} = 2.5 - \sqrt{\frac{2(-I_{D2})}{\mu_p C_{ox} (W/L)_2}}$$


$$v_{OUT,MAX} = 2.5 - 0.32 = 2.18 \text{ V}$$

What about  $M_4$ ?
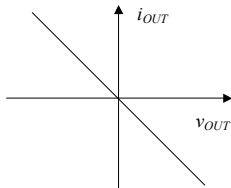
## Output Current Swing

Load resistor: pick  $R_L = 25 \text{ k}\Omega$

Output current:  $i_{OUT} = -v_{OUT} / R_L$



$$i_{OUT} = i_{D6} - (-i_{D2})$$

Limits: asymmetrical

$M_2$ : can increase  $-i_{D2}$

$M_6$ : can't increase  $i_{D6}$

## Output Current Limits

- Positive output current (negative  $v_{OUT}$ )

$$i_{OUT,MAX} = i_{D6} - (0) = 50 \mu\text{A} = -v_{OUT,MIN} / R_L$$

$$v_{OUT,MIN} = -(50 \mu\text{A})(25 \text{ k}\Omega) = -1.25 \text{ V}$$

(less negative than limit set by saturation of  $M_6$ )

- Negative output current (positive  $v_{OUT}$ )

No limit on current from  $M_2$ , so voltage swing sets current limit

$$i_{OUT,MIN} = -v_{OUT,MAX} / R_L = -(2.18 \text{ V} / 25 \text{ k}\Omega) = -87.2 \mu\text{A}$$

## Transfer Curves (for $R_L = 25 \text{ k}\Omega$ )

Loaded voltage gain  $= v_{out}/v_{in} = (g_{m1}R_{out1})(g_{m2}R_{out}\parallel R_L) = 490$

Loaded transconductance  $= i_{out}/v_{in}$   
 $= (-g_{m1}R_{out1})(g_{m2})(R_{out}\parallel(R_{out} + R_L)) = -19.5 \text{ mS}$

