

# Lecture 37

- Last time:
  - Complete “lecture design” of two-stage CMOS transconductance amplifier
- Today :
  - CMOS cascode transconductance amplifier design example


# Amplifier Topology

Goals:  $R_{in}$  and  $R_{out}$  should be maximized

Common source – common gate cascode makes sense


Share the current supply

# Amplifier Schematic

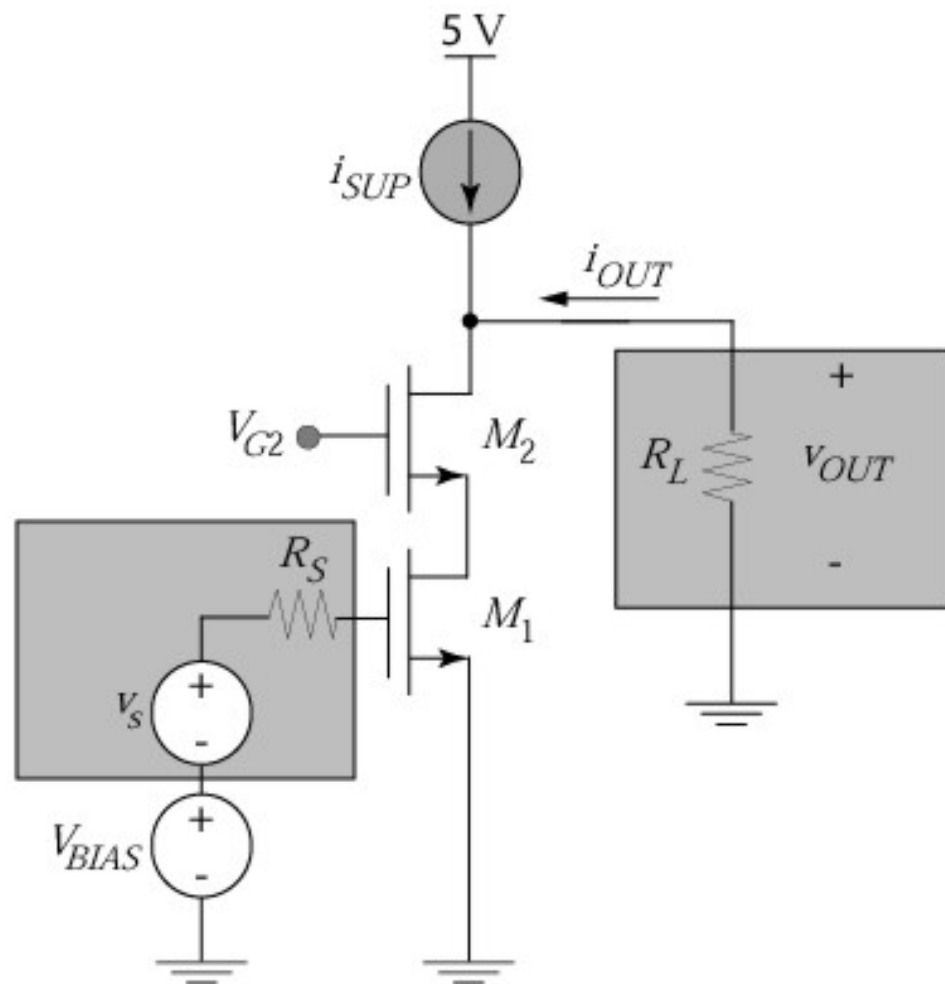

Note that the backgate connection for  $M_2$  is not specified: ignore  $g_{mb}$


# Current Supply Design

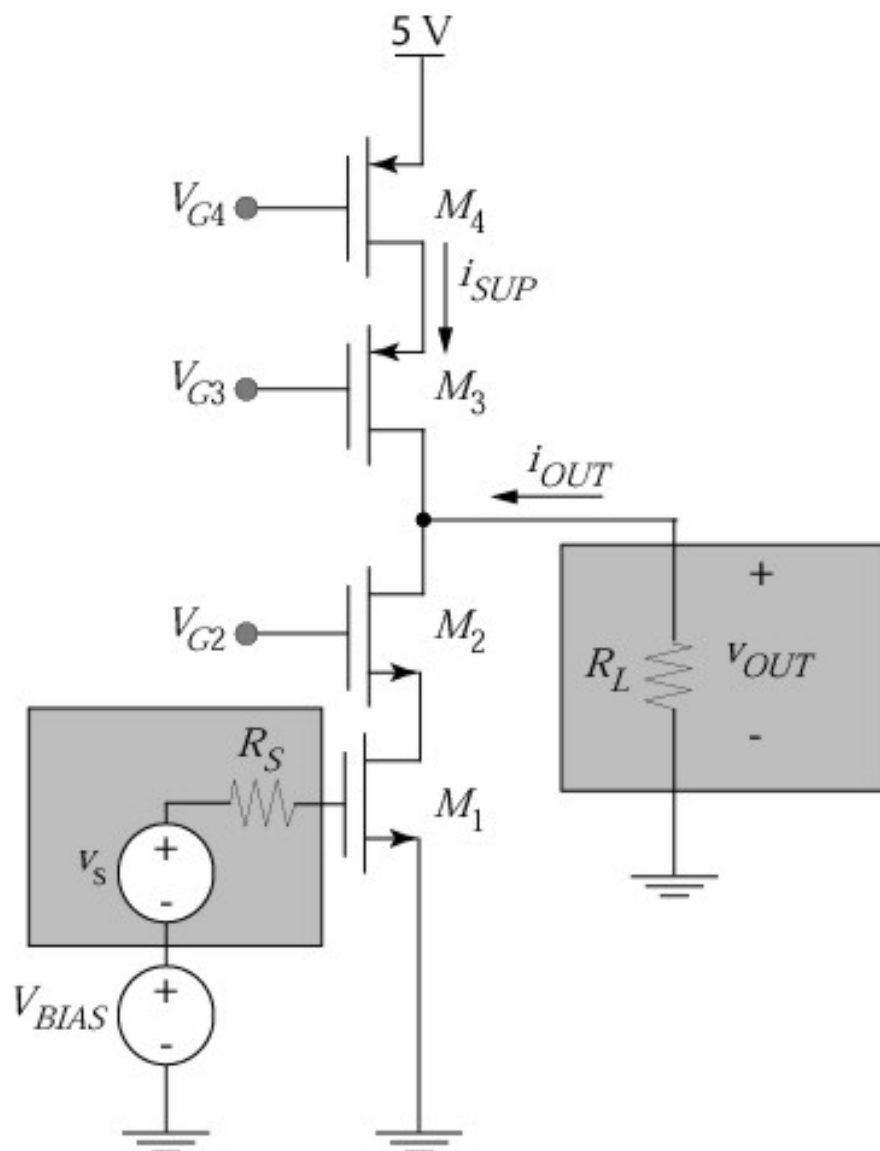

Output resistance goal  
requires large  $r_{oc} \rightarrow$   
use cascode current source

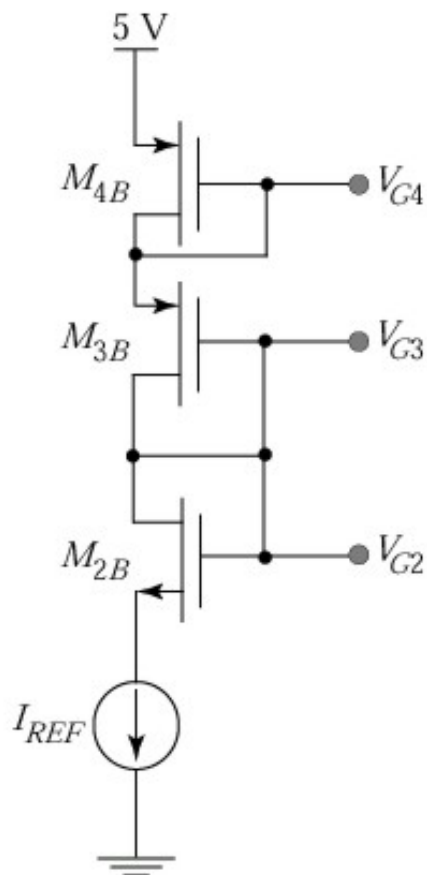
# Totem Pole Voltage Supply

DC voltages must be set for the cascode current supply transistors  $M_3$  and  $M_4$ , as well as the gate of  $M_2$ .



Why include  $M_{2B}$ ?

# Complete Amplifier Schematic

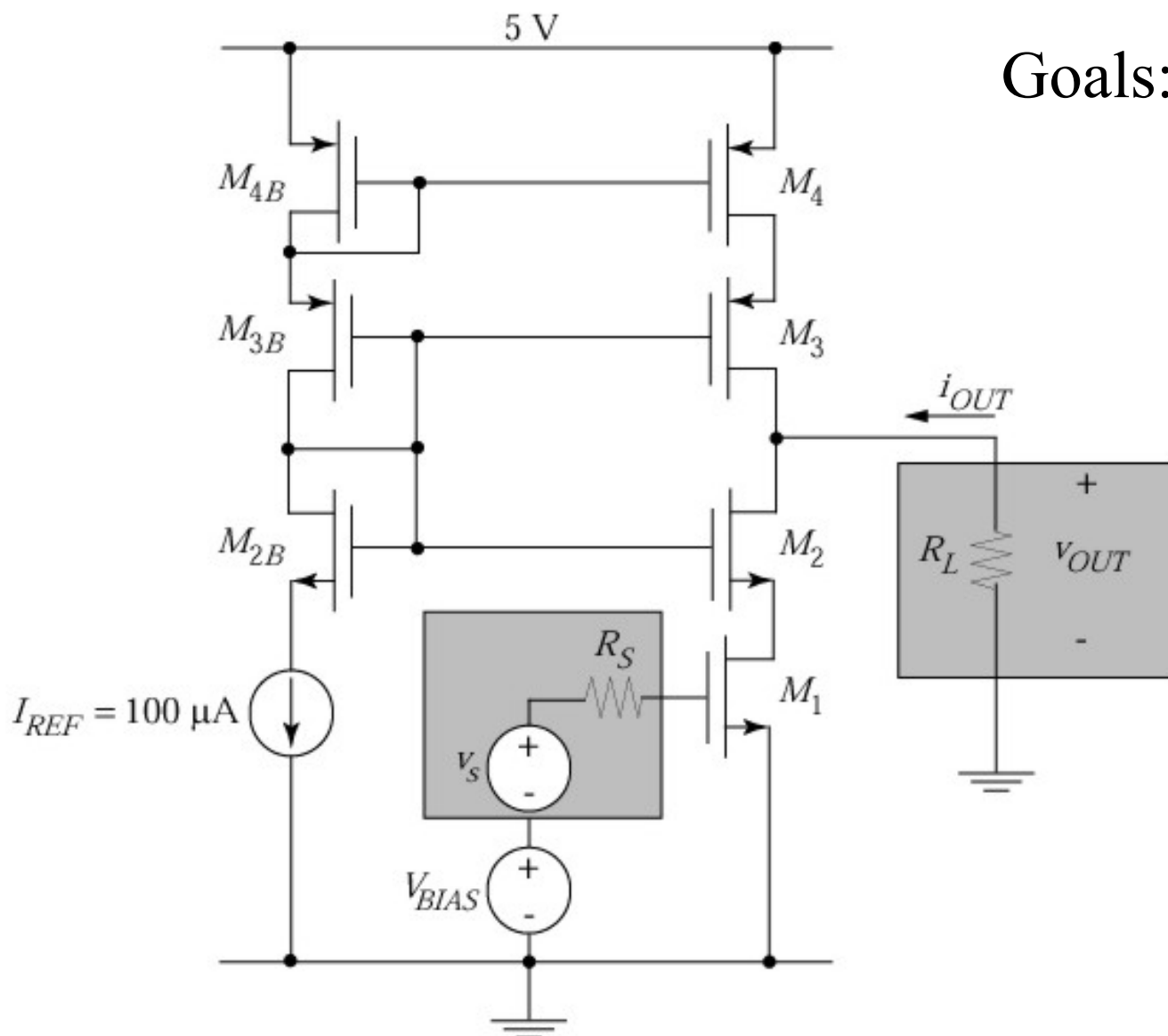

Goals:  $g_{m1} = 1 \text{ mS}$ ,  
 $R_{out} = 10 \text{ M}\Omega$

# Device Sizes

$M_1$ : select  $(W/L)_1 = 200/2$  to meet specified  $g_{m1} = 1 \text{ mS}$

→ find  $V_{BIAS} = 1.2 \text{ V}$

Cascode current supply devices: select  $V_{SG} = 1.5 \text{ V}$

$(W/L)_4 = (W/L)_{4B} = (W/L)_3 = (W/L)_{3B} = 64/2$


$M_2$ : select  $(W/L)_2 = 50/2$  to meet specified  $R_{out} = 10 \text{ M}\Omega$

→ find  $V_{GS2} = 1.4 \text{ V}$

Match  $M_2$  with diode-connected device  $M_{2B}$ .

Assuming perfect matching and zero input voltage,  
what is  $V_{OUT}$ ?

# Output (Voltage) Swing

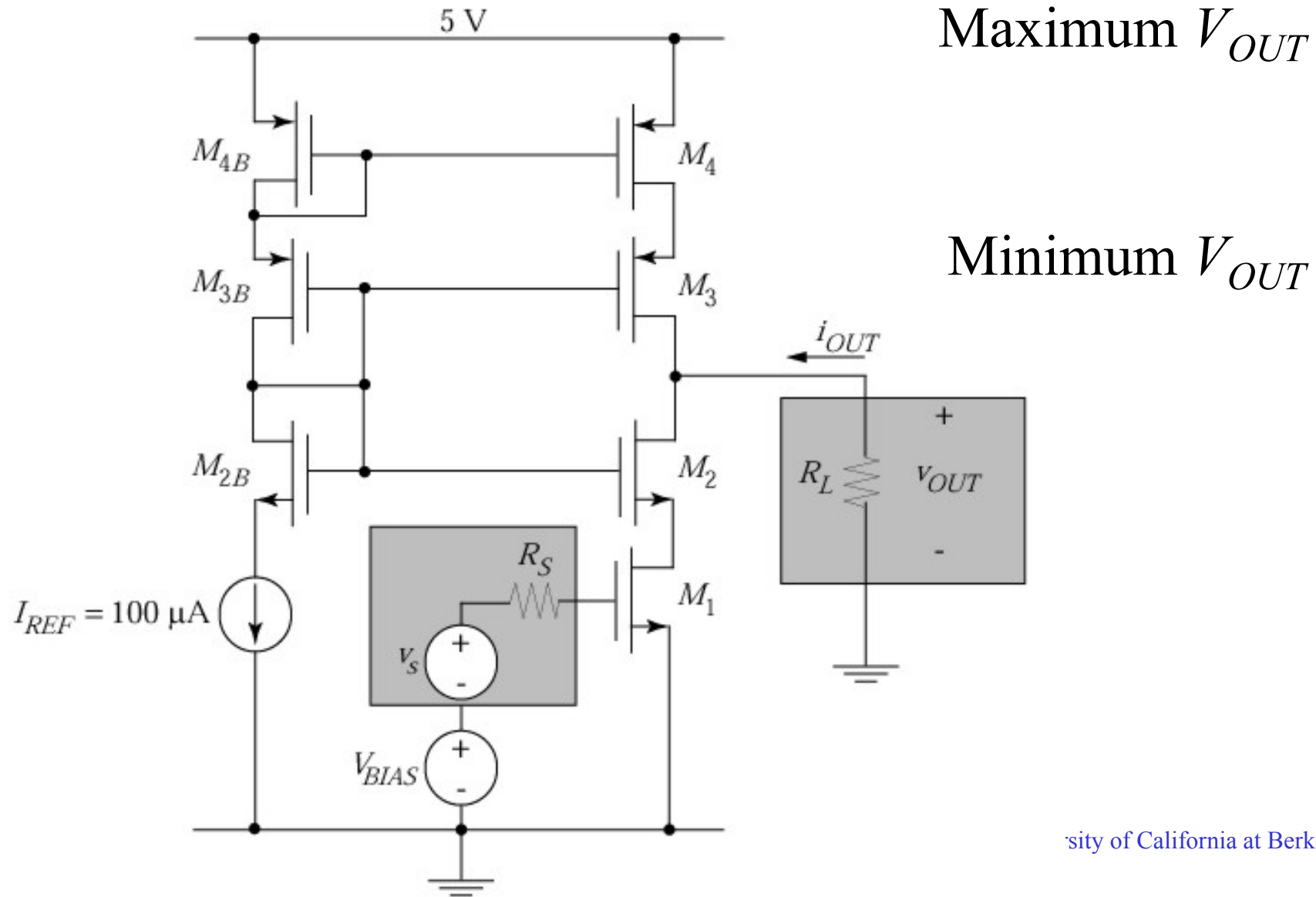



# Two-Port Model

Find output resistance  $R_{out}$

$$\lambda_n = (1/20) \text{ V}^{-1}, \lambda_n = (1/50) \text{ V}^{-1} \text{ at } L = 2 \mu\text{m} \rightarrow$$

$$r_{on} = (100 \mu\text{A} / 20 \text{ V}^{-1})^{-1} = 200 \text{ k}\Omega, r_{op} = 500 \text{ k}\Omega$$

$$g_{m2} = \frac{2I_{D2}}{V_{GS2} - V_{Tn}} = \frac{2(100 \mu\text{A})}{1.4\text{V} - 1\text{V}} = 500 \mu\text{S}$$

$$g_{m3} = \frac{2(-I_{D3})}{V_{SG3} + V_{Tp}} = \frac{2(100 \mu\text{A})}{1.5\text{V} - 1\text{V}} = 400 \mu\text{S}$$

$$R_{out} = r_{oc} \parallel r_{o2} (1 + g_{m2} R_{S2}) = r_{o3} (1 + g_{m3} R_{S3}) \parallel r_{o2} (1 + g_{m2} r_{o1})$$

# Voltage Transfer Curve

Open-circuit voltage gain:  $A_v = v_{out} / v_{in} = -g_{m1}R_{out}$

