

Lecture 4

- Last time:
 - Circuit analysis with phasors: impedances
 - Bode plot of low-pass filter (start)
- Today :
 - Bode plot sketching for first-order transfer functions
 - Low-pass and high-pass filters

Bode Plots for Low-Pass Filter

1. Plot magnitude $|H|$ in dB vs. ω (log scale)
2. Plot phase $\angle H$ in degrees vs. ω (log scale)

$$|H|_{dB} = \left| \frac{1}{1 + j\omega\tau} \right|_{dB} = \left[\frac{|1|}{|1 + j\omega\tau|} \right]_{dB}$$

Why?


Sketching the Magnitude Plot

$$|H|_{dB} = \left[\frac{|1|}{|1 + j\omega\tau|} \right]_{dB} = 20 \log \left[\frac{1}{\sqrt{1 + (\omega\tau)^2}} \right]$$

Low-frequency ($\omega \tau \ll 1$) asymptote

High-frequency ($\omega \tau \gg 1$) asymptote

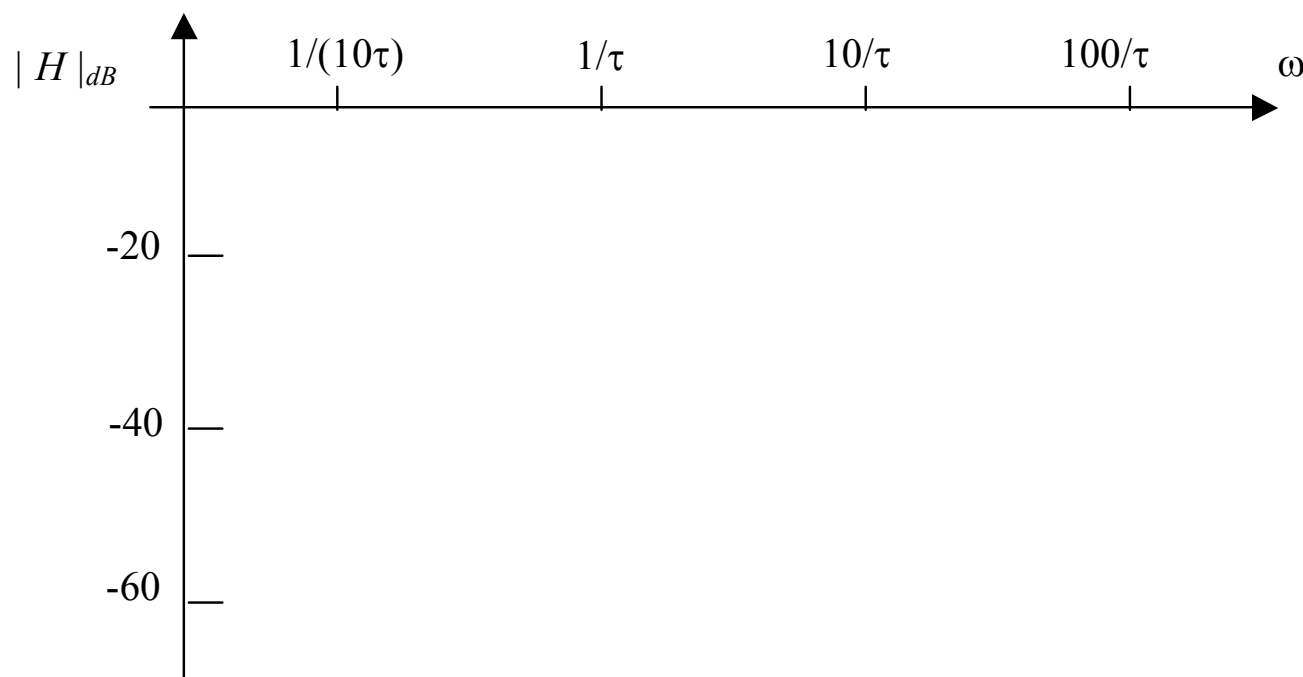The Break Frequency $\omega_{-3\text{dB}} = (1/\tau)$



Finding the Phase Plot

$$\angle(H) = \angle\left[\frac{1}{1 + j\omega\tau}\right] = 0 - \arctan(\omega\tau)$$


Why?

Low-frequency asymptote

High-frequency asymptote


Approx. linear with ω for $1/(10\tau) < \omega < 10/\tau$

Rapidly Sketching the Phase Plot

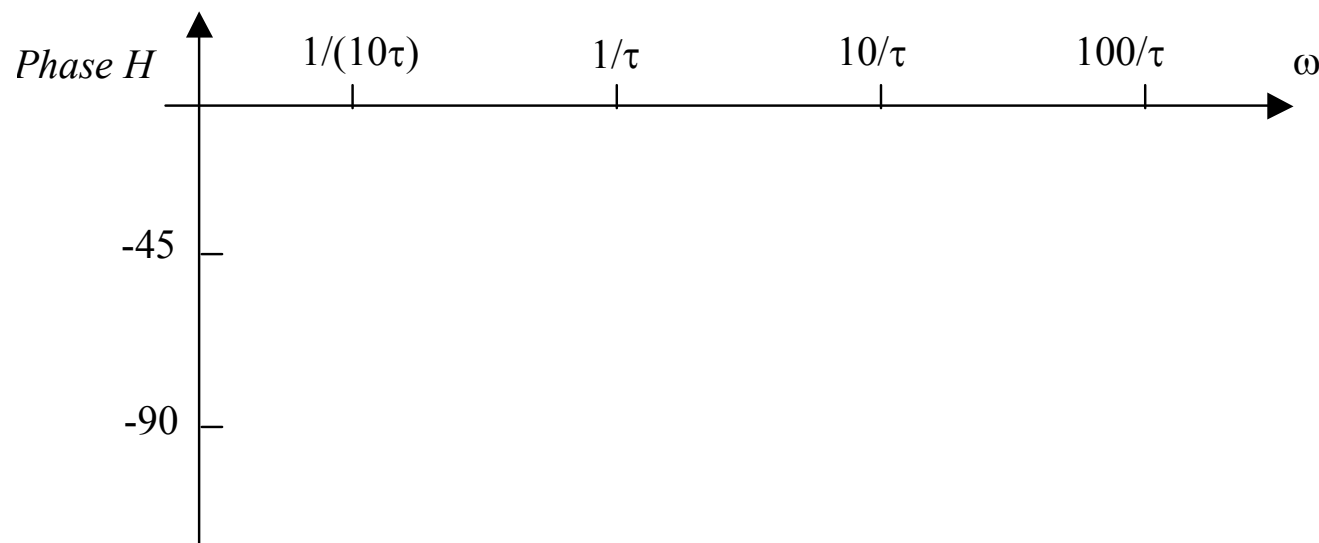

Average Power and Phasors

Integrate $P(t)$ over one period:

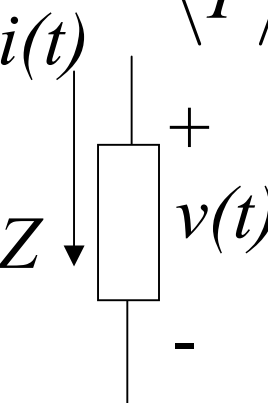

The diagram shows a rectangular load labeled Z . A downward arrow on the left is labeled $i(t)$. A voltage source is indicated by a '+' sign at the top and a '-' sign at the bottom, with the voltage labeled $v(t)$.


$$\langle P \rangle = \int_0^T i(t)v(t)dt = \int_0^T |I| \cos(\omega t + \angle I) |V| \cos(\omega t + \angle V) dt$$

$$= |I||V| \langle \sum \{ \cos(\omega t), \cos(2\omega t), \sin(\omega t), \sin(2\omega t) \} \rangle +$$


$$\frac{|I||V|}{2} \underbrace{(\cos \angle I \cos \angle V + \sin \angle I \sin \angle V)}$$

Result: $\langle P \rangle = \frac{|I||V|}{2} \cos(\angle I - \angle V) = \text{Re}\{I \cdot V^*\}$

The High-Pass Filter

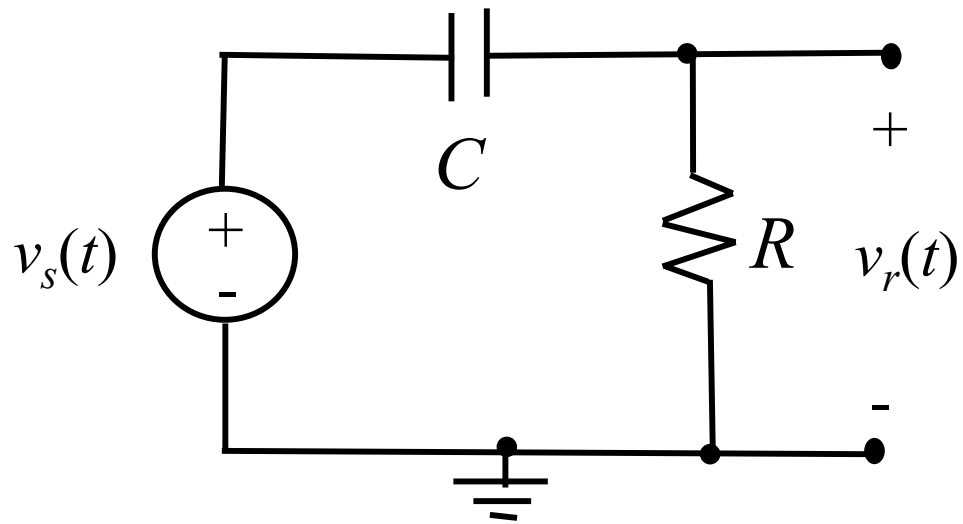

Impedance Divider

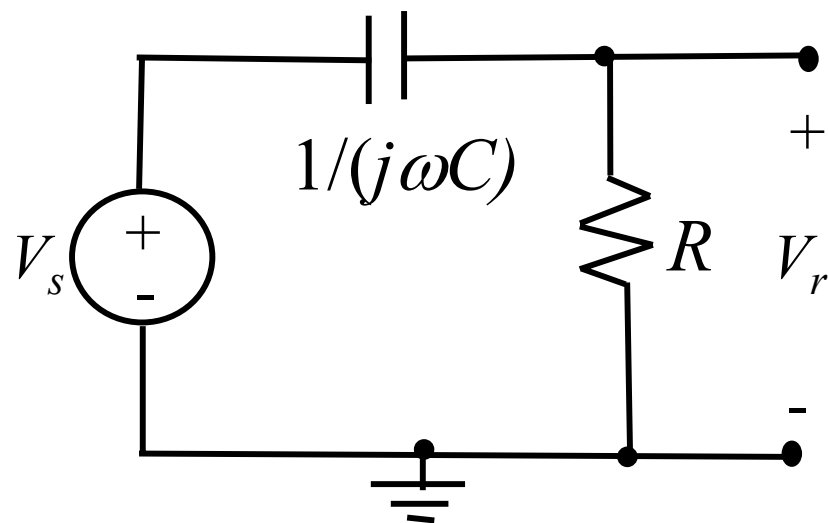

Insight:


$$H = \frac{V_r}{V_s} =$$

Magnitude Bode Plot

$$|H|_{dB} = \left| \frac{j\omega\tau}{1 + j\omega\tau} \right|_{dB} = |j\omega\tau|_{dB} + \left| \frac{1}{1 + j\omega\tau} \right|_{dB}$$

First term (numerator):

Graphical Addition of Magnitudes

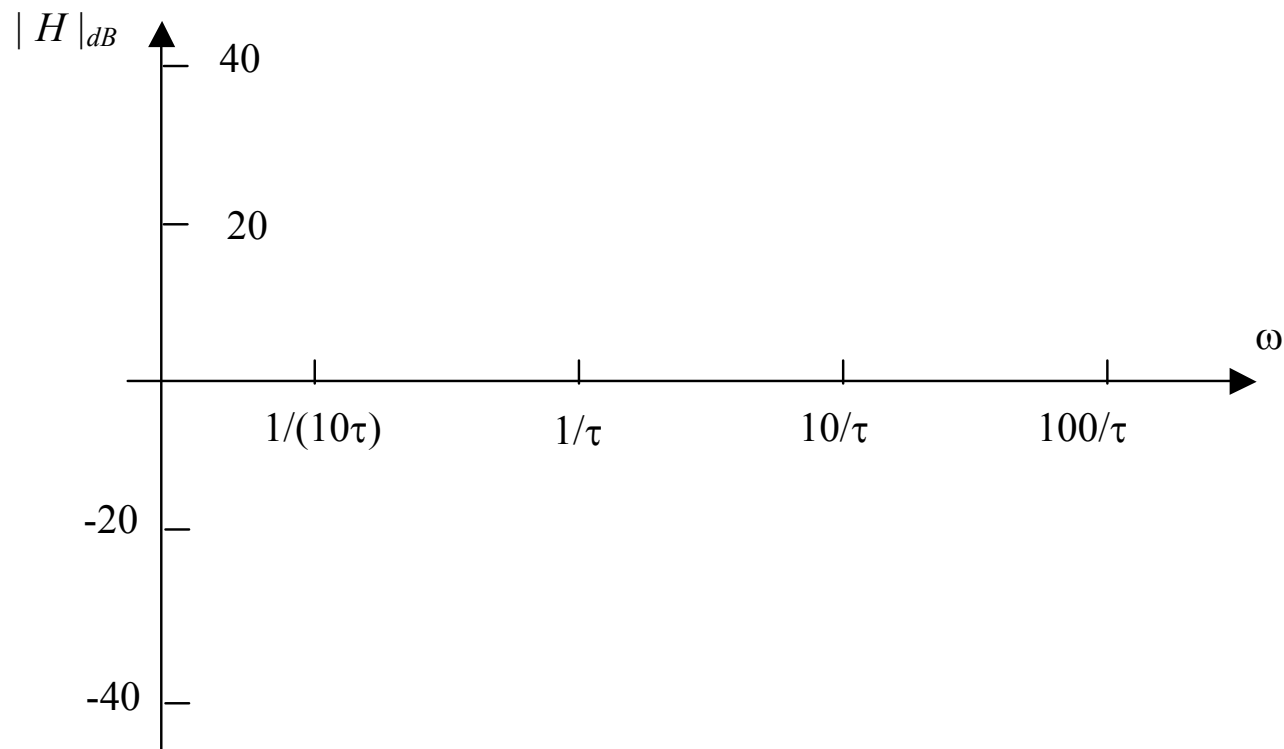

Phase Bode Plot for HPF

