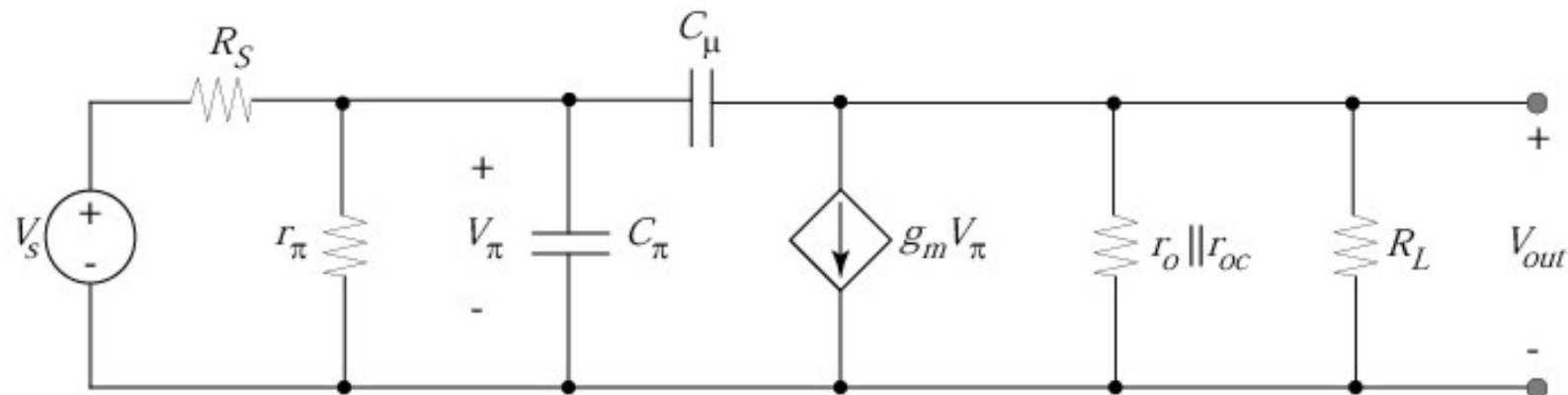


Lecture 40

- Last time:
 - Bias and output swing for BiCMOS voltage amp
 - Start open-circuit time constant analysis (back to Chapter 10)
- Today :
 - Applications of open-circuit time constant analysis: CE amplifier and cascode amplifier


Common-Emitter Voltage Amplifier



Time constant for base-emitter capacitance C_π :

Base-Collector Time Constant

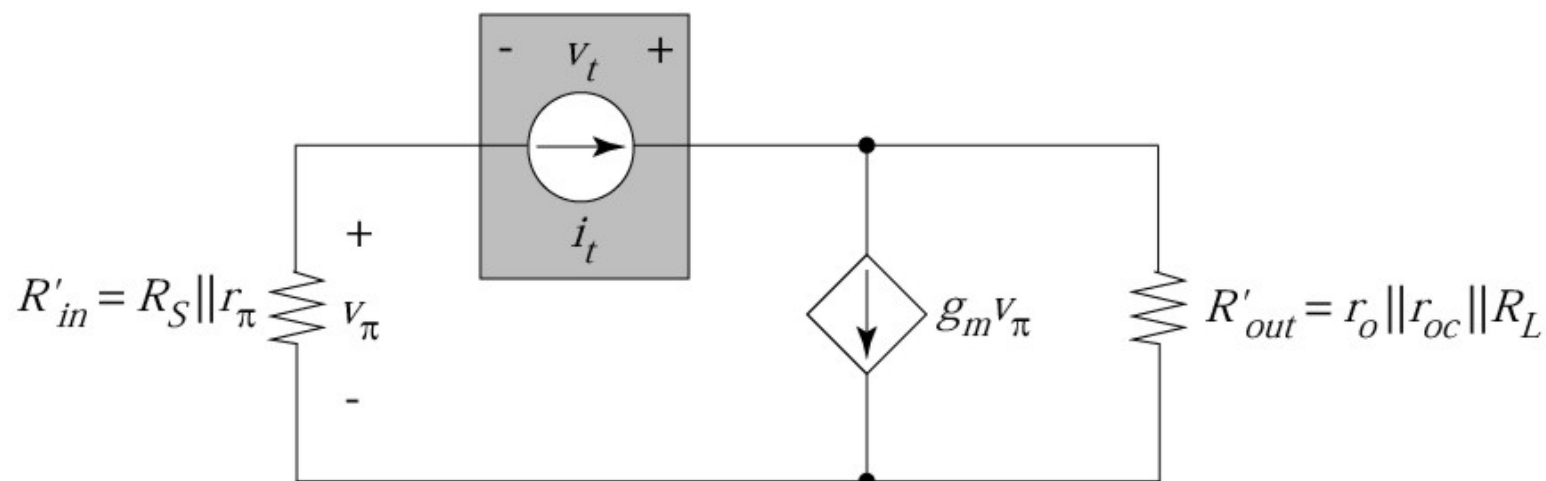Must apply a test source (can't see $R_{T\mu}$ by inspection):



Solving for $R_{T\mu}$

Find v_π :
$$v_\pi = -i_t (R_S \parallel r_\pi) = -i_t R'_{in}$$

Find v_o :
$$v_o = -i_o R'_{out} = (i_t - g_m v_\pi) R'_{out} = i_t (1 + g_m R'_{in}) R'_{out}$$

Find v_t :
$$v_t = v_o - v_\pi = i_t (1 + g_m R'_{in}) R'_{out} - (-i_t R_{in})$$

Solve for Thèvenin resistance:

Dominant Pole of CE Amplifier

Estimate dominant pole as inverse of sum of OCTCs:


$$\omega_1 \approx \frac{1}{\tau_{C_\pi} + \tau_{C_\mu}} = \left(R'_{in} C_\pi + [R'_{in} + R'_{out} + g_m R'_{in} R'_{out}] C_\mu \right)^{-1}$$

Identical to the “exact” analysis in Chapter 10

Why bother with the OCTC technique ... add effect of C_{cs}

Multistage Amplifier Frequency Response


CS*-CB cascode

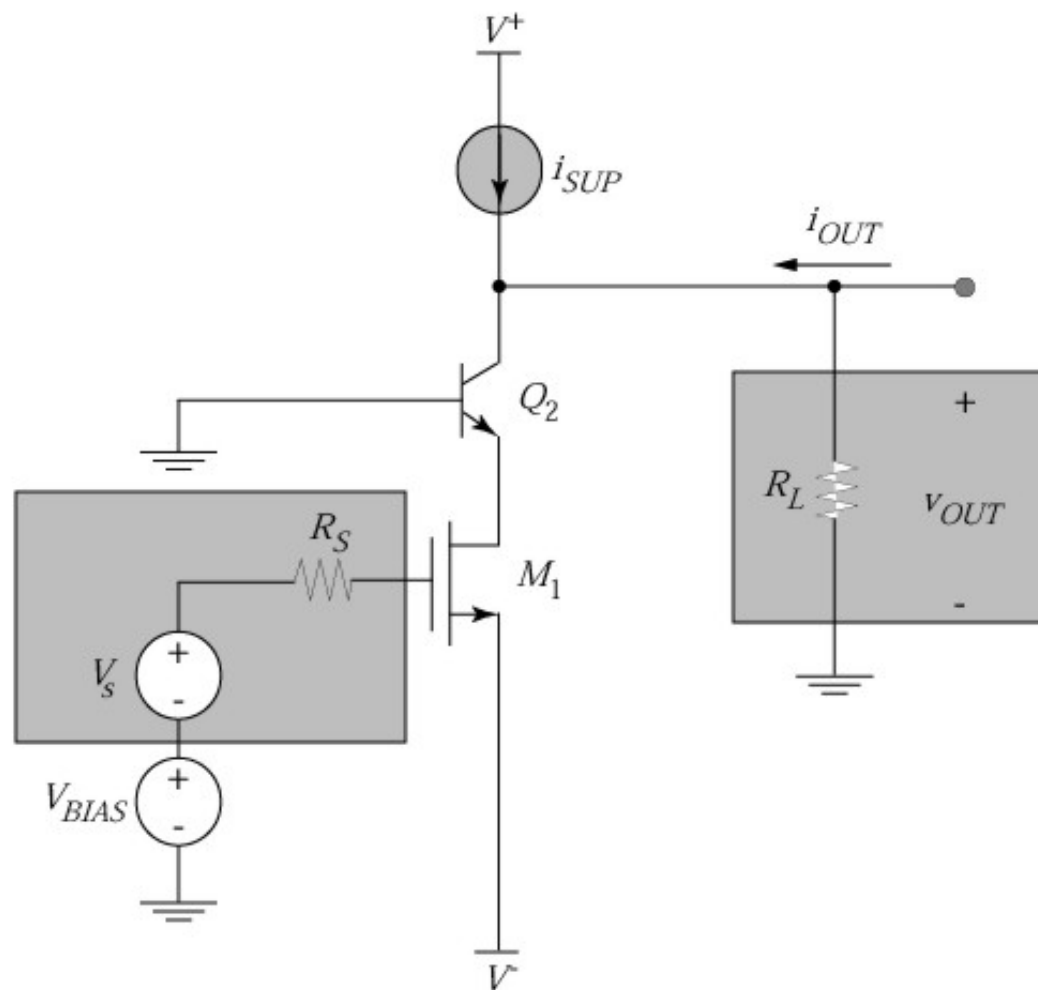

Systematic Approach

1. Construct *two-port* small-signal models for each stage
2. Add the capacitors for each device across the appropriate nodes in the two-port models. Make sure how the gate, drain, and source (or base, collector, and emitter) terminals of each device fit onto the two-port models!
3. (Optional) Use Miller's Theorem to transform capacitors across amplifiers into effective capacitances to ground (note that we ignore the "output Miller" in this course)

Cascode Two-Port Model

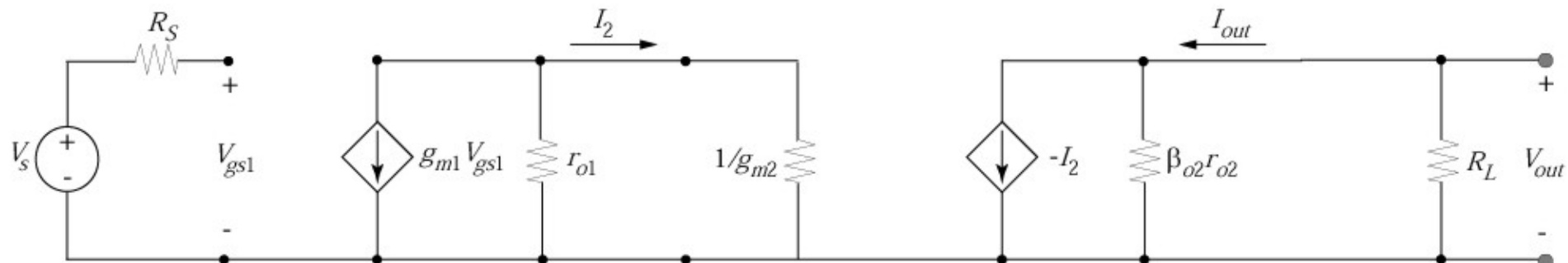

Add capacitors: C_{gs1} , C_{gd1} , $C_{\pi2}$, $C_{\mu2}$...
 what about C_{db1} , C_{cs2} ?

Finding the Thévenin Resistances

$$C_{gs1}: R_{TC_{gs1}} = R_S$$

$$C_{gd1}: R_{TC_{gd1}} = R'_{in} + R'_{out} + g_{m1} R'_{in} R'_{out} =$$

$$C_{\pi2}: R_{TC_{\pi2}} =$$

$$C_{\mu2}: R_{TC_{\mu2}} =$$

Dominant Pole

Applying the theorem:

$$\omega_1^{-1} \approx R_S C_{gs1} + R_S (1 + g_{m1} / g_{m2}) C_{gd1} + (1 / g_{m2}) C_{\pi 2} + R_L C_{\mu 2}$$

Find approximate voltage transfer function:

$$A_{vo} = \left. \frac{v_{out}}{v_s} \right|_{R_S, R_L} = -g_{m1} \left(\frac{r_{o1}}{r_{o1} + 1/g_{m2}} \right) (\beta_o r_{o2} \parallel r_{oc2} \parallel R_L)$$

Gain-Bandwidth Product

Metric for amplifier performance: note that

$$\left| A_v(j\omega^*) \right| = 1 \quad \text{when} \quad \omega^* = |A_{vo}| \omega_1$$

$$\left| A_{vo} \right| \omega_1 = \frac{g_{m1} R_L}{R_S C_{gs1} + R_S (1 + g_{m1} / g_{m2}) C_{gd1} + C_{\pi 2} / g_{m2} + R_L C_{\mu 2}}$$

Special case: small R_S

$$\left| A_{vo} \right| \omega_1 \approx \frac{g_{m1} R_L}{C_{\pi 2} / g_{m2} + R_L C_{\mu 2}}$$