

MY OH TUES:
 10:12
 2 → 3 PM

Lecture 19

EXAMS: PICK UP
 IN 497 COAY
 FROM ROBIN
REMOVES: DROP OFF
 IN 497 WITH ROBIN.

- Last time:

FINISH - DC and small-signal model of the forward-biased diode


- Today:

BJT - the npn bipolar junction transistor (BJT):
 large-signal characteristics

BIPOLAR TRANSISTOR LAB.


Dept. of EECS
 RETO: 391-325
 413-416 (E8025-MULT)

CIRCUIT DC/LARGE SIGNAL MODEL

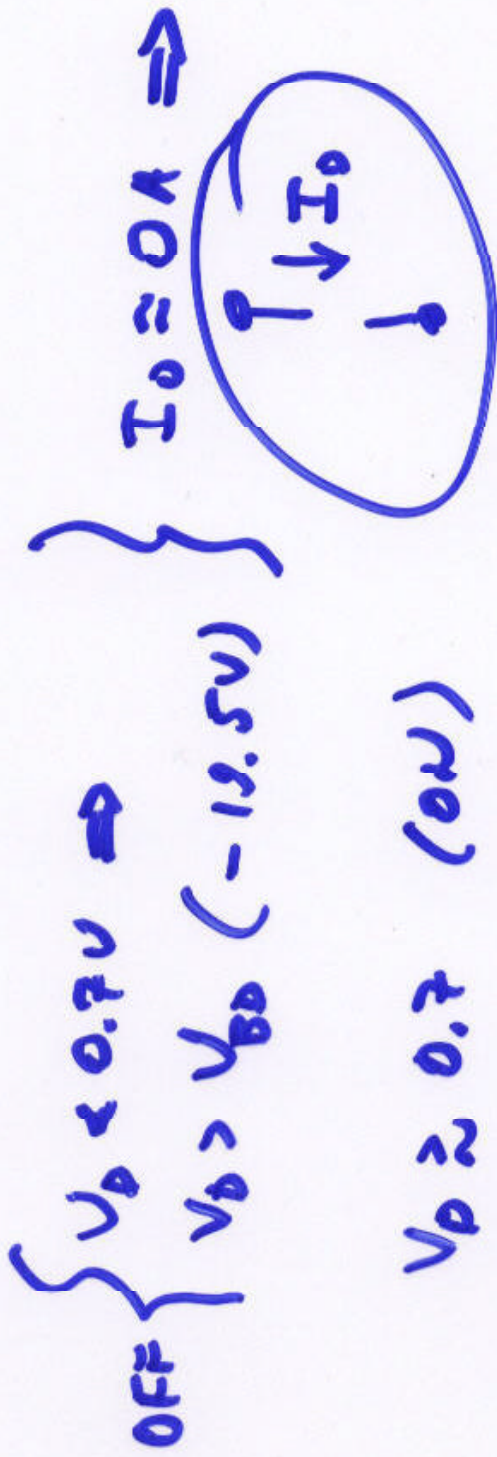


$$V_D \approx 0.7 (ON)$$

... VERTICAL LINE


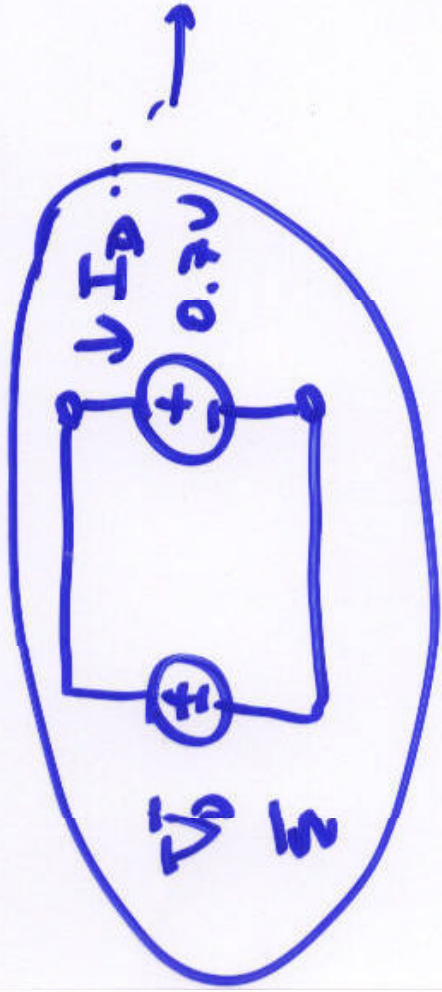


↑ "BETTER"

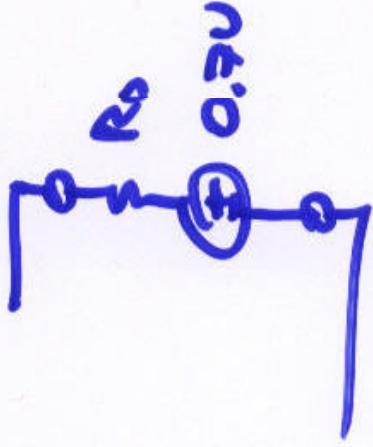

Power

Large-Signal Model

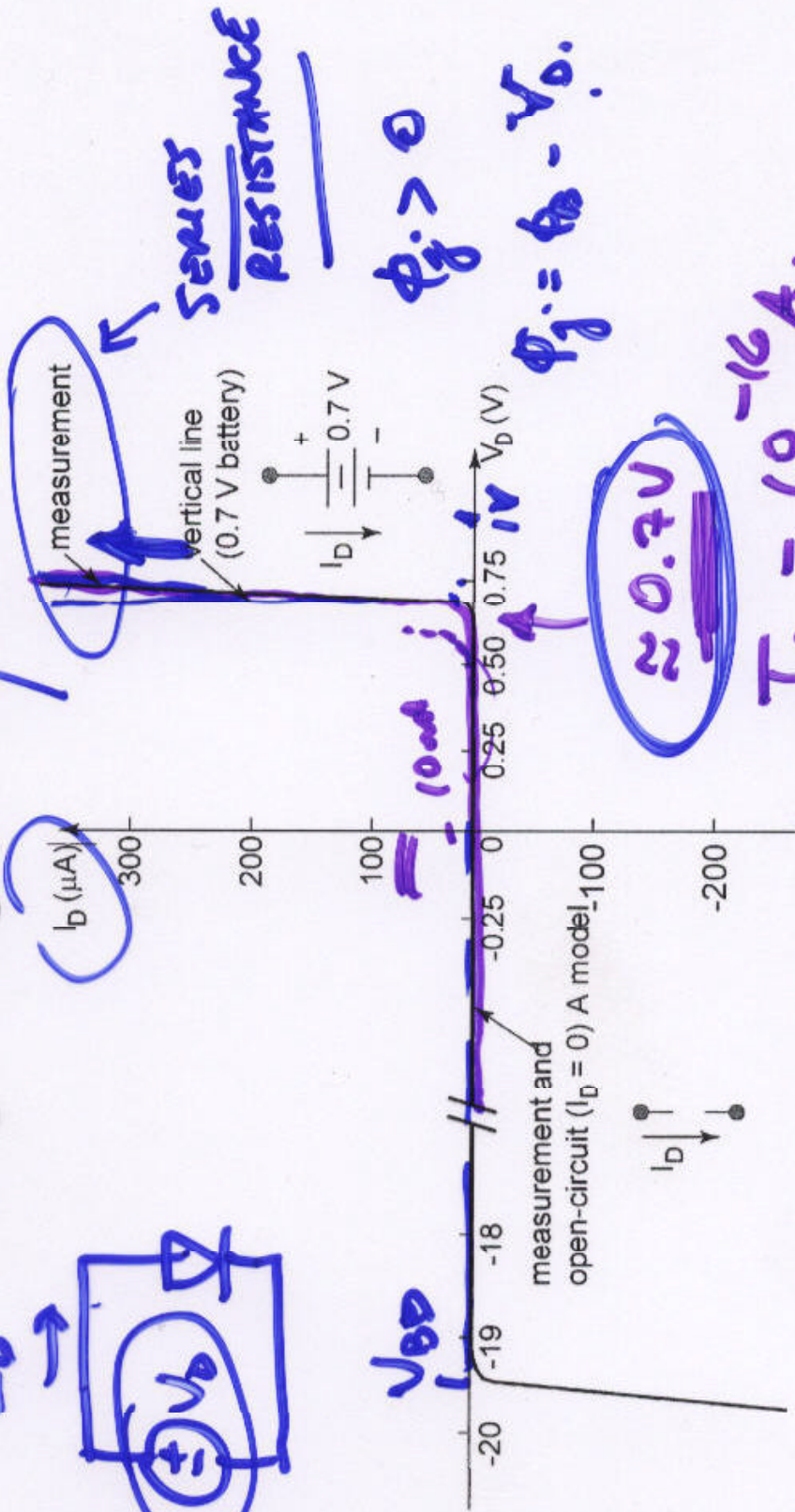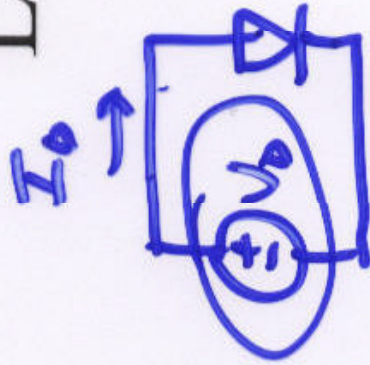

$$I_0 = I_0 (e^{V_D/V_T} - 1)$$

Dept. of EECS
University of California at Berkeley

NUMERICALLY!

Small-Signal Model: r_d

Forward-bias assumed $\rightarrow V_D = 0.7$ V (approx)

$$i_D(t) = I_0 (e^{v_D(t)/V_{th}} - 1) \cong I_0 e^{v_D(t)/V_{th}}$$

DROPPED -1

Substitute $v_D(t) = V_D + v_d(t)$:

$$i_D(t) = I_0 e^{[V_D + v_d(t)]/V_{th}}$$



QUASI-STATIC

ON

SLOPE... CONDUCTANCE

$$0.7/0.026 = \text{HUGE!!}$$

$$e^{0.7/0.026} = \text{HUGE!!}$$

$$10^{0.7/0.06} =$$

$$I_D \approx$$

$$10^{0.7/0.06} \approx 10^{12}$$

$$i_D(t) = I_0 e^{[V_D + v_d(t)]/V_{th}}$$

$$\frac{1}{20} \approx 0.05 = \frac{v_d}{2V_{th}} = \frac{v_d}{50mV}$$

$$v_d \approx 2.5mV$$

$$= \frac{50mV}{20}$$

$$= \frac{2.5mV}{1}$$

Power Series Expansion

$$e^x = 1 + x + \frac{1}{2!}x^2 + \frac{1}{3!}x^3 + \dots$$

x ... small

- Can quantify the limit of the linear approximation

$$e^x = 1 + \left(\frac{v_d}{V_{th}}\right) + \frac{1}{2} \left(\frac{v_d}{V_{th}}\right)^2 + \frac{1}{6} \left(\frac{v_d}{V_{th}}\right)^3$$

RATIO

$$\frac{\frac{1}{2} \left(\frac{v_d}{V_{th}}\right)^2}{\left(\frac{v_d}{V_{th}}\right)} = \text{error} = \frac{v_d}{2V_{th}}$$



5% →

$$i_D(t) = \frac{v_D(t)}{V_{th}} I_{D0} e^{v_D(t)/V_{th}}$$

$$\approx I_{D0} e^x = I_{D0} e^{v_d/V_{th}}$$

→ SMALL RESISTOR!
 NOT QUITE ZERO.

Graphical Interpretation

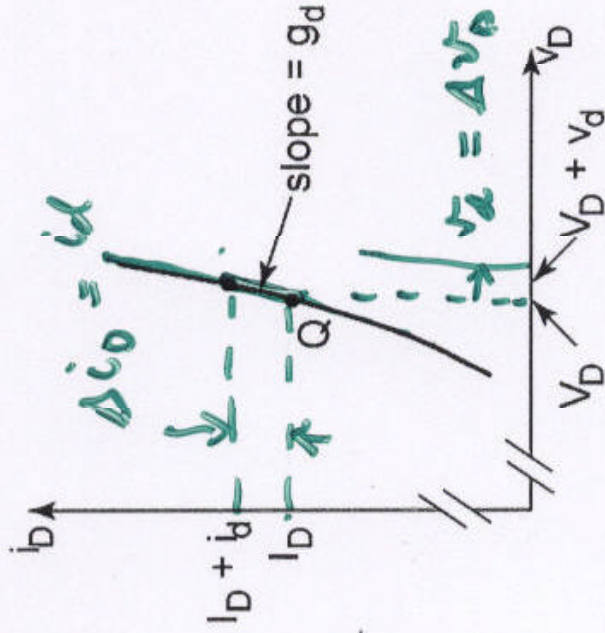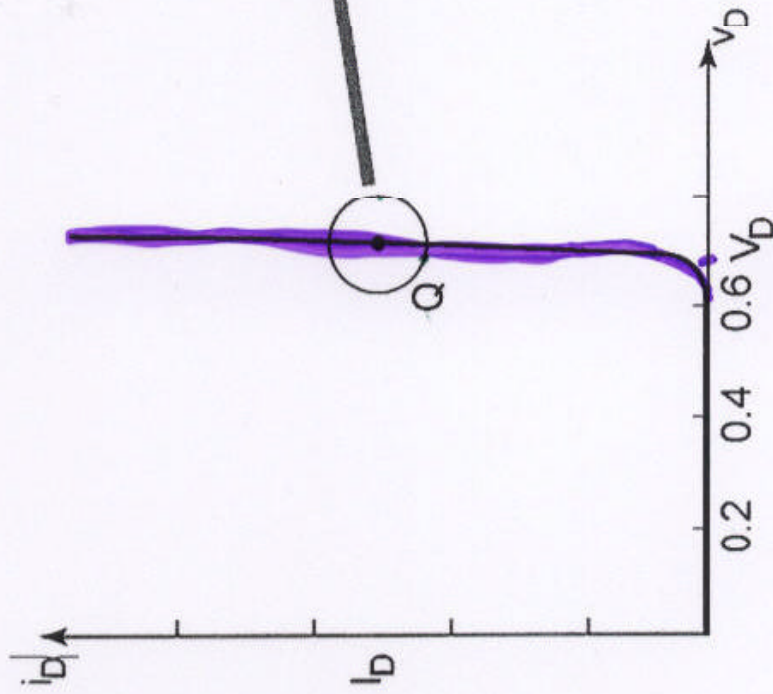

$$\frac{\partial i_D}{\partial V_D} \bigg|_{V_D} = \frac{1}{r_d} = \frac{\Delta i_D}{\Delta V_D} = \frac{i_d}{v_d}$$

0.9V
 $V_D = I_{D0} [1 + \frac{v_d}{V_D}]$

University of California at Berkeley


Dept. of EECS

$$i_D = I_D + \left(\frac{I_D}{V_{th}}\right) v_d$$

$$i_D = I_D + i_d \quad \text{where } i_d = \left(\frac{I_D}{V_{th}}\right) v_d$$

$$r_d = \frac{V_{th}}{I_D}$$

~~NOT $\frac{V_D}{I_D}$~~

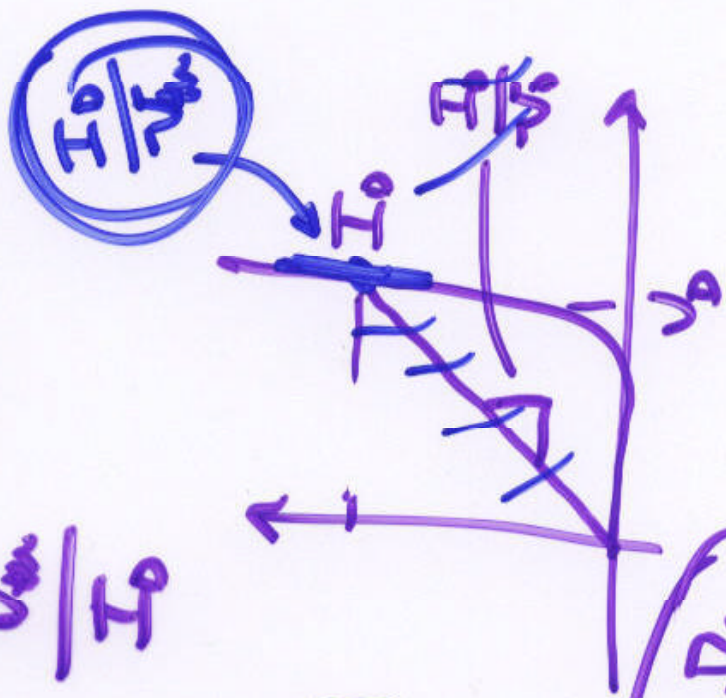


$$r_d = \frac{26 \text{ mV}}{100 \mu\text{A}} = 260 \Omega$$


WEIRD!

Physics of Diffusion Capacitance

carrier concentrations (cm^{-3})

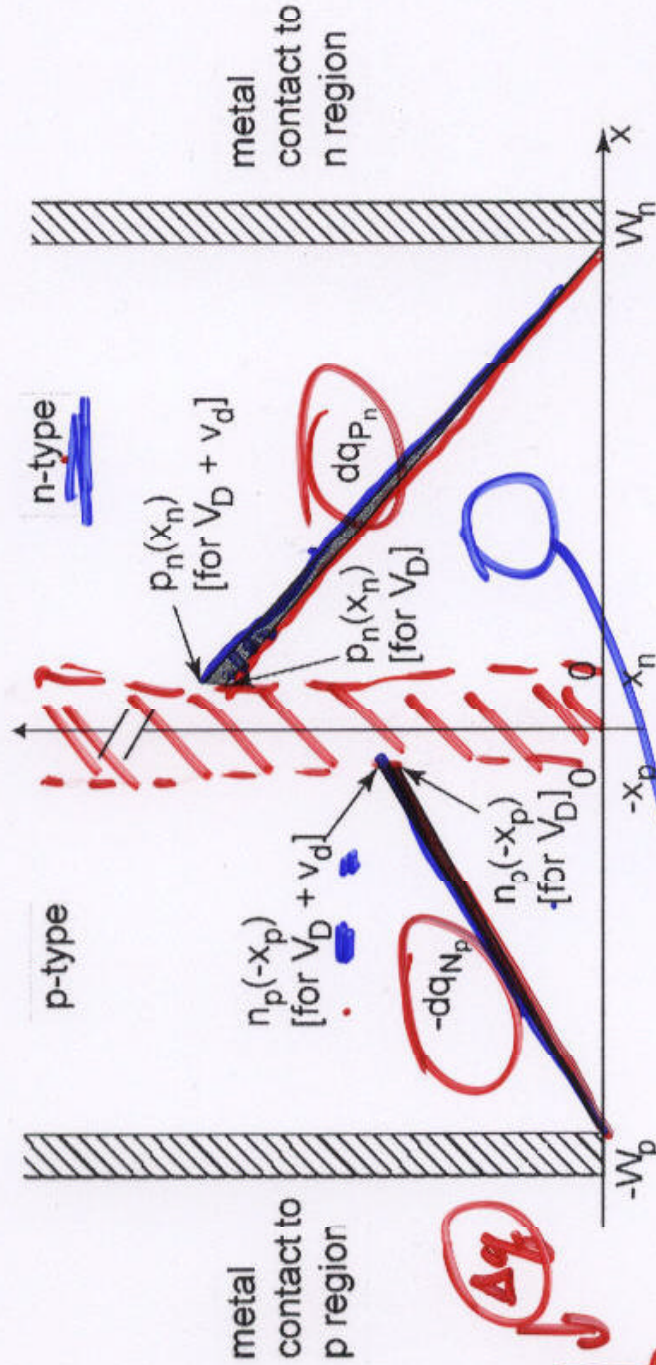

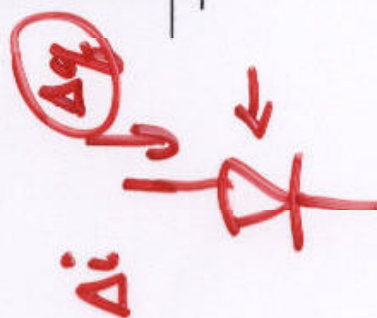
IMPORTANT POINT ... THESE REGIONS ARE NEUTRAL!



NEUTRALITY

$$n_a + n_p(x)$$

1017
 $n_m(x) = n_d + p_a(x)$
neutrality

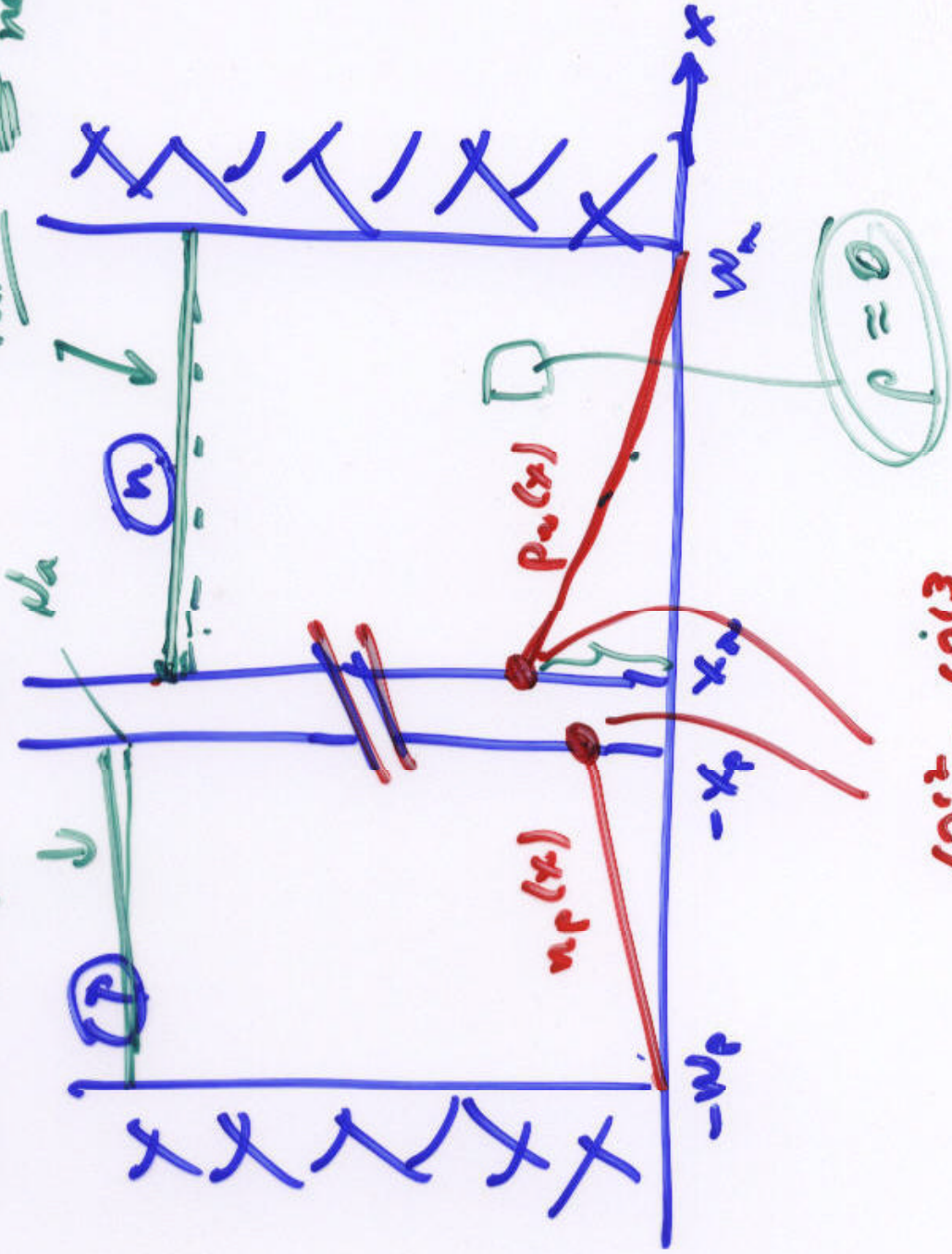

1012-1013

$$C_j = \frac{C_{j0}}{\sqrt{1 - V_d/V_0}} \dots \text{PUN IN}$$


Diffusion Capacitance $V_0 = 0.7V$

Depletion region narrows under forward bias, increasing capacitance to $C_j = 1.4 C_{j0} \dots$ **PUN IN ONLY**
BIG $\frac{V_0}{2}$ FOR V_0 .

Dominant capacitance is from storage of minority carriers in the diode's p and n regions: the *diffusion* capacitance

EE 231
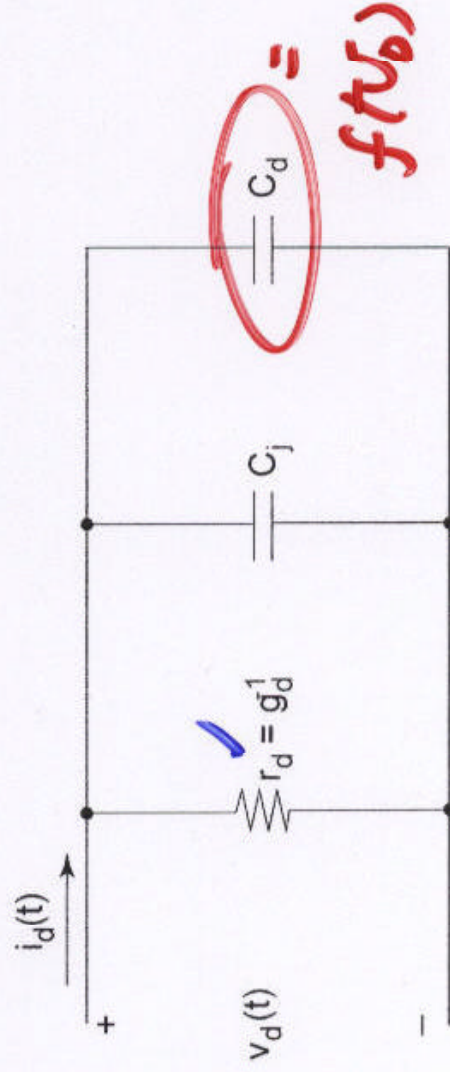
$$1.4 C_{j0} \uparrow C_j, C_{j0} \leftarrow C_{j0} \text{ jump}$$





Diffusion Capacitance

Minority carrier charge storage is proportional to the

DC diode current:


SEE CHAP. 6 (SEE 130)

$$C_d \approx \left(\frac{I_D}{V_{th}} \right) \tau_T = g_d \tau_T$$

SEE 130

$Z(\omega) \approx$

HUGE !!

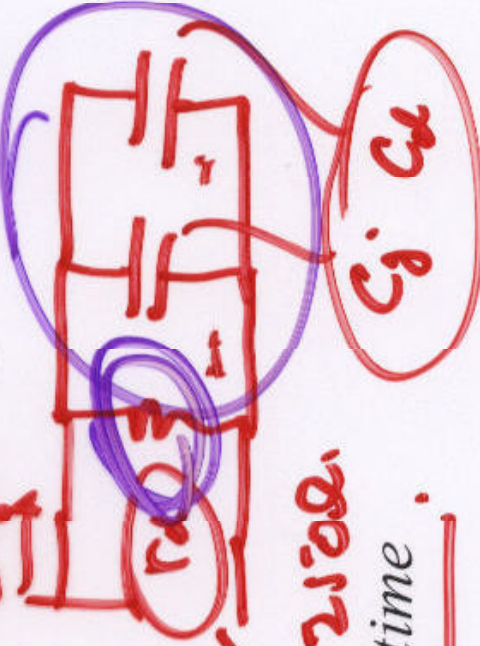

(2500)


where τ_T is the diode's transit time.

$\leq 1ps$

$C_j + C_d = 50ff.$

BUT C_d IS BIG! (RELATIVE TO C_j)


nnp Bipolar Transistor Structure

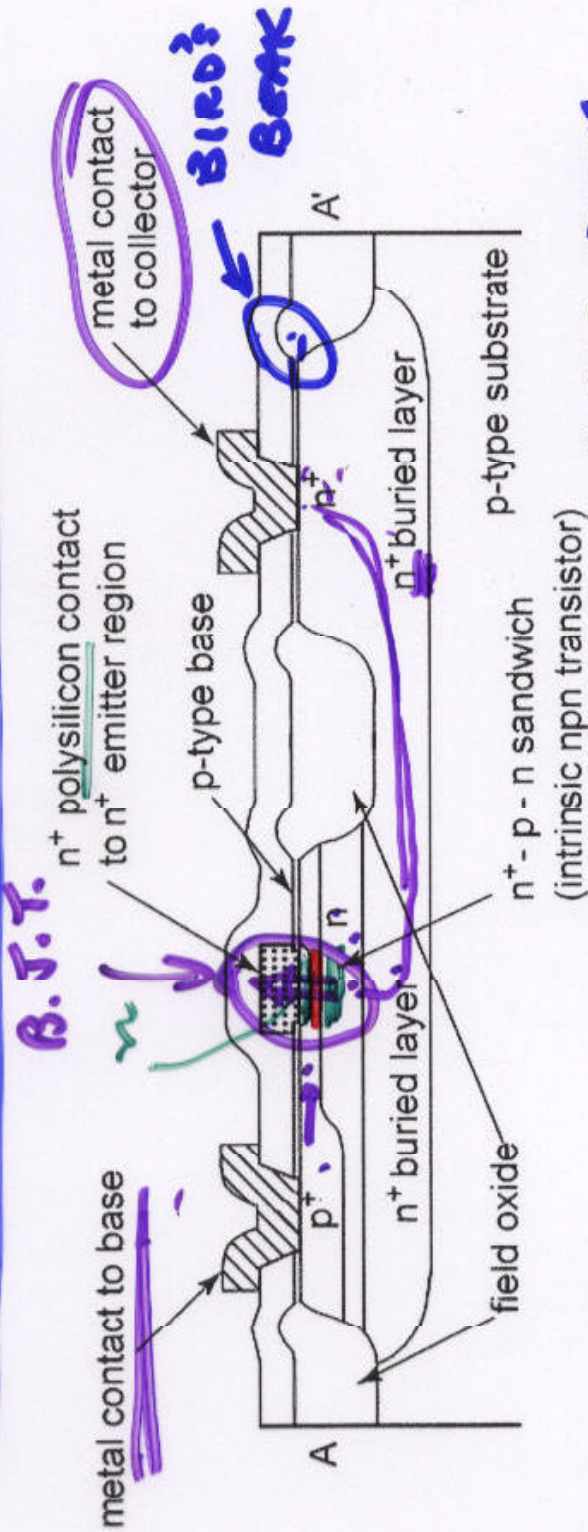



CIRCA 1992
 (MICROPROCESSOR
 VLSI CHIP)

CIRCA 2002
 B.J.T. ...
 SiGe (NOT Si) + CMOS.
 IBM.
 (npn only)


nnp Bipolar Transistor Layout

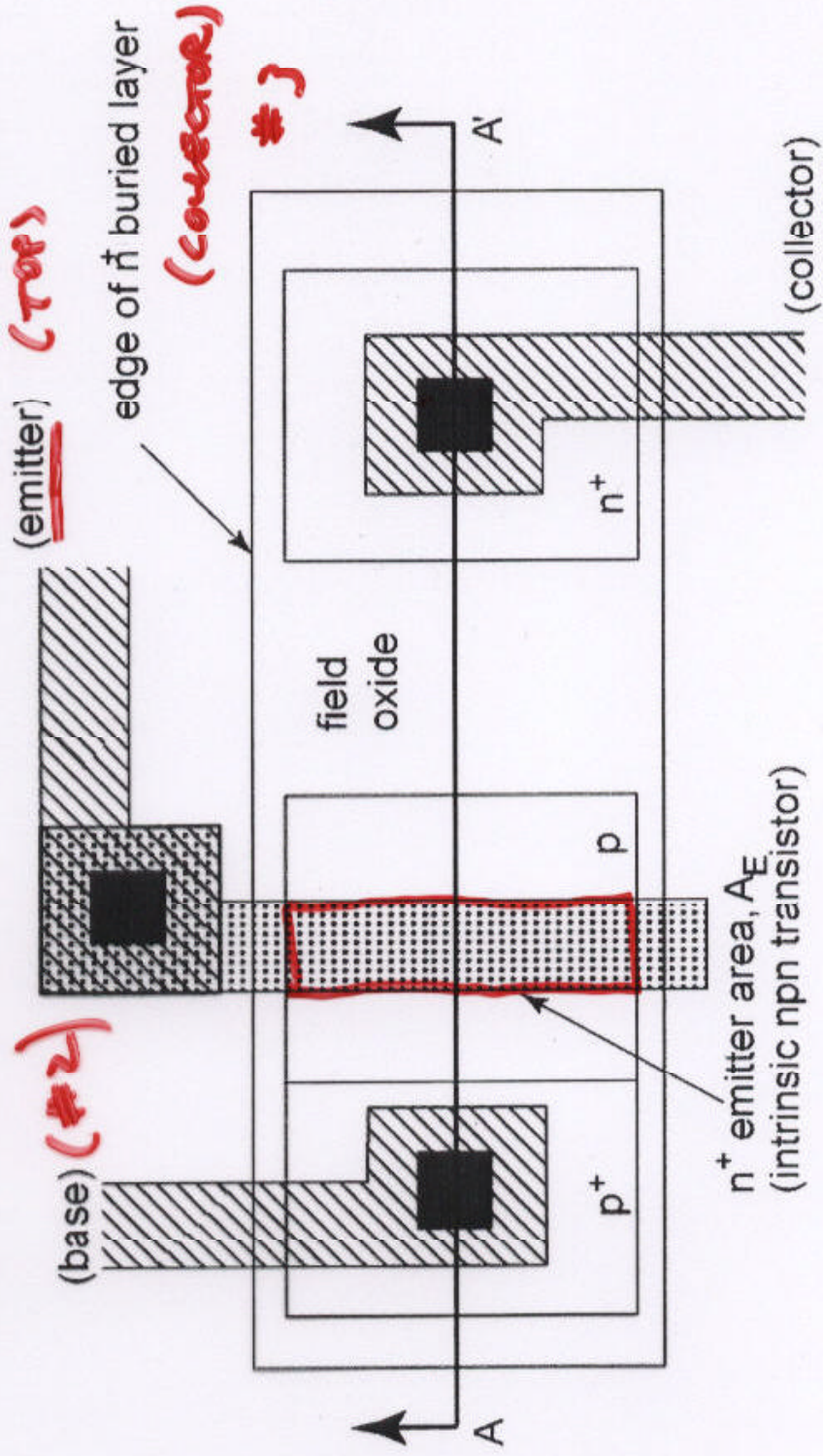


BJT Symbol

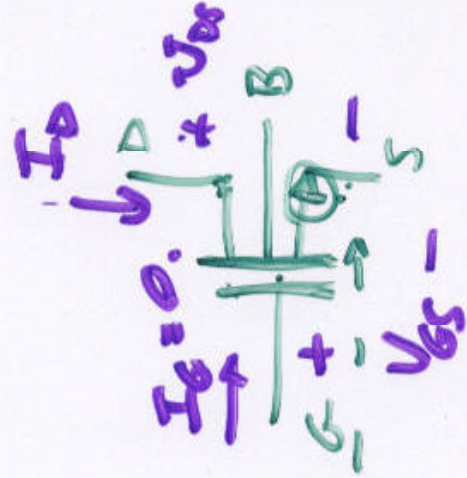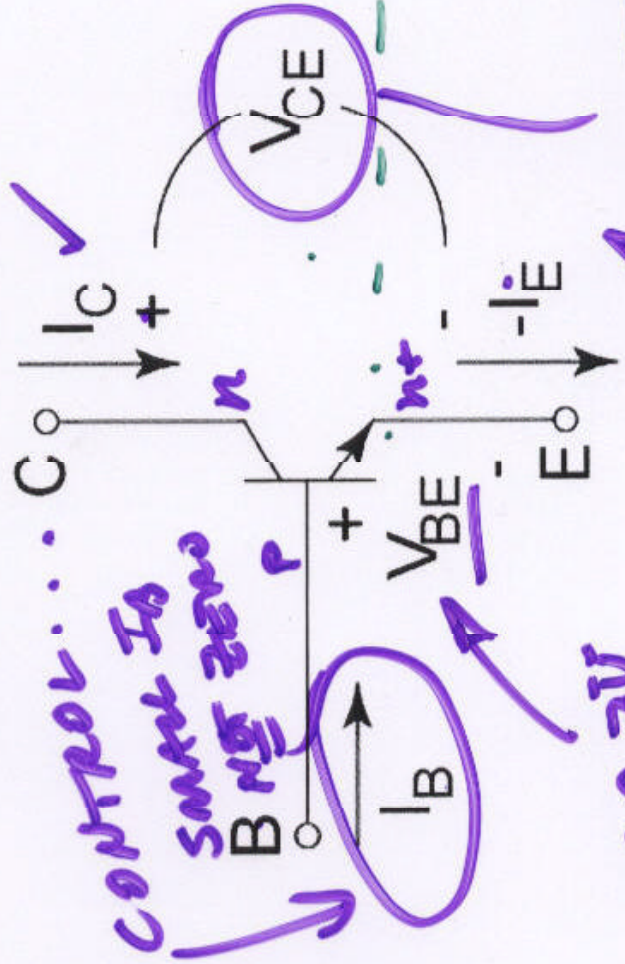

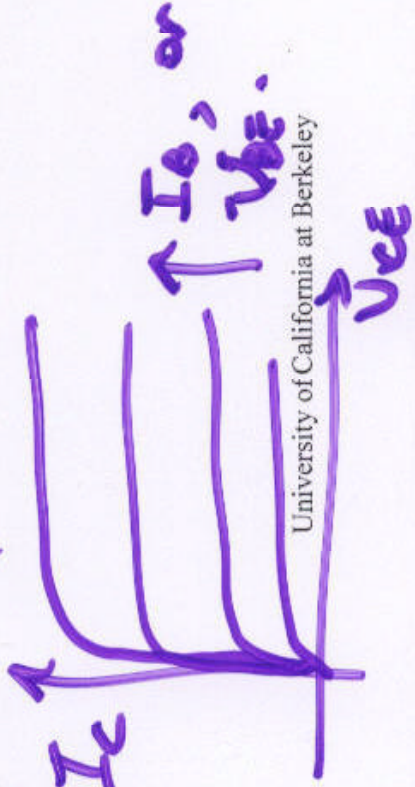CONTROL... IA
 SMALL IA
 BING ZERO
 V_{BE}
 I_B
 I_C
 $-I_E$
 ~0.7V
 VERY SMALL
 DEVIATIONS.



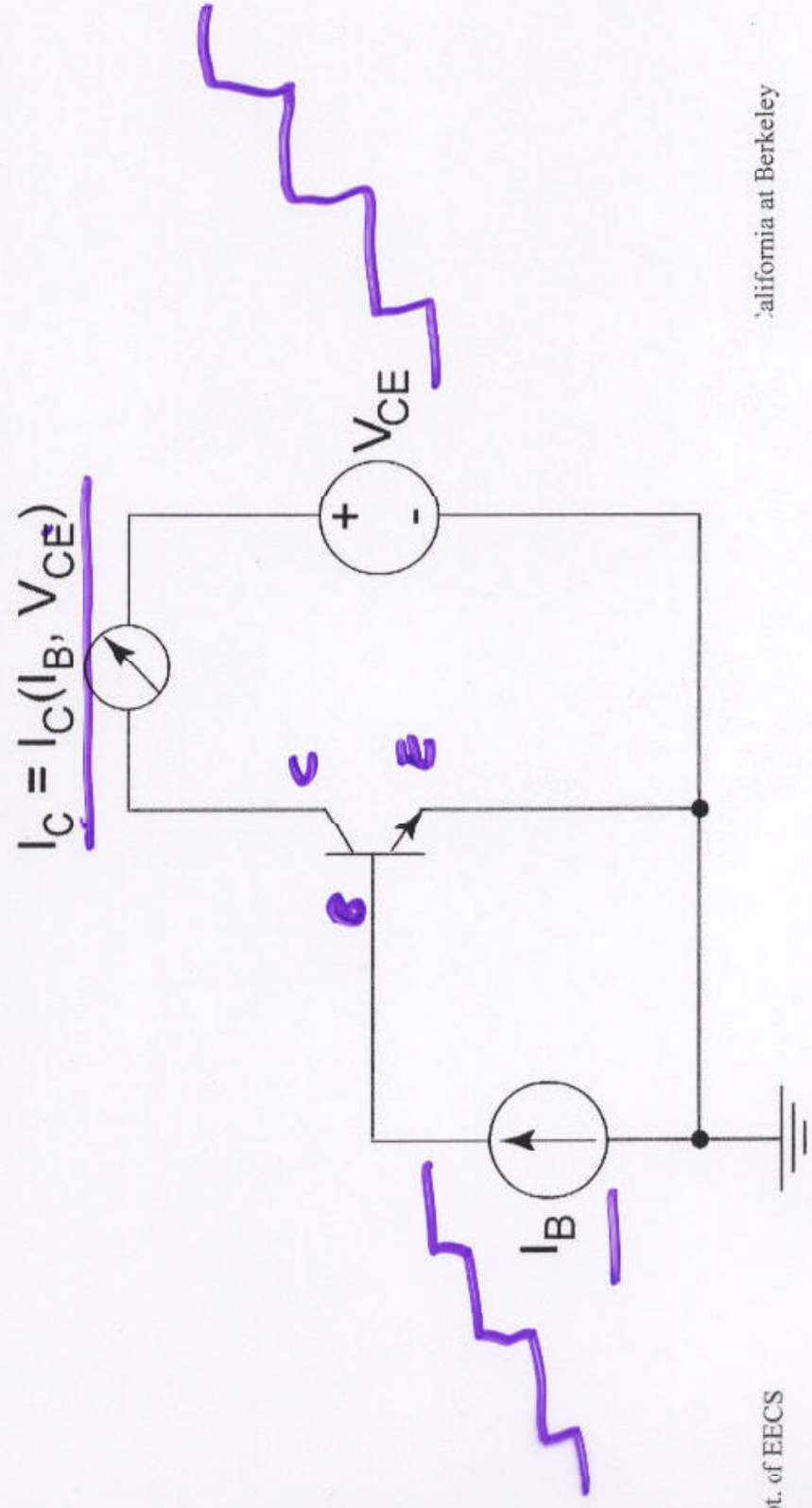Measuring the BJT's Collector Characteristics



Collector Characteristics

