

Lecture 21 ... END OF

"DEVICES" AMPS
START NEXT WEEK!


- Last time: INTERMEDIATE
 - Large-signal model under forward bias (3P)
 - Ebers-Moll model, start small signal model
- Today: & finish.
 - Small-signal model of the npn bipolar transistor

Forward-Active Model




- B-C junction is not forward-biased $\rightarrow I_R$ is very small

TYPICAL $V_{BE} = 0.7V$
 $V_{CE} = 2V$


$V_{BC} = -1.3V$

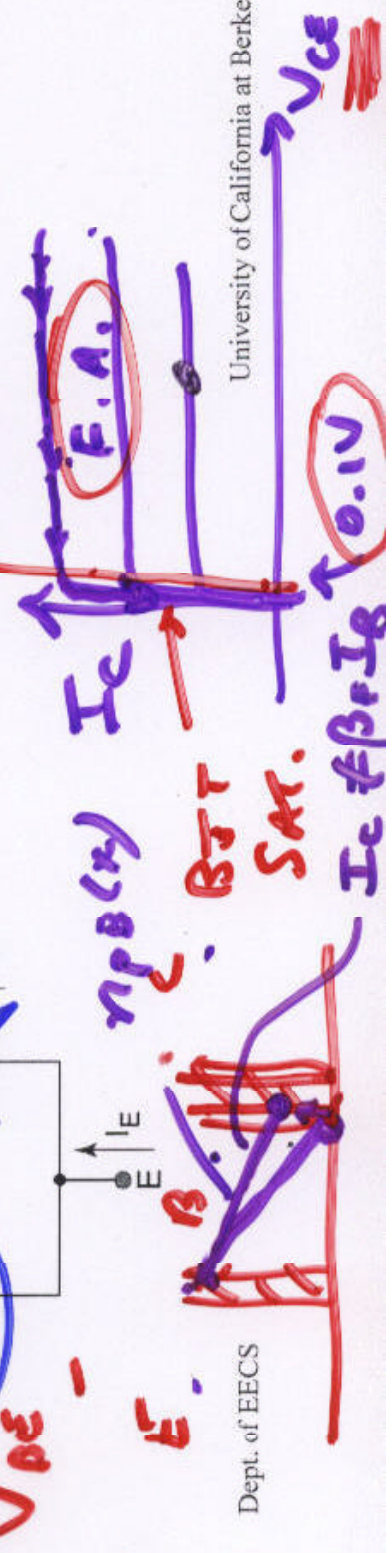

FORWARD ACTIVE

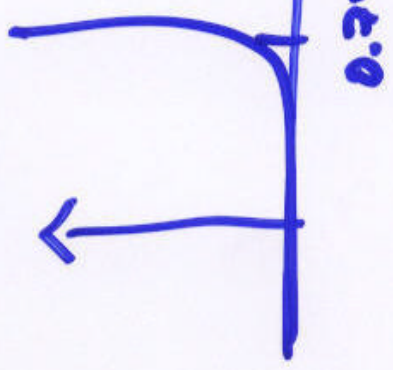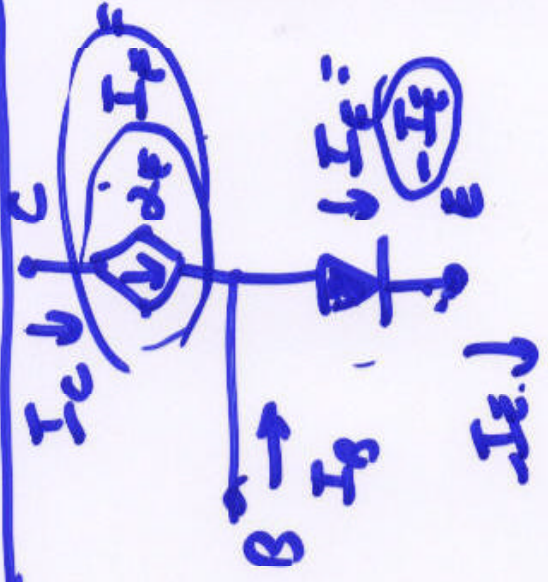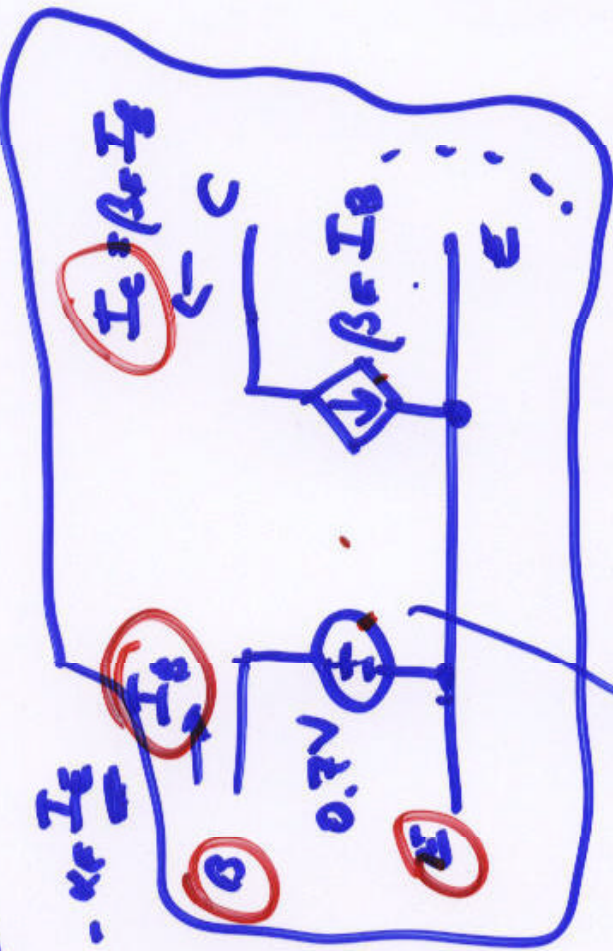


$+0.7$
 $-$
 LARGE SIGNAL
 SIGNAL

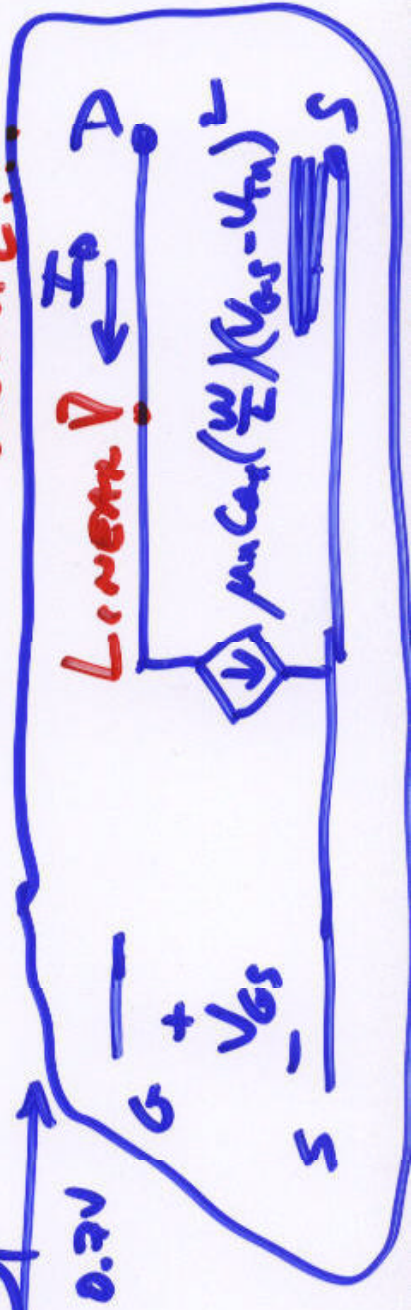


Ebers-Moll Equivalent Circuit

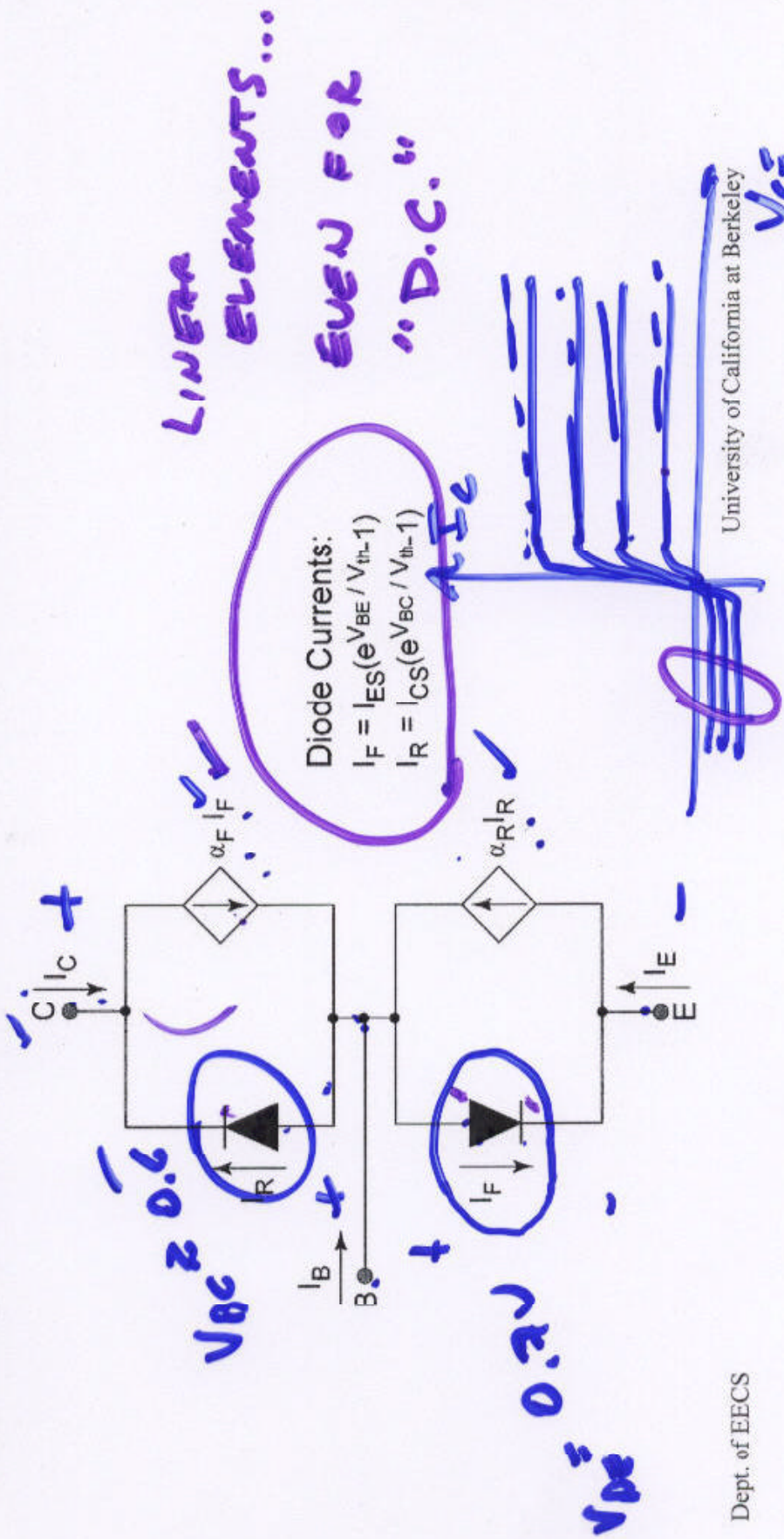Building blocks: diodes and I -controlled I sources




Simplified Ebers-Moll (Cont.)

~~Forward-Active Case~~ ✓

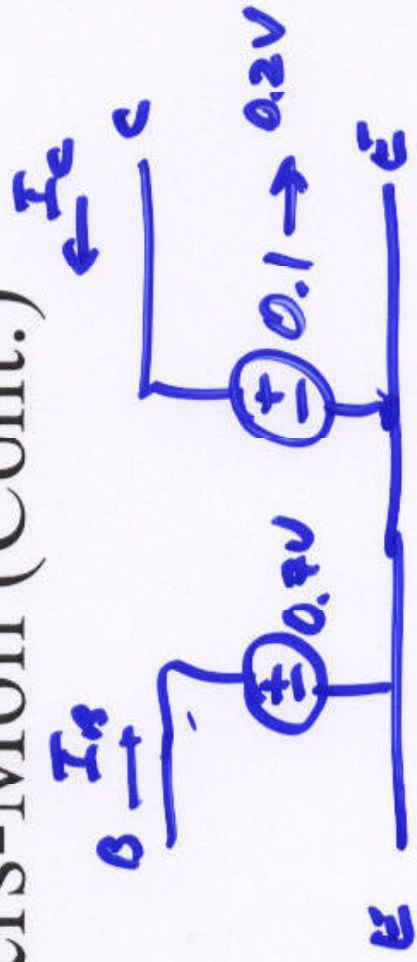

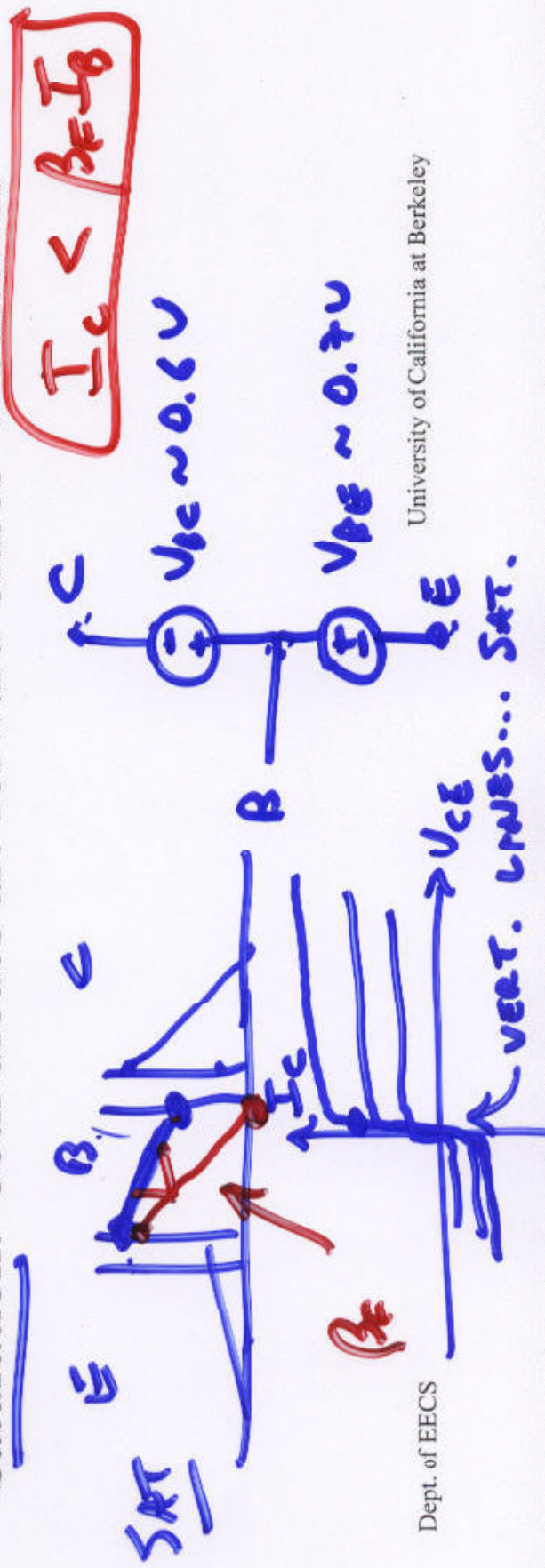Saturation: both diodes are forward-biased \rightarrow batteries



Small-Signal Model

Analogy from MOSFET s.s. model:



BACKGATE

$$i_D = f(v_{GS}, v_{DS}, v_{BS})$$

B. J. T.

$$i_C = f(v_{BE}, v_{CE})$$



$$i_B = g(v_{BE}, v_{CE})$$

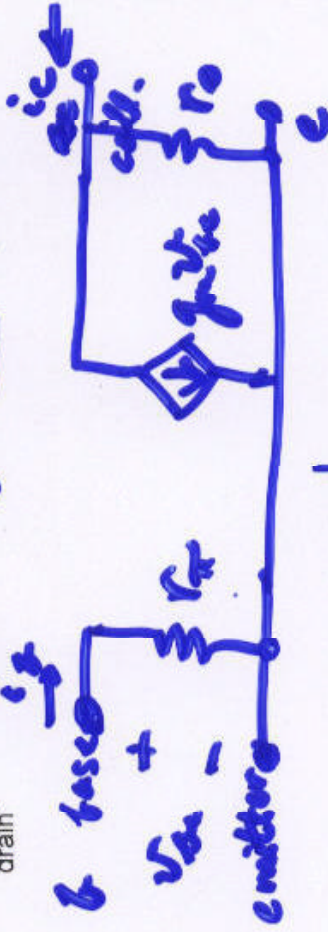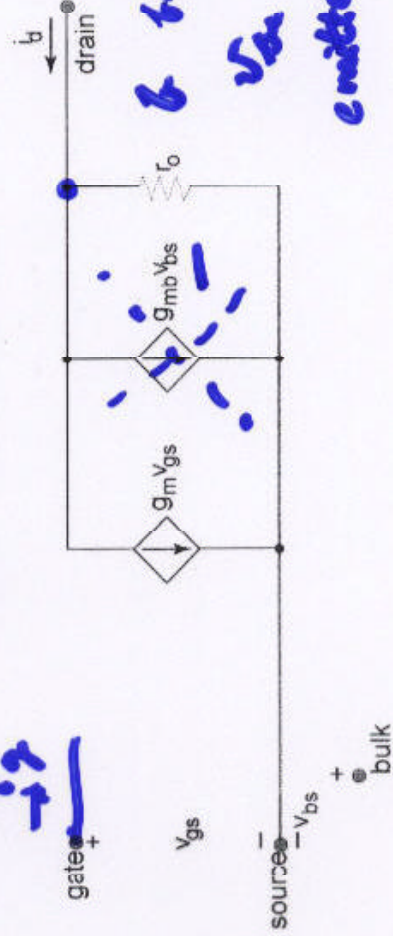

$$r_{\pi} = \left\{ \frac{\partial i_B}{\partial v_{BE}} \right\}^{-1}$$

University of California at Berkeley

Transconductance g_m

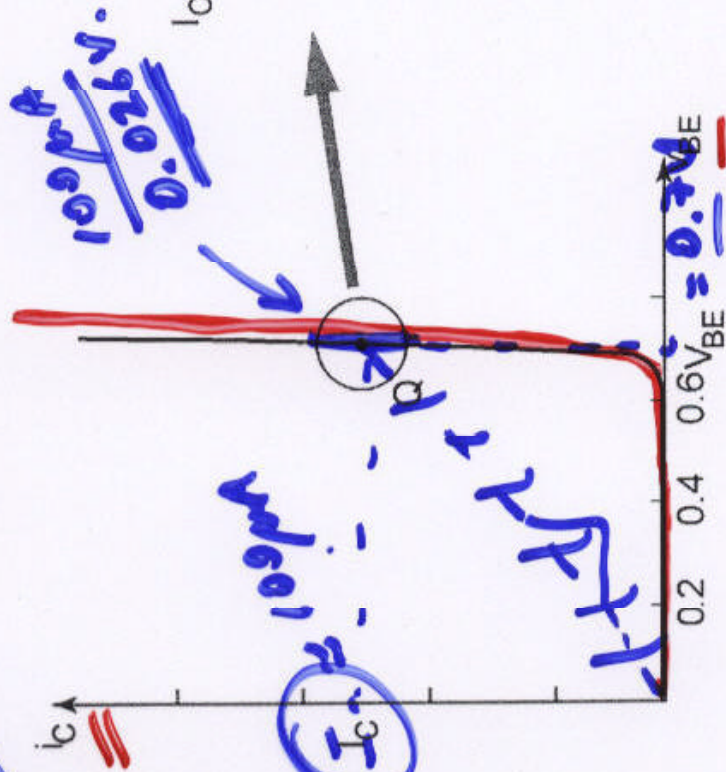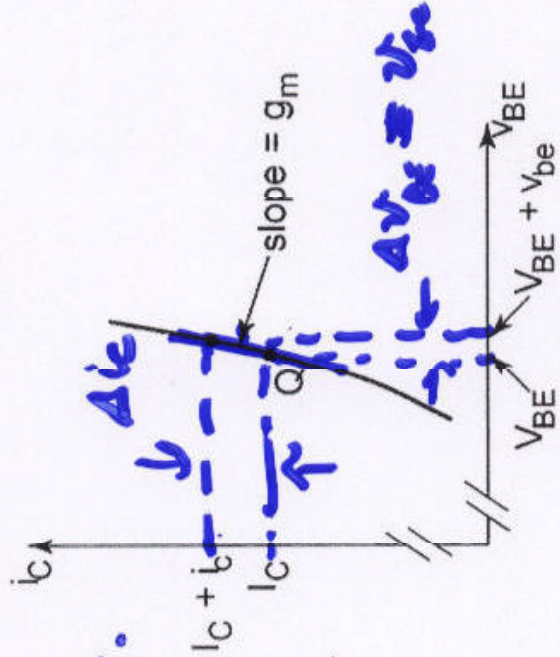

$$g_m = \left. \frac{\Delta i_c}{\Delta V_{BE}} \right|_Q$$

$$g_m = \frac{i_c}{V_{BE}}$$

$i_c = I_S e^{\dots}$
 $\frac{d i_c}{d V_{BE}} = \frac{I_S}{V_{BE}} e^{\dots} = \frac{i_c}{V_{BE}}$
 constants.

Transconductance (cont.)

- Forward-active large-signal current:

$$i_C = I_S e^{v_{BE}/V_{th}} \underbrace{(1 + v_{CE}/V_A)}_{\substack{\text{RUGGE FACTOR} \\ V_A}} \underbrace{(1 + \lambda_n v_{DS})}_{\substack{\text{channel length modulation}}} \underbrace{\frac{1}{V_A}}_{\substack{\text{Early Voltage}}}$$


- Differentiating and evaluating at $Q = (V_{BE}, V_{CE})$

$V_A = \text{Early voltage}$

$$g_m = \frac{\partial i_C}{\partial v_{BE}} \bigg|_Q = \left[\frac{I_S}{V_{th}} e^{v_{BE}/V_{th}} \right] \left[1 + \frac{v_{CE}}{V_A} \right]$$

Dept. of EECS

University of California at Berkeley

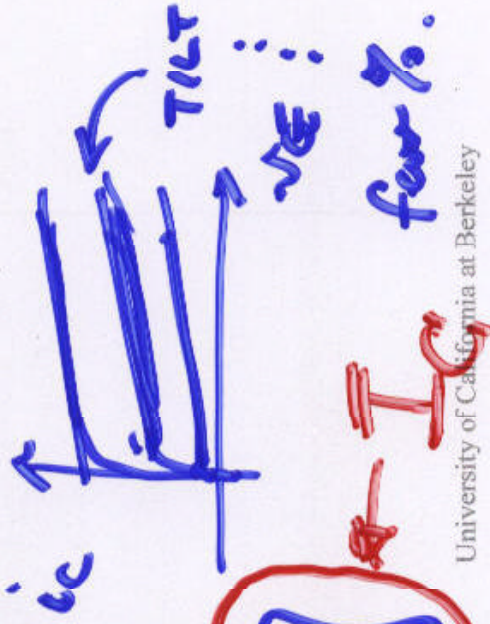

Comparison with MOSFET

$100 \mu A = \frac{I_D}{V} = 1000 \mu S$
 $g_m = 100 \mu S$
 $= \frac{2(100 \mu A)}{0.5 V}$

• Bipolar transistor: $g_{m,BJT} = \frac{I_C}{V_{th}}$

• MOSFET: $g_{m,MOS} \approx \mu_n C_{ox} \left(\frac{w}{L}\right) (V_{GS} - V_{th})$

• Typical bias point: drain/coll. current = 100 μA ;


Select $(W/L) = 8/1$, $\mu_n C_{ox} = 100 \mu A/V^2$

$$g_{m,MOS} = \frac{2 \left[\frac{1}{2} \mu_n C_{ox} \left(\frac{w}{L}\right) (V_{GS} - V_{th})^2 \right]}{V_{GS} - V_{th}}$$

$$V_{GS} - V_{th} = 0.5 V = \frac{2 I_D}{V_{GS} - V_{th}}$$

$= \frac{2 I_D}{V_{GS} - V_{th}}$
 ≈ 0.25
 $\approx -0.5 V$

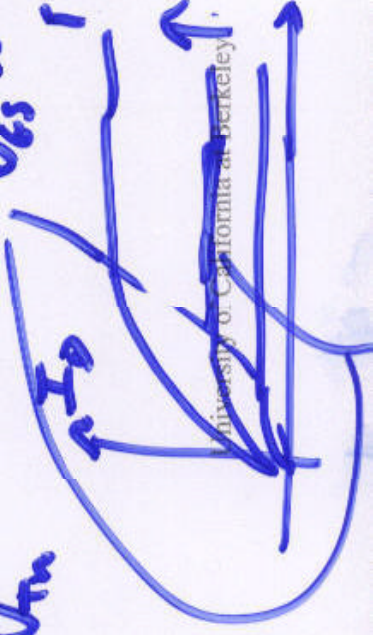$V_{GS} \approx 1.25 V$
 $V_{GS} = 1.5 V$



$$i_B = I_B + i_b \approx \frac{I_C}{\beta_F} \approx \frac{1.99 \mu\text{A}}{100} = 1 \mu\text{A}$$

What about the Base Current?

Unlike MOSFET, there is a DC current into the base terminal of a bipolar transistor:


$$I_B = I_C / \beta_F = (I_S / \beta_F) e^{V_{BE} / V_{th}} (1 + V_{CE} / V_{th})$$

To find the change in base current due to change in base-emitter voltage:

$$\frac{\partial i_B}{\partial V_{BE}} \bigg|_Q = \frac{\partial i_B}{\partial i_C} \bigg|_Q \cdot \frac{\partial i_C}{\partial V_{BE}} \bigg|_Q = \left(\frac{1}{\beta_F} \right) \beta_{00}$$

$$\beta_F = \frac{\alpha_F \beta_0}{1 - \alpha_F} \approx \dots \approx \alpha_F \approx 0.99$$

Small-Signal Current Gain β_o

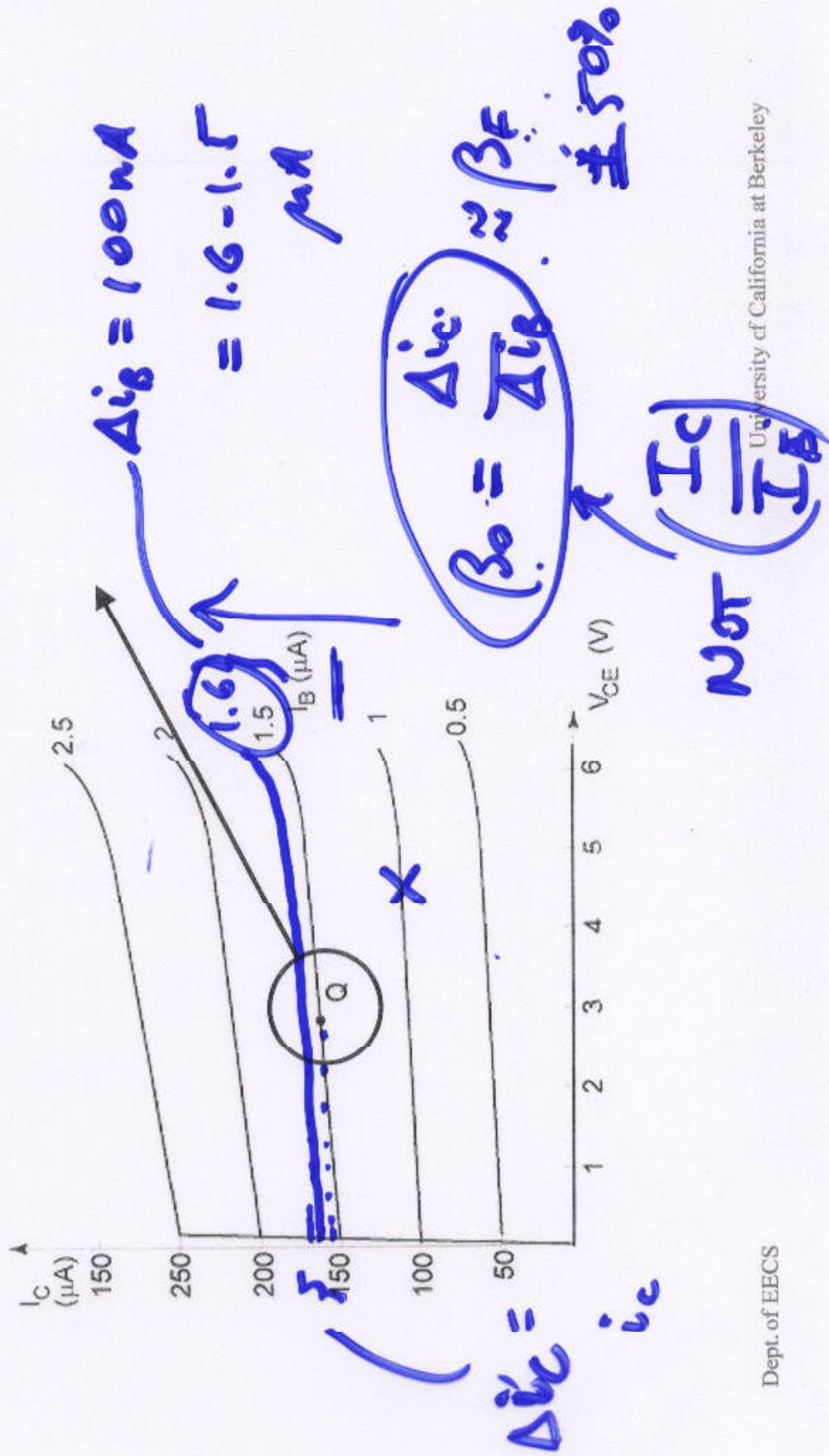


Input Resistance r_π

$$(r_\pi)^{-1} = \left. \frac{\partial i_B}{\partial v_{BE}} \right|_Q = \left(\frac{1}{\beta_o} \right) \left. \frac{\partial i_C}{\partial v_{BE}} \right|_Q = \frac{g_m}{\beta_o} \leftarrow \text{s.s.}$$

In practice, the DC current gain β_F and the small-signal current gain β_o are both highly variable (+/- ~~25%~~ ^{50%})

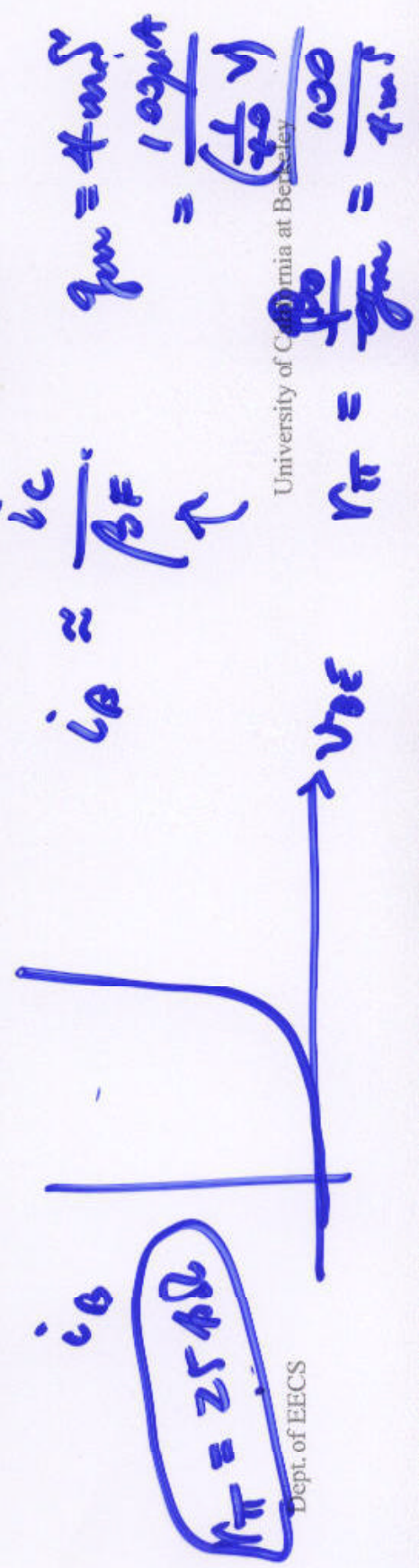
Typical bias point: DC collector current = 100 μA



EECS 105 Spring 2002 Lecture 21
 $v_{BE} = 0.7V$

Output Resistance r_o

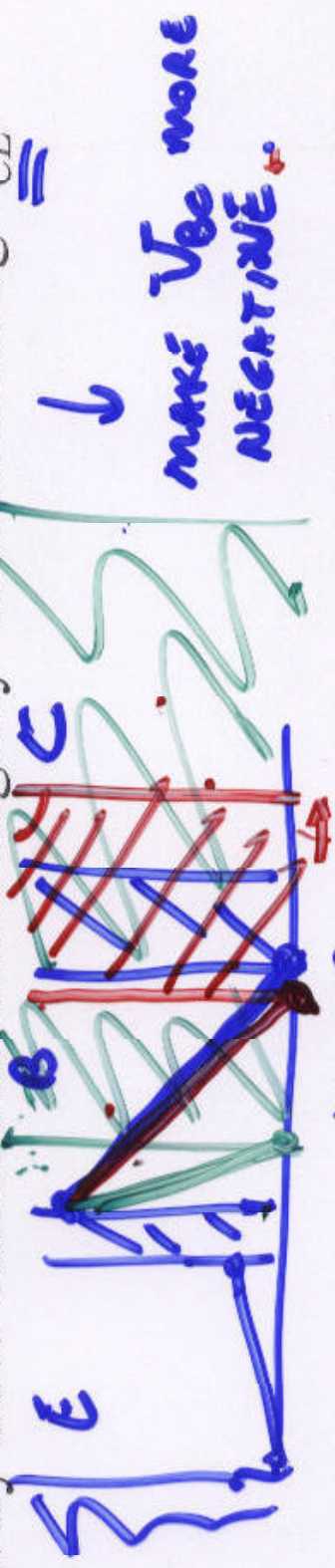Why does current increase slightly with increasing v_{CE} ?




Model: math is a mess, so introduce the Early voltage

$$i_C = I_S e^{v_{BE}/V_{th}} (1 + v_{CE}/V_A) \quad r_o = \frac{V_A}{I_C}$$

$$\frac{di_C}{dv_{CE}} = (I_S e^{v_{BE}/V_{th}}) \left(\frac{1}{V_A} \right) = \frac{I_C}{V_A} = \frac{1}{r_o}$$


Graphical Interpretation of r_o

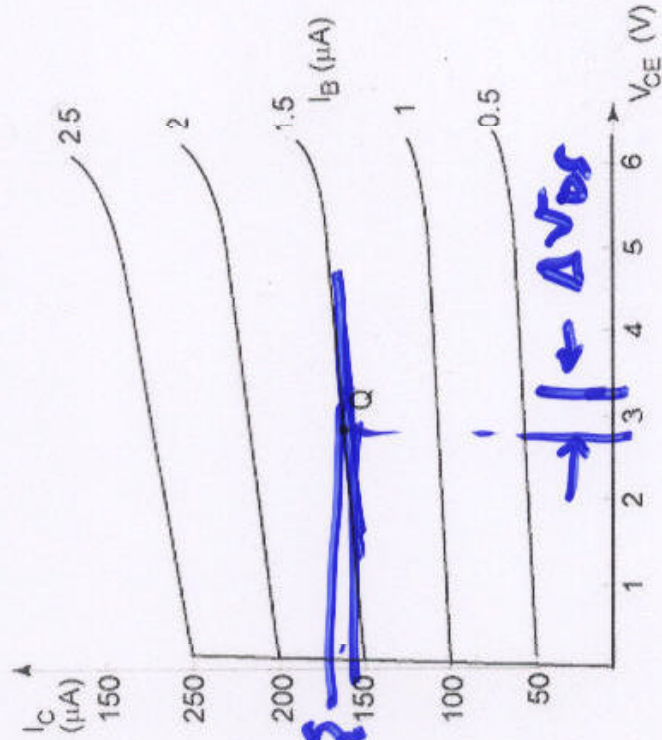

$$r_o \approx \frac{V_A}{I_C} = \frac{35\text{V}}{100\mu\text{A}} = \underline{\underline{350\text{k}\Omega}}$$

Typical value:
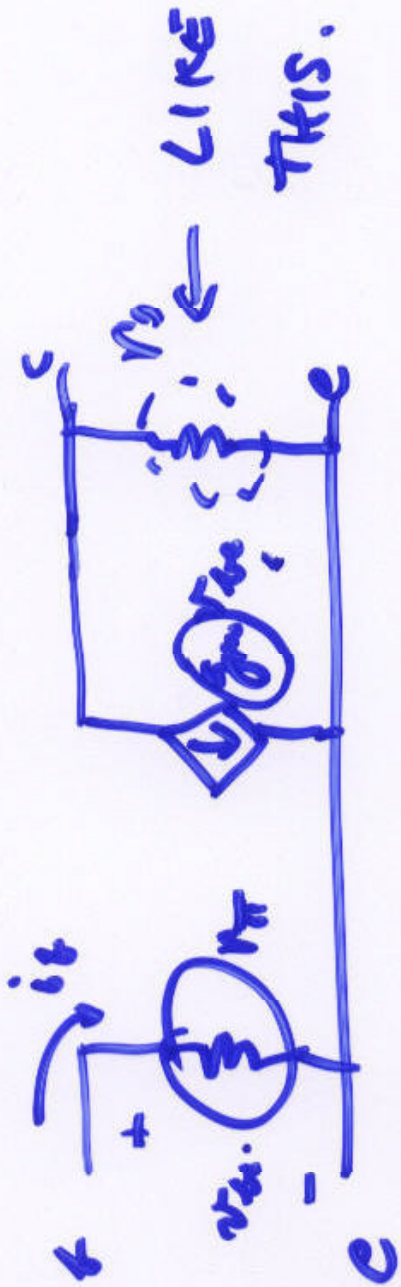
$$\underline{\underline{V_A = 35\text{V}}}$$



$$v_{ce} = r_0 i_c$$

~~gm vbe~~

$$i_c = g_m v_{be} = (g_m r_0) i_c = \beta_0 i_c$$