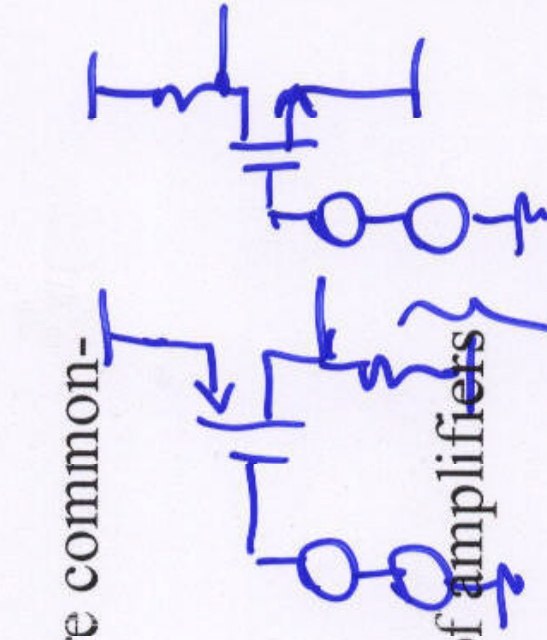


*Review - up computer 8.
TO*

Lecture 24

- Last time:

- Small-signal model for the entire common-source amplifier
- Limits to model



- Today :

- Two-port small-signal models of amplifiers

*START
OF 8*

PS 9 # 1. PMOS.


LECTURE 22/23 MATR.

ABSTRACTION -


REP RESENTATIONAL

Generalized Amplifier

Input sources ...

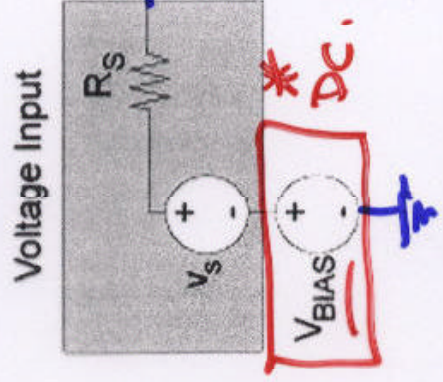

Thru.

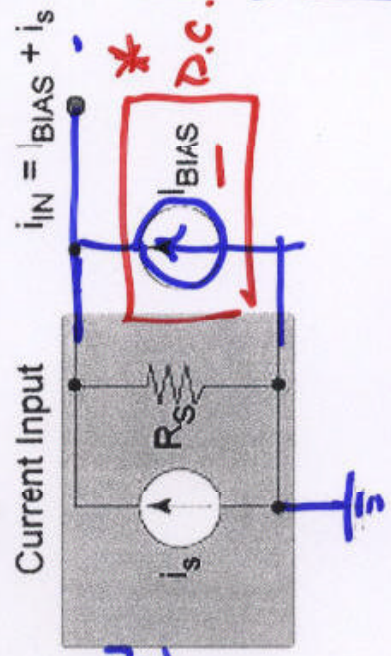

NOTION

or


TRANSDUCER SOURCE



Break ... why?



D = DEVICE.

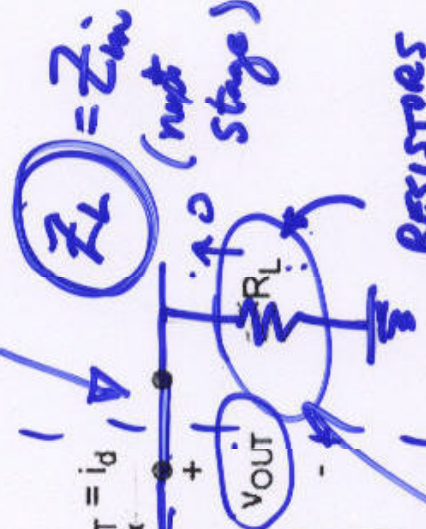

RESISTORS

AS LOADS...


MOSTLY WE

HAVE $R_L = \text{input resistance of next stage.}$

SMALL SIGNALS



* FUTURE ... ELIMINATE THESE DC SOURCES (240)

ACTIVE DEVICE :

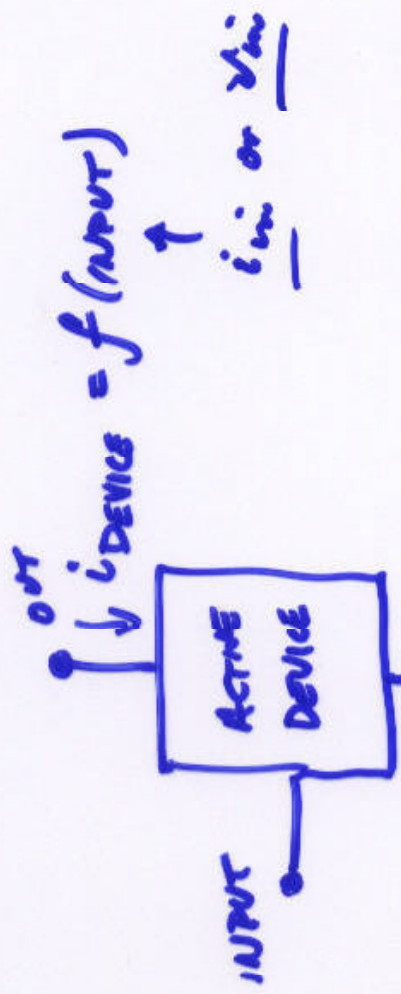

i_{in} or v_{in}

WHY WE NEED TO GENERALISE.

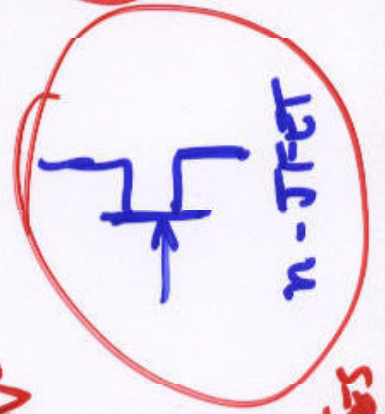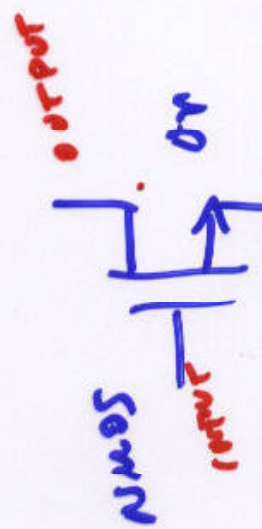

WEIRD DEVICES

Amplifier Terminology



✓ Sources: signal, its source resistance, and bias voltage
or current

Load: use resistor in Chap. 8, but could be a general

" impedance ... *Small-signal resistor.*

Port: a pair of terminals across which a voltage and
an associated current are defined

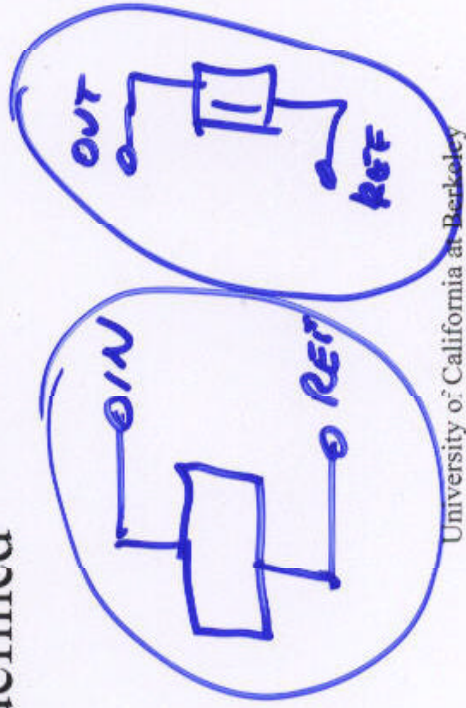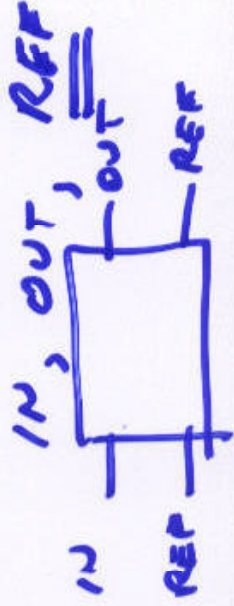- source, load: "one port"
- amplifier: "two port"



Amplifier Biasing

(PROBLEM 1:
D.C.)

Select V_{IN} (or I_{IN}) to set the DC device current to equal the supply current $I_{SUP} = I_D$

DC output current $I_{OUT} = \phi A.$

DC output voltage $V_{OUT} =$ WHAT WE WANT ... IN THE MIDDLE ...

$$V_{OUT} = 0V \neq v_{OUT}(t) = 0 = 0V.$$

Small-signal source voltage or source current results
in small-signal device current $i_d \rightarrow$


$$v_{OUT}(t) = \cancel{V_{OUT}} + \cancel{v_{OUT}(t)}$$

$$v_{out} = -i_d R_c$$

$$i_D^{(t)} = \frac{I_D}{I_{SUP}} + i_d(t)$$

$$i_{OUT} = I_{OUT} + i_{out}$$

$$i_{int} = i_d$$

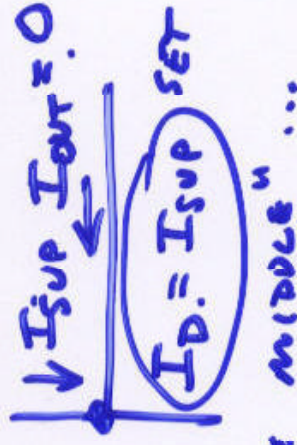

Math 54 Perspective

Can write linear system of equations for either i_{out} or v_{out} in terms of two of i_{in} , v_{in} , i_{out} , or v_{out} : possibilities are


$$i_{out} = \alpha_1 v_{in} + \alpha_2 v_{out}$$


$$i_{out} = \alpha_3 i_{in} + \alpha_4 v_{out}$$

$$v_{out} = \alpha_5 v_{in} + \alpha_6 i_{out}$$

$$v_{out} = \alpha_7 i_{in} + \alpha_8 i_{out}$$

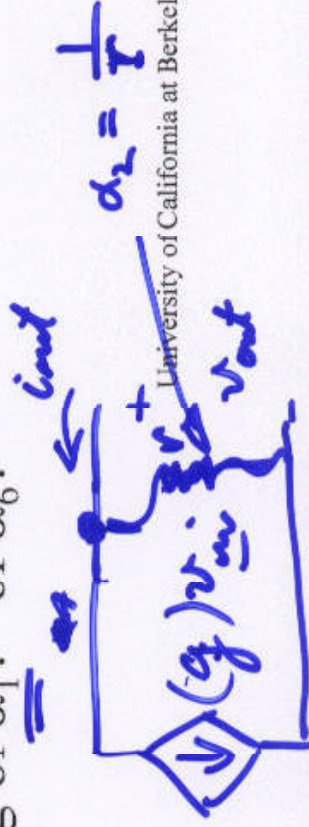What is physical meaning of α_1 ? of α_6 ?



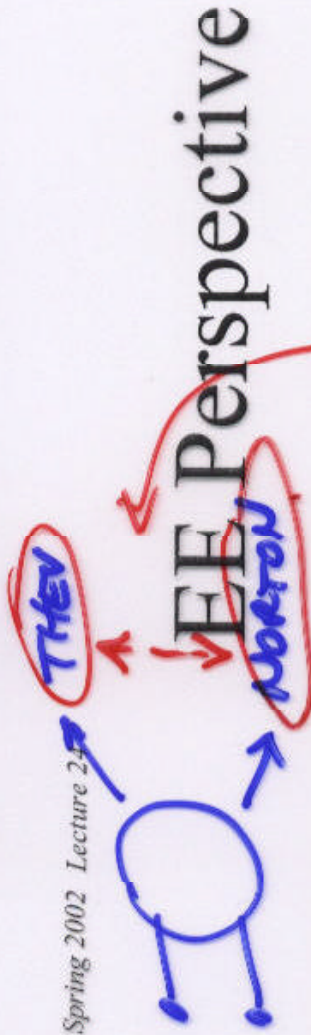


Four amplifier types: determined by the output signal and the input signal ... both of which we select (usually obvious)

INTECONVERTIBLE "LOW PAPER" ...
LESS SO IN REALITY.



- Voltage
- Current
- Transconductance
- Transresistance

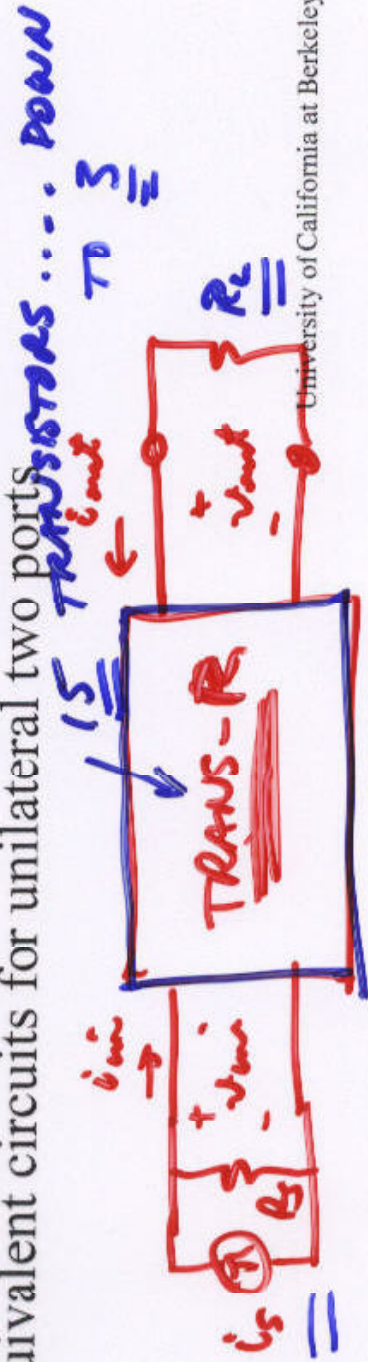We need *methods* to find the 6 α_i parameters for the four models and equivalent circuits for unilateral two ports





One-Port Models (EECS 40)

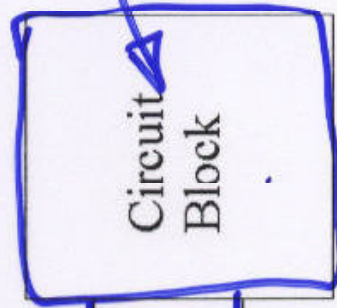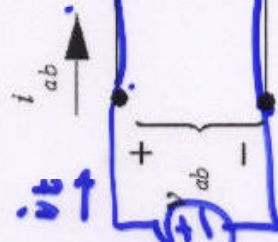
a terminal pair
across which a
voltage and associated
current are defined



LINER
ELEMENTS

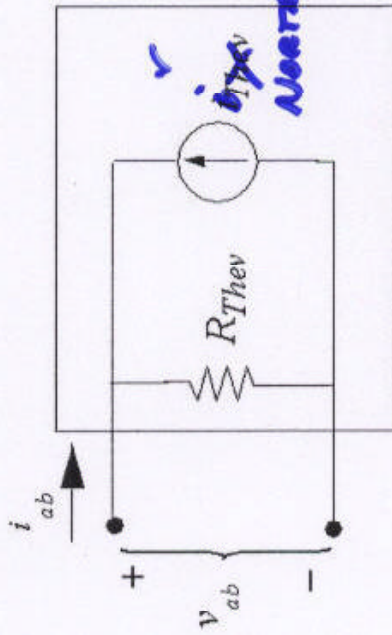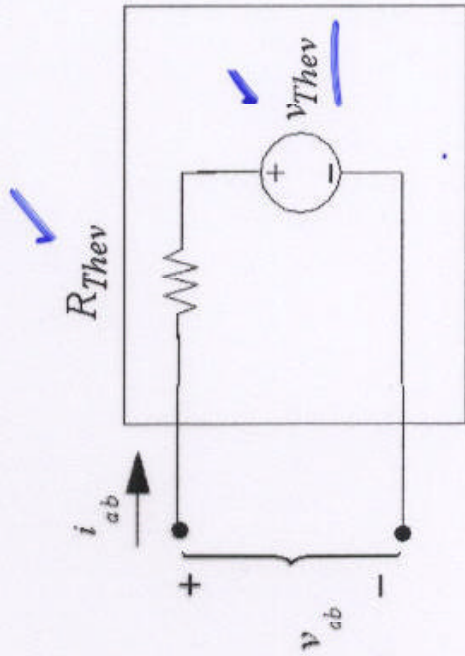

LINEARIZE
Small-Signal Two-Port Models

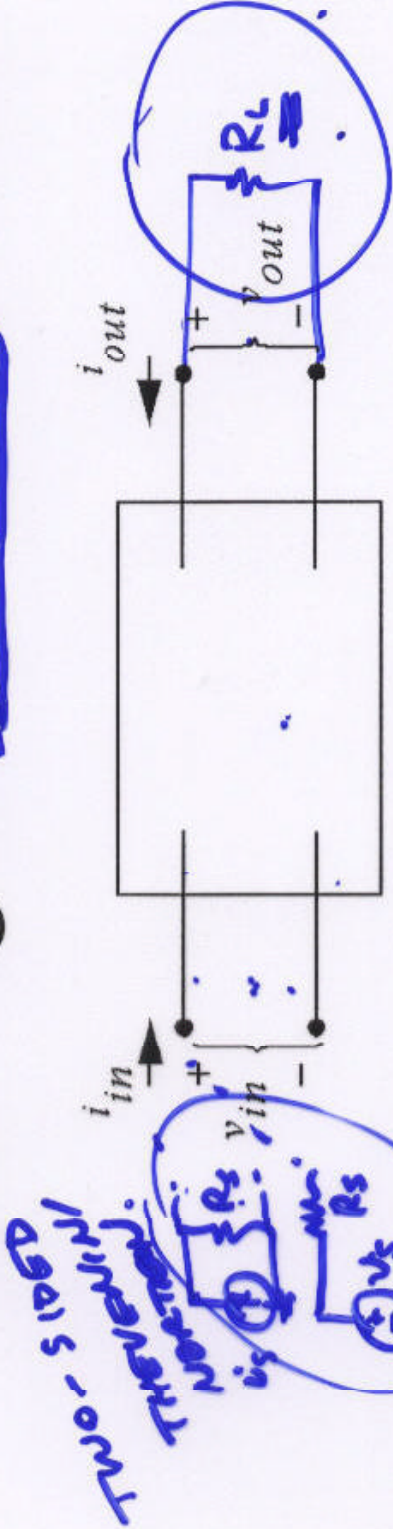

We assume that input port is linear and that the amplifier is

unilateral: DON'T HAVE INPUT PORT AFFECTED BY R_L
AND VICE VERSA. APPENDIX TO CHAP. 8

The output port: depends linearly on the current and voltage at the input and output ports

LATER

DON'T WORRY

input port ... depend on i_{in} , v_{in} only

(TRUE UP TO VERY HIGH FREQ)