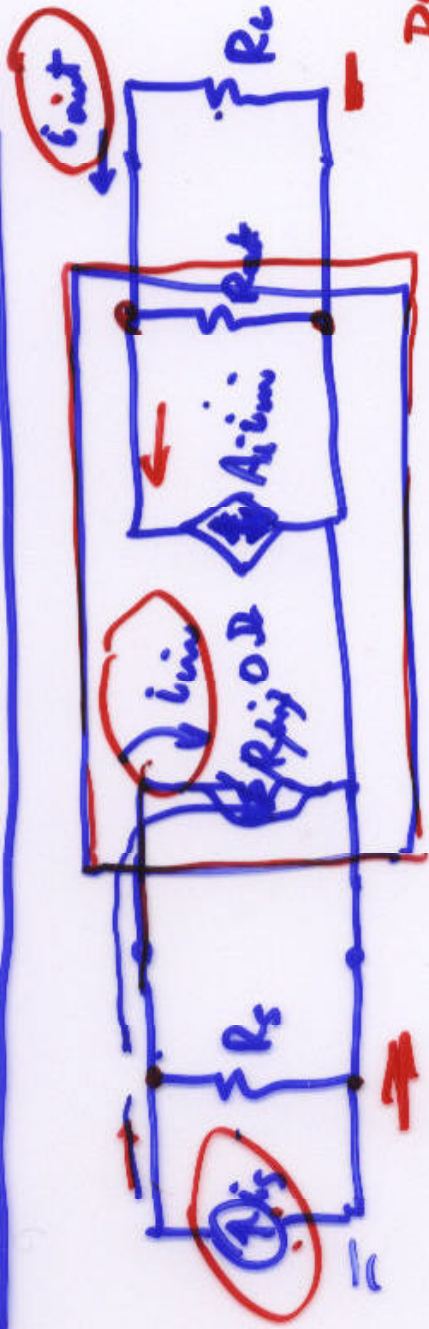


Lecture 25

- Last time: CHAPTER 8 (LEC. 22, 23 ...)
LEC. 24 ... CHAPTER 8
 - Two-port small-signal models of amplifiers
- Today: START
 - Finish methods for finding two-port model parameters
 - Start common-source amplifier

SMALL-SIGNAL
TWO-PORT S.S. MODELS

WHAT MAKES A GOOD CURRENT AMP?



DIVIDER

$$\frac{i_{out}}{i_{in}} =$$


$$\frac{i_{in}}{i_s} = \frac{R_s}{R_{in} + R_s}$$

$$\frac{i_{out}}{i_s} = \left(\frac{R_s}{R_{in} + R_s} \right) A_i \left(\frac{R_{out}}{R_o + R_{out}} \right)$$






= BIG (WE HOPE!)
 = OVERALL I-GAIN
 = LOADED I-GAIN
 LARGE: 10,000!

DIVIDERS ... MAX = 1. $\Rightarrow R_{in} = \infty \Omega$; $R_{out} = \infty \Omega$.

IDEAL CURRENT AMP:

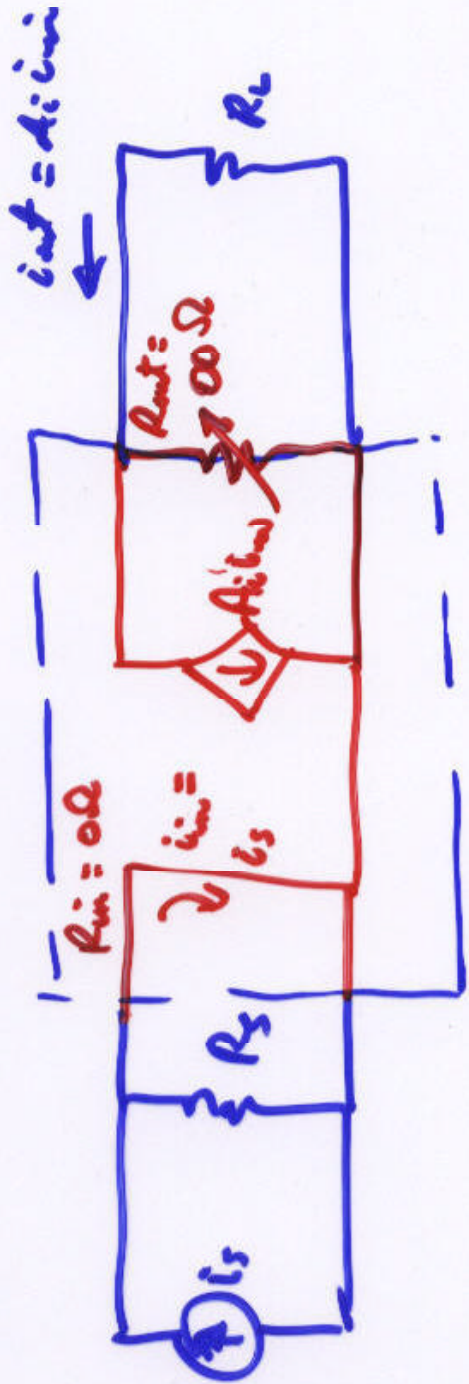


Two-Port Small-Signal Amplifiers

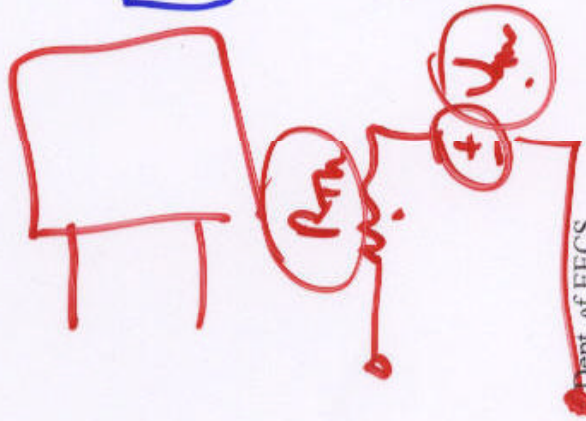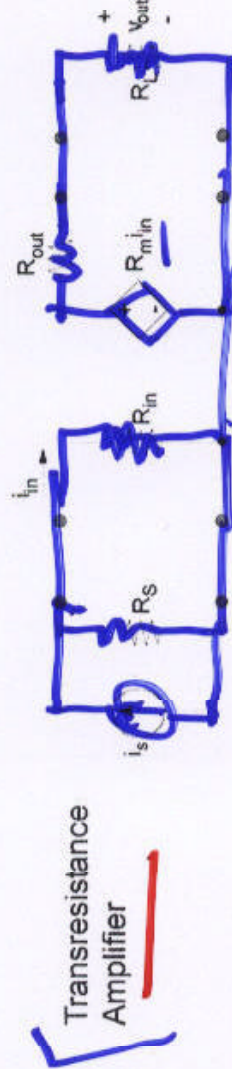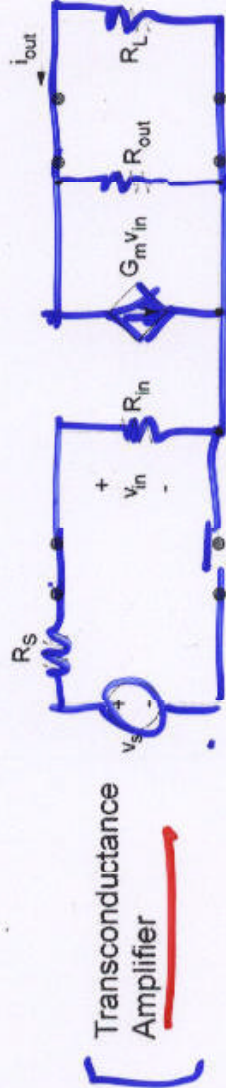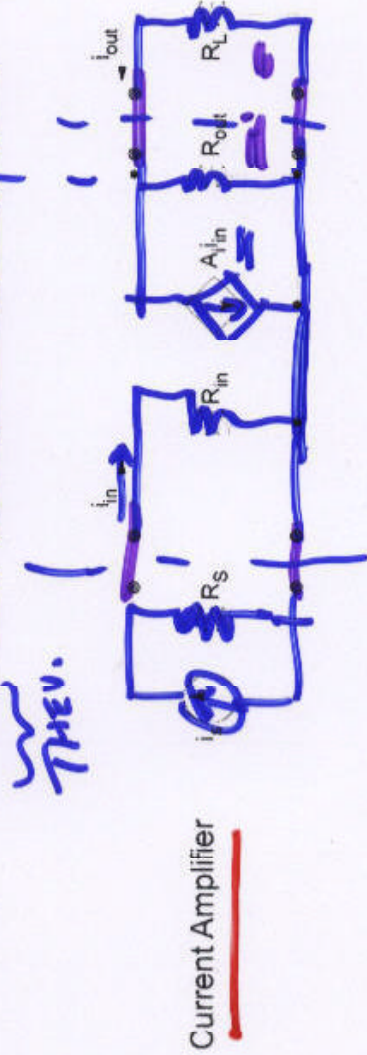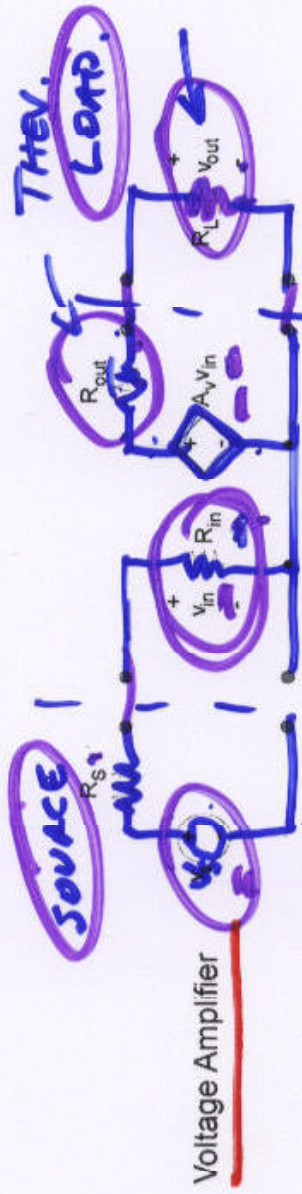

"EXPERIMENT" DEFINITION:

Input Resistance R_{in}

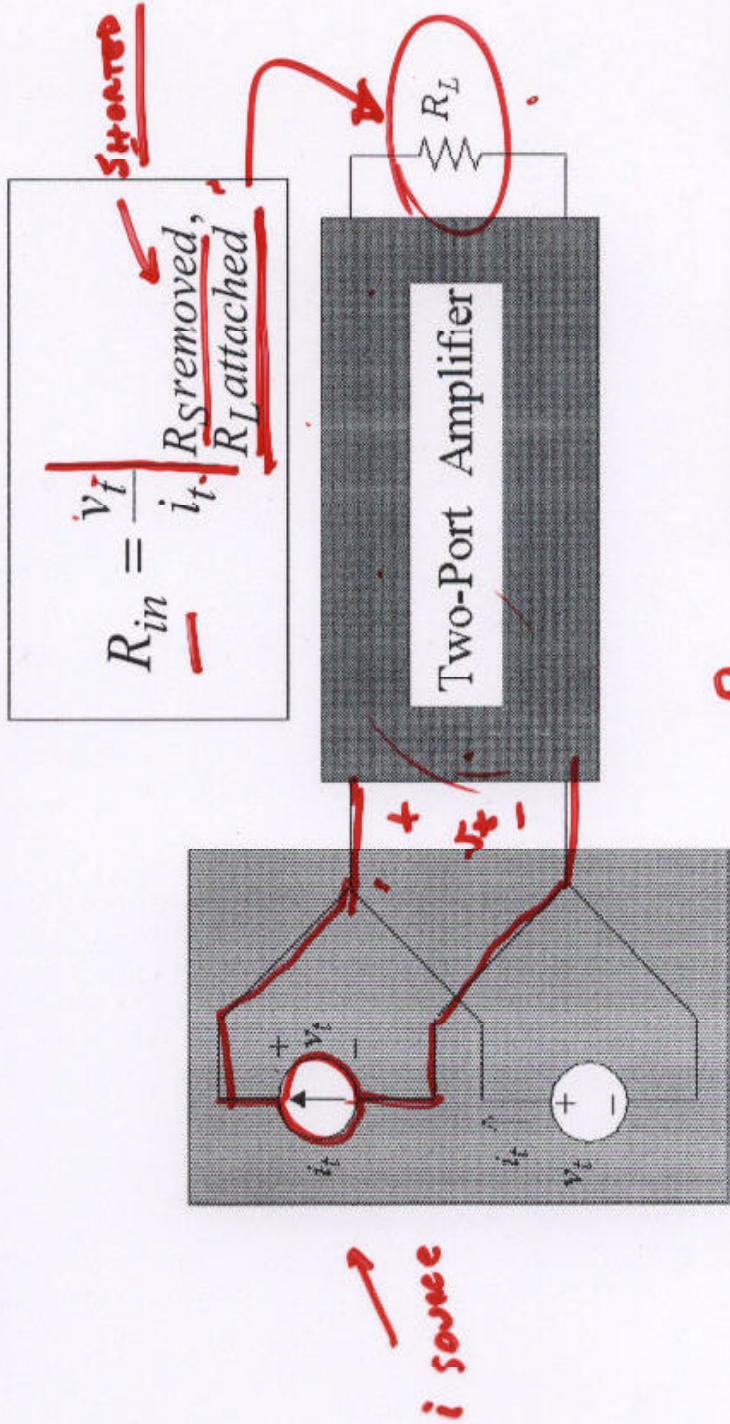
Looks like a Thevenin resistance measurement, but note that the output port has the load resistance attached



R_{in} COULD BE A FUNCTION OF R_L

Output Resistance R_{out}

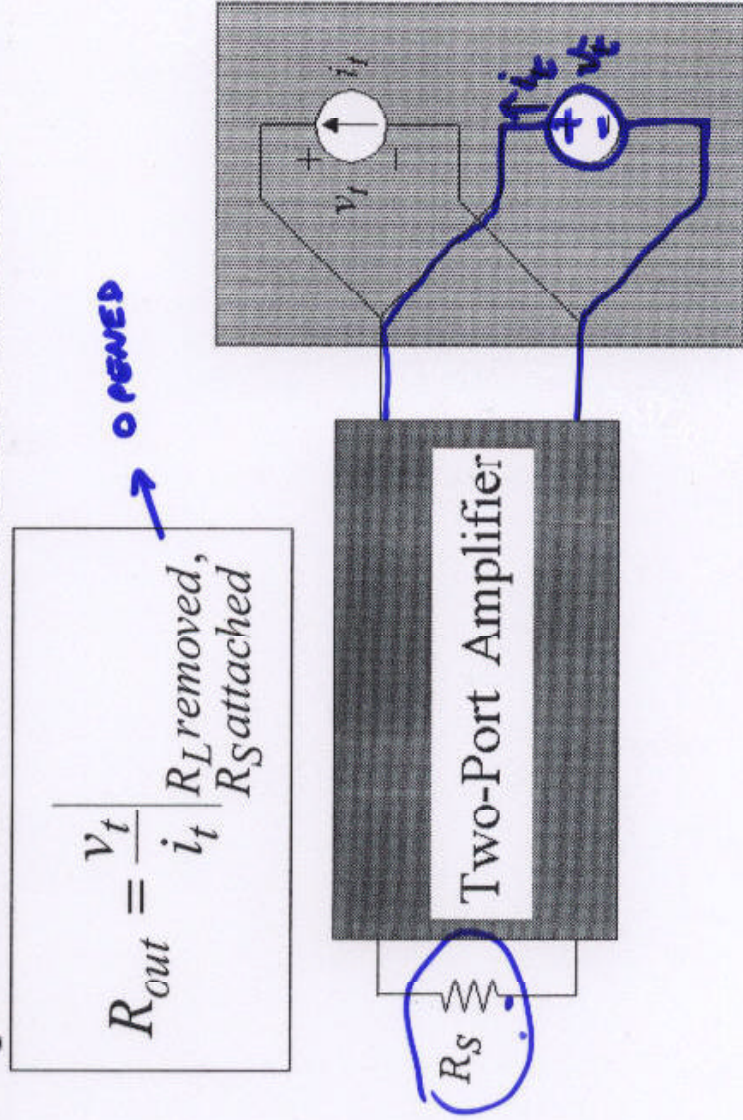
Looks like a Thevenin resistance measurement, but note that the *input* port has the *source* resistance attached



R_{out} COULD BE A FUNCTION OF R_S
NEVER R_L

Finding the Voltage Gain A_v

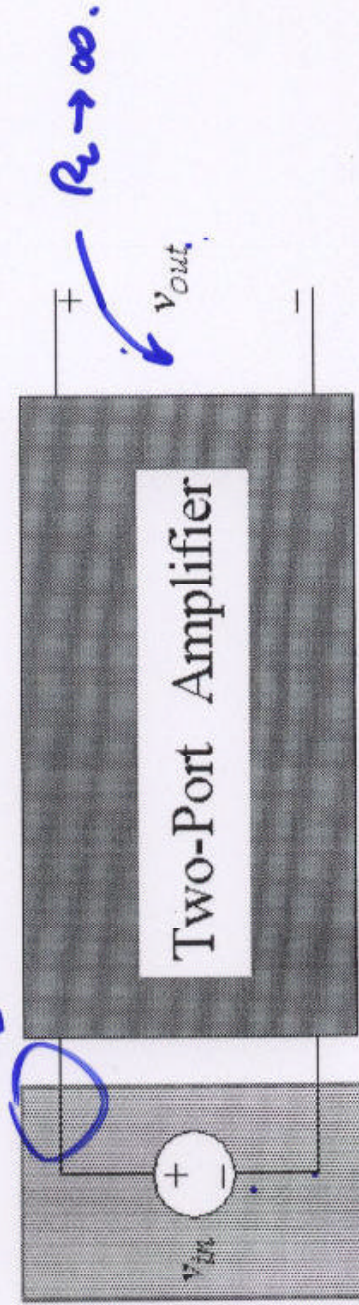Key idea: the output port is open-circuited and the source resistance is shorted



PURE / IDEAL
($R_s \rightarrow 0$)
V-SOURCE

$$A_v = \frac{v_{out}}{v_{in}} \quad R_s = 0, R_L \rightarrow \infty$$


BOTH DIVIDERS ARE = 1.0.

Finding the Current Gain A_i

Key idea: the output port is shorted and the source resistance is removed

D.C.
SMALL-SIGNAL
SHORT.


i_{out}

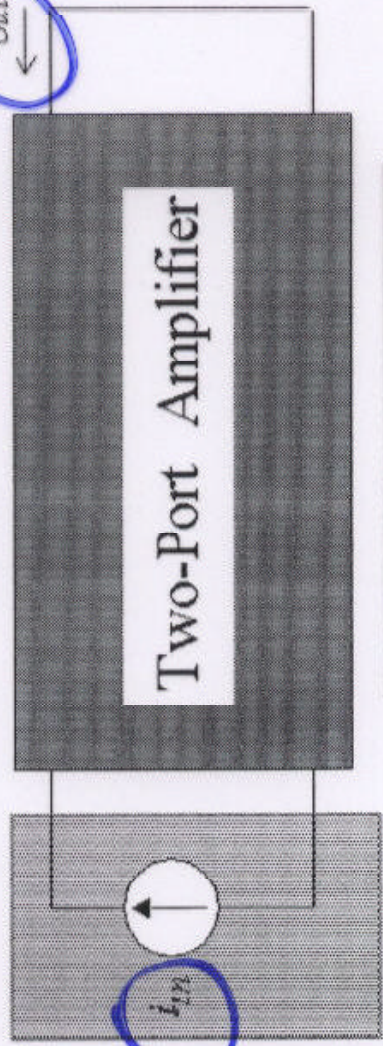

$$A_i = \frac{i_{out}}{i_{in}} \quad R_S \rightarrow \infty, R_L = 0$$

IDENTICAL...
 $R_S \rightarrow \infty$

Finding the Transresistance R_m

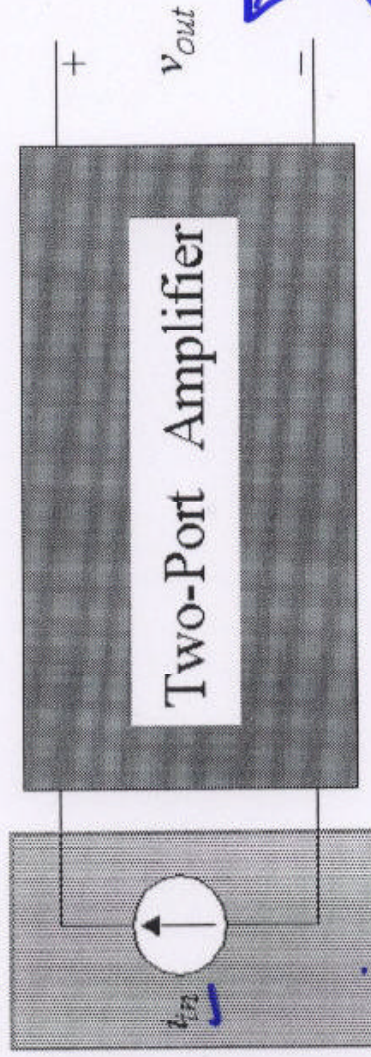

PURE CURRENT
 $R_s \rightarrow \infty$


$$R_m = \frac{v_{out}}{i_{in}} \quad R_s \rightarrow \infty, R_L \rightarrow \infty$$

OPEN ...
 $R_L \rightarrow \infty$

NO "LOADING" ...
OUTPUT VOLTAGE
DIVIDER

$$\left(\frac{R_L}{R_{out} + R_L} \right) \rightarrow 1$$

Finding the Transconductance G_m

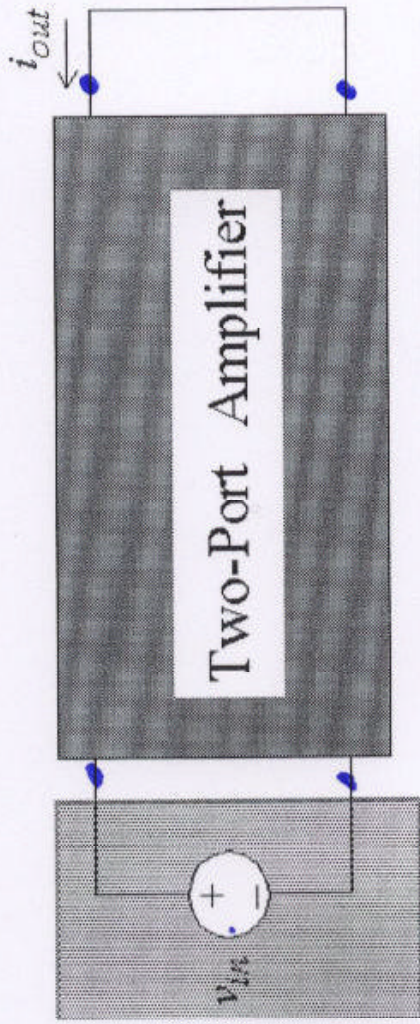

$$G_m = \left. \frac{i_{out}}{v_{in}} \right|_{R_S = 0, R_L = 0}$$

"PURE"


VOLTAGE

IN

$R_S \rightarrow 0 \Omega$



DC Bias

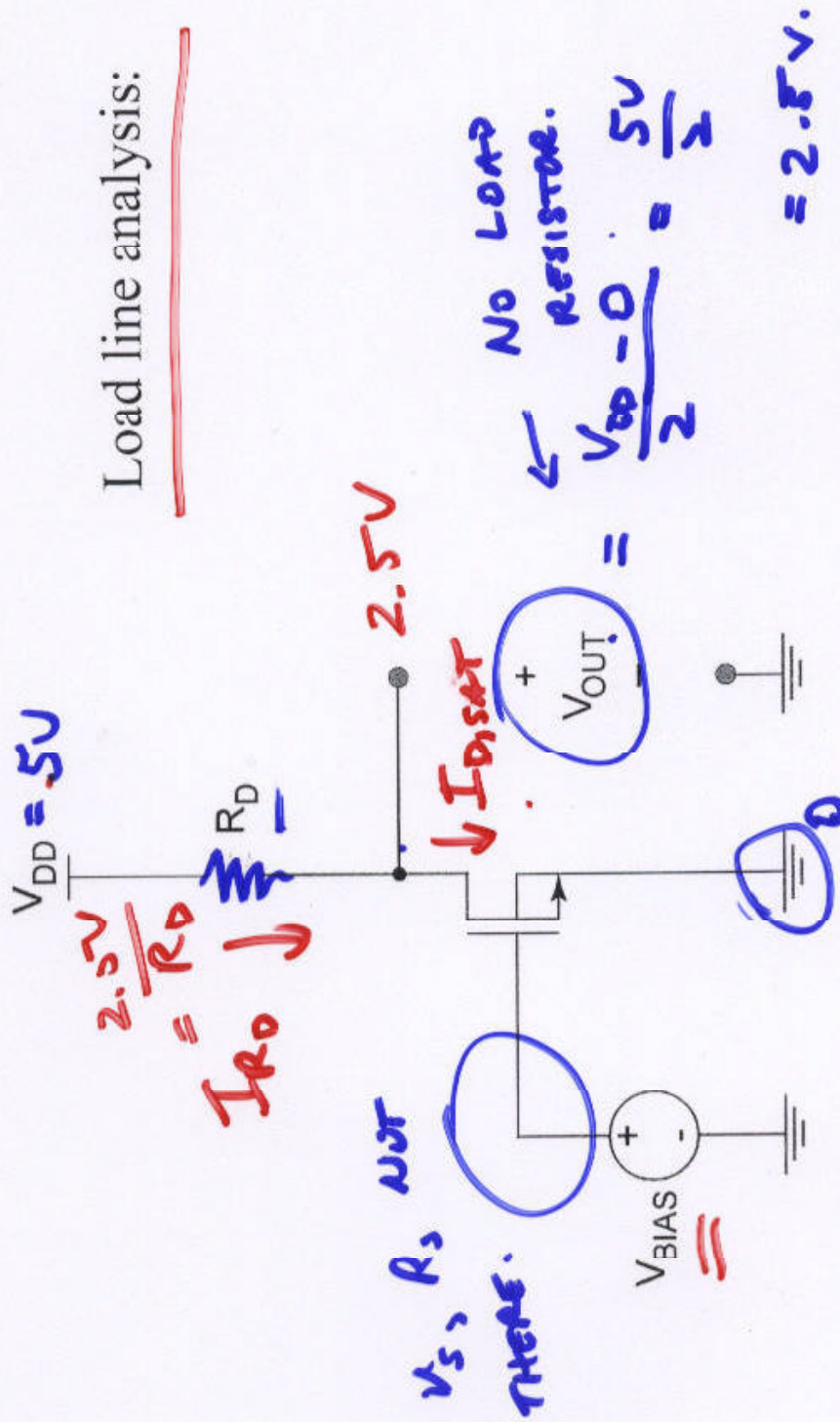

Load line analysis:

(w/L), $\mu_n C_{ox}$, V_{TH}


TOO TRIVIAL
TOO FAMILIAR

First Example: the

Common-Source Amplifier (again)


G, D, S ← "COMMON"

OUTPUT RESISTANCE
PREVIOUS STAGE.

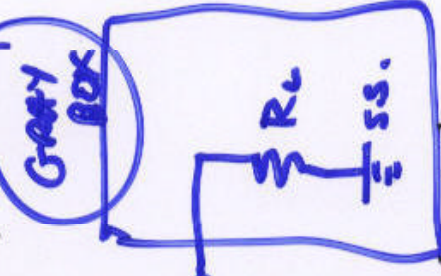

What about the load resistor?


INPUT RESISTANCE OF NEXT STAGE !!

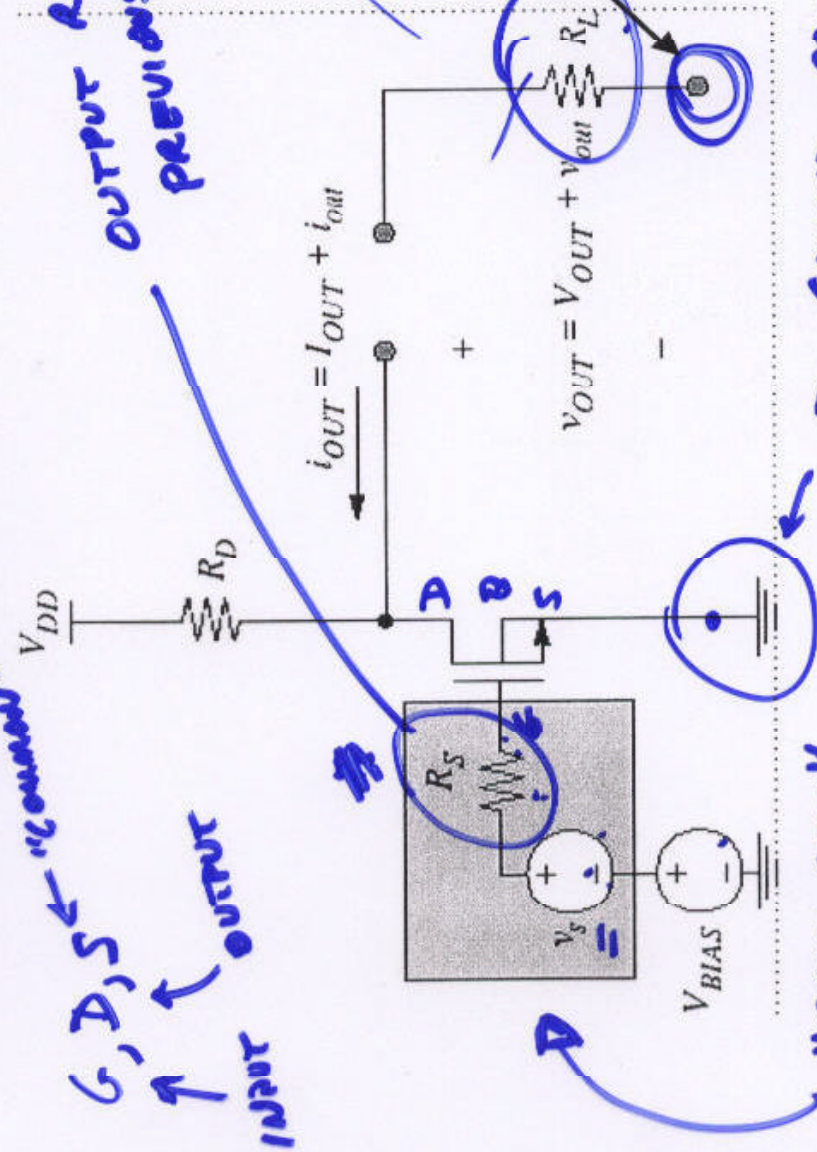

"GRAY BOX"

DC GROUND - OR BATTERY
SMALL-SIGNAL ELEMENT

Load-Line Analysis to find Q

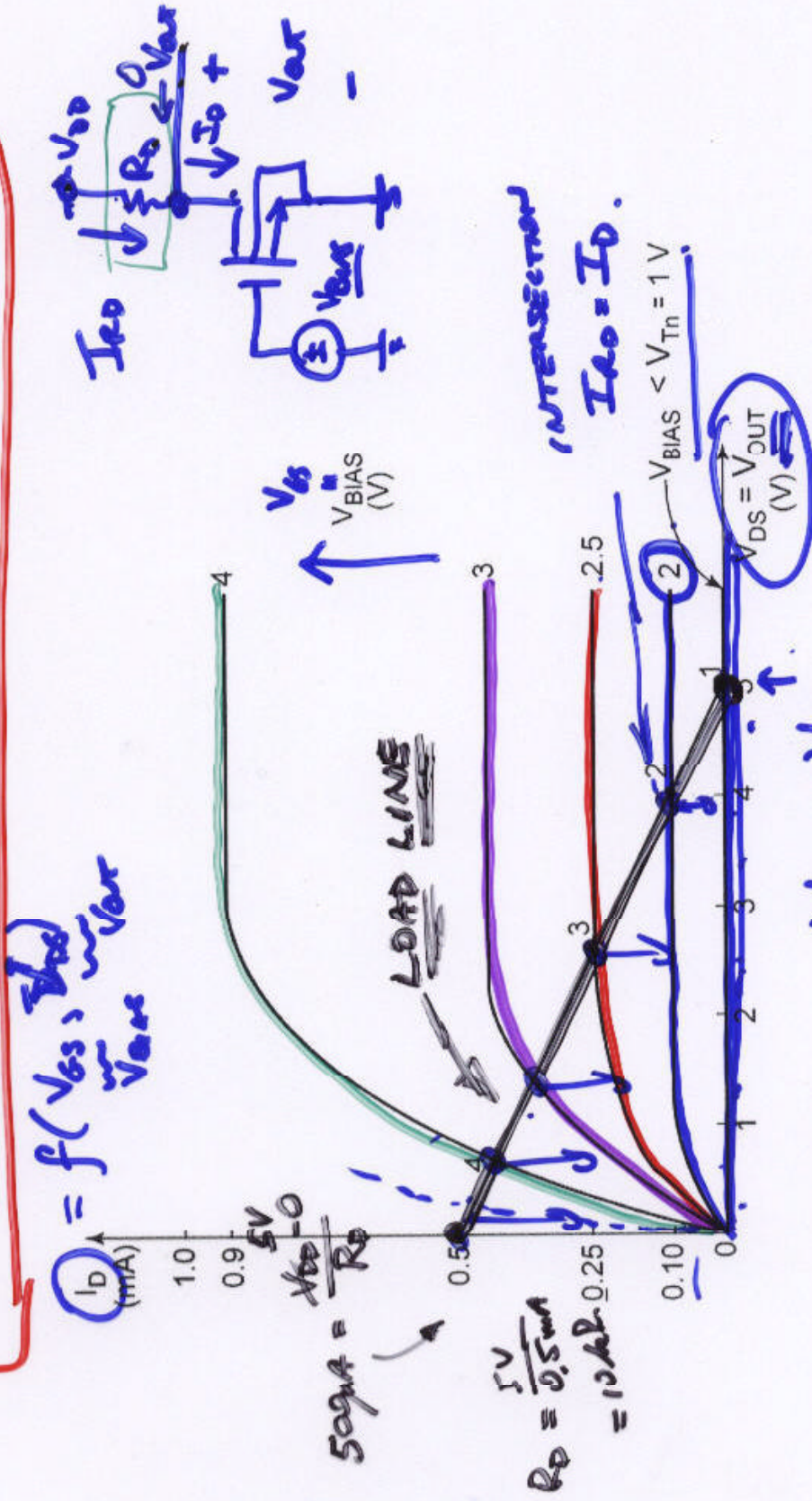

$$I_{RD} = \frac{V_{DD} - V_{out}}{R_D}$$


University of California at Berkeley

Dept. of EECS

... Plot it!

EE 40

DC Transfer Function

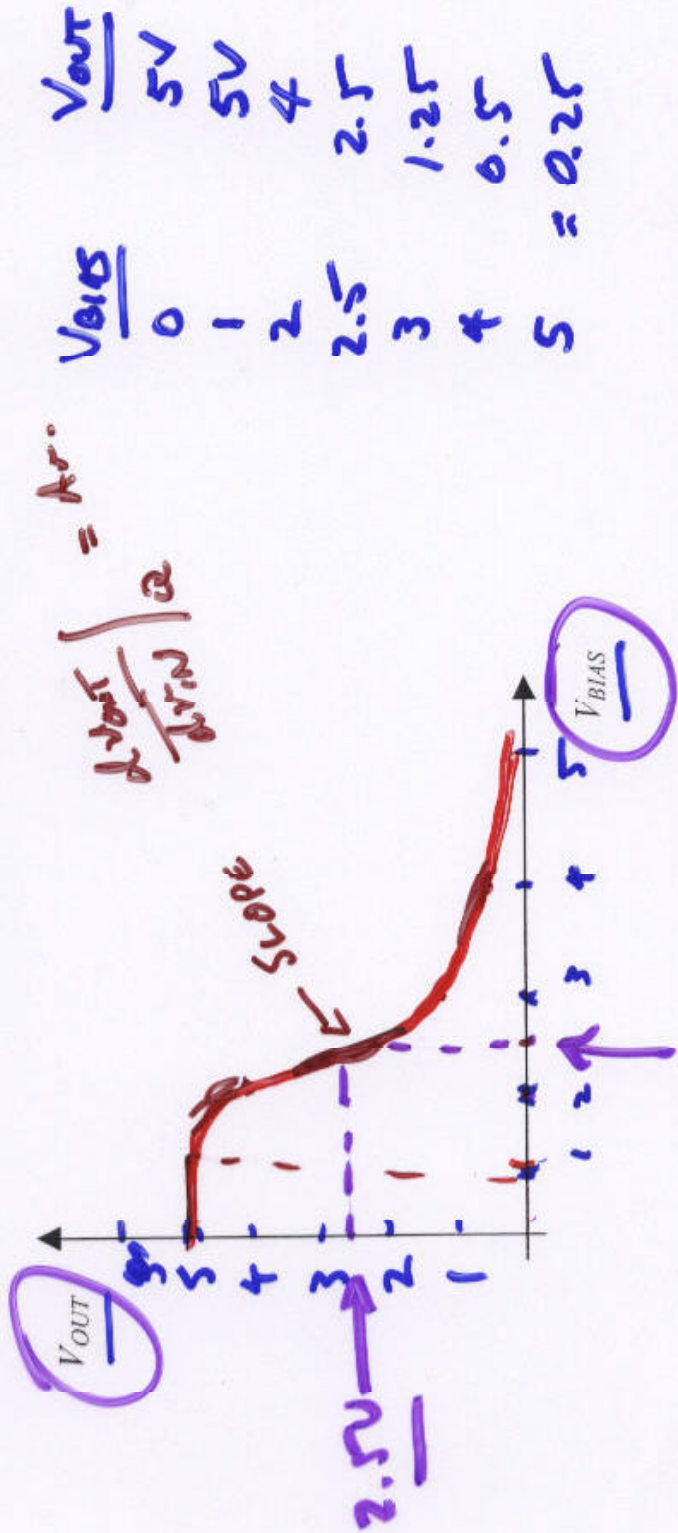

$\frac{dV_{out}}{dV_{in}} = Av$

$V_{BIAS} = 2.5V \dots$ HIGHER THAN NORMAL