

[LAST CHAPTER 8] LECTURE



Lecture 29

- FALL 2001 MIDTERM II POSTED W/O SOLUTIONS.
- SAMPLE MT. II ... } FRIDAY

- REVIEW SESSION → M 6-7:30 277 COBY

- Last time:
 - Bipolar single-stage amplifiers: biasing, common-emitter, common-base, common-collector

- Today: CEdy

- Overview of single-stage amplifiers

- ~~Frequency response of CS stage operated as a current amplifier~~


MILLER THEOREM...

FREQUENCY RESPONSE NOW IN LAB!

PITFALLS ...




TYPE IN P3 (0), #2 (e) SOLNS.

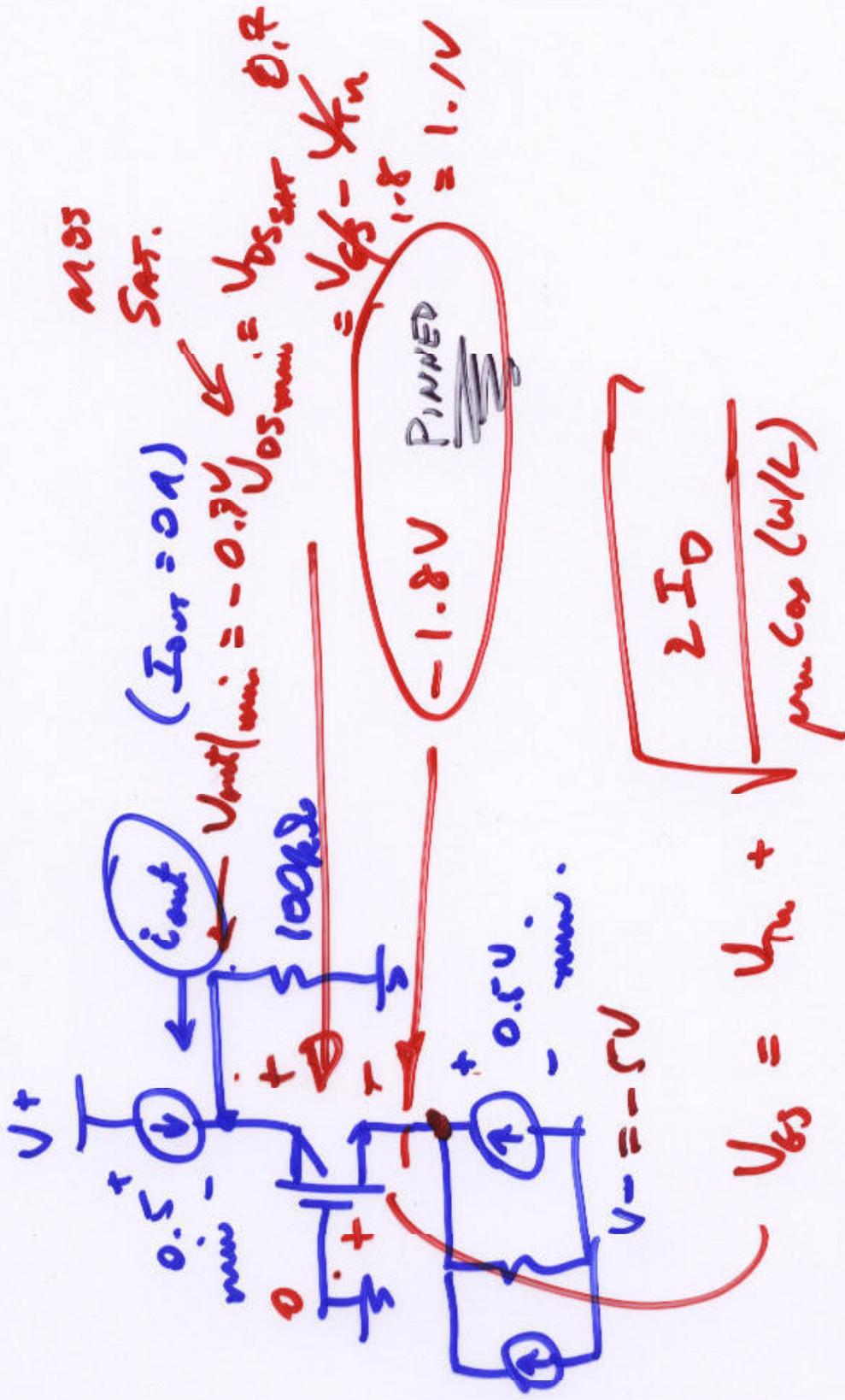

$I_{out(min)} = \frac{0.7}{100kR} = 7\mu A$

O.C.

Common-Collector Voltage Gain

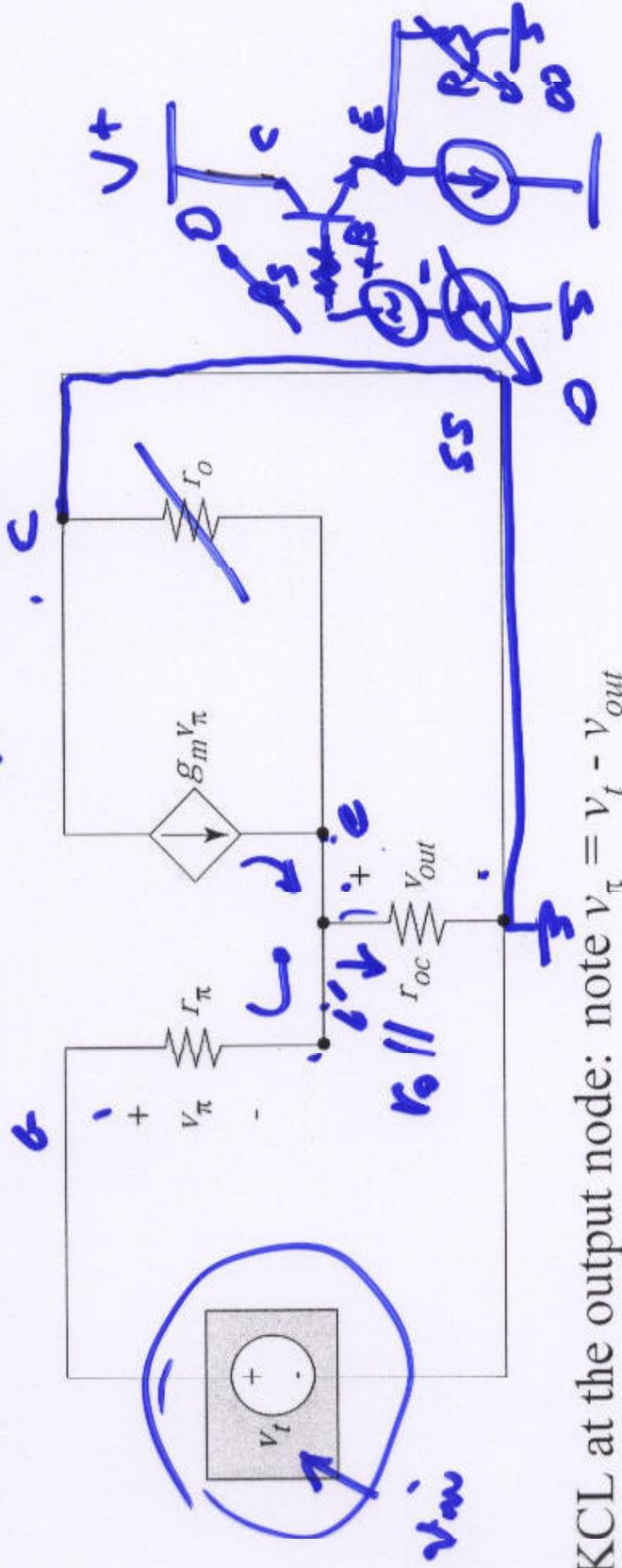

KCL at the output node: note $v_{\pi} = v_i - v_{out}$

$$A_v = \frac{v_{out}}{v_i} \Bigg|_{R_s=0, R_L=\infty}$$

$$v_c = v_{\pi} + v_{out}$$

$$v_{out} = \left[\frac{v_c}{R_L} + g_m v_{\pi} \right] \cdot r_o \parallel R_L \parallel R_E$$

University of California at Berkeley

~~$v_c = v_{out}$~~

SOLVE FOR v_c

$$v_{out} = v_T \left[\frac{1}{r_T} + g_m \right] \cdot r_o \parallel r_{oc}$$

$$v_T = \frac{v_{out}}{\left(\frac{1}{r_T} + g_m \right) \cdot (r_o \parallel r_{oc})} \quad \text{for } r_o = \frac{V_A}{V_{ov}}$$

$$\frac{f_\beta}{g_m} \left(\dots \frac{1}{r_o} = \frac{g_m}{f_\beta} \right) \quad r_o = \frac{V_A}{I_C}$$

$$v_T = \frac{v_{out}}{[m_{ESS}] + v_{out}}$$

$$g_m (r_o \parallel r_{oc}) = \frac{I_C}{V_{ov}} \quad \text{for } r_o \parallel r_{oc} = 0.5 \text{ms}$$

~~$\frac{I_C}{V_{ov}}$~~ (200k) = 100.


$$v_T = v_{out} \left[1 + \frac{1}{m_{ESS}} \right]$$

$$A_v = \frac{v_{out}}{v_T} = \left(\frac{1}{1 + \frac{1}{m_{ESS}}} \right) \approx 1$$

$$\Rightarrow \underline{m_{ESS}} = \left(\frac{1}{r_T} + g_m \right) \cdot r_o \parallel r_{oc} \approx 100$$

✓ SMALL! Common-Collector Output Resistance

$\approx \frac{1}{g_m}$

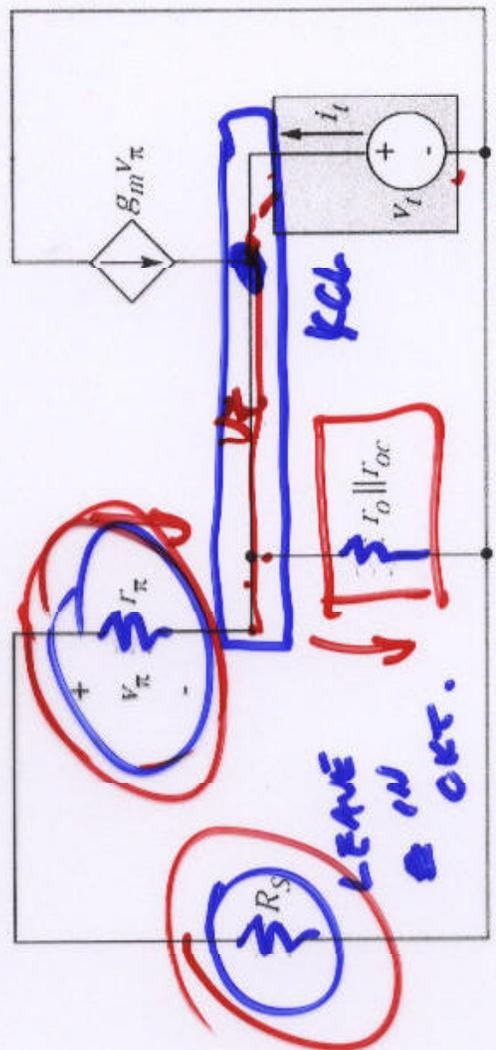

$$R_{out} = \frac{v_t}{i_t} \Big|_{v_{oc} = 0, R_S \checkmark}$$

Divider between v_t and v_π

$$i_t \approx + g_m v_\pi + \frac{v_t}{r_o \parallel r_{oc}} = 0$$

100x smaller

Want v_t/i_t ... get rid of v_{π} .

$$v_{\pi} = -v_t \left[\frac{r_{\pi}}{r_{\pi} + R_S} \right]$$



$$i_t + g_m \left[\frac{-v_t r_{\pi}}{r_{\pi} + R_S} \right] - \frac{v_t}{r_o || r_{oc}} = 0$$


$$R_{out} = \frac{v_t}{i_t} = \frac{g_m r_{\pi}}{r_{\pi} + R_S} + r_o || r_{oc} + \frac{1}{g_m || r_{oc}} \left[\frac{g_m r_{\pi}}{r_{\pi} + R_S} + \frac{1}{r_o || r_{oc}} \right]^{-1} v_t$$

$$R_{out} \approx r_{\pi} + R_S + \frac{R_S}{r_o} + \frac{g_m r_{\pi}}{g_m} \leftarrow g_m r_{\pi}$$

Common-Collector Two-Port Model

FIG. 8.47

HOS ✓

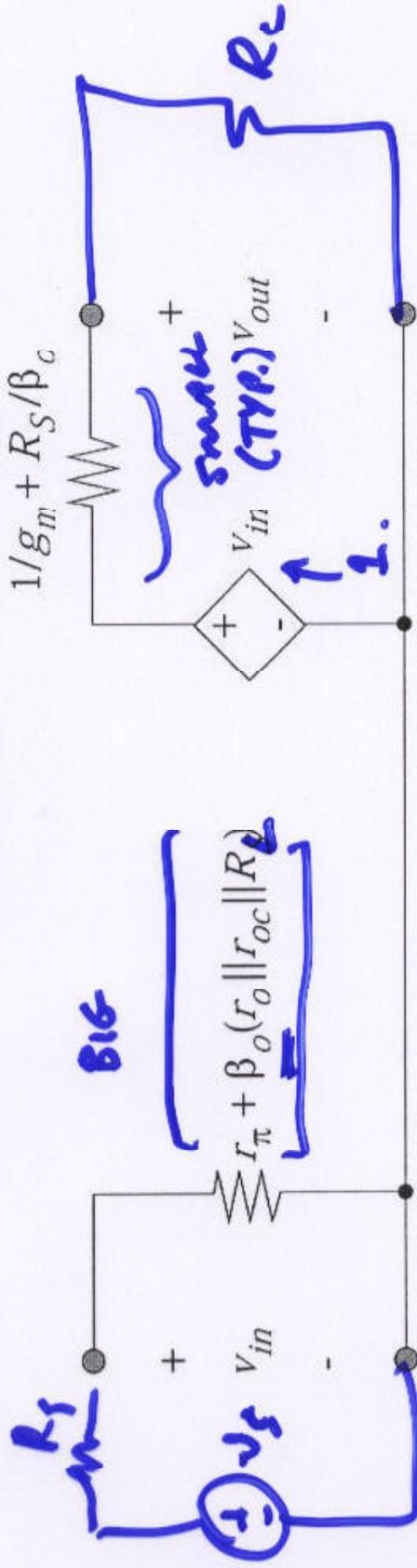


[BIG 100's of $k\Omega$]
 MOD 10's of $k\Omega$]
 SMALL $\leq 1 k\Omega$.

FOR $I_c, I_D \approx 100 \mu A.$

Common-Collector Summary

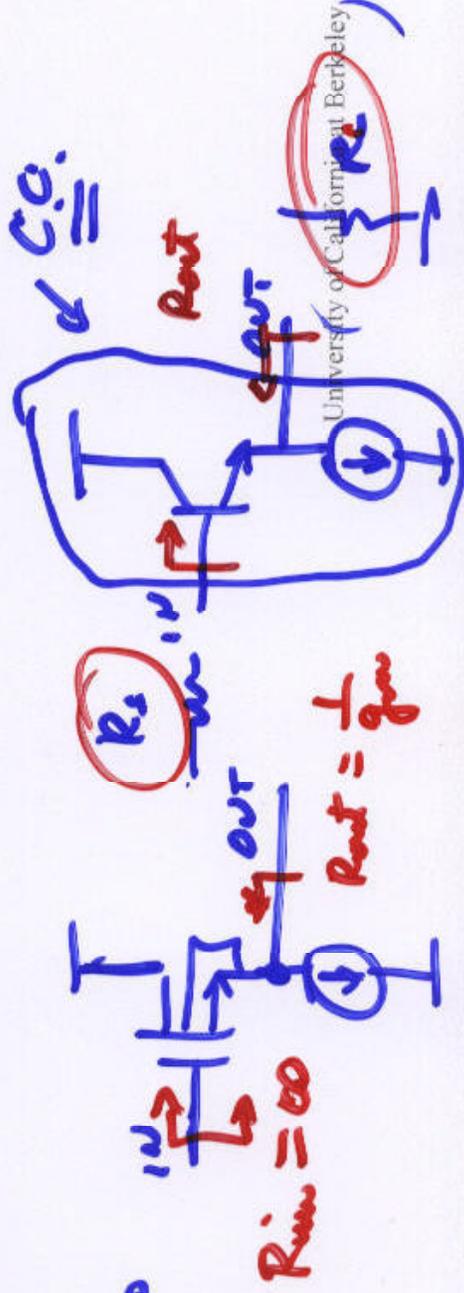- Typo in Fig. 8.47 in text ... R_{in} can't depend upon R_S !
- Input and output resistances depend on load and source resistances, respectively
- See Appendix to Chapter 8 for limits to using this model with very low values of R_L



- GOOD FOR EE 140 -

Summary of Two-Port Parameters for CE/CS, CB/CG, CC/CD Amplifiers

2nd.

Amplifier Type	Controlled Source	Input Resistance R_{in}	Output Resistance R_{out}
Common Emitter	$G_m = g_m$	r_π	$r_o \parallel r_{oc}$
Common Source	$G_m = g_m$	infinity	$r_o \parallel r_{oc}$
Common Base	$A_i = -1$	$1 / g_m$	$r_{oc} \parallel [(1 + g_m(r_\pi \parallel R_S)) r_o]$, for $g_m r_o \gg 1$
Common Gate	$A_i = -1$	$1 / g_m$, ($v_{sb} = 0$) -otherwise- $1 / (g_m + g_{mb})$	$r_{bc} \parallel [(1 + g_m R_S) r_o]$, ($v_{sb} = 0$) -otherwise- $r_{oc} \parallel [(1 + (g_m + g_{mb}) R_S) r_o]$ both for $r_o \gg R_S$
Common Collector	$A_v = 1$	$r_\pi + \beta_o(r_o \parallel R_L)$	$(1 / g_m) + R_S / \beta_o$
Common Drain	$A_v = 1$ if $v_{sb} = 0$, -otherwise- $g_m / (g_m + g_{mb})$	infinity	$1 / g_m$ if $v_{sb} = 0$, -otherwise- $1 / (g_m + g_{mb})$


FUNCTIONABLE

TRANSFORMER

SPECIFIC I-BUFFER

SPECIFIC BUFFER

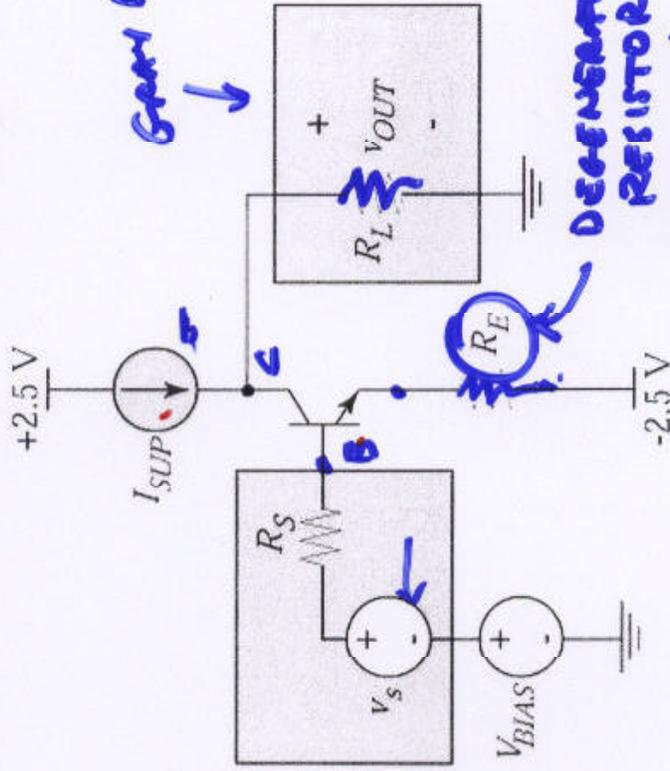
The "Chapter 8" Method for Single-Stage Amplifier Analysis.



1. What is it? ✓ NOTHING IS "COMMON"
2. DC Bias
3. Small-signal 2-port model R_{in}, R_{out}, G_m
4. Output swing

input on base
output on collector
⇒ emitter

DC Bias for CE deg

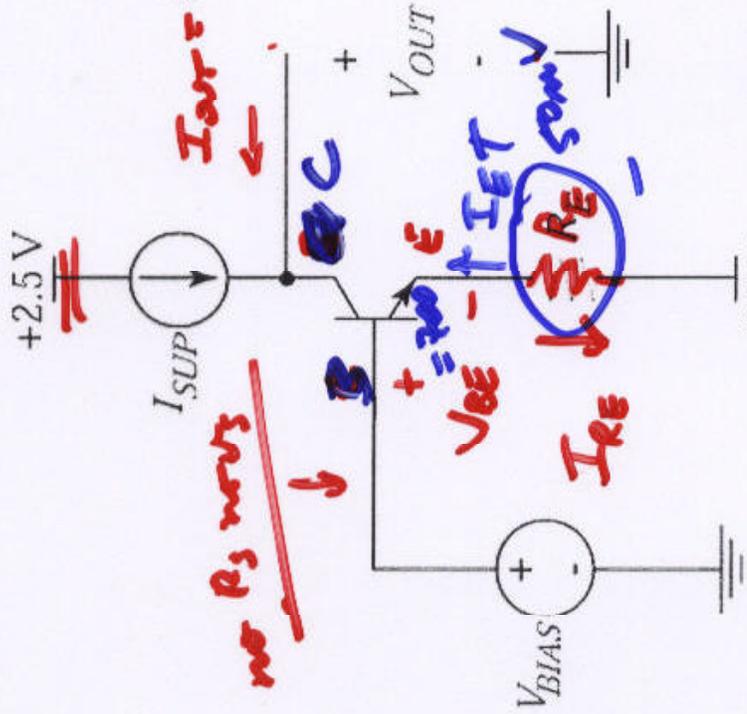

TYP.
 $R_E = 500 \Omega$
 $0.1 \text{ mA} = \frac{1}{2} I_C$
 $I_C R_E = 100 \mu\text{A} \cdot 500 \Omega$
 $= 0.05 \text{ V}$

$$V_{BE} = \left\{ V_{BE} \ln \left[\frac{I_C}{I_S} \right] + I_C R_E \right.$$

$$\approx 0.7 \quad I_{RE} R_E \approx I_C R_E = I_{SUP}$$

$$V_{BIAS} = V_{BE} + V_{RE}$$

$$I_{RE} = -I_E = \frac{1}{\alpha_F} I_C \approx I_C$$

$$0.99^{-1} = 1.01$$

$g_m = 50$
 $r_{\pi} = 500 \Omega$
 $R_E = 10 \Omega$

TWO-PORT Model for CE

APPLYING THE TABLE

Input looks like CC $\rightarrow R_{in} \approx R_{in,CC} = r_{\pi} + (\beta+1)R_E \parallel r_{\pi}$


Output looks like CB (see p. 504 for details) \rightarrow

$R_{out} \approx R_{out,CB} = (r_o \parallel (1 + g_m R_E)) \parallel R_E$

Transconductance: $G_m = \frac{g_m}{1 + g_m R_E}$

$\beta_0 + 1 \approx \beta_0 = g_m r_{\pi}$

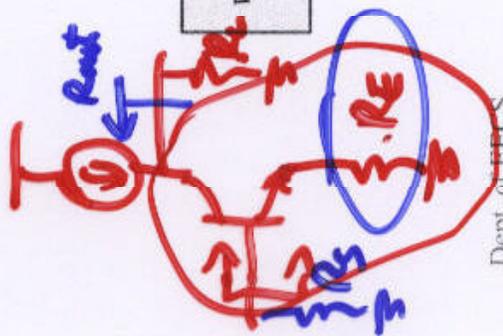$r_{\pi} + g_m R_E = \frac{r_{\pi}(1 + g_m R_E)}{\beta_0}$



$\frac{v_o}{v_i} = \frac{v_o}{v_{\pi}(1 + g_m R_E)}$

$\approx \frac{v_o}{v_{\pi}} = \frac{R_{out}}{R_{in}}$