

- WAITLISTS → CHECK THAT YOU'RE ENROLLED.


## Lecture 2

- LABS: START MONDAY → SHOULD CHECK ON WEB PAGE. STOP BY 353 COY AT 1 PM.

- Last time:
  - Course overview
  - Sinusoidal signals !
  - RC circuit with sinusoidal input voltage

- Today :
  - Finish RC circuit: introduce decibel (dB)
  - Introduce phasor representation of sinusoids

# RC Circuit with Sinusoidal Input

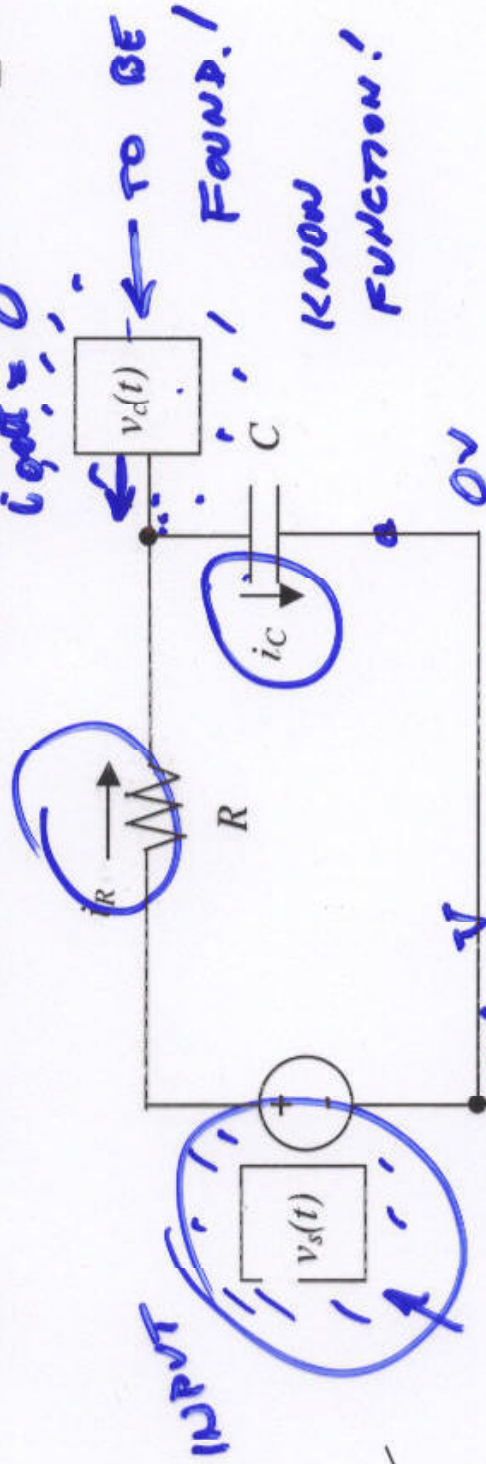

REM. NUMBER.  
 $v_s(t) = V_s \cos(\omega t)$  : set phase of source to zero (use as the reference)

$v_c(t) = V_c \cos(\omega t + \phi)$  : solution is a sinusoidal signal with the same frequency, but with a different amplitude and phase-shifted with respect to the source ✓



# Circuit Analysis

$$i_R = \frac{v_S - v_C}{R} ; \quad i_C = C \frac{dv_C}{dt} \quad \boxed{C = \text{const.}}$$

$$i_R = i_C \Rightarrow \frac{v_S - v_C}{R} = C \frac{dv_C}{dt}$$

$$\frac{v_S - v_C}{R} = RC \frac{dv_C}{dt} = \tau \frac{dv_C}{dt} \quad \checkmark$$

$\tau = RC = S.$

$$\boxed{v_S(t) = \tau \frac{dv_C}{dt} + v_C.}$$

$$V_S \cos \omega t = \tau \left[ -\omega V_C \sin(\omega t + \phi) + V_C \cos(\omega t + \phi) \right]$$

(we want  $(\phi, V_C/V_S)$ )

$$V_S \cos \omega t = V_C \cos(\omega t + \phi)$$

$$V_S \sin \omega t = -V_C \sin(\omega t + \phi)$$

$$\text{Dept. of EECS } \sin(x+y) = \sin x \cos y + \cos x \sin y.$$

$$v_{out}(t) = \cos(\omega t + \phi) = \cos \omega t \cos \phi - \sin \omega t \sin \phi$$

## Circuit Analysis (Continued)

$$\sin(\omega t + \phi) = \sin \omega t \cos \phi + \cos \omega t \sin \phi$$

$$V_s \cos \omega t = -\omega \tau V_c \left\{ \sin \omega t \cos \phi + \cos \omega t \sin \phi \right\} + V_c \cos(\omega t + \phi) \rightarrow \cos \omega t \cos \phi - \sin \omega t \sin \phi$$

$$\begin{aligned} \boxed{V_s \cos \omega t} &= \left\{ -\omega \tau V_c \cos \phi \right\} \sin \omega t - \omega \tau V_c \sin \phi \cos \omega t + V_c \cos \phi \cos \omega t \\ &= \sin \omega t \left\{ -\omega \tau V_c \cos \phi - V_c \sin \phi \right\} + V_c \cos \phi \cos \omega t \\ &= V_c \left[ -\omega \tau \cos \phi - \sin \phi \right] \sin \omega t + \cos \omega t \left\{ -\omega \tau V_c \sin \phi + V_c \cos \phi \right\} \end{aligned} \quad \#2$$

Dept. of EECS

University of California at Berkeley

$$\sin \phi / \cos \phi = -\omega \tau \Rightarrow \phi = \tan^{-1}(-\omega \tau)$$

• Know  $\phi$  ... FIND  $V_c/V_s$

$$V_s = -\omega\tau V_c \sin\phi + V_c \cos\phi$$

$$V_s/V_c = -\omega\tau \sin\phi + \cos\phi$$

$$\sin[\tan^{-1}(-\omega\tau)]$$

$$\sin\phi = \frac{-\omega\tau}{\sqrt{1+(\omega\tau)^2}}$$

$$\cos\phi = \frac{1}{\sqrt{1+(\omega\tau)^2}}$$

$$\bullet \frac{V_s}{V_c} = \frac{1 + (\omega\tau)^2}{\sqrt{1+(\omega\tau)^2}} = \sqrt{1+(\omega\tau)^2}$$

$$\bullet V_c/V_s = \frac{1}{\sqrt{1+(\omega\tau)^2}}$$



$$\frac{V_s}{V_c} = \frac{-\omega\tau(-\omega\tau)}{\sqrt{1+(\omega\tau)^2}}$$

$$+ \frac{1}{\sqrt{1+(\omega\tau)^2}}$$

# Graphical Result for Amplitude Ratio.

$$\frac{V_2}{V_3} = \frac{1}{\sqrt{1 + (\omega\tau)^2}}$$

LOW PASS

FILTER.

$$\frac{1}{\sqrt{1 + (\frac{1}{\tau}) \cdot \tau}} = \frac{1}{\sqrt{1 + 1}} = \frac{1}{\sqrt{2}}$$



$\omega \rightarrow -\infty$   
 $0 \text{ rad/s}$

$f$  (rad/s)

$\omega$  (rad/s)

(LOG SCALE)

$$\tau = 1/\mu\text{s}$$

$$1/\tau = 1 \text{ Mrad/s}$$

University of California at Berkeley

Dept. of EECS



$$v_c(t) = V_c \cos(\omega t + \phi)$$

↑


$$V_s \left( \frac{1}{\sqrt{1 + (\omega\tau)^2}} \right)$$

↑

$$\tan^{-1}(-\omega\tau)$$

$$\phi = \tan^{-1}(-\omega\tau)$$

# Graphical Result for Phase $\phi$

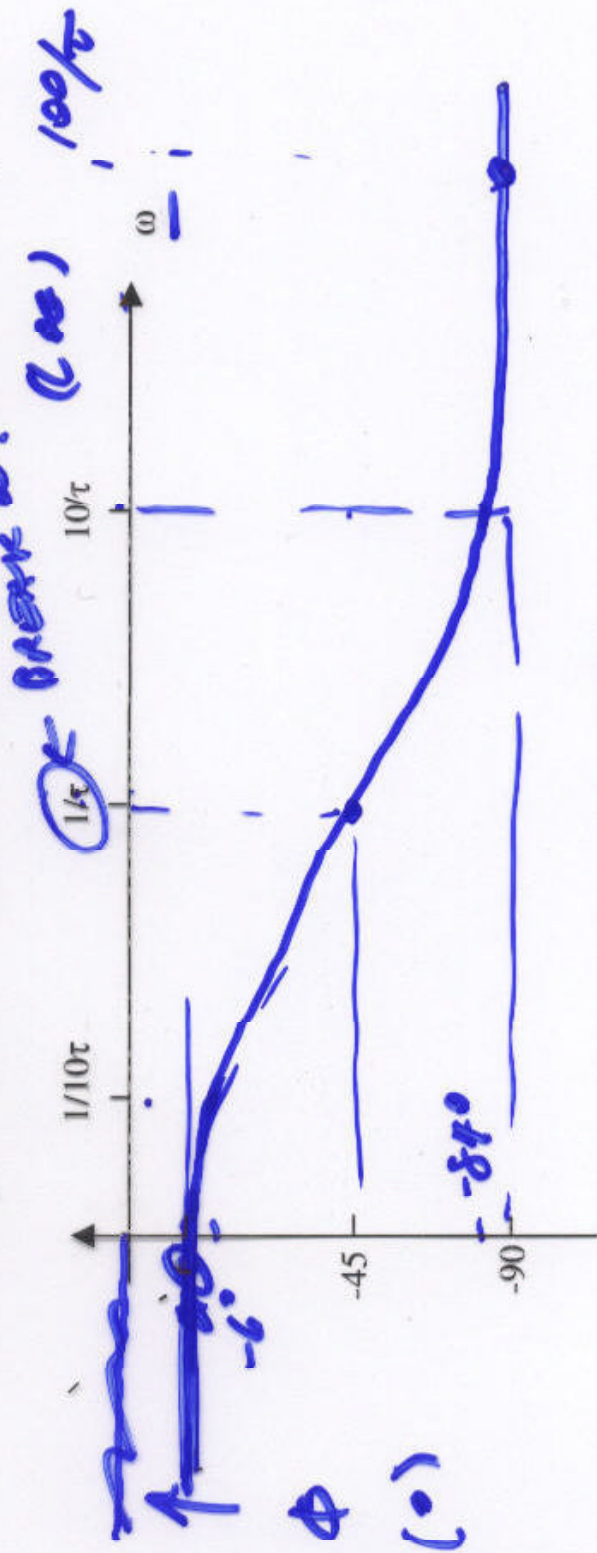

$$\phi = \tan^{-1}(\frac{1}{10}) \approx 0^\circ$$

$$\tan^{-1}(-1) = -45^\circ$$

$$\tan^{-1}(-\infty) = -90^\circ$$



# Amplitude: a new representation

- We are interested in *very* small ratios (e.g.,  $V_c/V_s = 0.0001$ )
- Therefore, we use a log plot ... but we also define a new function called the decibel (after Alex. Graham Bell)

$$(V_c/V_s)_{\text{dB}} = 20 \log_{10} (V_c/V_s)$$

*10<sup>-4</sup>*

$$\log x^2 = 2 \log x$$

- Examples:  $V_c/V_s = 0.0001 \rightarrow (V_c/V_s)_{\text{dB}} = -80 \text{ dB}$

$$V_c/V_s = 0.707 \rightarrow (V_c/V_s)_{\text{dB}} = -3 \text{ dB}$$

$$\omega = \frac{1}{\tau}$$

$$\omega \tau = 1$$

## A Better Technique.

- It is much more efficient to work with imaginary exponentials as “representing” sinusoids, since these functions are direct solutions of linear differential equations:

$$\frac{d}{dt}(e^{j\omega t}) = j\omega(e^{j\omega t})$$

- Note that EEs use  $j = (-1)^{1/2}$  rather than  $i$ , since the symbol  $i$  is already taken for current

# Using Imaginary Exponentials

From the example in Lecture 1:

$$\tau \quad RC \frac{dv_c}{dt} + v_c = v_s$$

Substitute:  $\left\{ \begin{array}{l} \underline{v_s(t)} = \underline{v_s} e^{j\omega t} \\ \underline{v_c(t)} = \underline{v_c} e^{j(\omega t + \phi)} \end{array} \right. \quad \text{Re} \{ \quad \}$

Result:

$$\tau(j\omega) \underline{v_c} e^{j(\omega t + \phi)} + \underline{v_c} e^{j(\omega t + \phi)} = \underline{v_s} e^{j\omega t}$$

# Finding the Amplitude Ratio

$$[\tau(j\omega)v_c e^{j\phi} + v_c e^{j\phi}] e^{j\omega t} = v_s e^{j\omega t}$$

$$[j\omega\tau e^{j\phi} + e^{j\phi}] v_c = v_s$$

Amplitude

$$\frac{v_c}{v_s} = \frac{1}{j\omega\tau e^{j\phi} + e^{j\phi}}$$

Ratio:

... use to find amplitude and phase

$$\frac{e^{-j\phi}}{(1 + j\omega\tau)}$$

- Answer is a real number, so take magnitude

$$\frac{v_c}{v_s} = \frac{1}{\sqrt{1 + (\omega\tau)^2}}$$

$$|e^{-j\phi}| = |\cos(\phi) + j\sin(-\phi)|$$

$$z = x + jy$$

$$|z| = \sqrt{x^2 + y^2}$$

## Finding the Phase

$$[j\omega\tau e^{j\phi} + e^{j\phi}] = \underline{v_s / v_c} \quad (\text{a real number})$$

Use Euler's formula to convert to rectangular form:

$$j\omega\tau(\cos\phi + j\sin\phi) + (\cos\phi + j\sin\phi) = v_s / v_c$$

Collect real and imaginary parts; latter must be zero:

$$\text{Im}(\cdot) = \omega\tau \cos\phi + \sin\phi = 0$$

$$\tan\phi = -\omega\tau$$