




- FALL 2002 MT II POSTER
- SAMPLE MIDTERM II
- INFO ON REVIEW SESSION, OH, ETC.

Lecture 30

- Last time:
 - Wrap-up of Chapter 8
- Today :
 - Frequency response of the CE and CS (?)
 - current amplifiers
 - Unity-gain frequency ω_T

} NOT
 ON
MIDTERM II

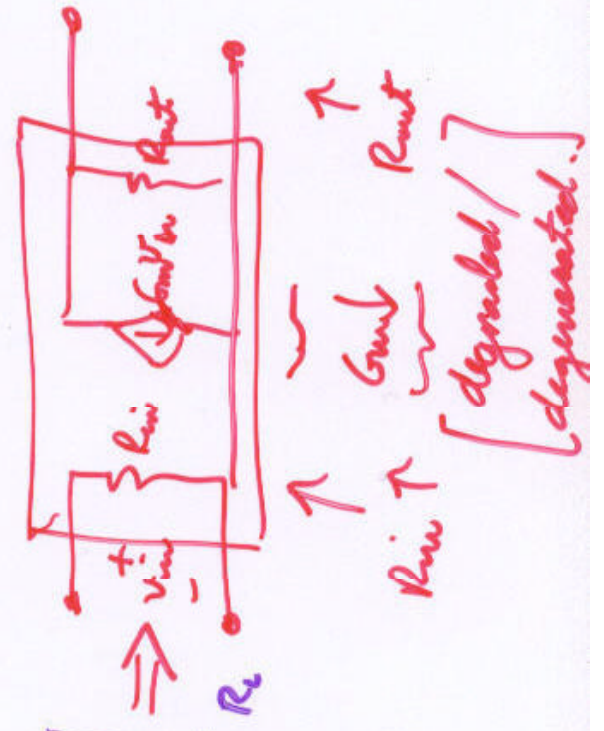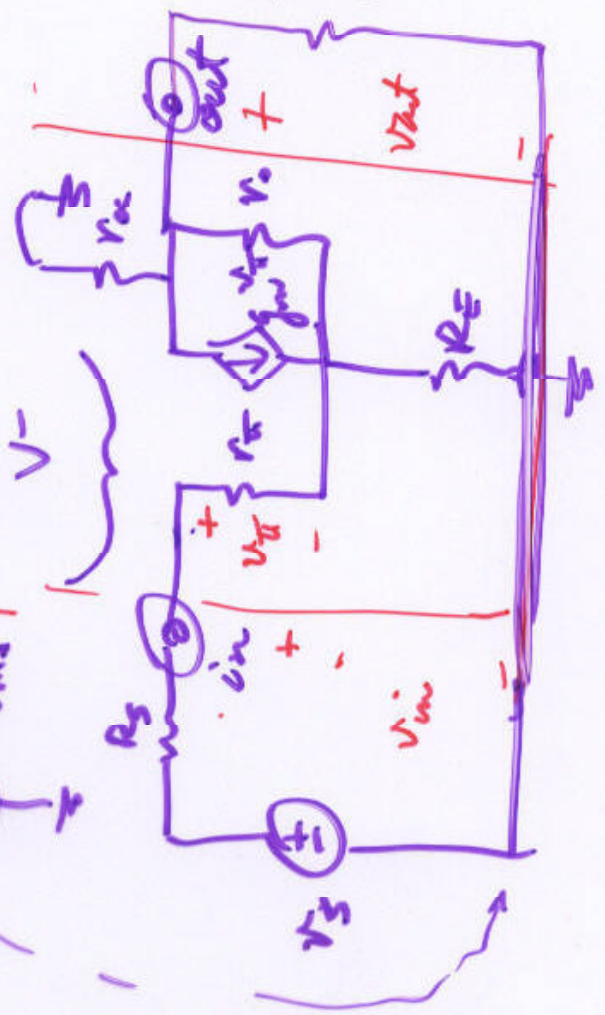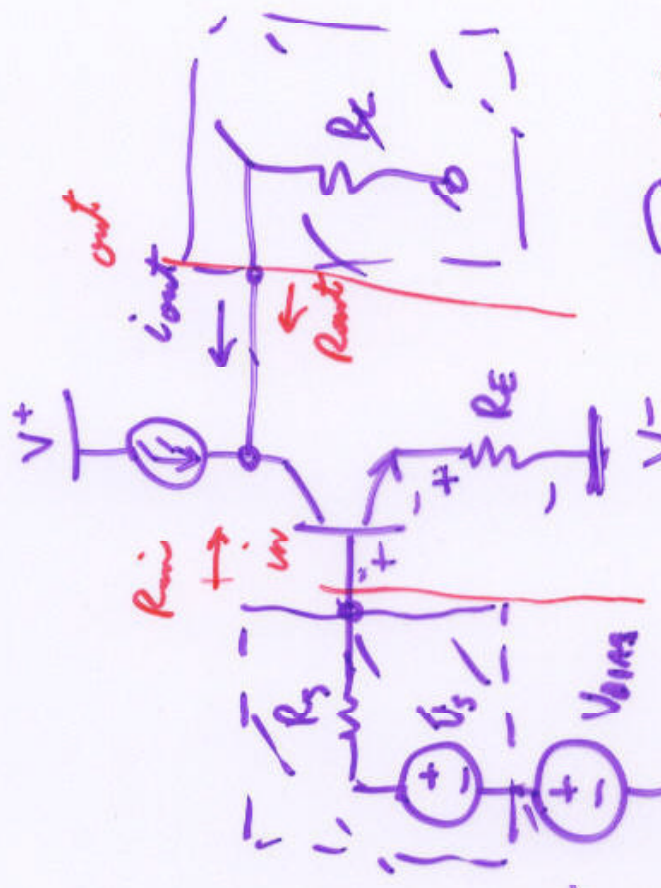$i_{out} = I_{out} + i_{out}$
 set $V_{out} = 0V$



Two-Port Model for CE_{deg} (cont.)

• Find $G_m = \frac{i_{out}}{v_E} \Big|_{R_s=0, R_e=0}$

1 + LOOP GAIN → $1 + g_m R_E$


$R_{in} \approx r_\pi (1 + g_m R_E)$; $R_{out} = r_{o2} \parallel V_o (1 + g_m R_E)$

• Voltage Gain:

LOADED/OVERALL
 R_s, R_e ATTACHED

UNLOADED/OPEN CKT.
 $R_s=0, R_e=\infty$

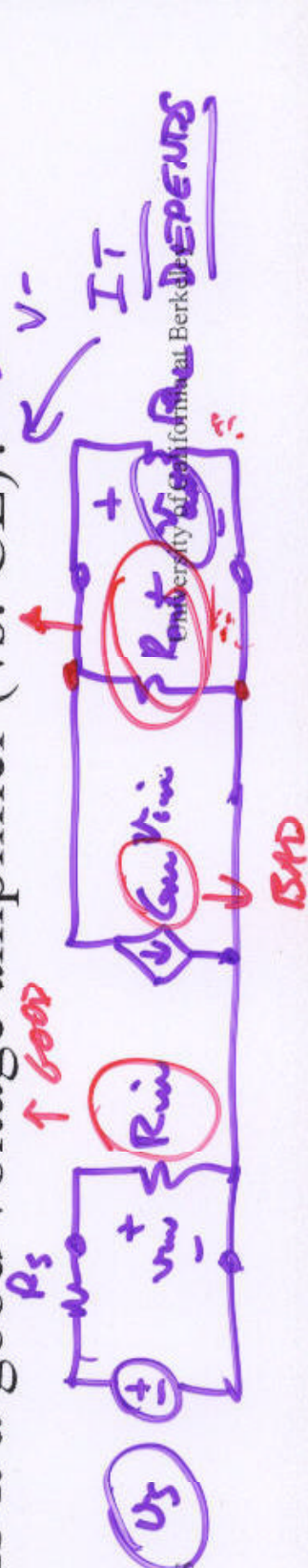• Is it a good voltage amplifier (vs. CE)?



$G_m = \frac{g_m}{1 + g_m R_E} \approx \frac{1}{R_E}$

GET A STABLE R_E


WHY CEleg?

Output "Swing"

$$G_{mCE} = g_m = \frac{I_C}{V_{th}}$$


$$g_m = \frac{\beta I_C}{kT}$$

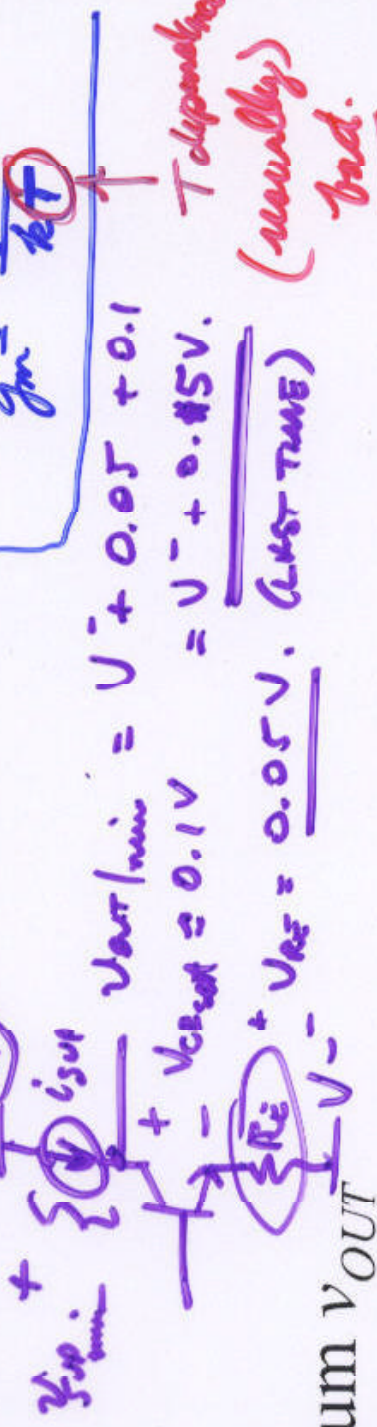• Maximum $v_{OUT} = v_{OUT} + v_{out} = v_{out}$



T dependence
 (usually)
bad.

• Minimum v_{OUT}

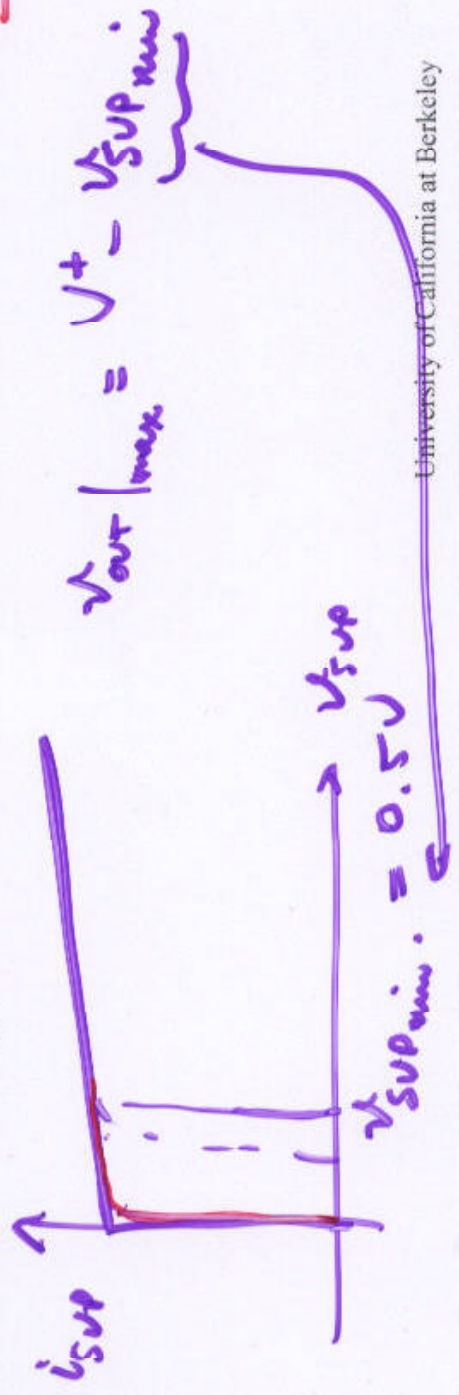

CHAPTER 10

CE Amplifier with Current Input

→ REVIEW OF PASTORS...

USE THEM

START:

① "CLASSIC EXAMPLES"

f_T ... TRANSITION

FREQUENCIES.

o ARTIFICIAL ...


SIMPLE.

② LOOK AT

CS, CD, CG, CE...

CHAPTERS

University of California at Berkeley

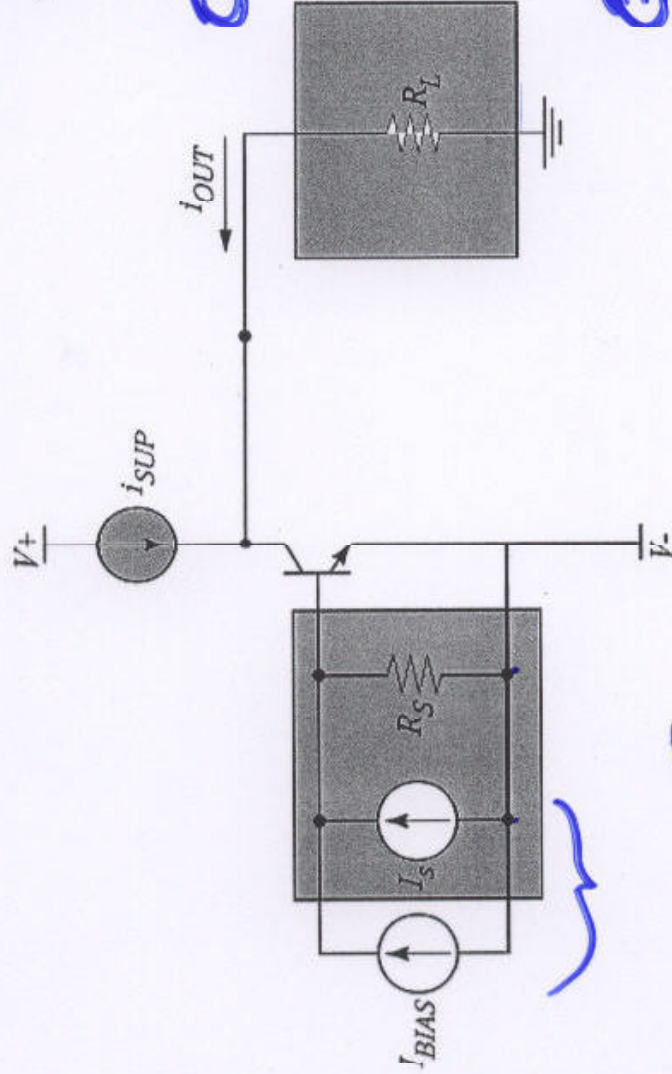


$$I_{BIAS} = \frac{I_C}{\beta F}$$

$$A_i(j\omega) = \frac{I_{out}}{I_s} \Big|_{R_s \rightarrow 0, R_L \rightarrow \infty}$$

phasors

Short-Circuit Current Gain


OUTPUT.

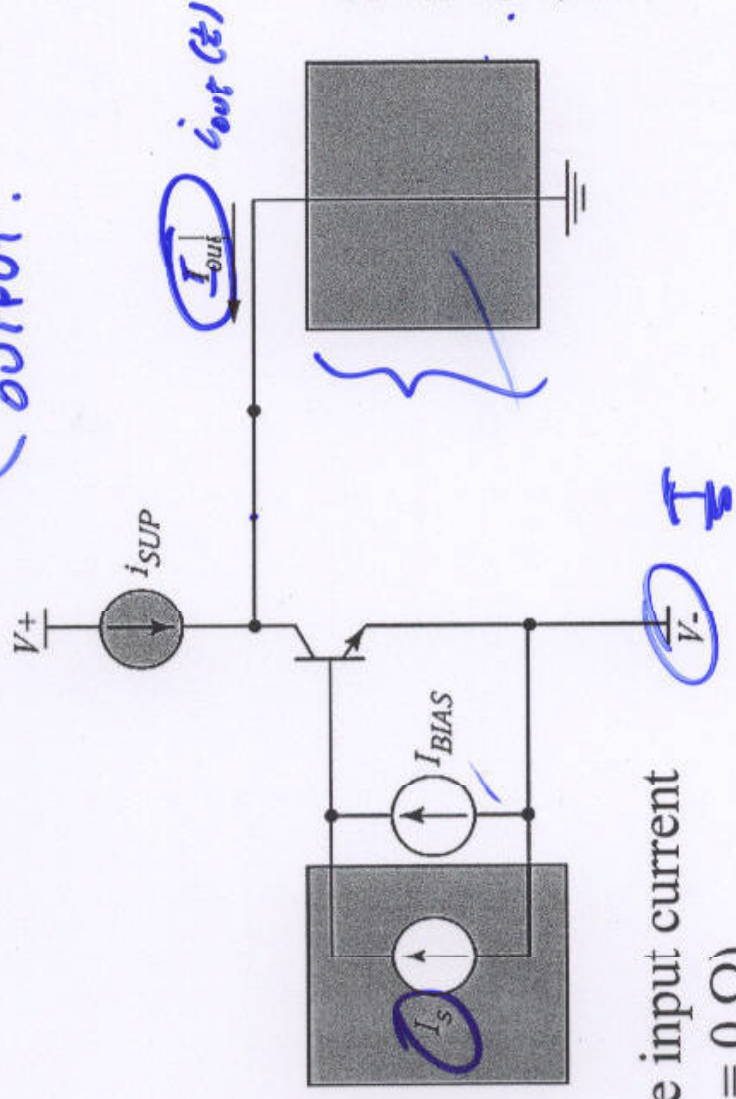

Pure input current
($R_s = 0 \Omega$)

Small-signal short circuit
(could be a DC voltage source)

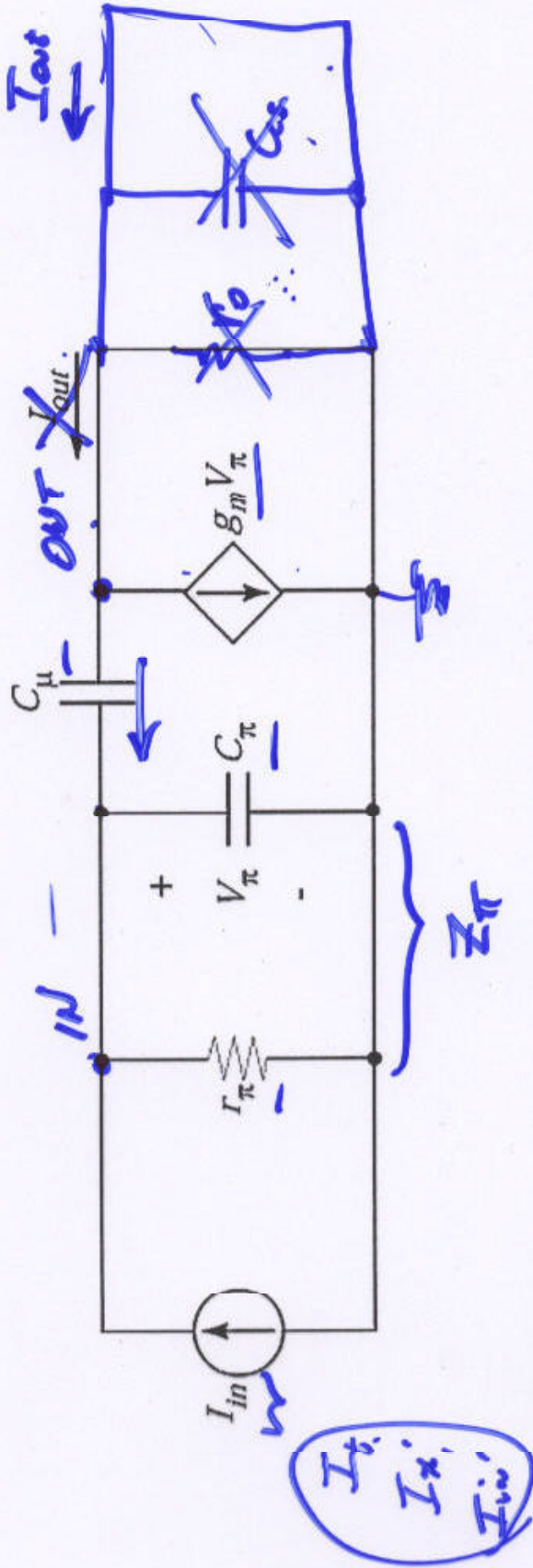Small-Signal Model: $A_i = \frac{I_{out}}{I_{in}}$



Note that r_o, C_{cs} play no role (shorted out)

**COMPLICATE ANALYSIS
NOT 'FUNDAMENTAL!'**

Phasor Analysis: Find A_i

- KCL at the output node: out

$$I_{out} = g_m V_{\pi} + \underbrace{(0 - V_{out}) / Z_{\mu}}_{out}$$


- KCL at the input node: in

$$I_{in} = V_{\pi} / Z_{\pi} + \underbrace{(V_{\pi} - 0) / Z_{\mu}}_{V_{out}}$$

- Solve for V_{π} :

$$I_{in} = V_{\pi} \left(\frac{1}{Z_{\pi}} + \frac{1}{Z_{\mu}} \right)$$
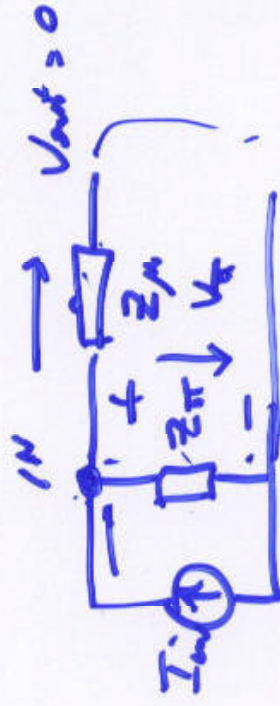
$$V_{\pi} = \frac{I_{in}}{\frac{1}{Z_{\pi}} + \frac{1}{Z_{\mu}}}$$



Phasor Analysis for A_i (cont.)

$$I_{out} = (g_m - j\omega C_\mu) V_\pi = \frac{g_m - j\omega C_\mu}{(1/2r_\pi) + j\omega C_\mu} I_{in}$$

Substituting for V_π

$$A_i(j\omega) = \frac{(g_m - j\omega C_\mu)}{(1/Z_\pi) + j\omega C_\mu}$$

$$= \frac{g_m [1 - j\omega \frac{C_\mu}{g_m}]}{r_\pi \left(\frac{1}{g_m C_\pi} + j\omega C_\mu \right) + \frac{1}{g_m C_\pi}}$$

Substituting for $Z_\pi = r_\pi \parallel (1/j\omega C_\pi)$

$$= \frac{r_\pi}{r_\pi + \frac{1}{g_m C_\pi}}$$

Short-Circuit Current Gain Transfer Function

Transfer function has one pole and one zero:


$$A_i(j\omega) = \beta_o (1 - j\omega [C_\mu / g_m]) / (1 + j\omega [r_\pi (C_\pi + C_\mu)])$$

$$\omega_z = \frac{g_m}{C_\mu}$$

$$A_i(j\omega) = \frac{\beta_o (1 - j\omega / \omega_z)}{(1 + j\omega / \omega_p)}$$


$$|A_i(j\omega)| = \beta_o$$

$\omega \rightarrow 0$

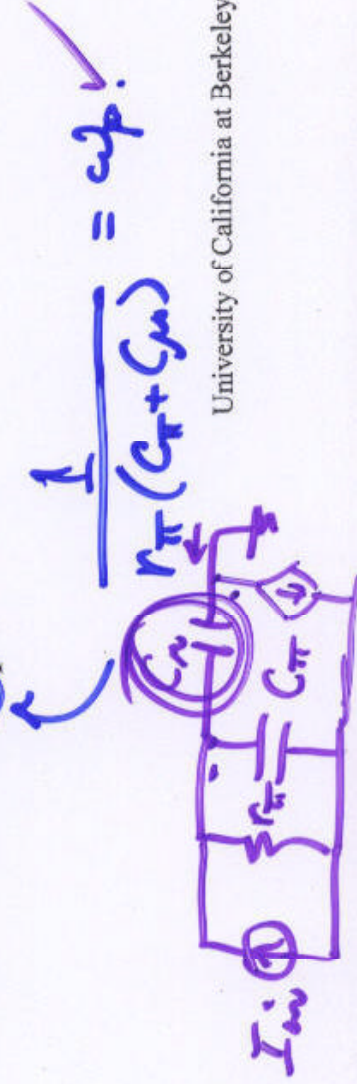

$$\frac{1}{r_\pi (C_\pi + C_\mu)} = \omega_p!$$

Magnitude Bode Plot

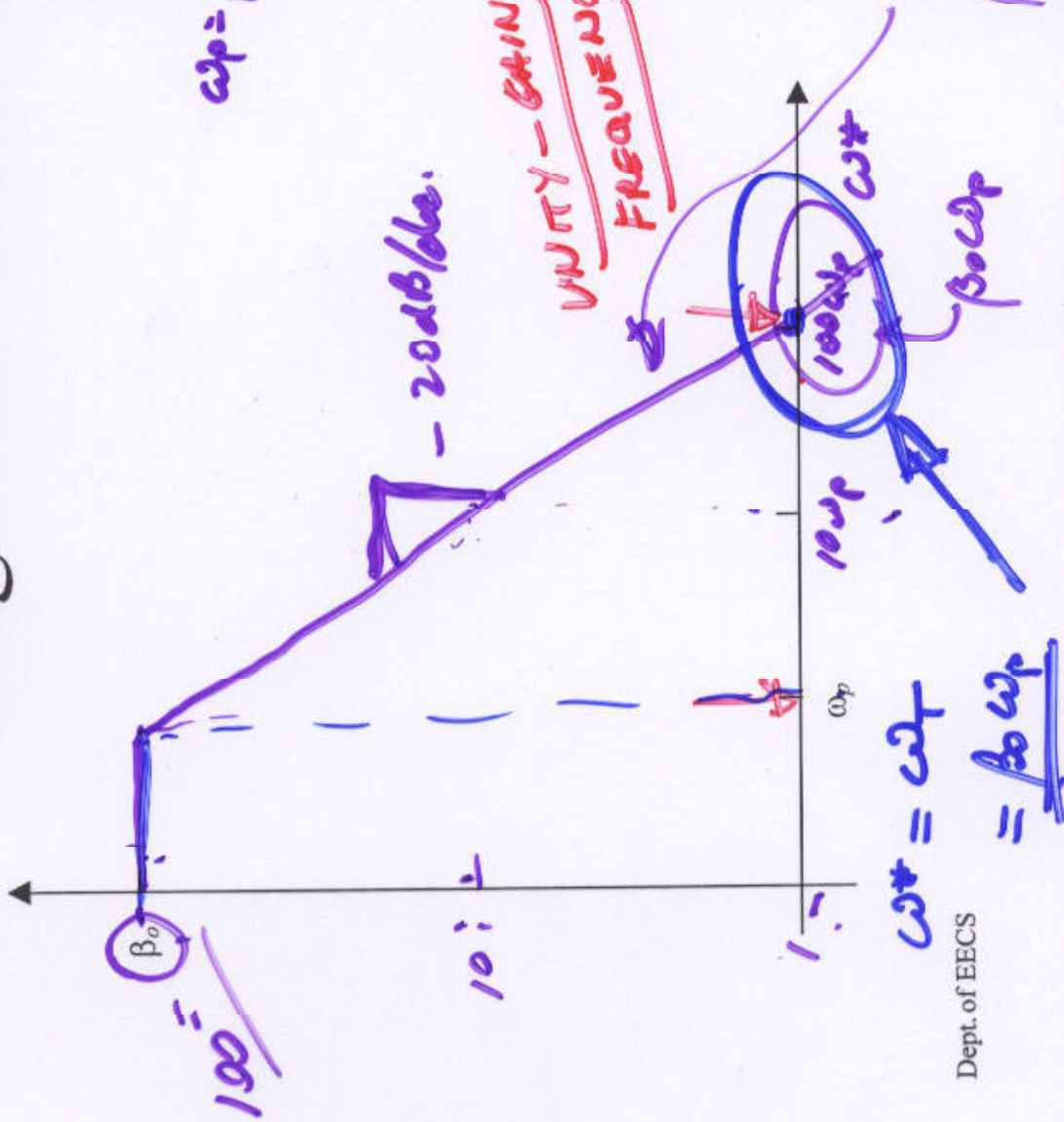

$\omega_p \ll \omega_z$

$$\omega_p = \frac{1}{R_T(C_T + C_M)} = \frac{1}{(\beta_0/g_m)(C_T + C_M)}$$

$$\omega_p = \frac{g_m}{\beta_0(C_T + C_M)}$$

$$\omega_z = \frac{g_m}{C_M}$$

$$A_i(j\omega) = \frac{\beta_0}{1 + j\omega/\omega_p}$$

$$|A_i(j\omega)| \approx \beta_0 \left(\frac{\omega_p}{\omega}\right)$$

$$|A_i(j\omega^*)| = 1 = \frac{\beta_0 \omega_p}{\omega^*}$$

UNITY-GAIN
FREQUENCY

-20dB/dec.

$$\omega^* = \omega_z = \beta_0 \omega_p$$

Dept. of EECS

University of California at Berkeley