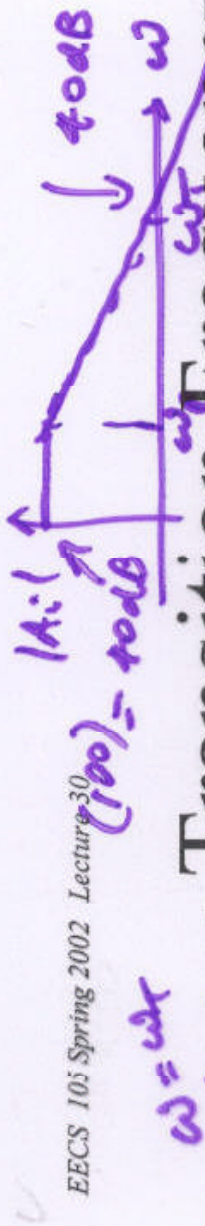


ALL SPECIALLY CASES.

Lecture 31

- Last time: CHAPTER 10 $A_i(j\omega)$
 - Short-circuit current gain of CE and CS amps
 - Unity-gain frequency ω_T ↑ TODAY / $A_i(j\omega)$
- Today :
 - Frequency response of the CE as voltage amp
 - The Miller approximation

FAIRBY'S } CD ✓
LECTURE } CG ✓



Transition Frequency ω_T

$$\omega_T = \frac{g_m}{C_\pi + C_\mu}$$

$$g_m = \frac{I_c}{V_{tn}} \quad \#7$$

$$C_\pi = C_{jE} + g_m \tau_F \quad \#7$$

Dependence on DC collector current:

$$\omega_T = \frac{I_c / V_{tn}}{C_{jE} + (I_c / V_{tn}) \tau_F + C_\mu} = \frac{1}{\frac{C_{jE}}{I_c} + \tau_F + \frac{V_{tn}}{I_c} \cdot C_\mu}$$

Small $\frac{C_{jE}}{I_c}$ $\frac{V_{tn}}{I_c} \cdot C_\mu$ *Small*


$\omega_T \uparrow \dots$ LET'S INCREASE I_c

$\omega_T \rightarrow \frac{1}{\tau_F} \quad (I_c \rightarrow \infty)$


Current record:

Limiting case: $f_T = \frac{\omega_T}{2\pi} \rightarrow \frac{1}{2\pi \tau_F}$

Common Source Amplifier: $A_i(j\omega)$


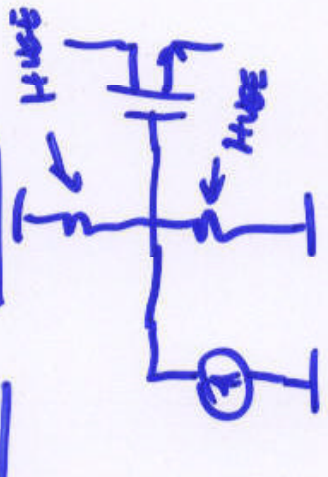


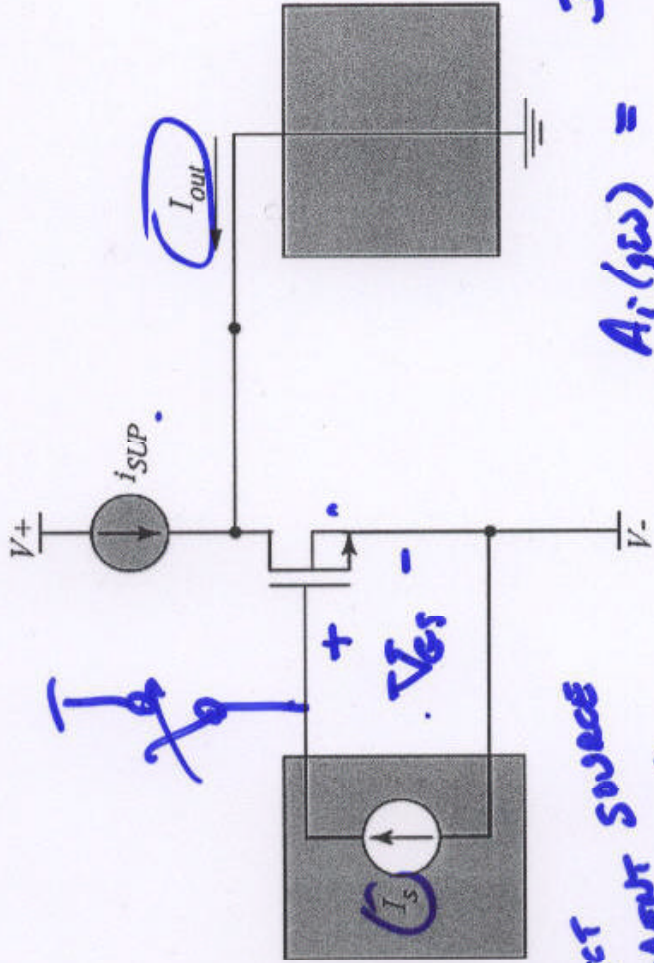← SHORT-CIRCUIT
($R_L \rightarrow 0$)
THE LOAD.




PERFECT CURRENT SOURCE ($R_S \rightarrow \infty$)
 $A_i(j\omega) = I_{out} / I_S$

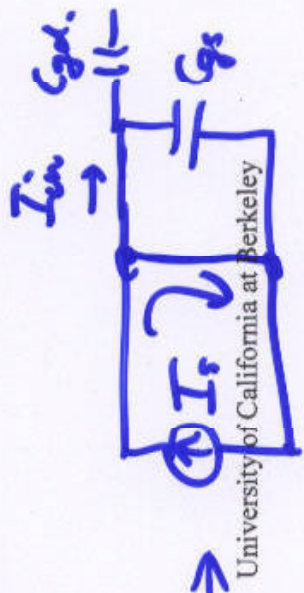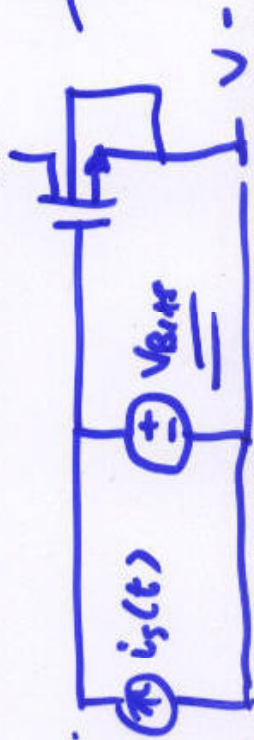DC Bias is problematic: what sets V_{GS} ?



CS Short-Circuit Current Gain

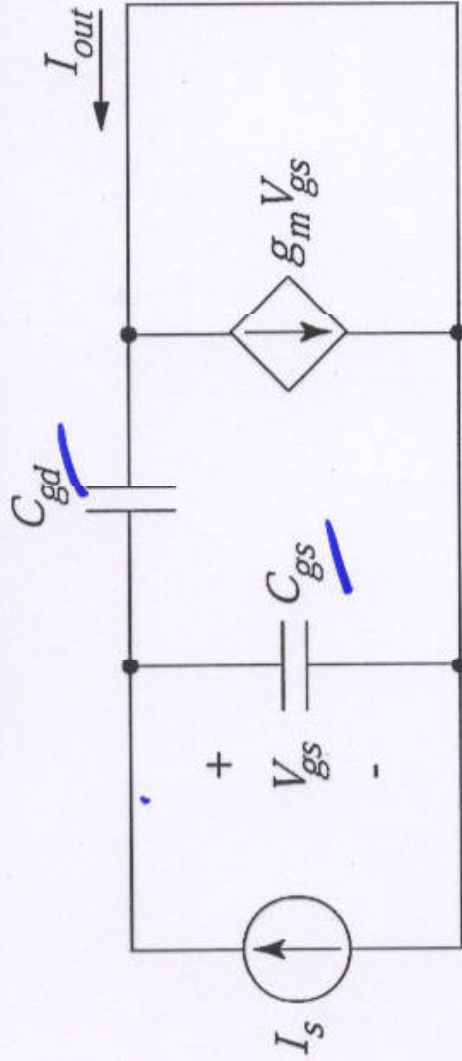

ZERO

$$A_i(j\omega) = \frac{g_m (1 - j\omega C_{gd} / g_m)}{j\omega (C_{gs} + C_{gd})}$$

(SEE CHAPTER 10)


$$\frac{g_m}{j\omega (C_{gs} + C_{gd})} \frac{1}{\omega_T}$$

$\omega_z = \frac{g_m}{C_{gd}}$ (MUCH HIGHER THAN ω_T)

$\omega_T = \text{UNITY-GAIN FREQUENCY (RAD/S)}$

$$|A_i(j\omega_T)| = 1 \approx \left| \frac{g_m}{j\omega_T (C_{gs} + C_{gd})} \right|$$
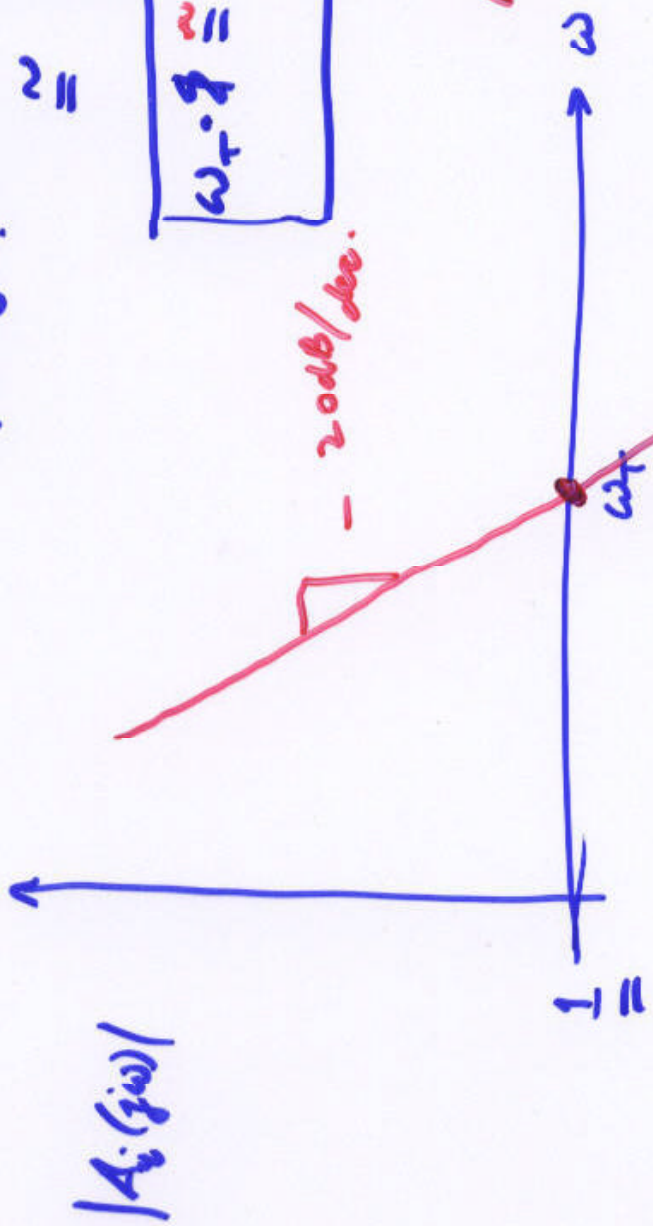
$$\omega_T \cdot f \approx \frac{g_m}{C_{gs} + C_{gd}}$$



$$\frac{g_m}{C_{gs} + C_{gd}}$$

$$\omega_f = \frac{g_m}{C_{gd}}$$

$$\omega_T \approx \frac{g_m}{C_{gs} + C_{gd}}$$

$$C_{gs} = \frac{2}{3} C_{ox} W \cdot L + C_{ov}$$

$$C_{gd} = C_{ov} \ll C_{gs}$$

• ASK ABOUT HOW/WHAT TO DO TO CONTROL/DESIGN MOSFET FOR $\omega_T \uparrow \uparrow$.

$$\omega_T = \frac{g_m}{C_{gs} + C_{gd}}$$


$$\frac{1}{\omega_T} = \tau_T = \frac{C_{gs} + C_{gd}}{g_m} \approx \left(\frac{C_{gs}}{g_m} \right) \quad C_{gd} \ll C_{gs}$$

$$C_{gs} \approx \frac{2}{3} C_{ox} W \cdot L \quad (C_{ov} \rightarrow 0)$$

$$g_m = \frac{\partial I_D}{\partial V_{gs}} \Big|_Q \approx \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{gs} - V_{tn})$$

THINK

BASICS!

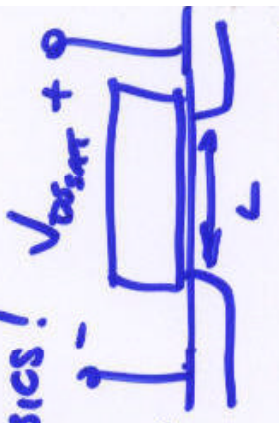


$$\tau_T = \frac{\frac{2}{3} C_{ox} W \cdot L}{\mu_n C_{ox} \left(\frac{W}{L} \right) (V_{gs} - V_{tn})} = \frac{L}{\left(\frac{3}{2} \right) \mu_n \left[\frac{V_{gs} - V_{tn}}{L} \right]} \approx \frac{L}{v_{dr.}}$$

$\frac{\text{DISTANCE}}{\text{VELOCITY}}$

$$V_{gs} - V_{tn} = V_{DSAT}$$

SPECIAL CASE


• Common-Emitter Voltage Amplifier

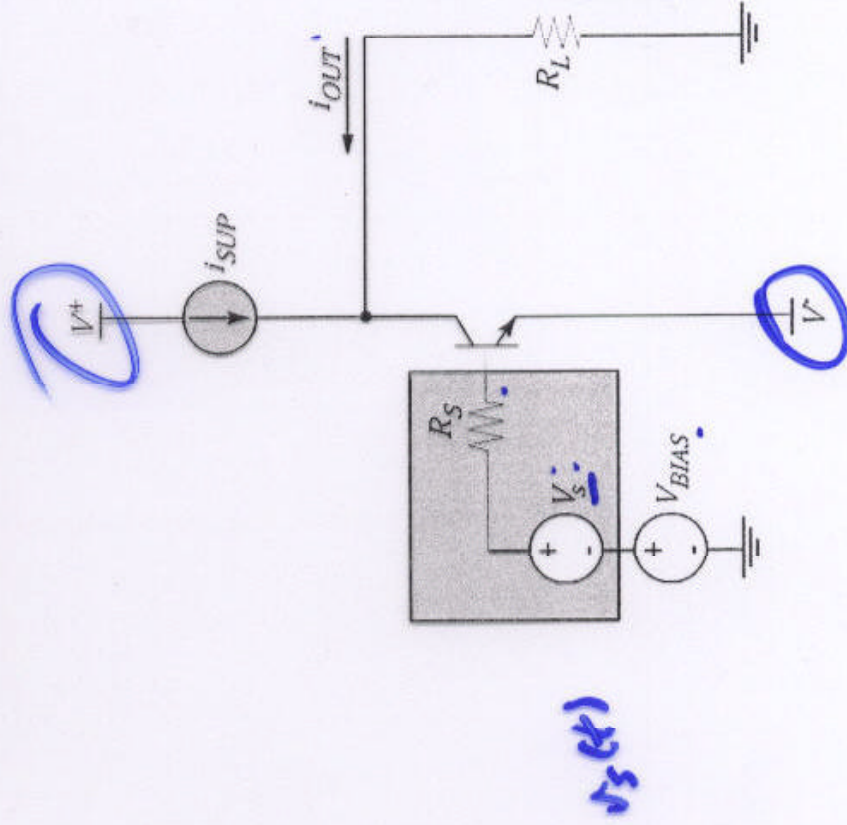


Small-signal model:
omit C_{cs} due to avoid
complicated analysis

CE Voltage Amp Small-Signal Model

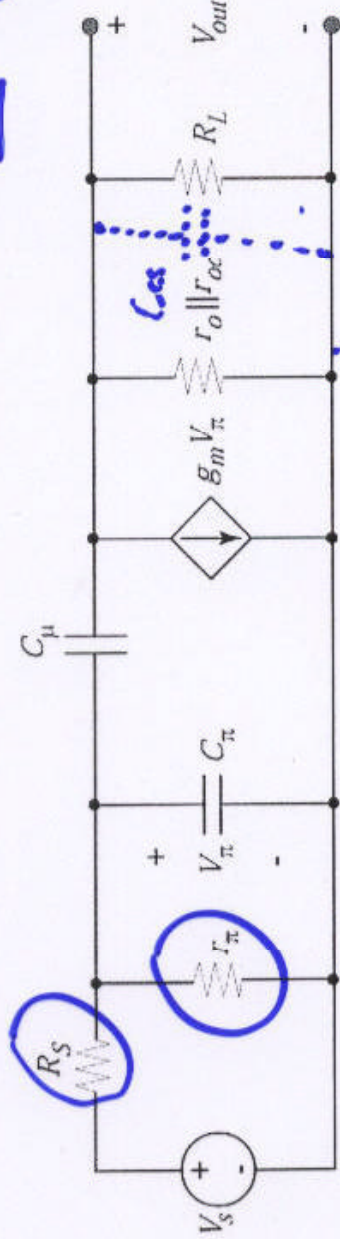Ces: BETWEEN COLLECTOR & SUBSTRATE... CAN'T HANDLE THE MESSY ANALYSIS.



PROBLEM

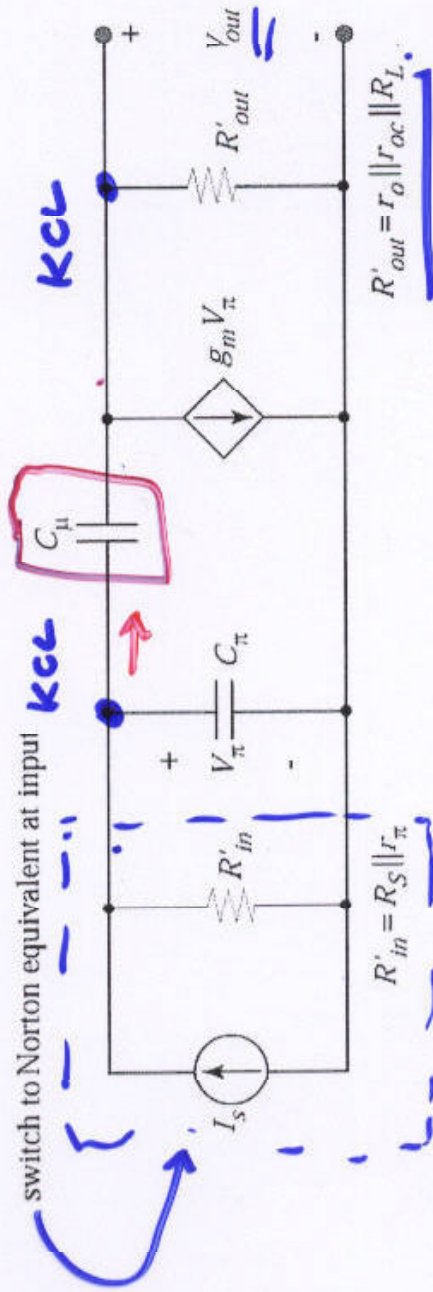

CHAPTER 8.

PRO ← low ω

Frequency Response

KCL at input and output nodes; analysis is made complicated due to Z_μ branch → see H&S pp. 639-640.

PLOTTING

$$\frac{V_{out}}{V_{in}} = \frac{-g_m \left(\frac{r_\pi}{r_\pi + R_S} \right) [r_o \parallel r_{oc} \parallel R_L] \cancel{[1 - j\omega / \omega_z]}}{(1 + j\omega / \omega_{p1}) (1 + j\omega / \omega_{p2})}$$

ω_z small

← 2 POLES ←

2 ENERGY STORAGE ELEMENTS

Low-frequency gain:

MAX. ω FOR $\omega_z > \omega_T = \frac{g_m}{C_\pi + C_\mu}$ OUR MODELS.

REALLY HIGH

Poles

NOT EXACT \approx

$$\omega_{p1} \neq \frac{1}{(R_S \parallel r_\pi) \{ C_\pi + (1 + g_m R'_{out}) C_\mu \} + R'_{out} C_\mu} \approx$$

$$\omega_{p2} \neq \frac{R'_{out} / (R_S \parallel r_\pi)}{(R_S \parallel r_\pi) \{ C_\pi + (1 + g_m R'_{out}) C_\mu \} + R'_{out} C_\mu} \approx$$

$$\frac{R'_{out}}{R_S \parallel r_\pi} = \frac{f_o \parallel r_{oc} \parallel R_c}{R_S \parallel r_\pi} \gg 1$$

R_S small v_s

BETTER WAY.


Decoupling Input and Output: the Miller Approximation

Results of complete analysis: not exact and little insight *if any*

Look at how Z_{μ} affects the transfer function: find Z_{in}

$$|k\Omega = \frac{1}{\omega \cdot C_{\mu}} \leftarrow \omega \approx \text{Grads}$$
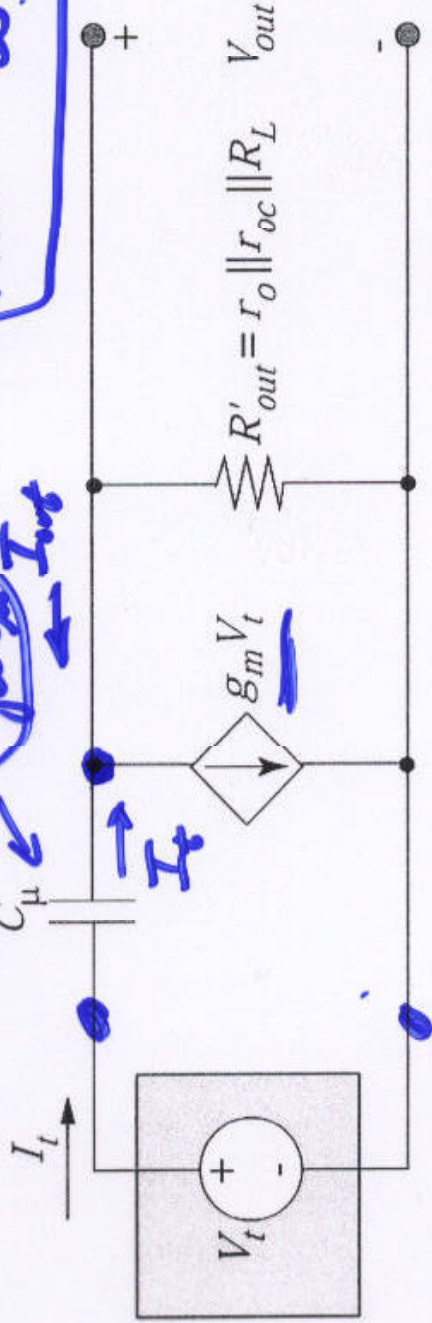
$$\frac{1}{g_m C_{\mu}} \leftarrow \text{Grads}$$



OMITTED
IN 105...

from Z_{eff} input ...
Dept. of EECS

$$\frac{V_t}{I_t} \equiv Z_{eff}$$



Input Impedance $Z_{in}(j\omega)$

$$I_t = (V_t - V_{out}) / Z_\mu$$



At output node:

Int: Rout' 0

$$V_{out} = (-g_m V_t - I_t) R'_{out} \approx -g_m V_t R'_{out}$$

neglect

$I_t \dots$ Why?

$$I_t = (V_t - A_{vC\mu} V_t) / Z_\mu$$

$$\approx 1 \text{ mS}$$

$$\frac{1}{g_m} = 1 \text{ k}\Omega$$

Answer

$$Z_{in} = V_t / I_t = \frac{Z_\mu}{1 - A_{vC\mu}}$$

$$A_{vC\mu} = \text{voltage gain across } C_\mu = -g_m R_{out}$$