

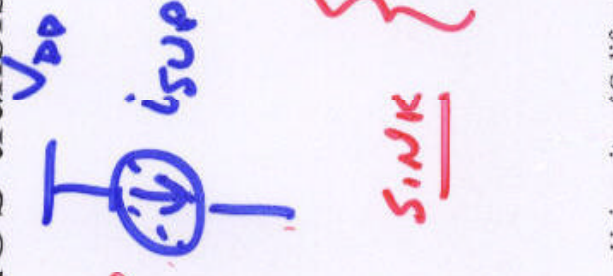
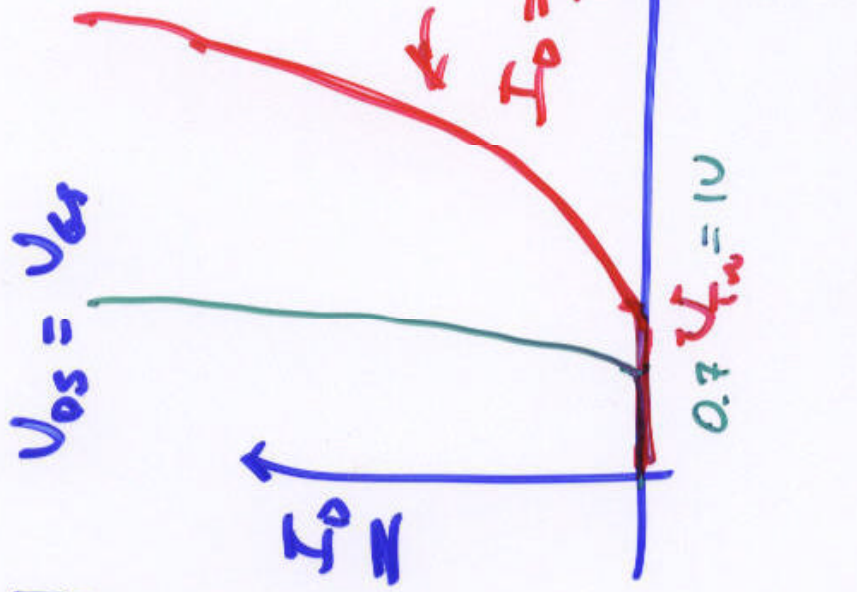

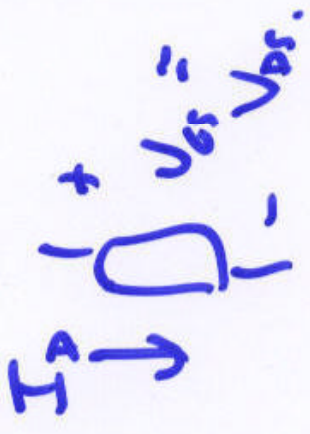
# Lecture 33

- Last time:
  - ✓ - Frequency response of voltage and current buffers
  - Voltage/Current sources using MOS transistors
- Today: FUN/EASY
  - Improved current sources
  - Current mirrors



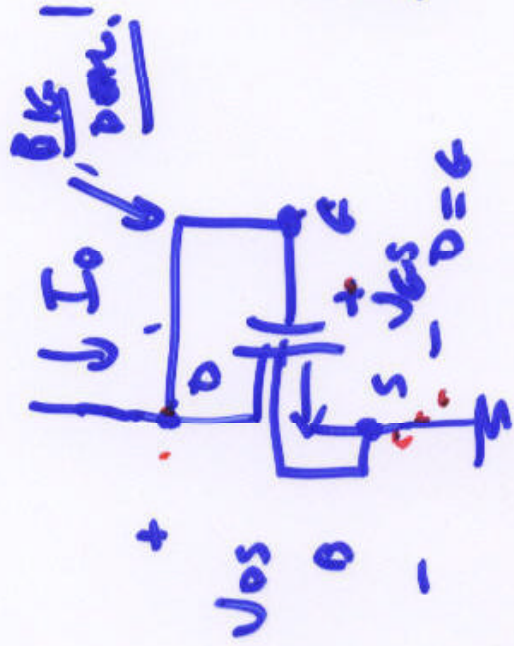


$V_{GS} = V_{DS} < V_T$

→ OFF

$I_D = 0$

$V_{DS} \geq V_{GS} - V_{TN}$


→ SATURATED

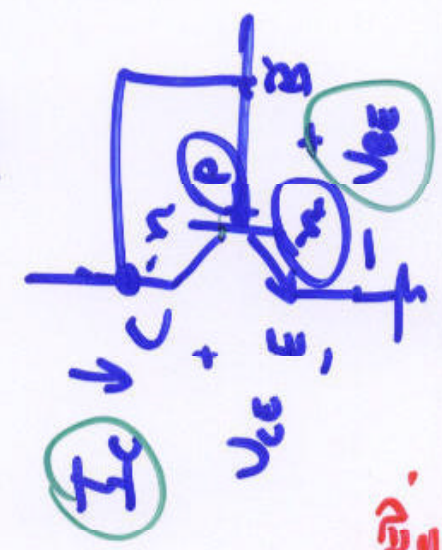
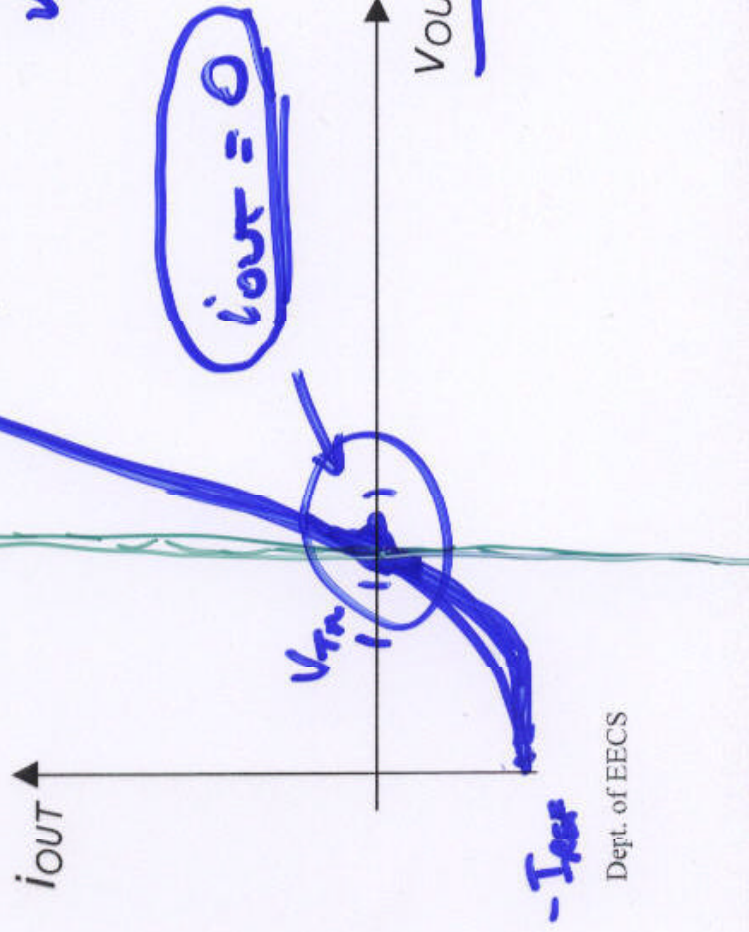
# Modeling the Voltage Source

- Find  $i_{OUT}$  versus  $v_{OUT}$  MOSFET is off or saturated: why?

$$i_{OUT} = i_{D,SAT} - I_{REF} = \mu_n C_{ox} \left( \frac{W}{2L} \right) (v_{GS} - V_{Th})^2 (1 + \lambda_n v_{DS}) - I_{REF}$$



Typical operating point:

$$i_{OUT} = 0 \text{ A}$$

University of California at Berkeley


# Small-Signal Source Resistance

$$R_S = \left( \frac{di_{OUT}}{dv_{OUT}} \Big|_{I_{OUT}=0} \right)^{-1} = \frac{v_t}{i_t}$$



$$i_t = g_m v_{gs} + \frac{v_t}{r_o}$$

$$i_t = v_t \left[ g_m + \frac{1}{r_o} \right]$$

$$\frac{v_t}{i_t} = \frac{1}{g_m}$$

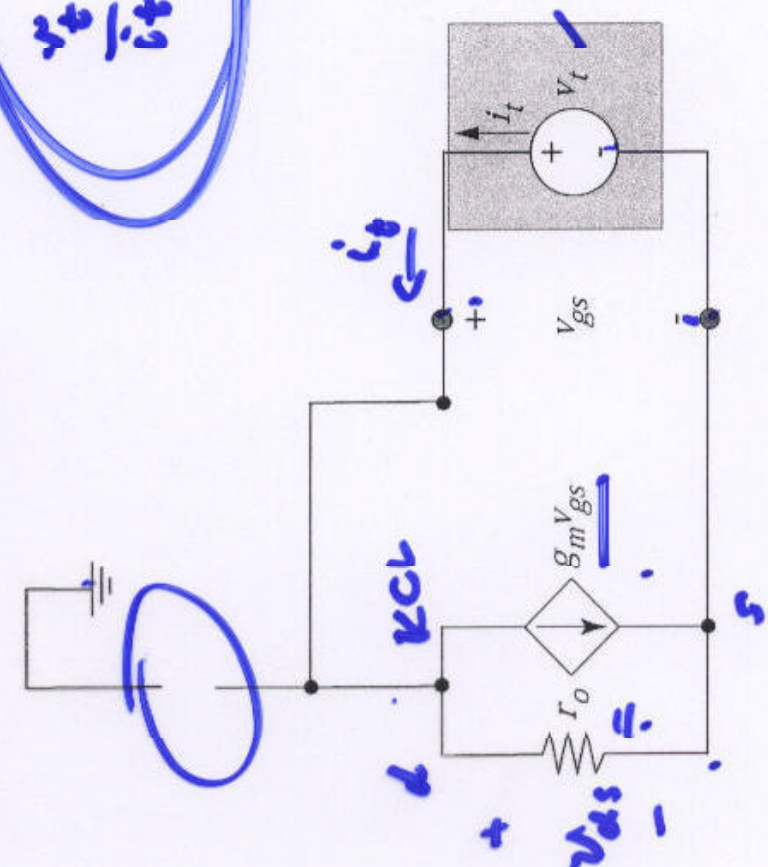

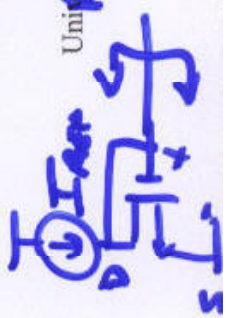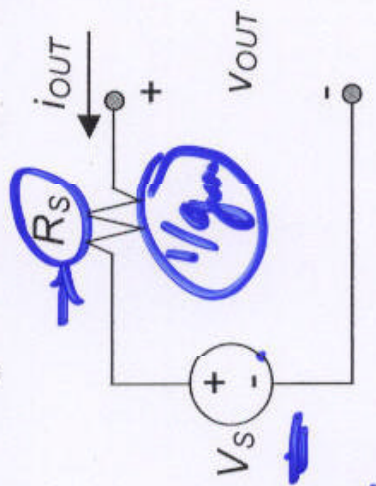
Equivalent Circuit: ( $A_T$   $i_{OUT} = 0$ )



FOR LABS...


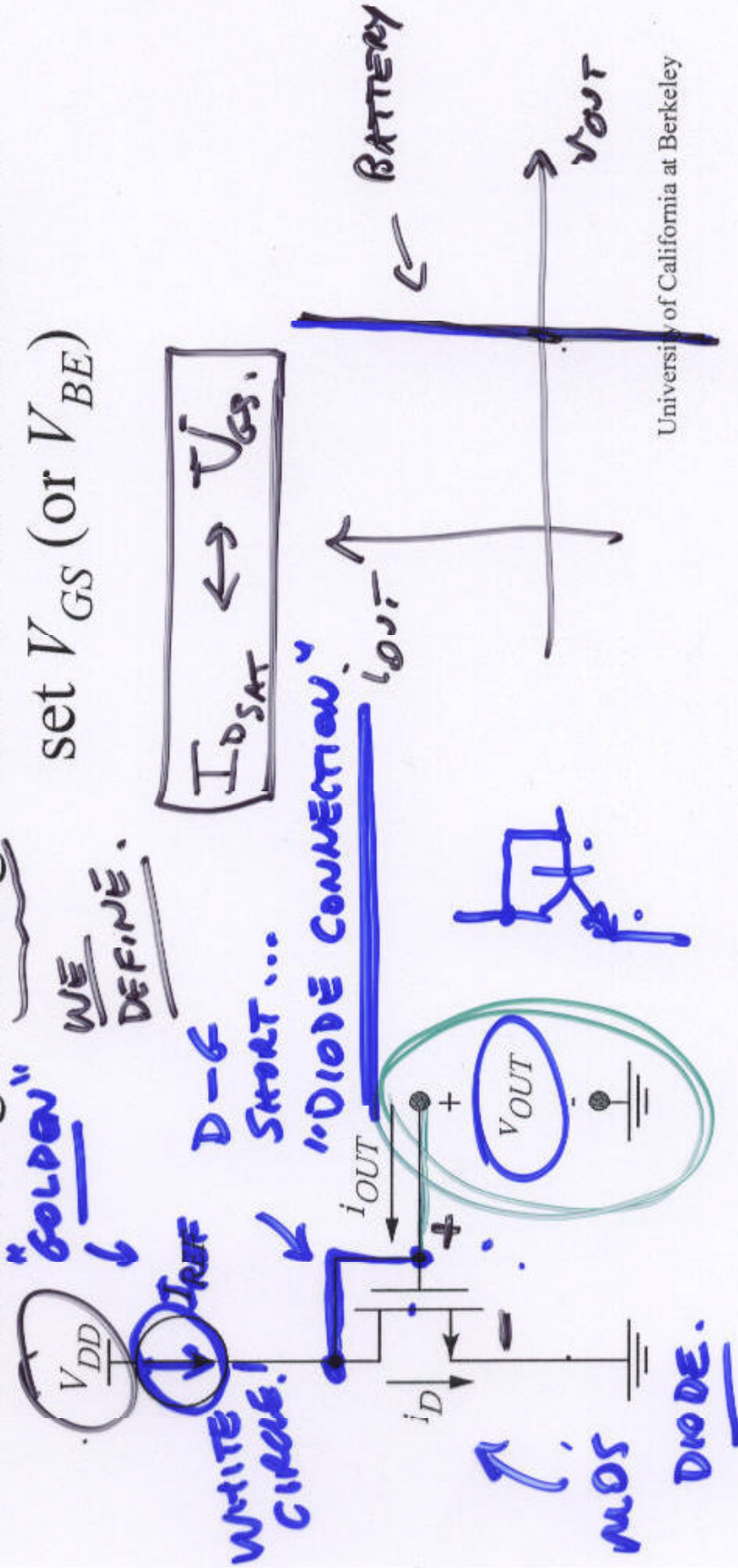
# Multi-Stage Amplifiers: Chap. 9

- First topic: voltage and current sources (9.4)
- Generating a voltage: use a current source to



$$V_{out} = V_{Tn} + \sqrt{\frac{2 I_{REF}}{(w/L) \mu_n C_{ox}}}$$

$I_D = I_{REF}$  FOR  $I_{out} = 0$ .

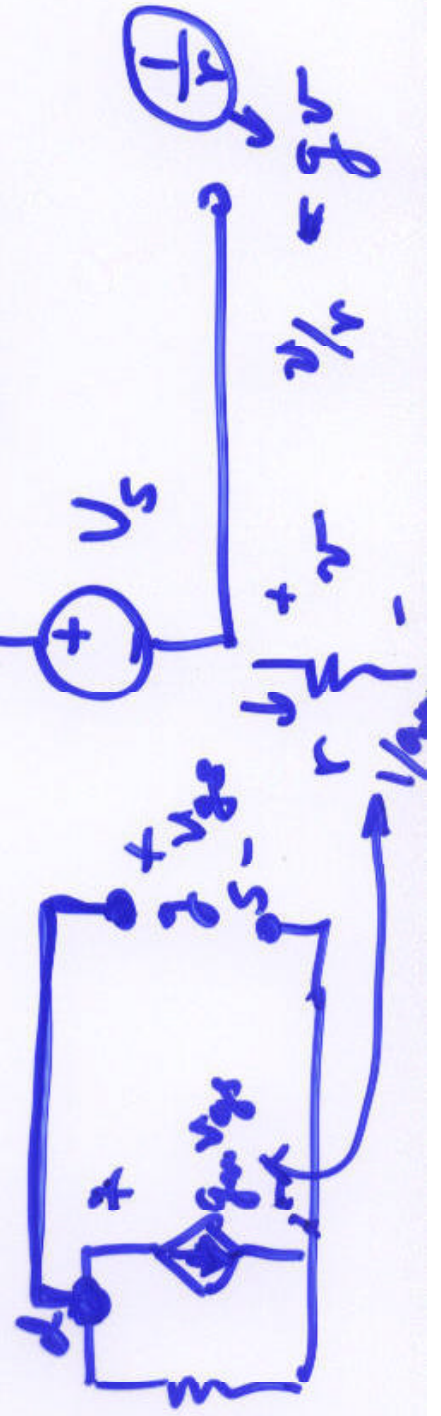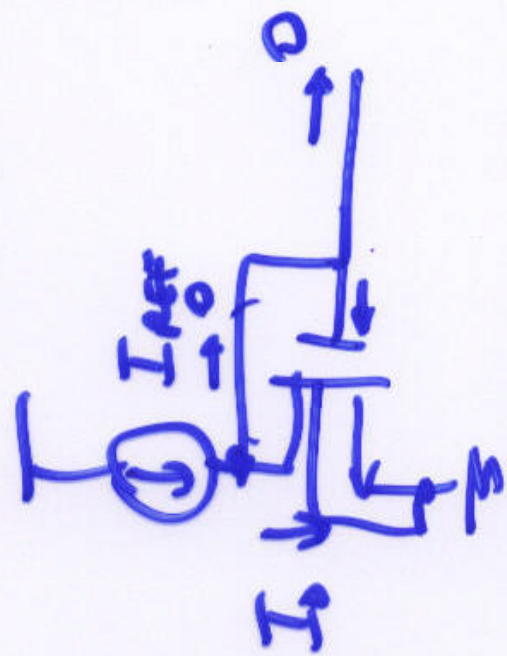

$$v/r = g_m v$$

YES!  $\mu_{n1} = \mu_{n2}$ ,  $V_{T1} = V_{T2}$ ,  $C_{ox,1} = C_{ox,2}$


# Equivalent Circuit for I-Source $C_{ox}$

Find the DC current for "gray circle" equivalent circuit

• **NEGLECT**  $(1 + \lambda_n V_{DS2})$  **HERE.**

$$I_{OUT} = \frac{\mu_n C_{ox}}{2} \left( \frac{W}{L} \right)_2 (V_{REF} - V_{Tn})^2$$

Substitute for  $V_{REF}$

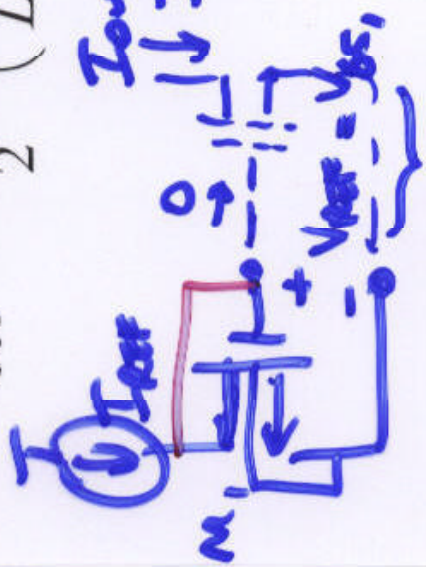

$I_{OUT} = I_{D2}$

$V_{REF} = V_{DS2}$

$I_{OUT,1} = 0$

$$V_{DS1} = V_{Tn,1} + \sqrt{\left( \frac{W}{L} \right)_2 \left\{ \frac{I_{OUT}}{\mu_n C_{ox}} + \sqrt{\left( \frac{I_{OUT}}{\mu_n C_{ox}} \right)^2} \right\}}$$


$$I_{OUT} = \frac{\mu_n C_{ox}}{2} \left( \frac{W}{L} \right)_2 \left\{ \frac{I_{OUT}}{\mu_n C_{ox}} + \sqrt{\left( \frac{I_{OUT}}{\mu_n C_{ox}} \right)^2} \right\}^2$$

$$= \frac{\mu_n C_{ox}}{2} \left( \frac{W}{L} \right)_2 \left\{ \frac{I_{OUT}}{\mu_n C_{ox}} + \frac{I_{OUT}}{\mu_n C_{ox}} \right\}$$

$$I_{OUT} = I_{D2} = I_{REF} \left\{ \frac{\left( \frac{W}{L} \right)_2^2}{\left( \frac{W}{L} \right)_1} \right\}$$


PICK  $L_1 = L_2$
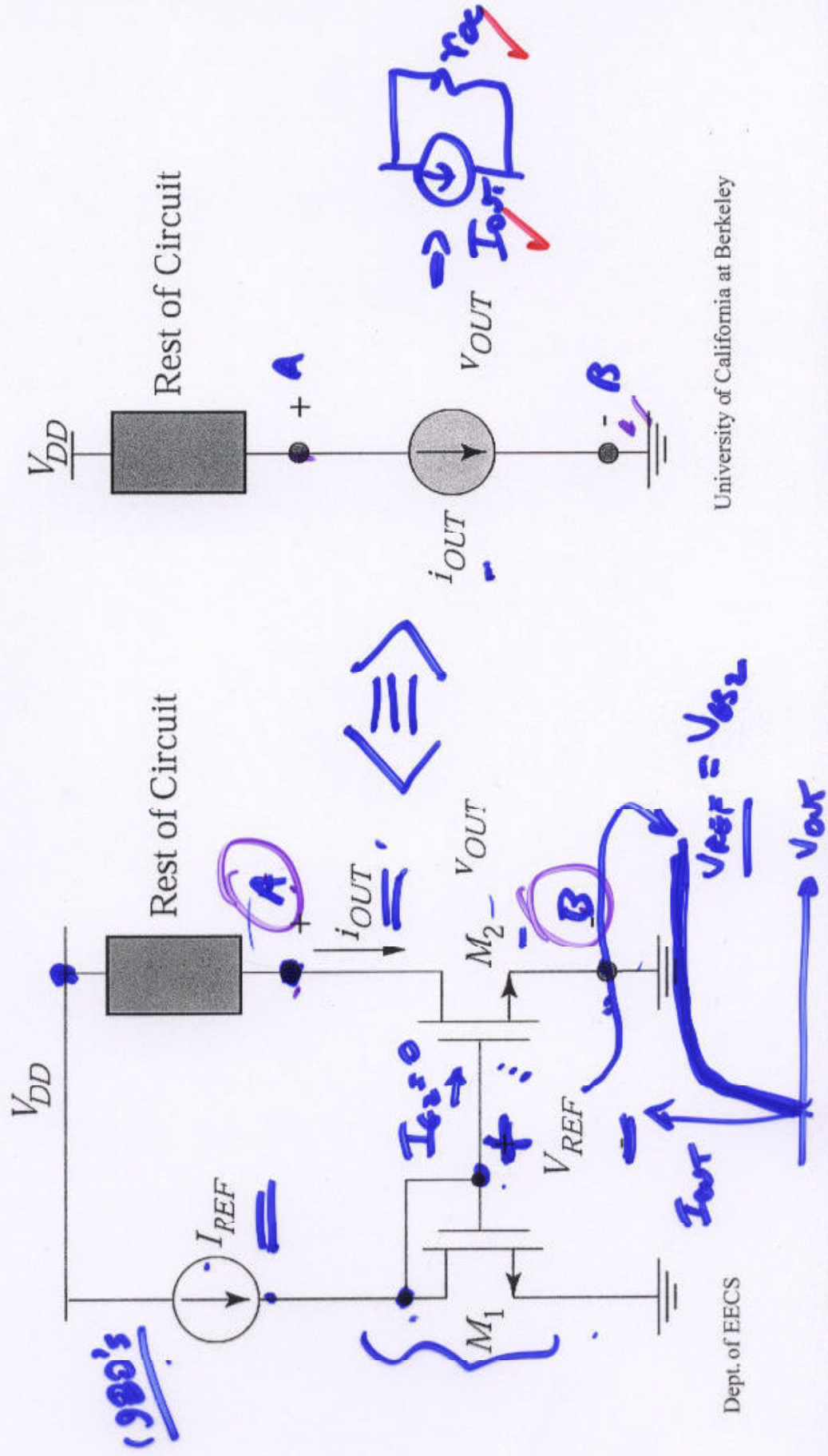
# Using a Voltage Source to Make a Current Source






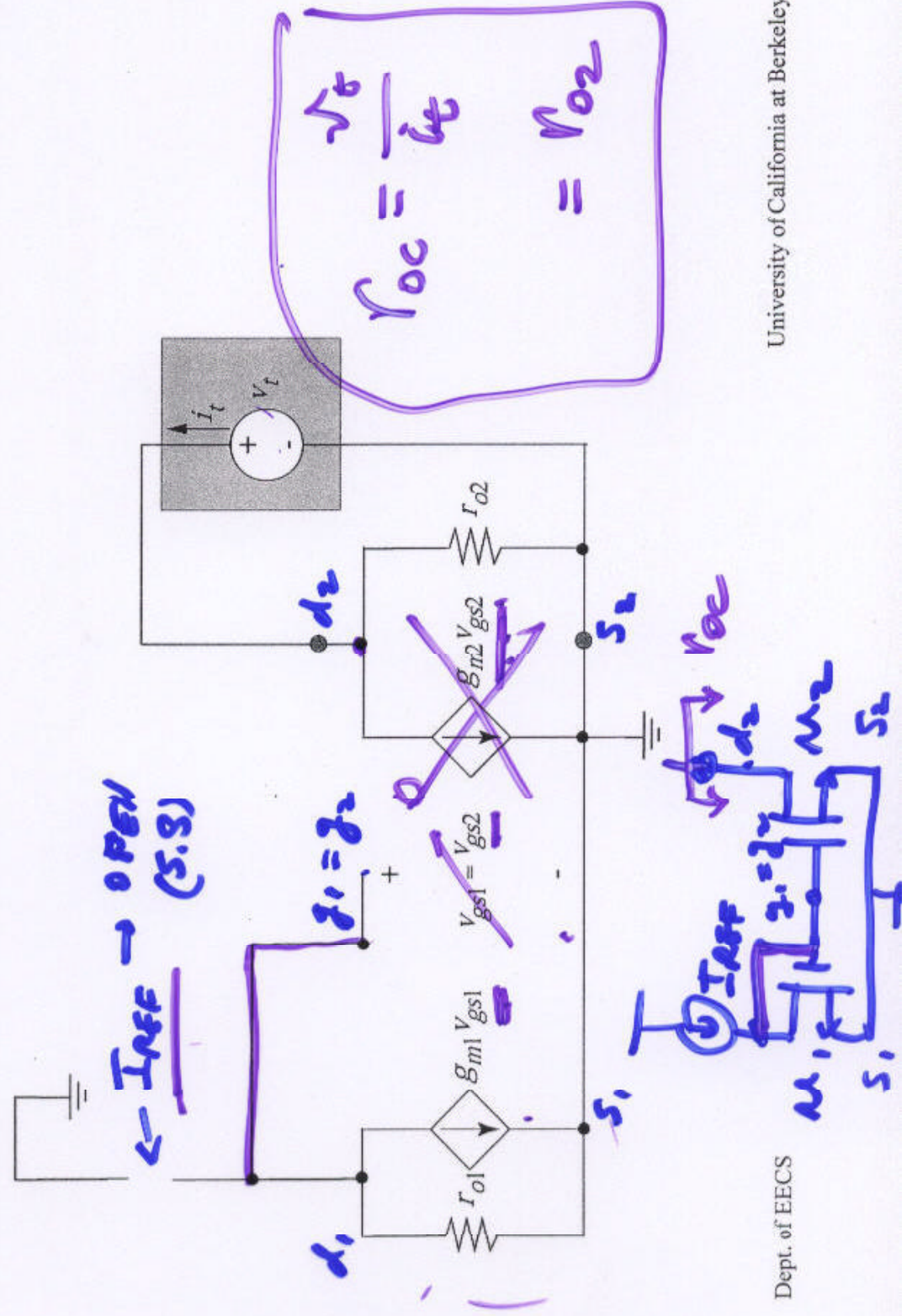
# Small-Signal Resistance of $I$ -Source $r_{oc}$



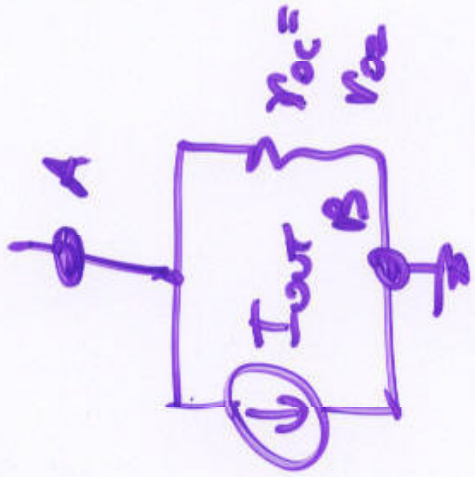$i_{out} \uparrow I_{out}$   
 $\frac{1}{SLOPE} = r_{o2}$   
 $V_{OS2} = V_{REF}$



$V_{out}$   
 $V_{out}$   
 $V_{out}$

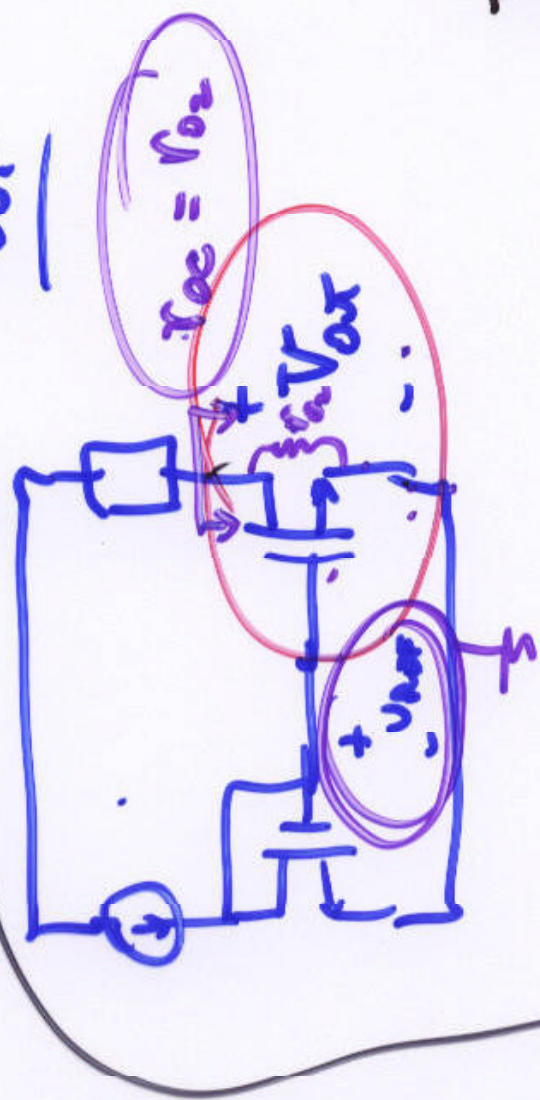

$V_{REF}$   
 $V_{OUT\ min} = V_{DS\ SAT} = V_{OS2} - V_{TN} \approx 0.5V$

$I_{D2} \dots$  BIG (100's of  $\mu A$ ) NOT HUNE!

# Improved Current Sources


Goal: increase  $r_{oc} \leftarrow 1\text{M}\Omega, 5\text{M}\Omega, 100\text{M}\Omega!!$

Approach: look at amplifier (?) output resistance results

IOEA... to see topologies that boost resistance

LARGE  $I_{out}$  CG  
LARGE  $r_{oc}$


$$R_{out} = r_{o2} (1 + g_m R)$$

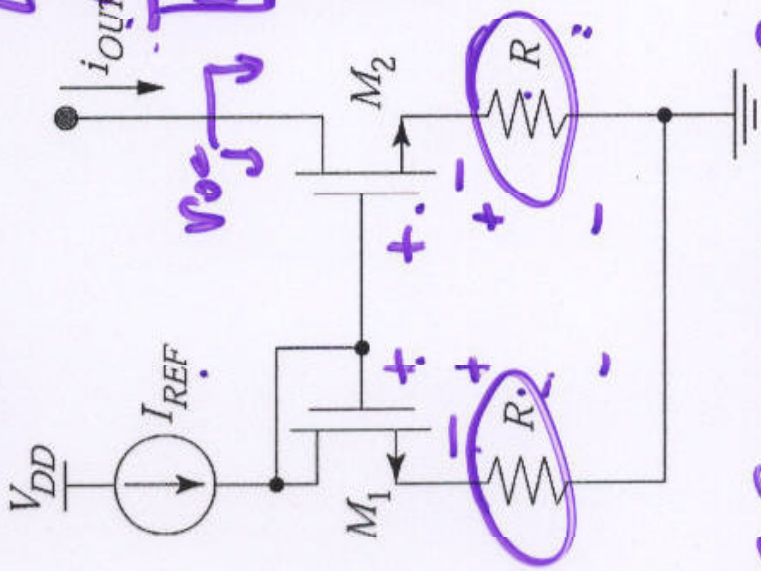


$R = 10\text{M}\Omega$   
 $R = 100\text{k}\Omega$   
 $R = 500\text{k}\Omega$

Too big!  $R_{out_{CG}} = r_{oc} || r_{o2} (1 + g_m R_s)$

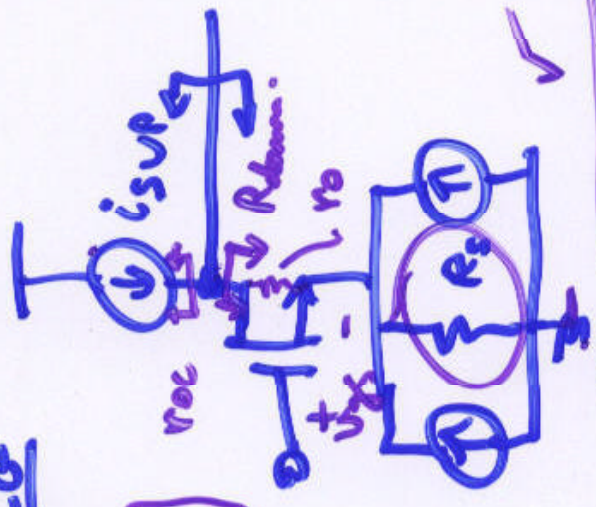SYMMETRY... ROW BOTH SIDES!  
 $\rightarrow M_2$   $\rightarrow M_1$   
 $\rightarrow R_{out_{CG}}$   $\rightarrow R_{out_{CG}}$



# "Cascode (or Stacked) Current Source

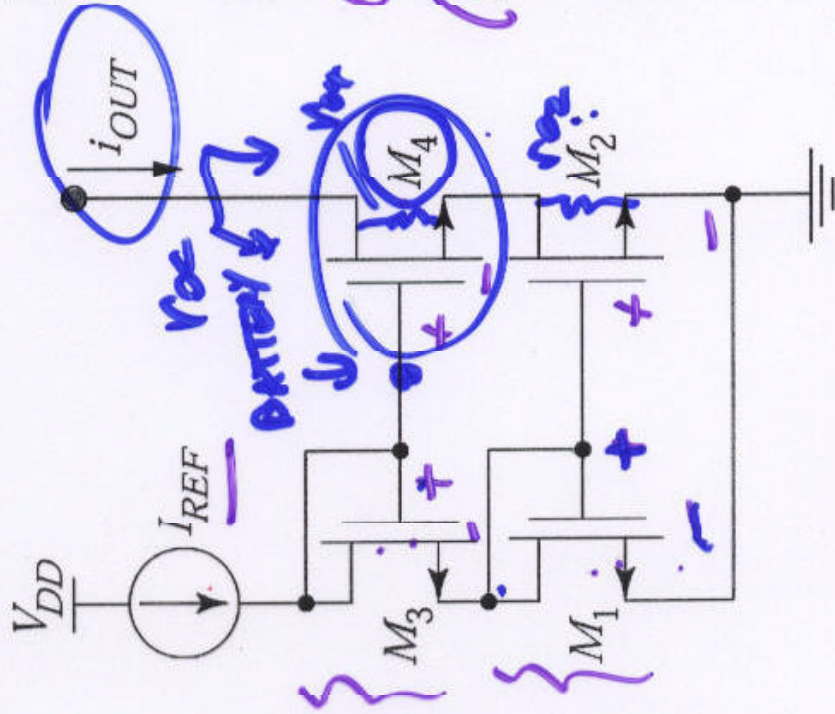

Insight:  $V_{GS2} = \text{constant AND}$   
 $V_{DS2} = \text{constant}$

Small-Signal Resistance  $r_{oc}$ :

$$\frac{(w/L)_2 / (w/L)_1}{(w/L)_4 / (w/L)_3} = 100 \dots$$

$$r_{oc} = \frac{r_o}{4} \approx r_{o4} (1 + g_{m4} \cdot r_{o2})$$

"Rollup" from  
 University of California at Berkeley  
 SAMPLE C.G. TRANSLE (Rout)  
 I-SOURCE

SYMMETRY