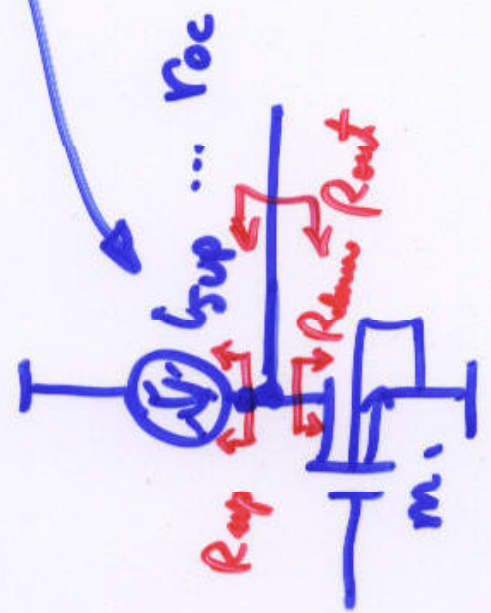


Lecture 34

- Last time: CASCODE.
 - Improved current sources and current mirrors
- Start multistage amplifiers 3.1
- Today: CHAPTER 9
 - More examples of cascades
 - DC coupling issues


• WHAT'S GOOD ENOUGH?



CS


$$V_o = \frac{1}{\lambda_n I_D} = \frac{1}{\lambda_n I_{bias}}$$

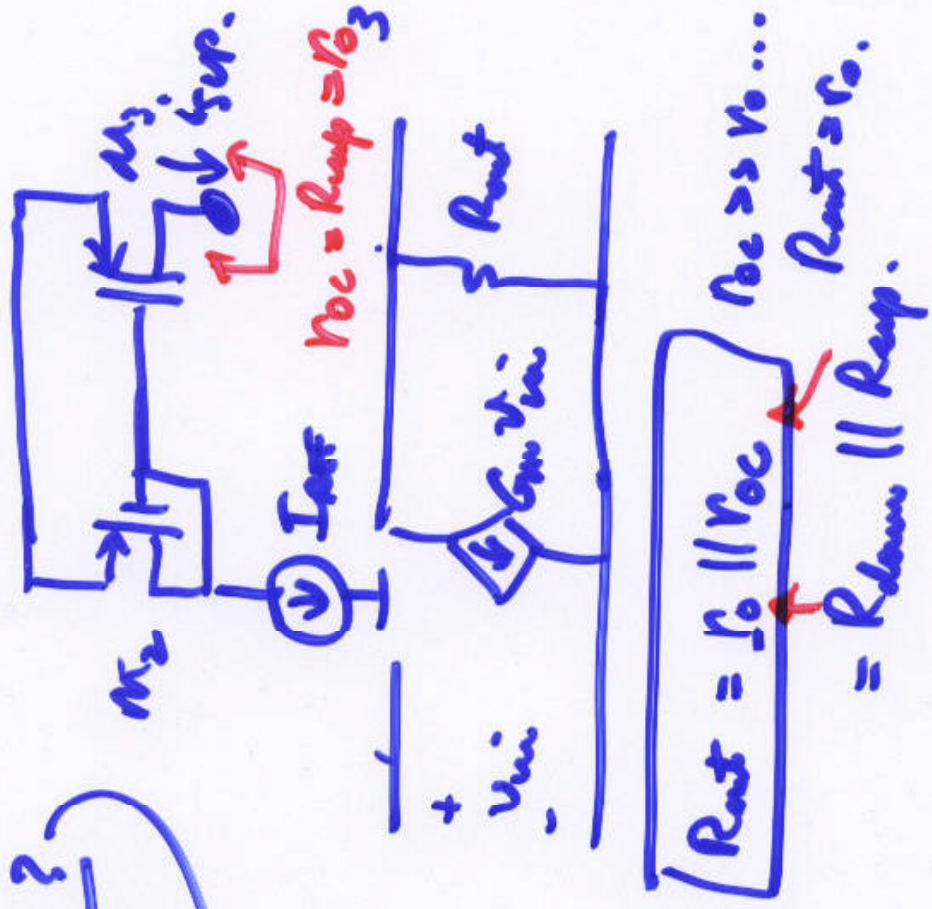USE SIMPLE / BASIC I-SUPPLY. (MODERATELY LARGE)



$$R_{out} = R_L \parallel V_{oc} = R_{sup} \parallel R_{bias}$$


CG STAGE ... NEED
CASCODES

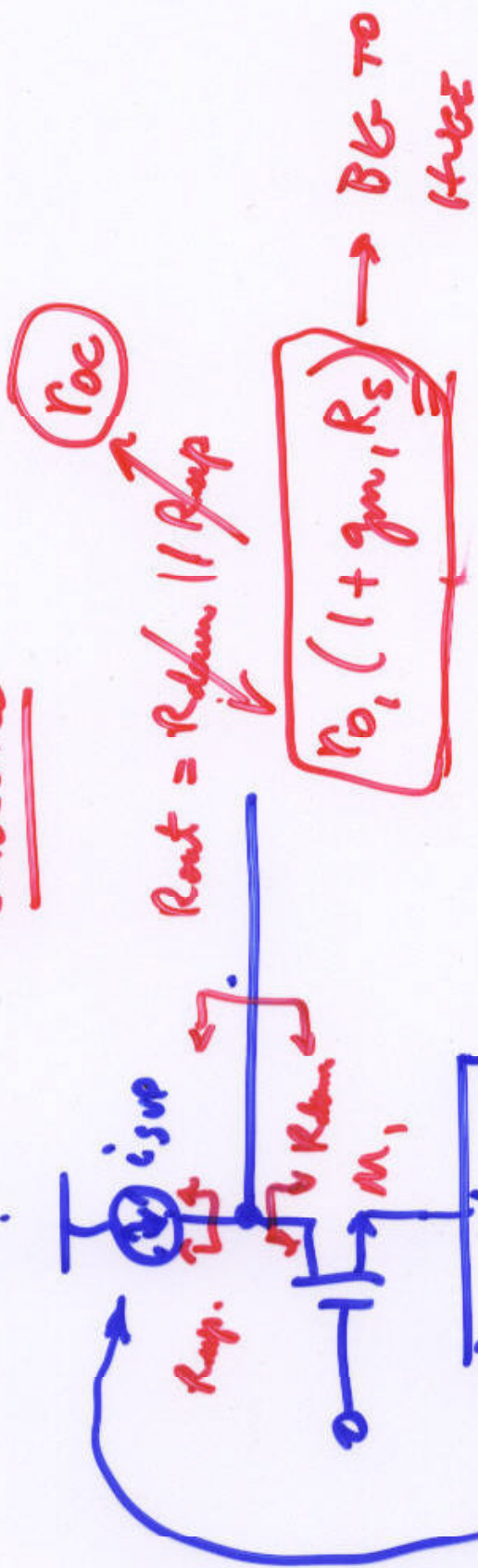

$R_{out} = R_{Lout} || R_{imp}$





$R_{o1}(1 + g_{m1} R_s) \rightarrow Bk \rightarrow$
 i_{sop}

R_{oc}

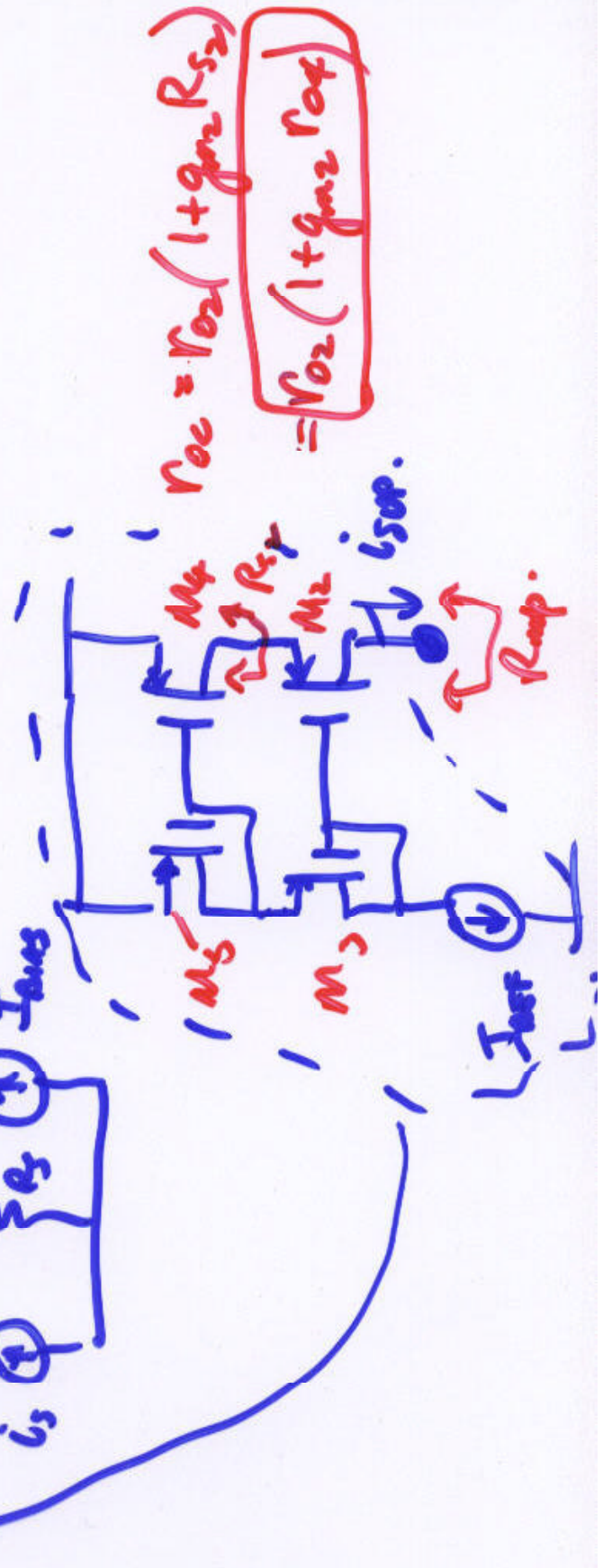

$R_{oc} = R_{o2}(1 + g_{m2} R_{s2})$



$= R_{o2}(1 + g_{m2} R_{o1})$

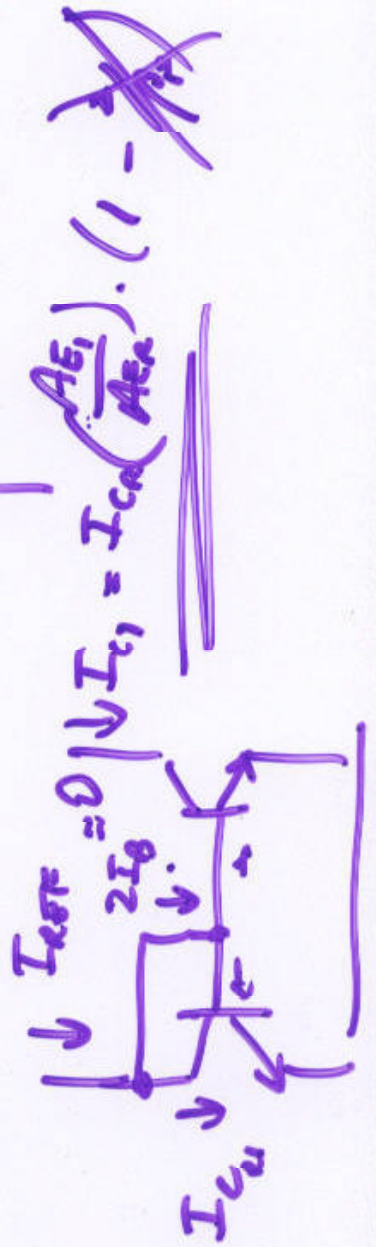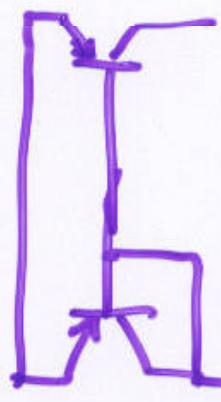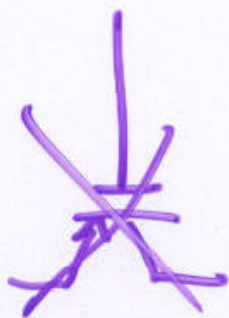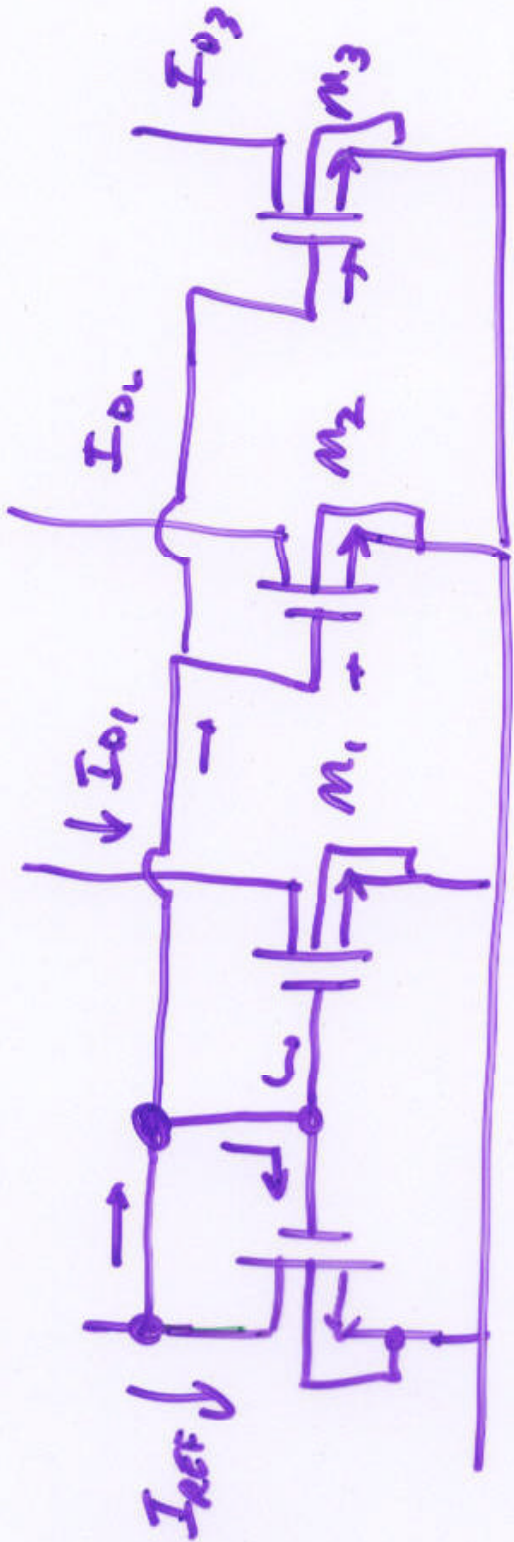

Current Sinks and Sources

Sink: output current goes to ground

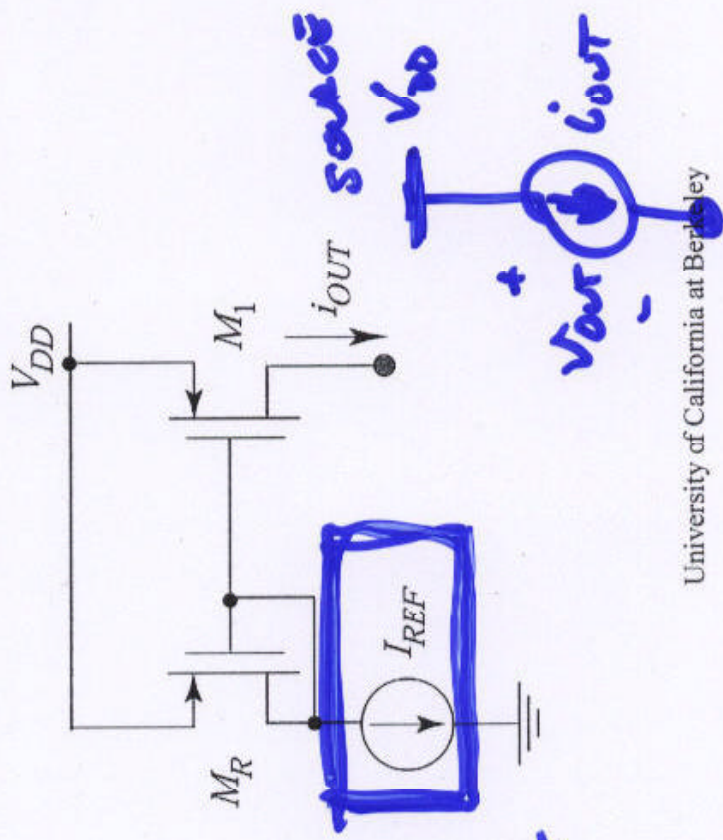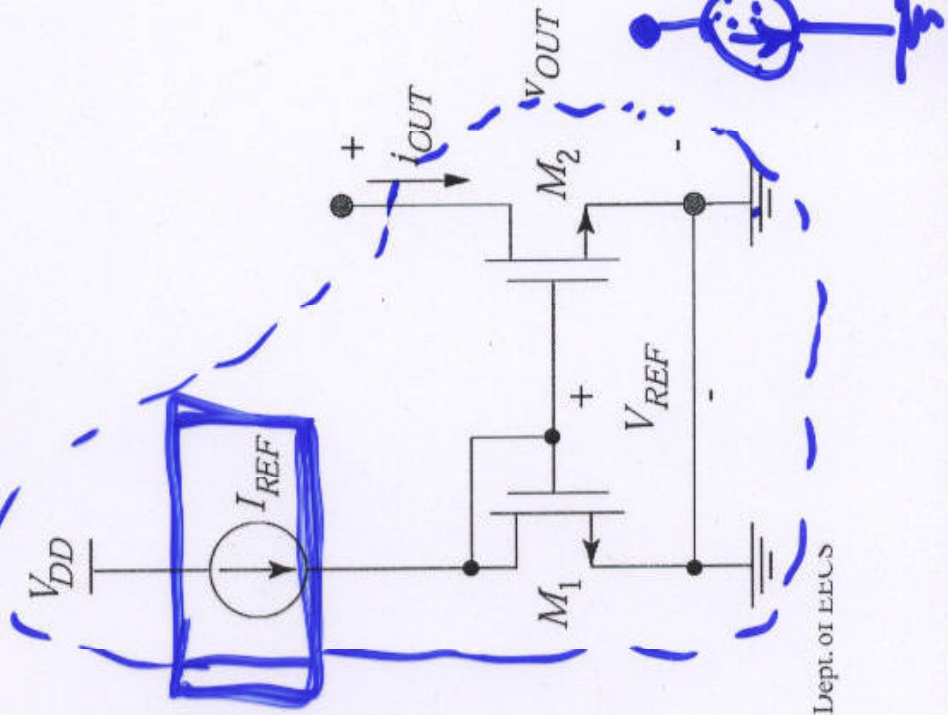Source: output current comes from voltage supply





Multistage Amplifiers

→ Necessary to meet typical specifications for any of the 4 types
CE, CS ... GAIN ... NOT ENOUGH; Rin, Rout GREAT.


We have 2 flavors (NMOS, PMOS) of CS, CG, and CD and the
 npn versions of CE, CB, and CC (for a BiCMOS process)

"PURE CMOS" ... NO BJT!
 What are the constraints?

o Vol CMOS amp [$R_{in} = \infty \Omega$,
 $R_{out} = 0 \Omega$.]

- 1. Input/output resistance matching ... GOALS IN CHAPTER 8.

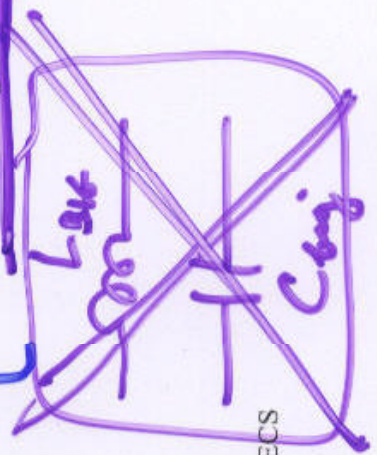- 2. DC coupling (no passive elements to block the signal)



Start: Two-Stage Voltage Amplifier

- Use two-port models to explore whether the combination "works"




$\approx R_{in}$
 $R_{in} = R_{o1} || R_{i2} || R_{i1}$
 (MS) MATCHING
 LOADING

$v_{in2} = -g_{m1} v_{in} (R_{out1} || R_{in2})$
 $= -g_{m1} g_{m2} \frac{v_{out1}}{v_{in1}} = -g_{m1} g_{m2} \frac{v_{out2}}{v_{in2}}$
 Results: $R_{in} = R_{in1} || R_{in2}$, $R_{out} = R_{out2}$, $A_v = \frac{v_{out}}{v_{in}}$
 $R_{in} = R_{in1} || R_{in2}$
 $R_{out} = R_{out2}$

$R_{in} = R_{in1} || R_{in2}$
 $R_{out} = R_{out2}$

Add a Third Stage: CC

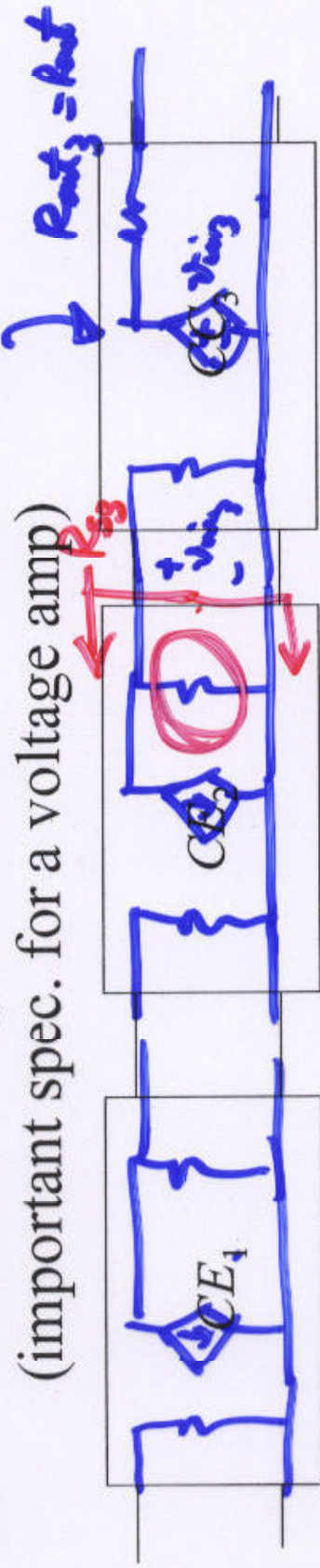Goal: reduce the output resistance R_{out} source
 (important spec. for a voltage amp)



Output resistance:

$$R_{out} = \left(\frac{1}{g_{m3}} \right) + \frac{R_{S3}}{\beta_0} + \frac{R_{o2} \parallel R_{oC2}}{\beta_0}$$

$$= \left(\frac{1}{g_{m3}} \right) + \frac{R_{o2} \parallel R_{oC2}}{\beta_0}$$

LAST SLIDE:
 $R_{S3} = R_{o2} \parallel R_{oC2}$
 $R_{S3} = R_{o2} \parallel R_{oC2}$
IMPROVEMENT!!