

LAB THIS WEEK

→ SEE THE ... TO
GET PSPICE!

Lecture 3

[PS 1 DUE @ 4 PM]
[TUESDAY ...]

- Last time:
 - Imaginary exponentials: simplify the math
 - **Phasor**: complex “prefactor” for $e^{j\omega t}$
- Today :
 - Complex number review
 - Circuit analysis with phasors

ACTUAL / MEASURED

FUNCTION
 $v(t)$

Finding the "Real" Waveform

- How to connect the imaginary exponential solution to the measured waveform $v(t)$? Conventionally, $v(t)$ is the real part of the imaginary exponential

$$\text{Re}(ve^{j(\omega t + \phi)}) = v \cos(\omega t + \phi)$$

ASSUMED

MEASURED.

$$\text{Re}\{x + jy\} = x$$

$v_c = \left(\frac{dv_c}{dt}\right) c$ \Rightarrow $V e^{small\ letters}$

Pushing This Idea Further ...

There are two parameters needed to define a sinusoidal signal:

- * magnitude
- * phase ✓

Why not work with a complex number as the signal and eliminate the imaginary exponential from the analysis (it cancelled out)?

Define the complex number consisting of the amplitude and phase a sinusoidal signal as a phasor V . **LECTURE 2**

~~DECEPTIVELY HARD CONCEPT~~

$$v(t) = v \cos(\omega t + \phi) \iff v(t) = V e^{j\omega t}$$

$$V = v e^{j\phi}$$

$$v \cos(\omega t + \phi) \rightarrow v e^{j(\omega t + \phi)} = [v e^{j\phi}] e^{j\omega t}$$

Complex Number Summary


- Rectangular form: $z = x + jy$
- Magnitude $|z| = \sqrt{x^2 + y^2}$
- Phase $\angle z = \tan^{-1}(y/x)$
- Polar form: $z = |z|e^{j\angle z}$
- Useful results (easily shown in polar form):

$$|z_1 z_2| = |z_1| \cdot |z_2| \quad \angle(z_1 z_2) = \phi_1 + \phi_2$$

$$|z_1 / z_2| = |z_1| / |z_2| \quad \angle(z_1 / z_2) = \phi_1 - \phi_2$$

Question: $\sqrt{j} = \sqrt{\sqrt{-1}}$

$$|z_1 z_2| = |z_1| e^{j\phi_1} \cdot |z_2| e^{j\phi_2} = |z_1| |z_2| e^{j(\phi_1 + \phi_2)}$$

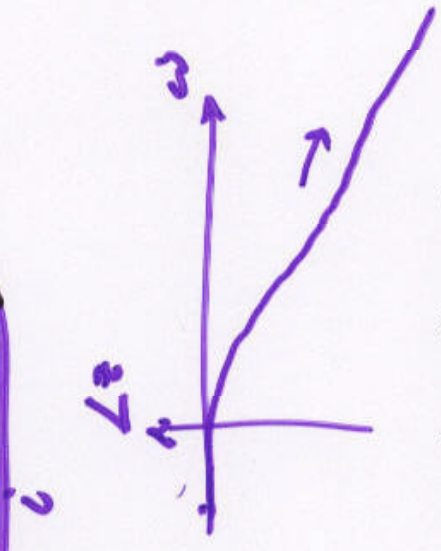

USEFUL →

$$|z_1 z_2| = |z| e^{i\phi} \quad \left\{ \begin{array}{l} \uparrow \\ |z_1 z_2| \end{array} \right. \quad \phi_1 + \phi_2$$

$$e^{j(\phi_1 + \phi_2)} = \cos(\phi_1 + \phi_2) + j \sin(\phi_1 + \phi_2)$$

$$|e^{j(\phi_1 + \phi_2)}| = 1.$$

Go Polar!


$$j = 0 + j1 \dots \text{POLAR FORM } e^{j\pi/2} = e^{j90^\circ}$$

$$\sqrt{j} = \sqrt{e^{j\pi/2}}$$

$$= \{e^{j\pi/4}\}^{1/2}$$

CHECK THIS...
 READ $j = e^{j\pi/2}$
 π

Using Phasors: Capacitor Current

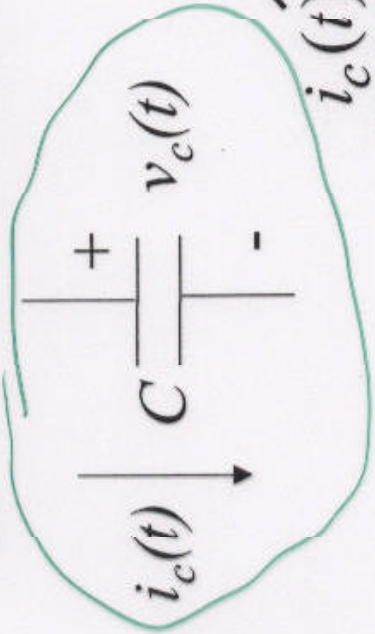

$$i_c(t) = C \frac{dv_c}{dt}$$

PHASOR

$$v_c(t) = V_c e^{j\omega t}$$

PHASOR
TIME FUNCTION

$$i_c(t) = I_c e^{j\omega t}$$

$$I_c e^{j\omega t} = C \left\{ \frac{d}{dt} \cdot [V_c e^{j\omega t}] \right\}$$


$$I_c e^{j\omega t} = C \cdot V_c \cdot j\omega e^{j\omega t}$$

Result:

$$I_c = (j\omega C) \cdot V_c$$

$i_R(t) = \left(\frac{1}{R}\right) \cdot v_R(t)$
 \Rightarrow
 $Z = \frac{V}{I} = F$

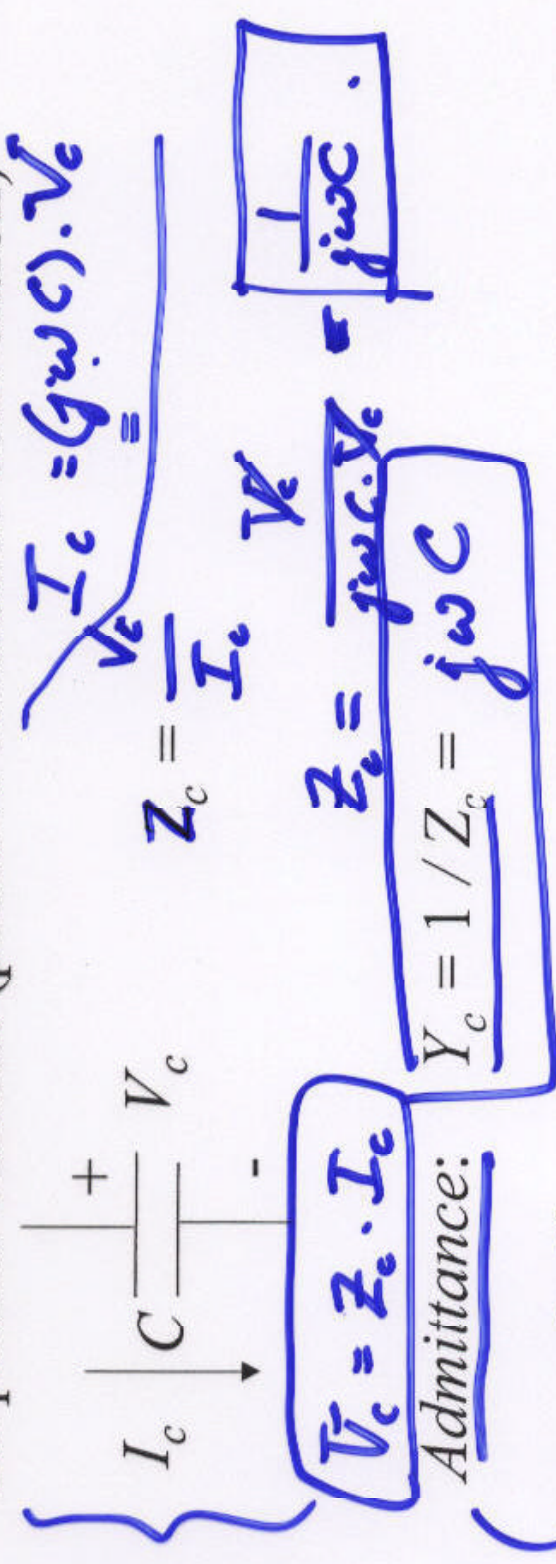
Definition: the impedance Z of a two-terminal circuit element is the ratio of the phasor voltage to the phasor current (positive reference convention)



Admittance:

\rightarrow conductance G

Using Phasors: Inductor Voltage

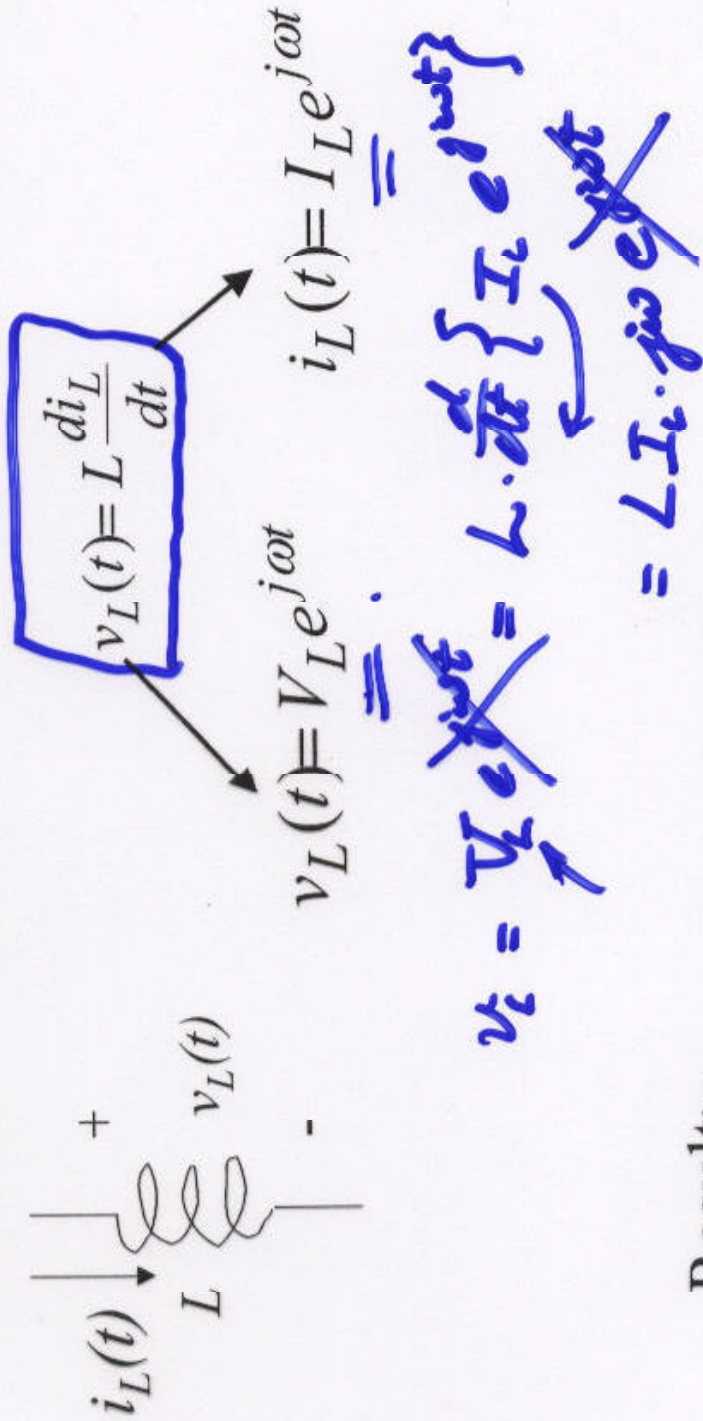


Result:

$$\boxed{V_L = (j\omega L) \cdot I_L}$$

$$\uparrow Z_L = j\omega L$$

Inductor Impedance

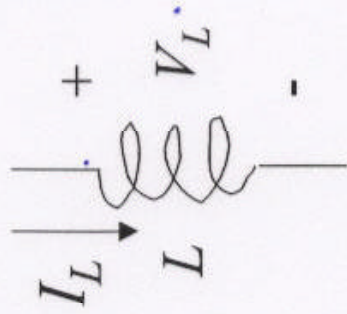

$\boxed{\Omega = S^{-1} \cdot H}$

$Z_L = j\omega L$

$\omega \rightarrow 0 \text{ rads}^{-1} \dots Z_L = j \cdot 0 = 0 \Omega$
SMART.

$\omega \rightarrow \infty \quad Z_L = j \infty \text{ } \Omega!$

Admittance: $Y_L = 1 / Z_L = \frac{1}{j\omega L}$

$\omega^* \Rightarrow Z_L(\omega^*) = \frac{1}{j\omega^* L} = Z_L$

$Z_C(\omega^*) = \frac{1}{j\omega^* C} = Z_C$
Dept. of EECS
 $Z_C(\omega^*) = \frac{1}{j\omega^* C} = Z_C$
 0Ω

$i_R(t) \downarrow \quad \begin{cases} + \\ - \end{cases} \quad R \quad v_R(t) = R \cdot i_R(t)$

$\begin{cases} i_R(t) = I_R e^{j\omega t} \\ v_R(t) = V_R e^{j\omega t} \end{cases}$

$V_R e^{j\omega t} = R \cdot I_R e^{j\omega t}$


$V_R = R \cdot I_R$

$Z_R = \frac{V_R}{I_R} = R$

University of California at Berkeley

KCL

Kirchhoff's Current Law Example

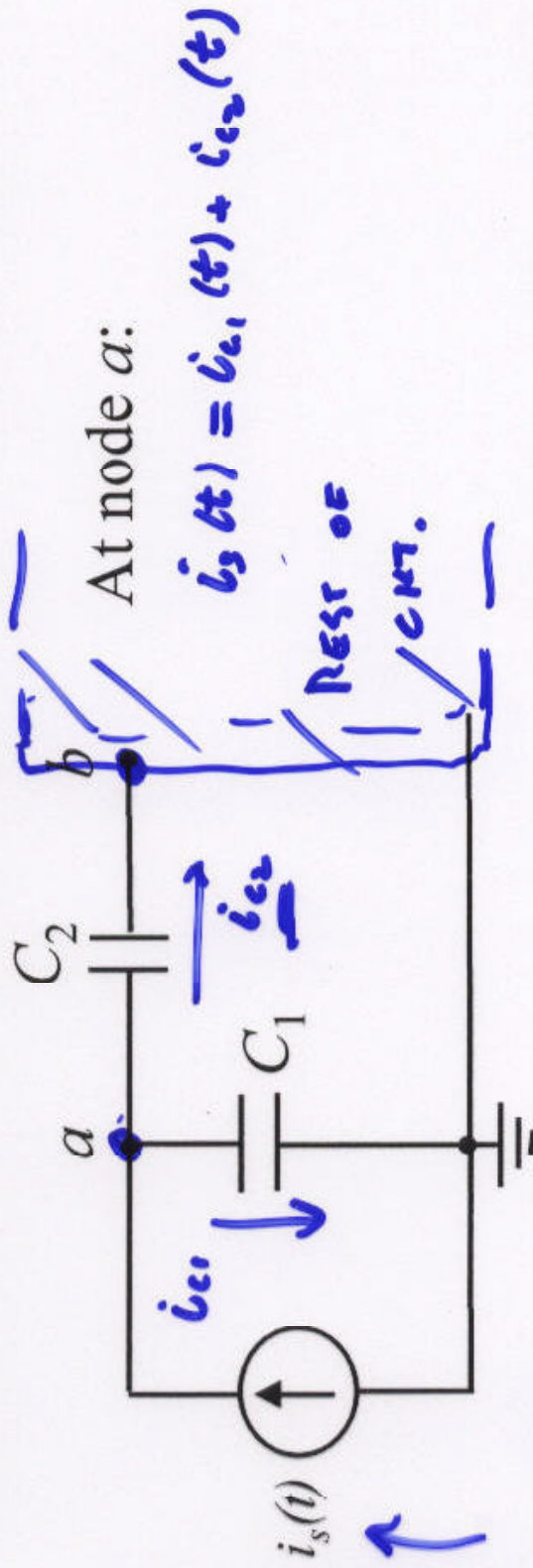

$$I_s e^{j\omega t}$$

$$i_{c_2} = I_{c_2} e^{j\omega t} = C_2 \frac{d(v_a - v_b)}{dt} = C_2 \frac{d(v_a - v_b)}{dt}$$


$$i_{c_1} = I_{c_1} e^{j\omega t} = C_1 \frac{dv_a}{dt} = C_1 \frac{dv_a}{dt}$$

$$v_a(t) = V_a e^{j\omega t}; \quad v_b(t) = V_b e^{j\omega t}$$

Circuit Analysis with Phasors


Assumption: sources are sinusoidal, steady-state!

$$i_{\text{out}}(t) = 0$$

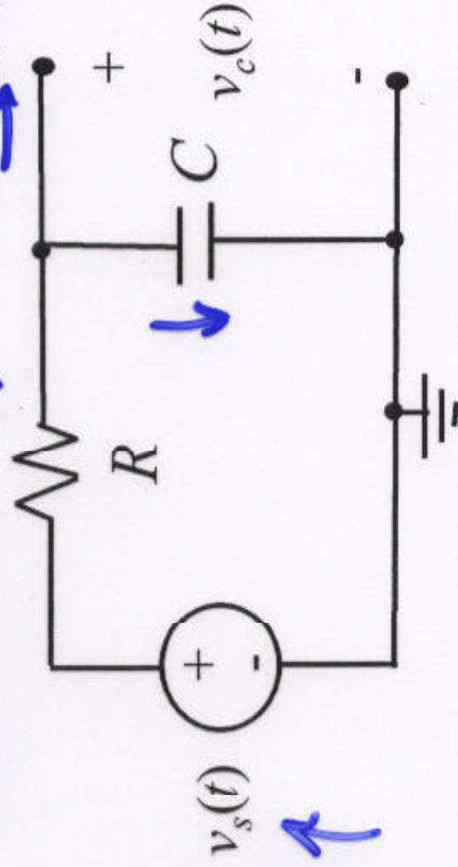

$$v_s(t) = v_s \cos(\omega t + 0^\circ)$$

PICK 0°

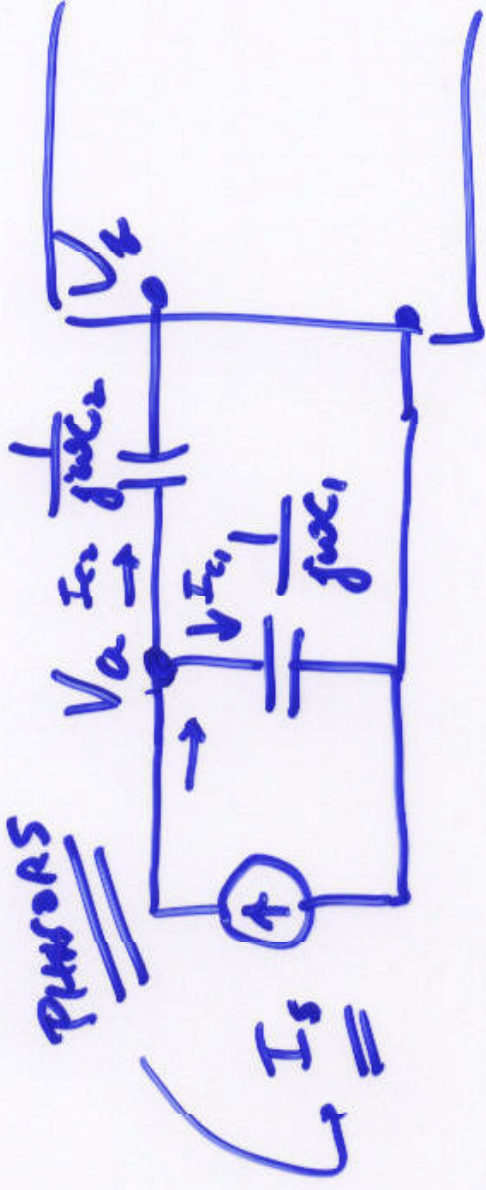

PHASORS!

$$I_s = I_{c1} + I_{c2}$$

$$I_s = \underbrace{(j\omega C_1) \cdot V_a}_{\text{PHASORS!}} + (j\omega C_2)(V_a - V_c)$$

$$\frac{V_a}{Z_{c1}} = \frac{V_a}{\left(\frac{1}{j\omega C_1}\right)}$$