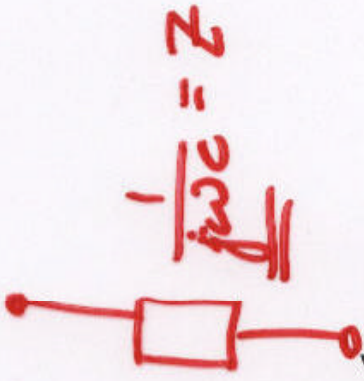


Lecture 4

I_c, V_c



- Last time:
 - Circuit analysis with phasors: impedances
 - Bode plot of low-pass filter (start)
- Today: MAT, PHASE → VS. ω . or f
 - Bode plot sketching for first-order transfer functions
 - Low-pass and high-pass filters

MONDAY 1-2 DISCUSSION

{ 2/4: 476 CORY HALL

{ 2/11 AND LATER: 9 EVANS HALL

KCL, KVL, Norton, Thev.

Redrawing the Circuit


~~First GONE~~

I_R

NO TIME


with Impedances $V = V_s \left(\frac{R_2}{R_1 + R_2} \right)$

IMPEDANCE DIVIDER!

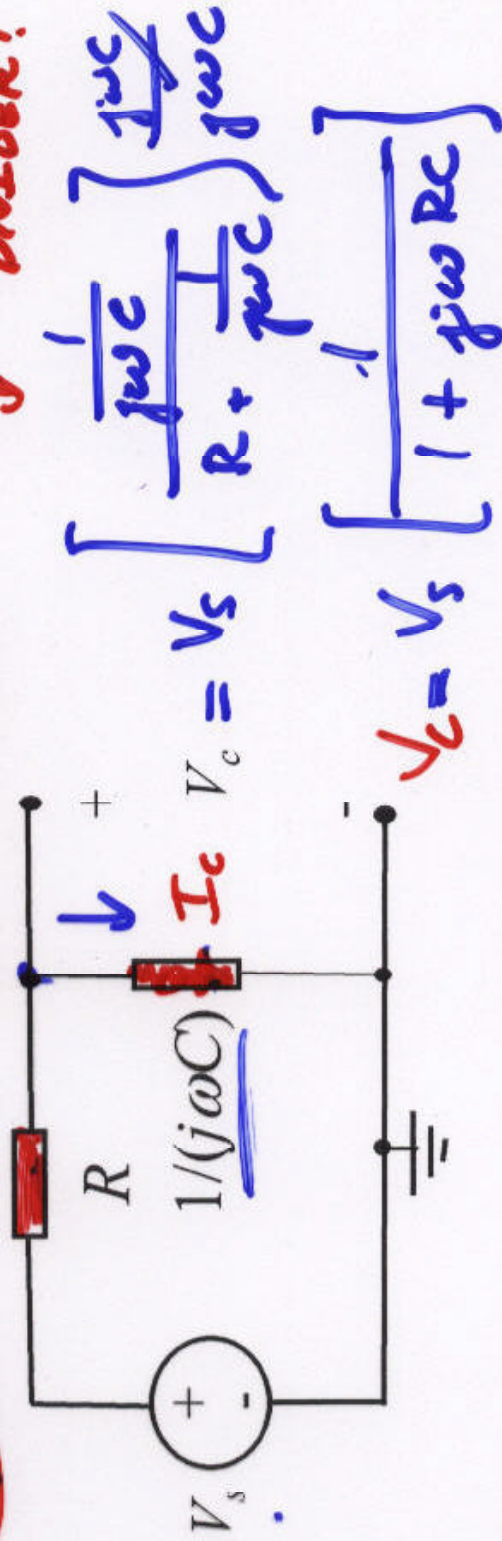

$$V_c = V_s \left[\frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \right]$$

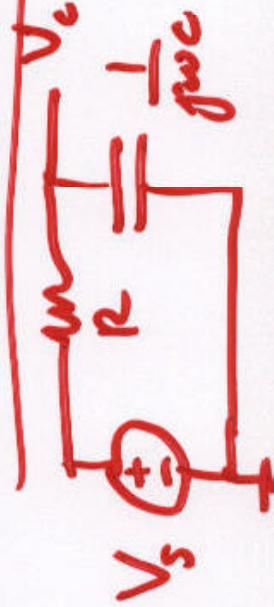Note: this is not a "real" circuit that could be built and tested!



$$H = \frac{V_c}{V_s} \dots \frac{I_{out}}{I_s}$$

$$H = \frac{V_c}{V_s} \dots$$

Transfer Function

$$H(s); s = \sigma + j\omega$$

Ratio of output to input phasor is called the transfer function of the circuit:

$$H = \frac{V_c}{V_s} = \frac{1}{1 + j\omega RC}$$

$$H(j\omega) \quad \omega^2 \rightarrow -(j\omega)^2$$

$$\frac{1}{1 + j\omega RC}$$

$$|H|_{dB} = 20 \log_{10} \left| \frac{1}{1 + j\omega RC} \right|$$

$$\angle H = \angle \frac{1}{1 + j\omega RC} = -\tan^{-1} \left[\frac{\omega RC}{1} \right]$$

Bode Plots for Low-Pass Filter

1. Plot magnitude $|H|$ in dB vs. ω (log scale)
2. Plot phase $\angle H$ in degrees vs. ω (log scale)

$$|H|_{dB} = \left| \frac{1}{1 + j\omega\tau} \right|_{dB} = \left[\frac{|1|}{|1 + j\omega\tau|} \right]_{dB}$$

$$= 20 \log_{10} \left\{ \frac{\sqrt{1+0^2}}{\sqrt{1^2 + (\omega\tau)^2}} \right\}$$

Why?

$$\begin{aligned} |H(j\omega)|_{dB} &\equiv 20 \log_{10} |H(j\omega)| \\ &= 20 \log_{10} \left\{ \frac{|1 + j0|}{|1 + j\omega\tau|} \right\} \end{aligned}$$


$$|z_1/z_2| = |z_1|/|z_2|$$

$$\frac{1}{1 + j\omega/\omega_{-3dB}} = \frac{1}{1 + j\omega}$$

-3dB

The Break Frequency $\omega_{-3dB} = (1/\tau)$

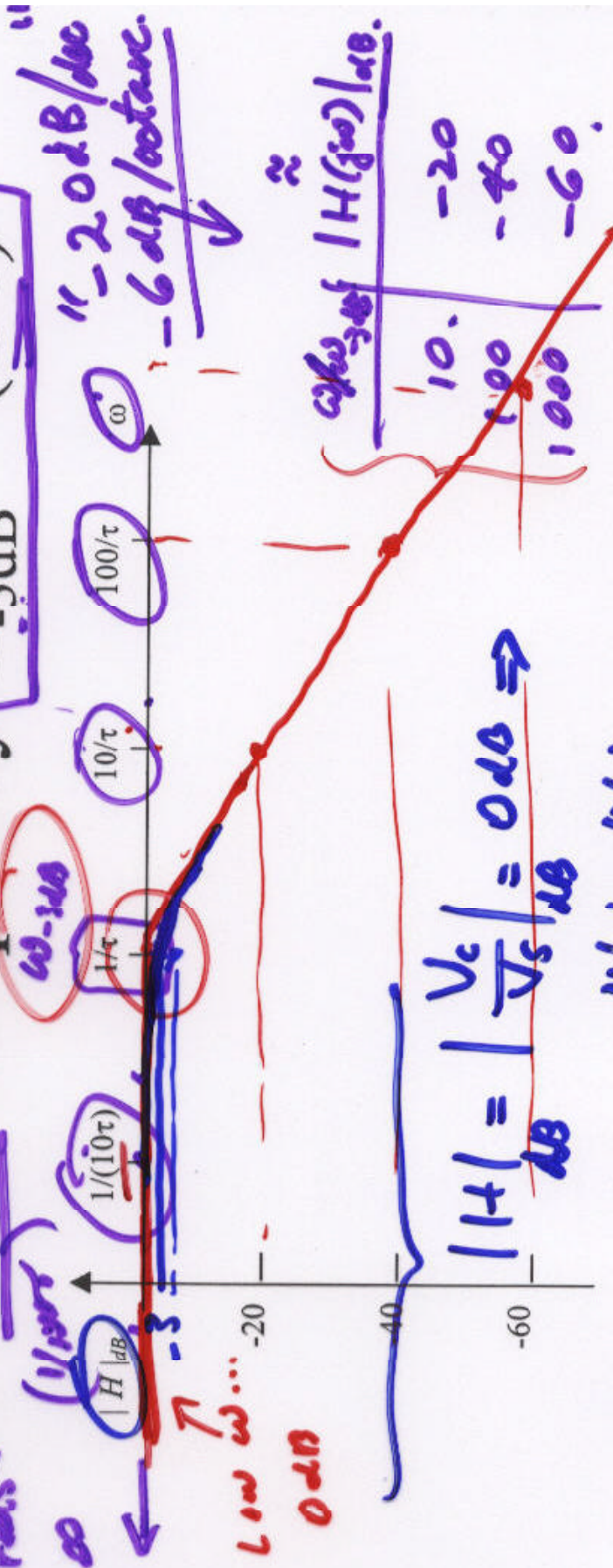0 rad/s \leftarrow ω \rightarrow ∞
 " -20 dB/dec"
 " -6 dB/octave"



$$|H| = \left| \frac{V_c}{V_s} \right| = 0 \text{ dB} \Rightarrow$$

$$|V_c| = |V_s|$$

$\omega\tau \gg 1 \Rightarrow$

$$|H(j\omega)| = 20 \log_{10} \left[\frac{1}{\sqrt{1 + (\omega\tau)^2}} \right]$$

$$\approx -20 \log_{10}(\omega\tau) = -20 \log_{10} \left(\frac{\omega}{\omega_{-3dB}} \right)$$

$$20 \log\left(\frac{1}{x}\right) = 20 \log_{10}(x^{-1})$$

$$= -20 \log_{10} x$$

Sketching the Magnitude Plot

$$|H|_{dB} = \left[\frac{|1|}{|1 + j\omega\tau|} \right]_{dB}$$

$$\stackrel{\omega \rightarrow 0}{=} 20 \log \left[\frac{1}{\sqrt{1 + (\omega\tau)^2}} \right]$$

$\omega \rightarrow 0$

Low-frequency ($\omega\tau \ll 1$) asymptote :

$$|H(\omega)| = 1; |H(\omega)|_{dB} = 0 \text{ dB}$$

High-frequency ($\omega\tau \gg 1$) asymptote

$$\omega\tau = 10$$

$$\omega\tau = 0.1 \dots \Rightarrow \phi_{dB}$$

$$\frac{1}{\sqrt{1 + (0.1)^2}} \approx \frac{1}{0.01}$$

$$\frac{1}{\sqrt{1 + (\omega\tau)^2}} = \frac{1}{\sqrt{1 + 100}}$$

$$\approx \frac{1}{10}$$

$$(1 + 0.01)^{-1/2} \approx 1 + 0.005$$

$$= 1.005$$

Dept. of EECS

University of California at Berkeley

$$|H(\omega)|_{dB} \approx 10 \log\left(\frac{1}{10}\right) = -20 \text{ dB}$$

$$\angle z_1/z_2 = \angle z_1 - \angle z_2$$

Finding the Phase Plot

$$\angle 1+j\omega = \tan^{-1}[\omega/1] = 0$$

$$\angle(H) = \angle \left[\frac{1}{1+j\omega\tau} \right] = 0 - \arctan(\omega\tau)$$

Why? **Theorem!**

$$\tau = \frac{1}{\omega_{3dB}}$$

• Low-frequency asymptote $\omega\tau \ll 1$ $\arctan(x \approx 0) = 0$


$$\angle(H) \approx 0$$

High-frequency asymptote

$$\omega\tau \gg 1 \quad \angle(H) = 0 - \tan^{-1}\{\infty\} = 0 - 90^\circ = -90^\circ$$

Approx. linear with ω for $1/(10\tau) < \omega < 10/\tau$

Rapidly Sketching the Phase Plot

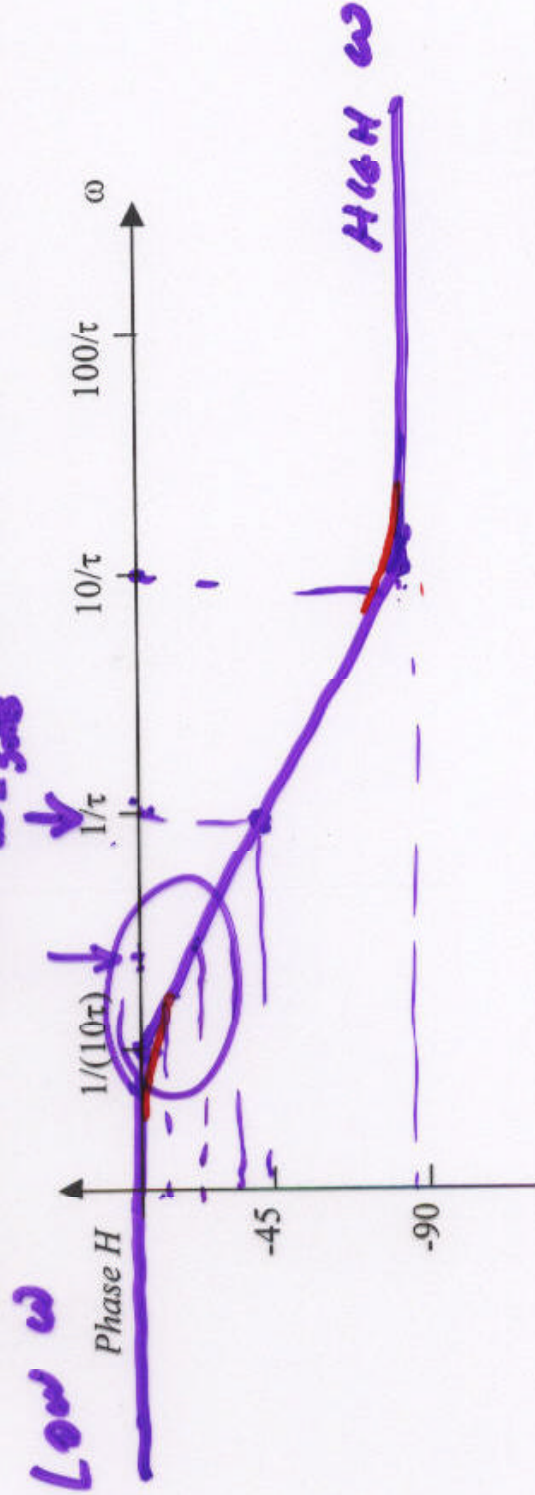


$$\left[\begin{array}{l} \tan^{-1}\left(\frac{1}{10}\right) \approx 6^\circ \checkmark \\ \tan^{-1}(10) \approx 84^\circ \checkmark \end{array} \right. \quad \omega = \frac{1}{\tau} \quad \tan^{-1}[1] = 45^\circ$$

$$i \downarrow \frac{1}{Z} i^* R = i \cdot v$$

Average Power and Phasors,

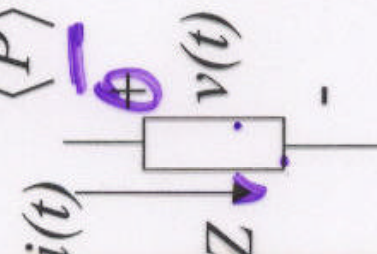Integrate $P(t)$ over one period: $\underline{P(t)}$.




$$\begin{aligned} \langle P \rangle &= \int_0^T i(t)v(t) dt = \int |I| \cos(\omega t + \angle I) |V| \cos(\omega t + \angle V) dt \\ &= |I||V| \langle \cos(\omega t), \cos(2\omega t), \sin(\omega t), \sin(2\omega t) \rangle + \frac{|I||V|}{2} (\cos \angle I \cos \angle V + \sin \angle I \sin \angle V) \end{aligned}$$

$\langle \rangle = 0$

$$\text{Result: } \langle P \rangle = \frac{|I||V|}{2} \cos(\angle I - \angle V) = \text{Re}\{I \cdot V^*\}$$


$$V = |V| e^{j\angle V} \quad V^* = |V| e^{-j\angle V}$$

The High-Pass Filter

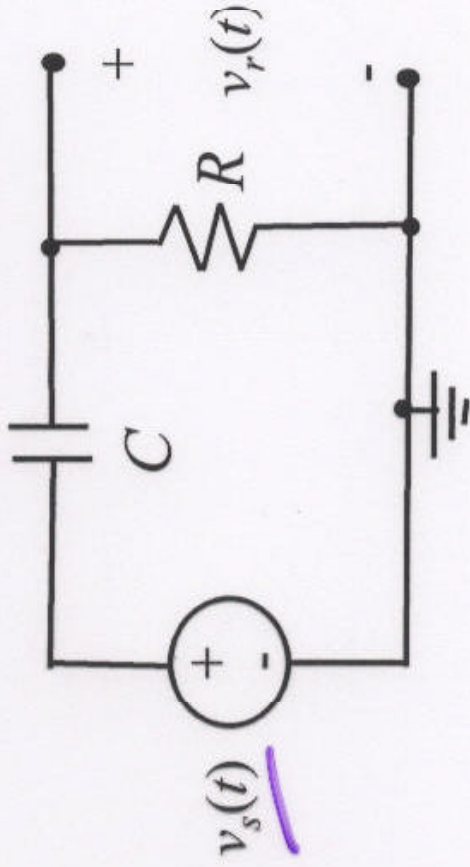

$$\begin{cases} v_s(t) = v_s \cos \omega t \\ v_r(t) = v_r \cos [\omega t + \phi_r] \end{cases}$$

Impedance Divider

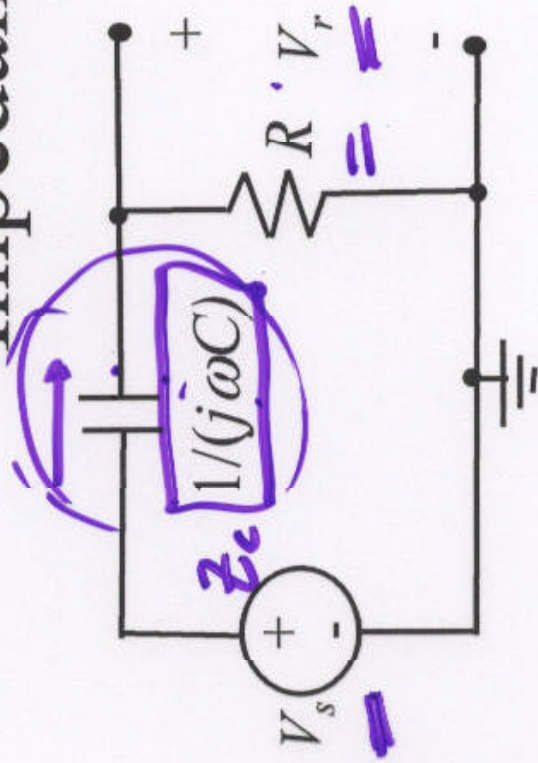

Insight:

$|Z_c| \propto \omega$


$\frac{1}{j\omega C}$

Low $\omega \Rightarrow$ Beams up!

$V_r \rightarrow \phi$

$H = \frac{V_r}{V_s} =$

High ω ✓

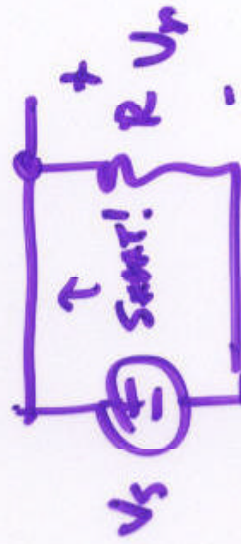

Low ω ✓



$$H = \frac{V_r}{V_c} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC}.$$

$$= \frac{j\omega\tau}{1 + j\omega\tau}.$$

$$\omega \rightarrow \infty$$

$$H \rightarrow \frac{j\omega\tau}{j\omega\tau} \Rightarrow 1 \checkmark$$

$$\omega \rightarrow 0$$

$$H \rightarrow \frac{0}{1+0} \rightarrow 0 \checkmark$$

Graphical Addition of Magnitudes

BLACK: $\left(\frac{1}{1 + \gamma \omega \tau} \right)_{dB}$

