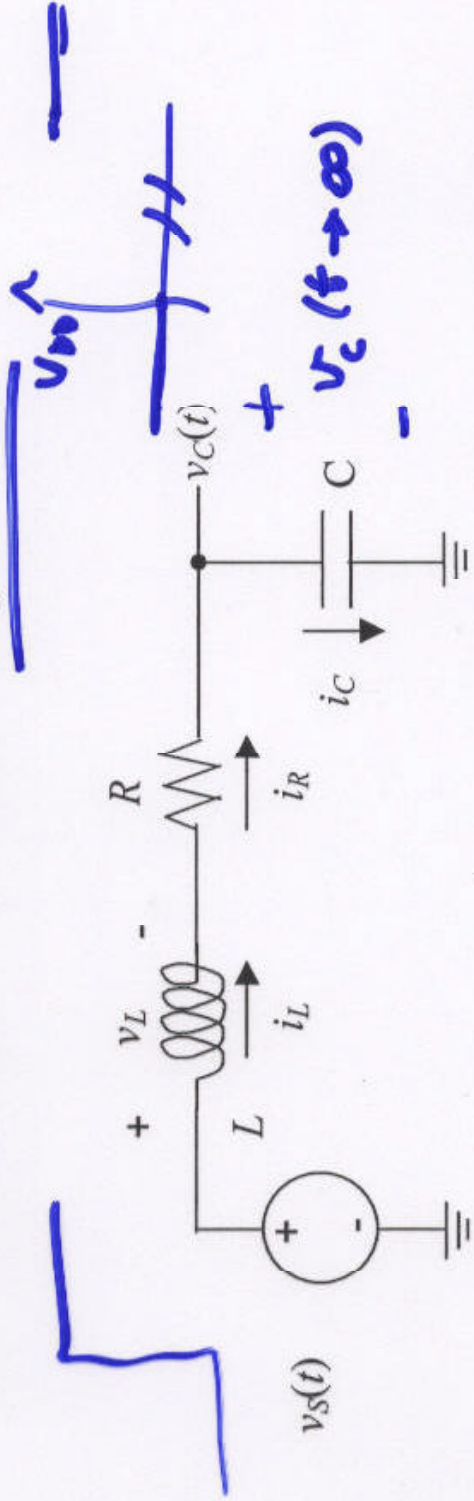


Lecture 6

- Last time:
 - Rapid sketching techniques for more complicated transfer functions
- Today: -RLC-
 - { – 2nd order circuits in the time and frequency
domains



"FIRST ORDER" A Second Order System



10x
↓
10x

• Where does the inductor come from? Make one!

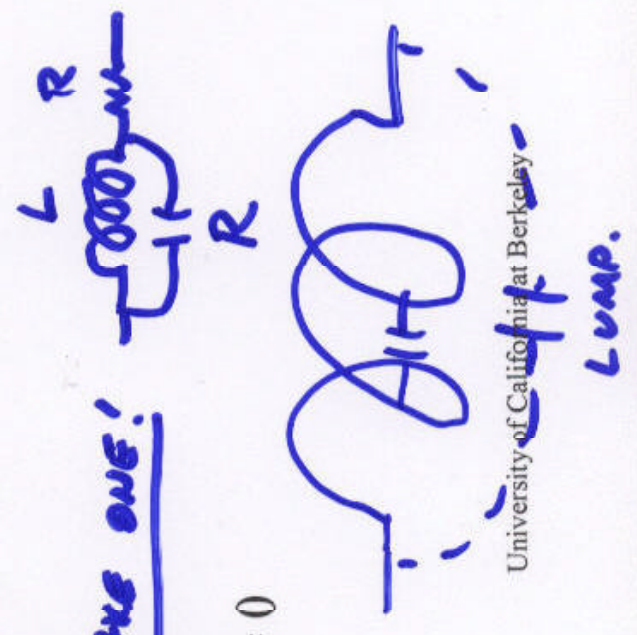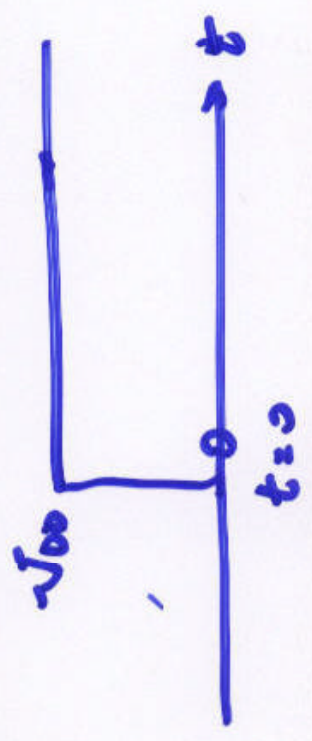→ Do step response: $v_S(t)$ jumps to V_{DD} at $t = 0$



Dept of EECS
University of California at Berkeley
Lump.

Step Response of L-R-C Circuit

Initial conditions: $v_C(t=0) = 0 \text{ V}; i_L(t=0) = 0 \text{ A}$

$$i_L = i_C \longrightarrow \left(\frac{1}{L} \right) \int_0^t v_L(t') dt' = C \frac{dv_C}{dt}$$

$$\text{Inductor voltage: } v_L = V_{DD} - \left(\left(C \frac{dv_C}{dt} \right) R + v_C \right)$$

Solving the 2nd Order ODE

$$\rightarrow \boxed{LC \frac{d^2 v_C}{dt^2} + RC \frac{dv_C}{dt} + v_C = V_{DD}}$$

- Steady-state solution: $v_{C,ss} = V_{DD}$ ($t \rightarrow \infty$) *complex.*

Transient solution. $v_{C,tr} = ?$... guess $v_{C,tr} = ae^{st}$

and substitute: $LCs^2(\cancel{ae^{st}}) + RCs(\cancel{ae^{st}}) + \cancel{ae^{st}} = 0$

$$\boxed{s^2 + (L/R)s + (1/LC) = 0}$$

Characteristic Equation

$$s = ? \rightarrow s^2 + (L/R)s + (1/LC) = 0$$

Use quadratic formula to find the roots:

$$s_{1,2} = -\left(\frac{R}{2L}\right) \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \left(\frac{1}{LC}\right)}$$

OVER DAMPED

[CRITICALLY DAMPED

{ IDENTICAL ROOTS →
{ REAL ROOTS

e^{st}

" UNDER DAMPED " → BORING!

→ $s_{1,2}$ COMPLEX

Underdamped Case

$$s_{1,2} = -\left(\frac{R}{2L}\right) \pm \sqrt{\underbrace{\left(\frac{R}{2L}\right)^2 - \left(\frac{1}{LC}\right)}_{< 0}} = -\left(\frac{R}{2L}\right) \pm j\sqrt{\left(\frac{1}{LC}\right) - \left(\frac{R}{2L}\right)^2}$$

$\zeta = \sqrt{-1}$

- $v_C(t) = V_{DD} + a_1 e^{-(R/2L)t} e^{j\sqrt{(1/LC) - (R/2L)^2}t} +$

$$a_2 e^{-(R/2L)t} e^{-j\sqrt{(1/LC) - (R/2L)^2}t}$$

α ω_d

$$e^{j[\dots]t}$$

"ω"


$$e^{j\omega t} + e^{-j\omega t}$$

Form of solution ...

$$v_C(t) = V_{DD} + [\dots] e^{-\alpha t} \cos(\omega_d t + \phi)$$

Qualitative Underdamped Waveform

$V_{DD} = 2.5V$

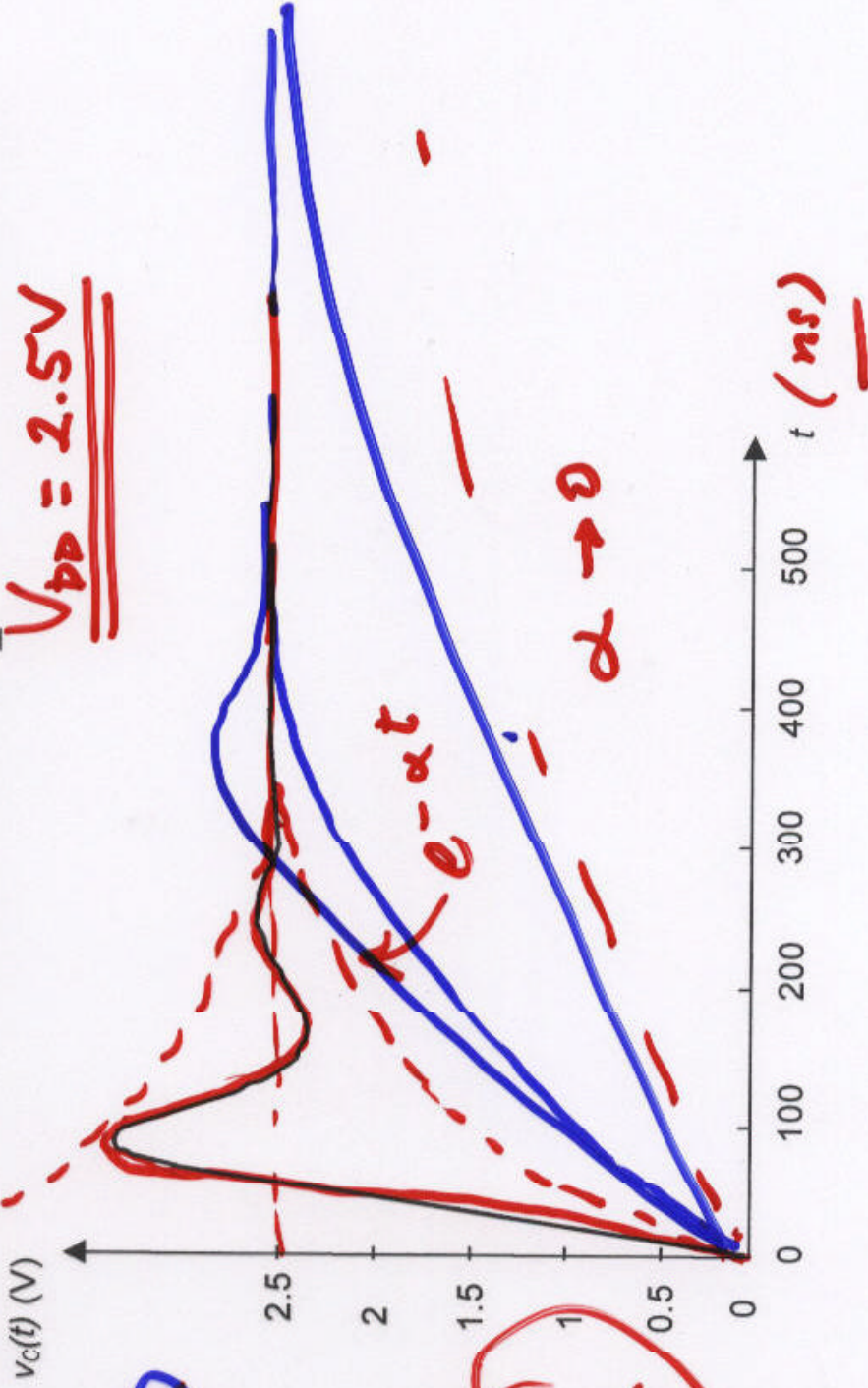

→ Extreme Underdamped Case

Exponential decay time is set by $\alpha = \underline{R/(2L)}$ $e^{-\alpha t}$
 $R \rightarrow 0$.


[Small $\underline{R/L}$ → decay takes a long time and oscillation has a frequency that's nearly $\sqrt{1/(LC)}$]

EE 142 ✓

Number of cycles during “ringdown” is


$$\bullet N \approx \frac{(1/\alpha)}{(1/\sqrt{1/(LC)})} = \frac{2L/R}{\sqrt{LC}} = \frac{2\sqrt{L}}{R\sqrt{C}}$$

What happens when $R = 0 \Omega$?

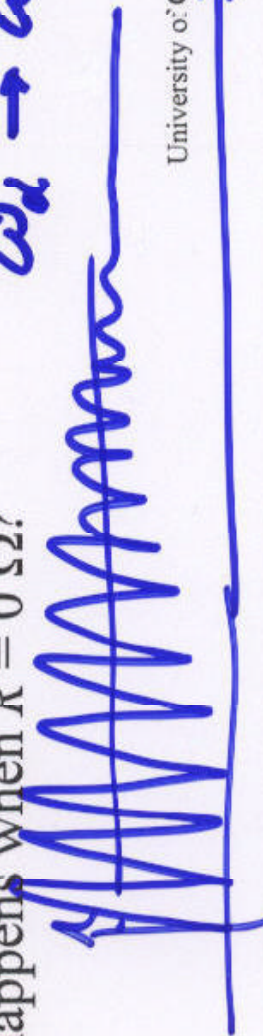 $\omega_d \rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$ ($R \rightarrow 0$)

R → O.
ELECTRO MECHANICAL OSCILLATOR.

thin-Film Bulk Acoustic Resonator (FBAR)

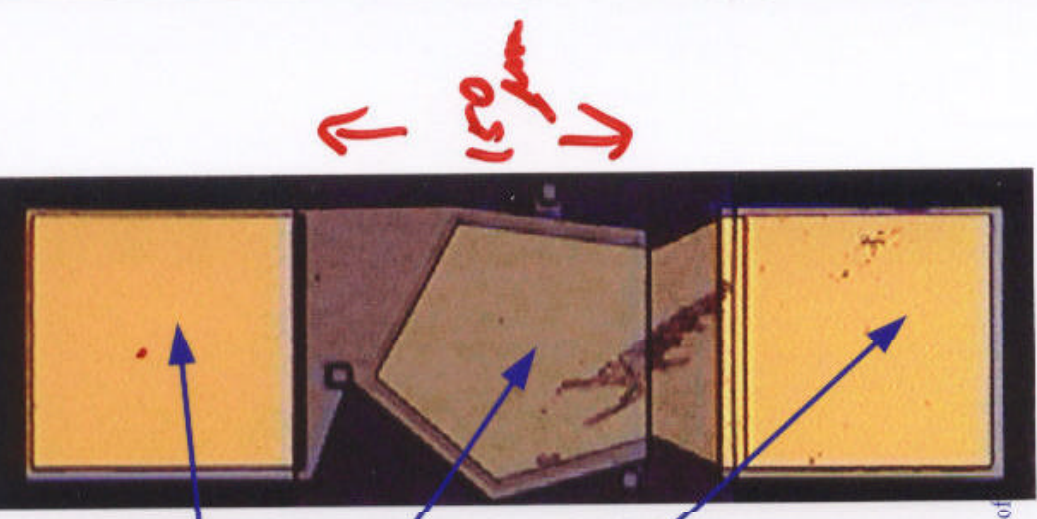


- **Rich Rube.**
- Agilent Technologies
- IEEE ISSCC 2001.
- 2 GHz resonator
- $N > 1000$
- Brian Otis, Jan Rabaey. low-noise oscillator (BWRC)
- Equivalent Circuit: ✓ ✓ ✓ ✓ ✓


Drive Electrode

Thin Piezoelectric Film
AlN

Sense Electrode

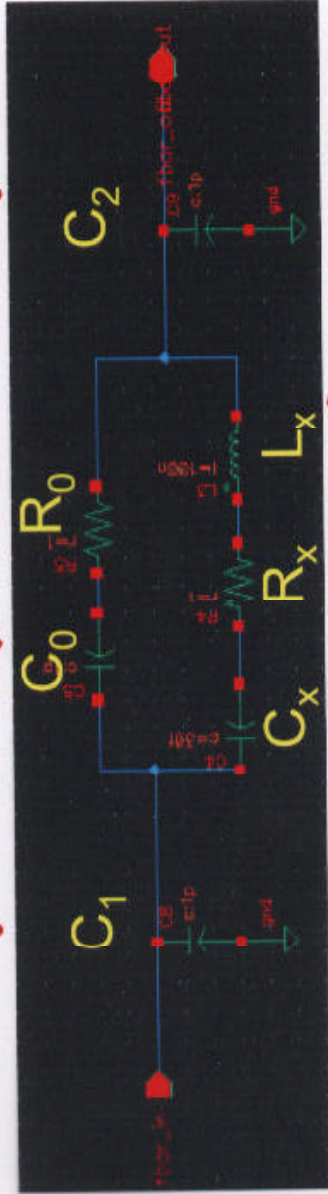

Phasor Analysis of 2nd Order Circuit

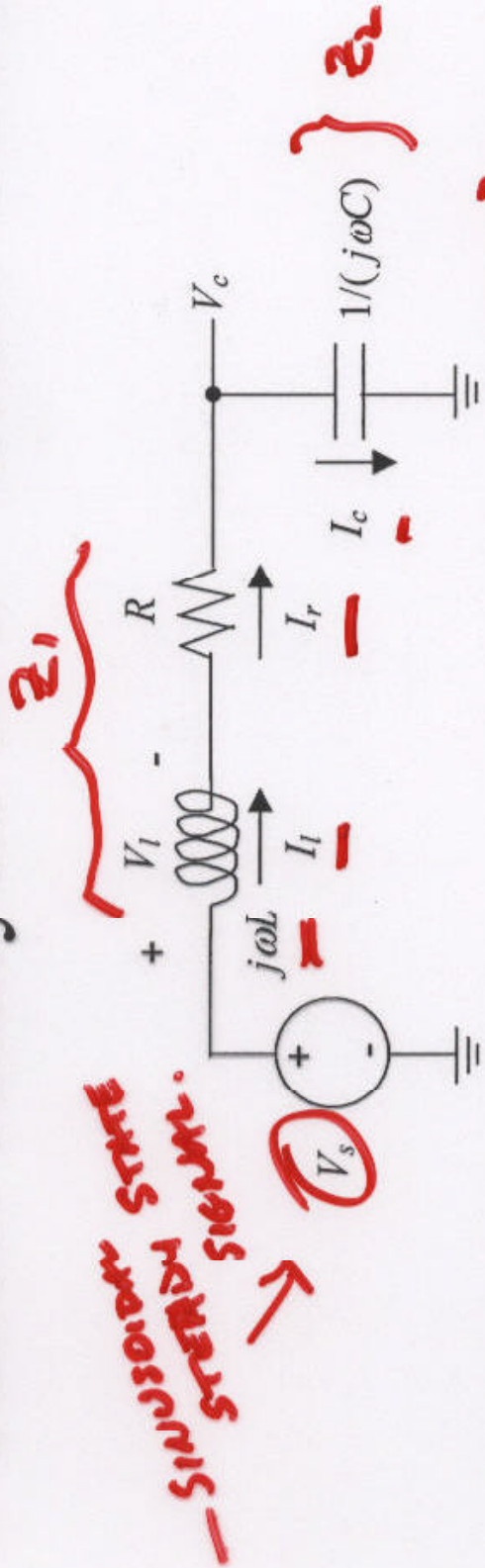

→ Impedance divider:

$$V_c = V_s \left(\frac{Z_2}{Z_1 + Z_2} \right)$$

$$V_c = V_s \left[\frac{1/j\omega C}{(1/j\omega C) + R + (j\omega L)} \right]$$

$$f^2 \omega^2 = LC$$

Transfer Function

Simplifying:

$$H(j\omega) = \left[\frac{1}{1 + j\omega RC - \omega^2 LC} \right]$$

Define parameters:

$$\omega_0 = 1/\sqrt{LC}$$

$$\tau = RC$$

**-NEW-
"STANDARD"
FORM"**

$$H(j\omega) = \left[\frac{1}{1 - (\omega/\omega_0)^2 + j\omega\tau} \right]$$

Limiting Cases: Magnitude and Phase

• Low frequency: $\omega \ll \omega_0$

$$|H|_{dB} = 0 \text{ dB} \quad (1)$$

$$\angle H = 0^\circ$$

• High frequency: $\omega \gg \omega_0$

$$|H|_{dB} = \left| \frac{1}{1 - (\omega/\omega_0)^2 + j2\zeta(\omega/\omega_0)} \right|_{dB}$$

$$\approx \left| \frac{1}{(\omega/\omega_0)^2} \right|_{dB}$$

"-40 dB/dec."

Resonant frequency: $\omega = \omega_0$

$$|H|_{dB} = \left| \frac{1}{K-1 + j2\zeta\tau} \right|_{dB}$$

$\omega = \omega_0$

$$= \left| \frac{1}{2\zeta\tau} \right|_{dB}$$

Dept of EECS

$$\angle H = -90^\circ$$

$$\angle H = \angle \frac{1}{1 - (\omega/\omega_0)^2 + j2\zeta(\omega/\omega_0)}$$

$$\lim_{\omega \rightarrow \infty} = \angle -(\cdot)$$

$$\underline{\underline{180^\circ!}}$$

• Inductor-Capacitor “Tuning”

At resonance, the impedance of the capacitor cancels the impedance of the inductor \rightarrow phasor current is maximum and capacitor voltage peaks


Fall 2001

\rightarrow How “sharp” or “narrow” is the resonance?

$\Delta\omega = \text{width of } 1/2 \text{ peak of transfer function}$

Define the quality factor $Q = \frac{\omega_0}{\Delta\omega}$

$Q = \frac{1}{\omega_0 \tau}$

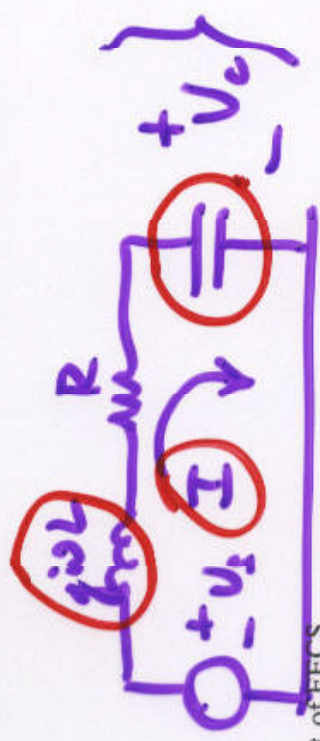

$\omega = \omega_0 = \frac{1}{\sqrt{LC}} \cdot N.$

$j\omega_0 L = j\sqrt{\frac{L}{C}} = j\sqrt{\frac{L}{C}}$

Dept of EECS

University of California at Berkeley

$Z_{in} = j\omega_0 L + R + \frac{1}{j\omega_0 C} = R.$


$$\omega = \omega_0 \dots$$

$$\frac{1}{j\omega_0 C} =$$

$$\frac{1}{j\sqrt{LC}} \cdot C$$


$$= -j \sqrt{\frac{C}{L}}$$
$$= \underline{\underline{-j}}$$

Magnitude Bode Plot

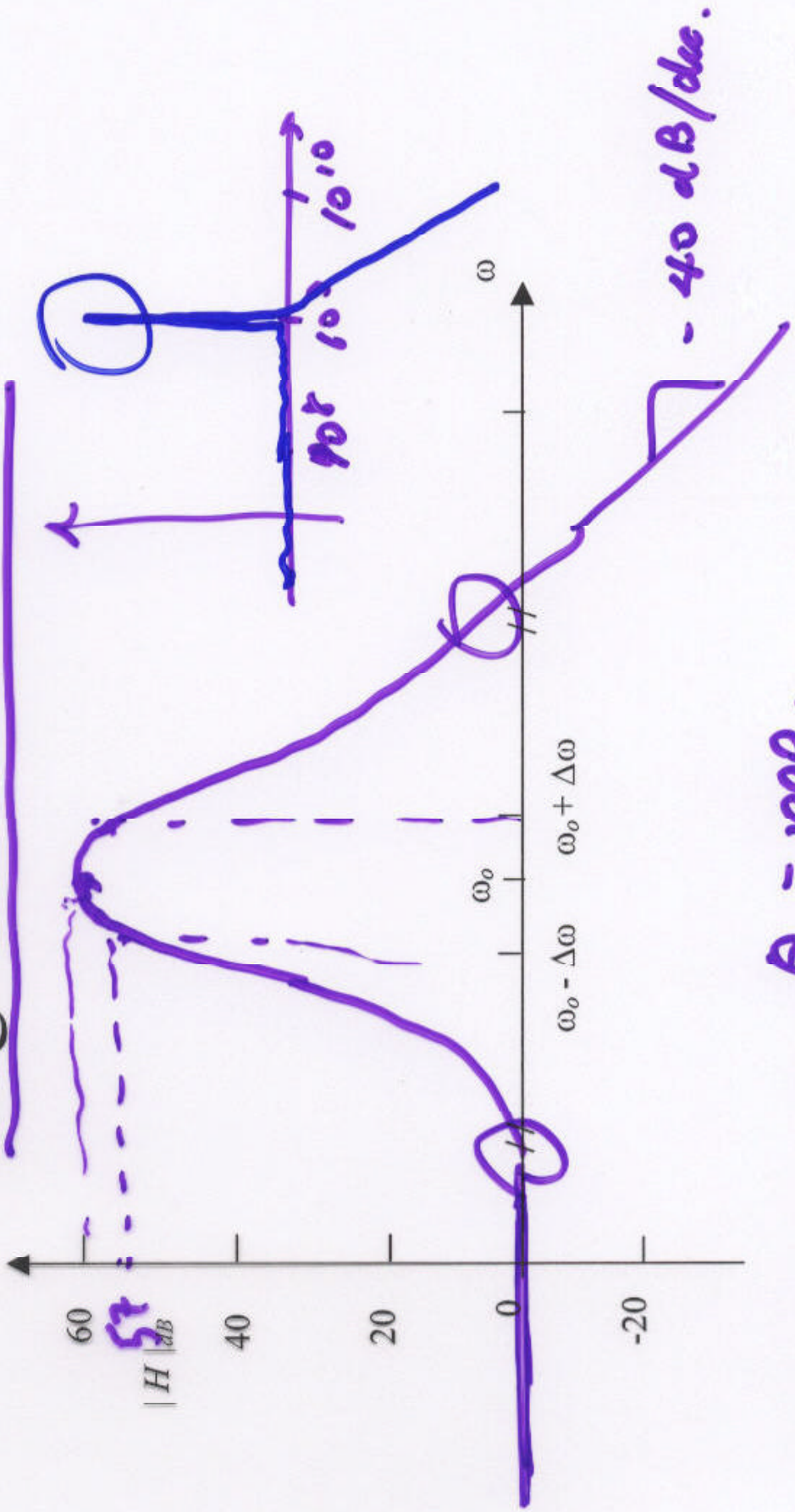

$Q = 1000$
 $|H| = 10Q = 60 dB$

Phase Bode Plot

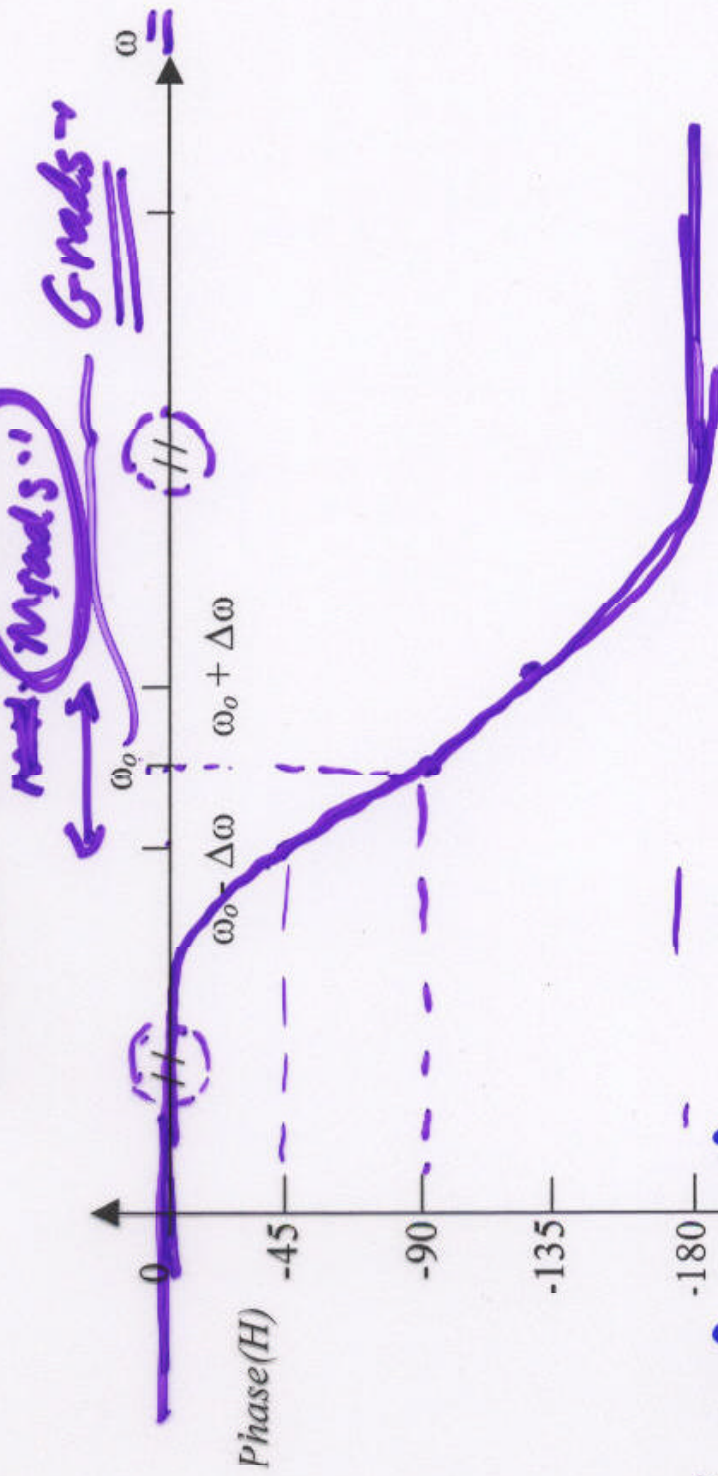

FBAR

$$Q = 1000$$

$$\Delta\omega = \frac{\omega_0}{Q} \dots$$

$$\omega_0 = 2\pi(2 \times 10^9) \text{ rads}^{-1}$$