

a) Find  $I_D$  given  $V_{GS} = 0.9V$ ,  $V_{DS} = 1V$

$$I_D = \mu_n V_{th} \left( \frac{w}{L_0(1 - KV_{DS})} \right) (4.95 \times 10^{-9} \text{C/cm}^2) e^{V_{GS} - V_t / V_{th}}$$

$$= (500 \text{cm}^2/\text{Vs})(0.026V) \left( \frac{45\mu\text{m}}{1.5\mu\text{m}(1 - 0.01(1))} \right) (4.95 \times 10^{-9} \text{C/cm}^2) e^{(0.9 - 1)/0.026}$$

$$\boxed{I_D = 41.7 \text{ nA}}$$

b) Transconductance

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{1}{V_{th}} \left( e^{(V_{GS} - V_t)/V_{th}} \right) \mu_n V_{th} \left( \frac{w}{L_0(1 - KV_{DS})} \right) (4.95 \times 10^{-9} \text{C/cm}^2)$$

$$\Rightarrow g_m = \frac{I_D}{V_{th}} = \frac{41.7 \times 10^{-9} \text{A}}{0.026V} = \boxed{1.60 \mu\text{S}}$$

this is just  $I_D$

c) Output Resistance

$$r_o = \left( \frac{\partial I_D}{\partial V_{DS}} \right)^{-1} \Rightarrow r_o^{-1} = \frac{\partial}{\partial V_{DS}} \left[ (1 - KV_{DS})^{-1} \left( \mu_n V_{th} \left( \frac{w}{L_0} \right) (4.95 \times 10^{-9} \text{C/cm}^2) e^{V_{GS} - V_t / V_{th}} \right) \right]$$

$$= -(1 - KV_{DS})^{-2} (-K) \left( \mu_n V_{th} \left( \frac{w}{L_0} \right) (4.95 \times 10^{-9} \text{C/cm}^2) e^{V_{GS} - V_t / V_{th}} \right)$$

$$= \frac{K}{(1 - KV_{DS})} \left( \mu_n V_{th} \left( \frac{w}{L_0(1 - KV_{DS})} \right) (4.95 \times 10^{-9} \text{C/cm}^2) e^{V_{GS} - V_t / V_{th}} \right)$$

this is just  $I_D$

$$\Rightarrow r_o^{-1} = \frac{K I_D}{1 - KV_{DS}} ;$$

$$r_o = \frac{1 - KV_{DS}}{K I_D} = \frac{1 - 0.01}{(0.01)(41.7 \text{ nA})} = \boxed{2.37 \text{ G}\Omega}$$

d)  $g_m r_o$  product:

$$g_m = \frac{I_D}{V_{th}} \text{ (from part b)} ; \quad r_o = \frac{1 - KV_{DS}}{K I_D} \text{ (from part c)}$$

$$\Rightarrow g_m r_o = \left( \frac{I_D}{V_{th}} \right) \left( \frac{1 - KV_{DS}}{K I_D} \right) = \boxed{\frac{1 - KV_{DS}}{V_{th}}} \quad \text{* NOTE that this product is independent of } I_D.$$

(stays constant so long as  $V_{DS}$  does)

2a)  $C_M$ : the depletion capacitance of the base-collector junction

- It's just a reverse-biased pn junction;

$$C_M = \frac{\epsilon_s A_c}{X_{bc}} \quad \left. \begin{array}{l} A_c = \text{area of base-collector junction interface} \\ X_{bc} = \text{depletion width of base-collector junction} \end{array} \right\}$$

From the cross-section:  $X_{bc} = 0.6 \mu\text{m}$

From the layout:  $A_c = (1.5 \mu\text{m} + 0.25 \mu\text{m})(2 \mu\text{m}) = 3.5 \times 10^{-8} \text{cm}^2$

$$C_M = \frac{(11.7 \times 8.85 \times 10^{-14} \text{F/cm})(3.5 \times 10^{-8} \text{cm}^2)}{0.6 \times 10^{-4} \text{cm}} = \boxed{0.604 \text{fF}}$$

b) By the law of the junction:


$$n_{pB}(x=0) = n_{pB0} e^{V_{BE}/V_{th}} \quad ; \quad n_{pB} = \text{concentration of electrons in p-type base}$$

$$n_{pB0} = \frac{n_i^2}{N_{dB}} \quad (\text{equilibrium concentration of electrons in p-type base})$$

$$n_{pB}(x=0.5) = 0$$

(since this is at the edge of the reverse-biased base-collector junction)

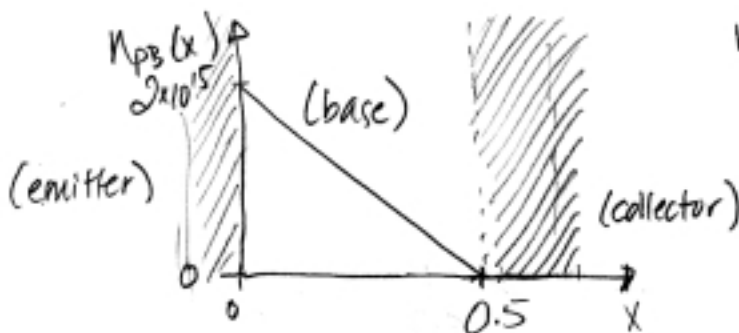And in between, the minority electron concentration falls linearly:



$$n_{pB0} = \frac{10^{20}}{10^6} = 10^4 \text{cm}^{-3}$$

$$n_{pB}(x=0) = 10^4 e^{650/26} = 2 \times 10^{15} \text{cm}^{-3}$$

A few things to note about this minority-carrier concentration plot:

1. At  $x=0.5$  micron, the concentration appears to go to zero. The actual value of at the depletion-region edge is equal to  $n_{pB0}$ , or  $10^4 \text{cm}^{-3}$ .
2. **But this doesn't matter:** by the law of the junction, the concentration at  $x=0$  is more than *ten orders of magnitude* greater. Keep in mind that what we really care about is the slope of this concentration plot; whether the value at  $x=0.5$  is 0 or  $10^4$  doesn't make a difference, since it is much less than the value at the other junction edge. So in the end, you can assume it is zero and still be ok.

3. a) To get  $V_{out} = 0V$  (large signal)

$I_{BIAS}$  must be  $-I_{RD}$  (the current through the resistor)

$$I_{RD} = \frac{5V - V_{out}}{R_D} = \frac{5V}{10k\Omega} = 500\mu A; \quad \boxed{I_{BIAS} = -500\mu A}$$

b) To remain in saturation:

$V_{DS} \geq V_{GS} - V_{TN}$ ;  $V_{DS} = V_{out} - V_S$ , but we also know  $V_S = V_G - V_{GS}$   
 so  $V_{DS} = V_{out} - (V_G - V_{GS}) = V_{out} + V_{GS}$  (since  $V_G$  is 0)

$$\Rightarrow (V_{out} + V_{GS}) \geq V_{GS} - V_{TN} \Rightarrow V_{out} \geq -V_{TN}$$

or:  $\boxed{V_{out, min} = -1V}$

c) To find  $R_m$ :

first, we recognise that this is just a common-gate amplifier;

$$R_m = \frac{1}{g_m}$$

$$g_m = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D} = \sqrt{2(50\mu A/V^2) \left(\frac{50}{2}\right) (500\mu A)} = 1.12 mS$$

$$\text{so } R_m = \frac{1}{1.12 mS} = \boxed{894\Omega}$$

d) To find transresistance: start w/ the CG small-signal model:



By Thevenin/Norton Equivalence:  $-A_i i_{in}(R_{out}) = R_m i_{in}$

$$\Rightarrow R_m = -A_i R_{out}$$

But since this is a CG amp, we know  $A_i = -1$

$$\Rightarrow R_m = R_{out}$$


So for a CG amp:

$$R_{out} = R_{up} \parallel R_{down} = R_D \parallel r_o(1 + g_m R_S)$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.05)(500\mu A)} = 40k\Omega; \quad R_{out} = 10k\Omega \parallel 488k\Omega \approx \boxed{10k\Omega = R_m}$$

3 e) Find  $\frac{V_{out}}{i_s}$  :

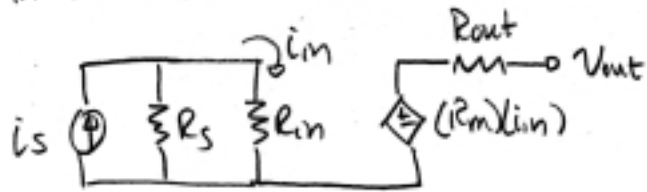Plug in this "new" transresistance model, and hook up the ~~sig~~ input  $i_s/R_s$



By the current-divider equation,  $i_{in} = i_s \left( \frac{R_s}{R_{in} + R_s} \right)$

$$V_{out} = R_{min} = R_m i_s \left( \frac{R_s}{R_{in} + R_s} \right)$$

$$\Rightarrow \frac{V_{out}}{i_s} = R_m \left( \frac{R_s}{R_{in} + R_s} \right) = (10 \text{ k}\Omega) \left( \frac{10 \text{ k}\Omega}{8945 \Omega + 10 \text{ k}\Omega} \right) = \boxed{9.18 \text{ k}\Omega}$$