

EE105 Lab Experiments

## Report 3: Bipolar Junction Transistor Characterization

Name:

Lab Section:

3.1 & 3.2 For each measurement of  $V_{BE}$ ,  $V_{BC}$ ,  $I_B$ , and  $I_C$ , fill in the corresponding entry in Table 1 and compute the resulting  $\beta$  and  $\alpha$ .

Parameters	Forward Active	Saturation	Cutoff	Reverse Active
$V_{BE}$				
$V_{BC}$				
$I_B$				
$I_C$				
$\beta$		N/A	N/A	
$\alpha$		N/A	N/A	

**Table 1:** Regions of operations and measurements

3.1.2 Measure  $V_{BE}$  and  $V_{BC}$ . What is the region of operation?

$V_{BE} =$

$V_{BC} =$

3.1.3 Measure  $I_B$  and compute  $\beta$ .

$I_B =$

$\beta =$

3.1.4 Calculate  $I_E$  using  $\alpha$  and measure  $I_E$ . Do the results agree?

(Calculated)   
 (Measured)

3.1.5 Measure  $I_B$  and  $I_C$  with your fingers around the BJT. How do the values compare to the values without heating the BJT?

3.1.6 Explain, using the equation you know for collector current, how you'd expect  $I_C$  to vary with temperature. Does this agree with your experimental results? If not, explain why this might be the case. *Hint:  $I_S$  depends on the intrinsic carrier concentration  $n_i$  and the diffusion coefficients  $D_n$  and  $D_p$ . Intuitively, how would  $n_i$ ,  $D_n$ , and  $D_p$  change with temperature? How would  $I_S$  change with temperature as a result?*

3.1.7 Does  $\beta$  agree with the value listed in the datasheet? If not, explain why you might see discrepancies.

3.1.8 Set  $V_{BB}$  to 4 V and  $V_{CC}$  to 2 V. Measure  $I_B$ ,  $I_C$ ,  $V_{BE}$ , and  $V_{BC}$ . What is the region of operation?

3.1.9 Set  $V_{BB}$  to  $-3$  V and  $V_{CC}$  to  $5$  V. Measure  $I_B$ ,  $I_C$ ,  $V_{BE}$ , and  $V_{BC}$ . What is the region of operation?





3.1.10 Swap the emitter and collector. Set  $V_{BB}$  to  $4$  V and keep  $V_{CC}$  at  $5$  V. Measure  $I_B$ ,  $I_C$ ,  $V_{BE}$ , and  $V_{BC}$ . What is the region of operation?





Use all of the data you've collected up to this point to fill out Table 1.

3.2.2 Attach the plot of the I-V curve to this worksheet. Label the two regions of operation and draw the boundary between them.

3.2.3 Use the I-V curve to determine  $V_A$ .

3.2.4 Repeat your calculation of  $V_A$  for base voltages of  $0.625$  V,  $0.65$  V,  $0.675$  V, and  $0.7$  V (you can step the base voltage in ICS to get this data). Does  $V_A$  depend on  $V_B$ ? Why?

$V_B$	$V_A$
0.600 V	
0.625 V	
0.650 V	
0.675 V	
0.700 V	

**Table 2:** Early voltage calculations

3.3.2 Attach the plot of the I-V curve to this worksheet. What semiconductor device does this I-V curve look like?

3.4.2 Measure  $I_{B1}$ ,  $I_{C1}$ ,  $I_{B2}$ , and  $I_{C2}$ . Calculate  $\beta_1$  and  $\beta_2$ .

$I_{B1} =$
$I_{C1} =$
$I_{B2} =$
$I_{C2} =$
$\beta_1 =$
$\beta_2 =$

3.4.3 What is the overall current gain,  $\beta_{tot}$ ? Use the formula you derived in the prelab to calculate the total current gain from  $\beta_1$  and  $\beta_2$  and compare the calculation to your measurement.

(Measured)	$\beta_{tot} =$
(Calculated)	$\beta_{tot} =$