

Use the device parameters from the handout and spice level 1 model

- 1) For the circuit in figure 1, assume that W/L for all devices is $100\mu\text{m}/1\mu\text{m}$, and I_{ref} is 1mA
 - a) Calculate the expected output resistance and turn-on voltage.
 - b) Use SPICE to plot I_{out} vs. V_{out} , and use expression-builder in awaves to plot the output resistance as a function of output voltage.
- 2) For the circuit in figure 2, assume that W/L for all devices is $100\mu\text{m}/1\mu\text{m}$, and I_{ref} is 1mA
 - a) Calculate the minimum value for V_{BN} for which all transistors will be in saturation, and calculate the resulting turn-on voltage for the current source and its output resistance.
 - b) Use SPICE to plot the output current vs. V_{BN} for $V_{\text{out}} = 2\text{V}$. Make another current sink (identical copy of M1 and M2) and bias its output at $V_{\text{out}2} = 3\text{V}$. Use the difference between the two output currents to plot the output resistance as a function of V_{BN} .
 - c) Make a table with the calculated and simulated values for the output resistance and turn-on voltage of each of the current sources in problems 1 and 2. Which current source gives the best performance? Why?
- 3) Generate V_{BN} from part 2a using a diode-connected NMOSFET and another 1mA current. Verify that the bias voltage, turn-on voltage, and output resistance are what you expect.
- 4) For the circuit in figure 3, assume that the current source has a finite output resistance R_L , and that the MOSFETs are identical.
 - a) Write an expression for the four small signal gains: from the two inputs to the two outputs.
Assume that the current source is 1mA , and the devices are $100\mu\text{m}/1\mu\text{m}$:
 - b) Calculate the four small-signal gains assuming that the current source is made with a PMOSFET with an output resistance equal to the NMOS devices.
 - c) Calculate the four small-signal gains assuming that the current source is made with a PMOS cascode with an output resistance equal to the NMOS cascode output resistance.
- 5) Design a telescopic cascode amplifier to pull no more than 1mW of power from a 5V supply with a gain of at least $10,000$. Draw a schematic of your amplifier and label all transistors with their sizes, bias conditions, and small-signal parameters. What is the input common mode range of your amplifier? Estimate the pole frequency and unity gain frequency with no load, and with a 10pF load. Use SPICE to calculate the phase margin with no load, and with a 10pF load, and label the plots with your estimated frequencies. Will the amplifier be stable in unity gain feedback in both cases?

