

EECS140

Solution Fall '09

HW4, due Thursday 9/24 at 8am

(This was Midterm 1, Spring 2008)

Name \_\_\_\_\_

SID \_\_\_\_\_

Prob.	Score
1	/10
2	/30
3	/20
4	/15
5	/25
Total	

1) Fill in the following table. Do NOT use a calculator!

dB	Power ratio
13	$10 \times 2 = 20$
-7	$\frac{1}{10} \times 2 = 0.2$
16	$10 \times 2 \times 2 = 40$
-1	$0.2 \times 2 \times 2 = 0.8$
-9	$0.5 \times 0.5 \times 0.5 = 0.125$
1	$10/8 = 1.25$
17	$100/2 = 50$
4	$10/4 = 2.5$
-14	$\frac{1}{120} \times 2 \times 2 = 0.04$

$$\because 13\text{dB} = 10\text{dB} + 3\text{dB}$$

$$\because -7\text{dB} = -10\text{dB} + 3\text{dB}$$

$$\because 16\text{dB} = 10\text{dB} + 3\text{dB} + 3\text{dB}$$

$$\because -1\text{dB} = -7\text{dB} + 3\text{dB} + 3\text{dB}$$

$$\because -9\text{dB} = -3\text{dB} - 6\text{dB}$$

$$\because 1\text{dB} = 10\text{dB} - 9\text{dB}$$

$$\because 17\text{dB} = 20\text{dB} - 3\text{dB}$$

$$\because 4\text{dB} = 10\text{dB} - 6\text{dB}$$

$$\because -14\text{dB} = -20\text{dB} + 6\text{dB}$$

(If you include this factor, you would have got slightly smaller  $L \neq W$ , which is also acceptable.)

2) Design an NMOS-input common source amplifier with a PMOS load with a low frequency gain of approximately 200, a unity gain frequency of 1G rad/sec with a 1pF load, and an output swing of at least 500mV to 2V with a 2.5V single-sided supply. Clearly indicate what values you are using for  $g_m$ ,  $r_o$ ,  $I_D$ ,  $V_{dsat}$ , gate bias,  $W$ ,  $L$  for each transistor. Assume our standard process model.  $(1 + \lambda V_{DS}) \approx 1$  is assumed.

	$g_m$	$r_o$	$I_D$	$V_{dsat}$	$V_G$	$W$	$L$
NMOS	1mS	400kΩ	250μA	0.5V	1V	100μm	10μm
			100μA	0.2V	0.7V	100μm	4μm
			50μA	0.1V	0.6V	100μm	2μm
PMOS	1mS	400kΩ	250μA	0.5V	1.5V	200μm	10μm
			100μA	0.2V	1.8V	200μm	4μm
			50μA	0.1V	1.9V	200μm	2μm

There are countless number of ways to meet the specification. You'll get the full point as long as your design satisfies the following equations.

spec.  
 $A_v = 200$   
 $C_L = 1pF$   
 $\omega_u = 1Grad/s$   
 $V_{OSAT} \leq 500mV$

-  $\omega_u = A_v \cdot \omega_p = \frac{g_m R_o}{R_o \cdot C_L}$   
 $\Rightarrow g_m = 1mS$   
 $\Rightarrow R_{int} = \frac{A_v}{g_m} = 200k$

$r_{on} \approx r_{op} = 400k$  (You can choose other values as long as  $(r_{on} || r_{op}) = 200k$ )

Now, you need to pick either  $V_{OSAT}$  or  $I_D$ . Let's fix  $V_{OSAT}$  first,

$I_D = \frac{g_m \cdot V_{OSAT}}{2}$ ,  $V_{G,n} = V_{OSAT} + V_{t,n}$ ,  $V_{G,p} = 2.5 - (V_{OSAT} + V_{t,p})$

$\lambda = \frac{1}{r_o I_D} = \frac{1}{L(\mu m)}$ ,  $\therefore L = r_o I_D$

$(\frac{W}{L}) = \frac{g_m}{\mu_n C_{ox} V_{OSAT}}$ ,  $\therefore W = \frac{g_m \cdot L}{\mu_n C_{ox} V_{OSAT}}$

Some example design values are given in the table.

3) Fill in the following table where each row is a different single-pole amplifier

$G_m$ [S]	$R_o$ [ $\Omega$ ]	$C_L$ [F]	$A_v$	$\omega_p$ [rad/s]	$\omega_u$ [rad/s]
50u	1M	50f	$50\mu \cdot 1M$ = 50	$\frac{1}{1M \cdot 50f}$ = 20M	$50 \cdot 20M$ = 1G
$\frac{200}{200K}$ = 0.8m	$\frac{1}{40M \cdot 100f}$ = 250K	100f	200	40M	$200 \cdot 40M$ = 8G
30m	$\frac{150}{30m}$ = 5K	$\frac{30m}{15G}$ = 2p	150	$\frac{15G}{150}$ = 100M	15G
$\frac{500}{1M}$ = 0.5m	1M	$\frac{1}{11M \cdot 50M}$ = 20f	$\frac{25G}{50M}$ = 500	50M	25G


$$A_v = G_m \cdot R_o$$

$$\omega_p = \frac{1}{R_o \cdot C_L}$$

$$\omega_u = A_v \cdot \omega_p = \frac{g_m}{C_L}$$


4) You have a single-pole amplifier with a gain of 20 at 200MHz, and a low frequency gain of 1000. What is the gain at 100kHz, 10MHz, and 2GHz?

Frequency	Gain
100kHz	1000
10MHz	$20 \times \left(\frac{200M}{10M}\right) = 400$
2GHz	$1 \times \left(\frac{4G}{2G}\right) = 2$

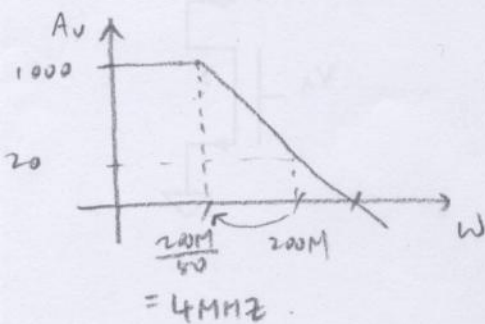

5) What is the total low frequency impedance and the low frequency impedance seen "looking up" and "looking down" at the output node indicated in each circuit? Write your answer in terms of  $g_{mp}$ ,  $g_{mn}$ ,  $r_{on}$ , and  $r_{op}$ . Assume that all nmos devices have transconductance  $g_{mn}$  and output resistance  $r_{on}$ , and all pmos devices have transconductance  $g_{mp}$  and output resistance  $r_{op}$ . Write the full expression for up and down, and then the simplified total impedance assuming that  $g_m \cdot r_o \gg 1$  for all combinations of  $g_m$  and  $r_o$ . You may ignore all capacitors.

	Full expression	Simplified expression for $R_o$ , assuming $g_m r_o \gg 1$
$R_{o1, up}$	$\frac{1}{g_{mn}} \parallel r_{on}$	$\frac{1}{g_{mn}} \parallel \frac{1}{g_{mp}}$ $= \frac{1}{g_{mn} + g_{mp}}$
$R_{o1, down}$	$\frac{1}{g_{mp}} \parallel r_{op}$	
$R_{o2, up}$	$r_{op}$	$r_{op}$
$R_{o2, down}$	$r_{on} + r_{op} + g_{mn} \cdot r_{on}^2$	
$R_{o3, up}$	$\frac{r_{on} + r_{op}}{1 + g_{mn} r_{on}} = \frac{1}{g_{mn}} \left( \frac{r_{on} + r_{op}}{\frac{1}{g_{mn}} + r_{on}} \right)$	$r_{on} \parallel \frac{1}{g_{mn}} \left( \frac{1 + \frac{r_{op}}{r_{on}}}{1 + \frac{1}{g_{mn} r_{on}}} \right) \approx r_{on} \parallel \frac{1}{g_{mn}} \left( 1 + \frac{r_{op}}{r_{on}} \right)$
$R_{o3, down}$	$r_{on}$	
$R_{o4, up}$	$\infty$	$g_{mn} \cdot r_{on} \cdot g_{mn} \cdot r_{on}^2$ $= g_{mn}^2 r_{on}^3$
$R_{o4, down}$	$r_{on} + R_{o2, down} + g_{mn} \cdot r_{on} \cdot R_{o2, down}$	

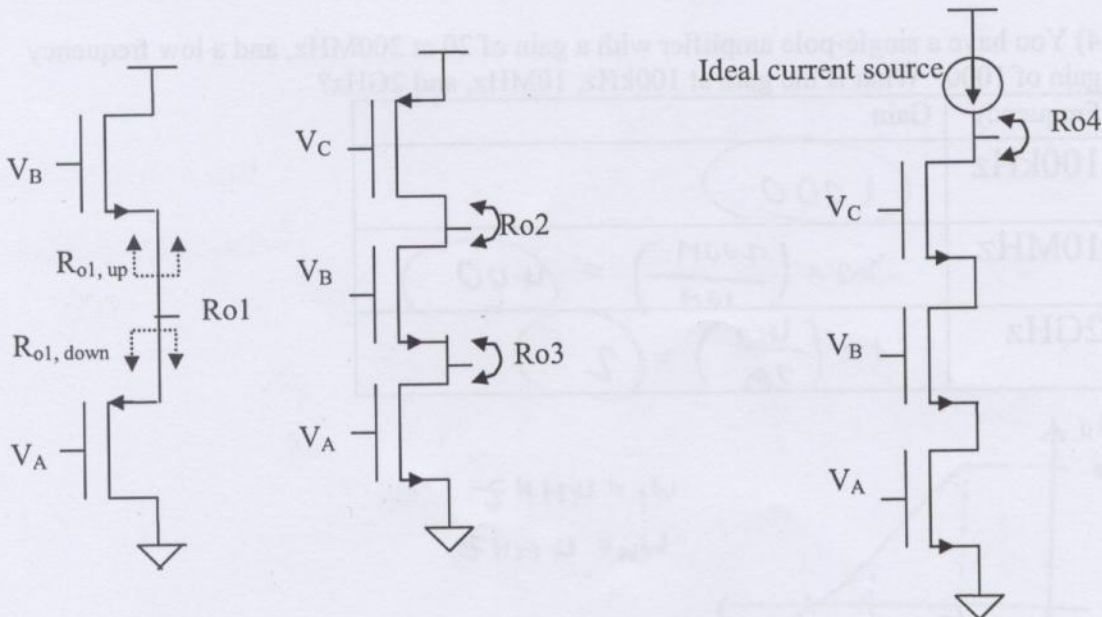

[prob. 6]

(1) Node A:  $G_m = g_{mn}$   
 $R_{o3} \approx r_{on} \parallel \frac{1}{g_{mn}} \left(1 + \frac{r_{op}}{r_{on}}\right)$

$$A_{v,A \rightarrow o3} = -G_m R_{o3}$$

$$\therefore C_m = C_{gs} + C_{gd} \left[ 1 + g_{mn} \left( r_{on} \parallel \frac{1}{g_{mn}} \left( 1 + \frac{r_{op}}{r_{on}} \right) \right) \right]$$

If we assume that  $r_{on} \approx r_{op}$ ,  $r_{on} \gg \frac{1}{g_{mn}}$ ,

$$\begin{aligned} C_m &\approx C_{gs} + C_{gd} \left( 1 + g_{mn} \cdot \frac{2}{g_{mn}} \right) \\ &= C_{gs} + 3C_{gd} \end{aligned}$$

(2) Node B:

see appendix for derivation

$G_{m,B \rightarrow o3} = \frac{g_{mn} r_{on}}{r_{on} + r_{op}}$	$G_{m,B \rightarrow o2} = \frac{-g_{mn}}{2 + g_{mn} r_{on}}$
$R_{o,B \rightarrow o3} = \frac{r_{on} + r_{op}}{2 + g_{mn} r_{on} + \frac{r_{op}}{r_{on}}}$	$R_{o,B \rightarrow o2} \approx r_{op}$
$A_{v,B \rightarrow o3} = \frac{g_{mn} r_{on}}{2 + g_{mn} r_{on} + \frac{r_{op}}{r_{on}}}$	$A_{v,B \rightarrow o2} = \frac{-g_{mn} r_{op}}{2 + g_{mn} r_{on}}$

$$\begin{aligned} \therefore C_m &= (1 - A_{v,B \rightarrow o3}) C_{gs} + (1 - A_{v,B \rightarrow o2}) C_{gd} \\ &= \left( \frac{2 + \frac{r_{op}}{r_{on}}}{2 + g_{mn} r_{on} + \frac{r_{op}}{r_{on}}} \right) C_{gs} + \left( \frac{2 + g_{mn} (r_{on} + r_{op})}{2 + g_{mn} r_{on}} \right) C_{gd} \end{aligned}$$

If we assume  $r_{on} \approx r_{op}$ ,  $g_{mn} r_{on} \gg 1$ ,

$$C_m \approx 2C_{gd}$$

(3) Node C:  $G_m = g_{mp}$   $A_{v,C \rightarrow o2} = -g_{mp} r_{op}$   
 $R_{o2} \approx r_{op}$

$$\therefore C_m = C_{gs} + (1 + g_{mp} r_{op}) C_{gd}$$

[prob. 7] Above  $w_u$

(1) Node A :  $A_{v,A \rightarrow 02} \rightarrow 0$

$$\therefore C_m \approx \underline{C_{gs} + C_{gd}}$$

(2) Node B :  $A_{v,B \rightarrow 02}, A_{v,B \rightarrow 03} \rightarrow 0$

$$\therefore C_m \approx \underline{C_{gs} + C_{gd}}$$

(3) Node C :  $A_{v,C \rightarrow 02} \rightarrow 0$

$$\therefore C_m \approx \underline{C_{gs} + C_{gd}}$$

[prob. 8]

$$A_v = -27 \text{ (mid-range gain)}$$

$$C_{gs} = \frac{2}{3} W L C_{ox} + W \cdot C_{ox}'$$

$$= \frac{2}{3} \times 100 \mu\text{m} \times 1 \mu\text{m} \times 5 \text{ fF}/\mu\text{m}^2 + 100 \mu\text{m} \cdot 0.5 \text{ fF}/\mu\text{m}$$

$$= 333.33 \text{ fF} + 50.0 \text{ fF} = \underline{383.3 \text{ fF}}$$

$$C_{gd} = W \cdot C_{ox}' = \underline{50.0 \text{ fF}}$$

(1) low frequency approximation

$$C_m = C_{gs} + (1 - A_v) C_{gd}$$

$$= 383.3 \text{ fF} + 28 \times 50.0 \text{ fF}$$

$$= 383.3 \text{ fF} + 1400.0 \text{ fF}$$

$$= \underline{1783.3 \text{ fF}} \quad \left( \text{overlap capacitance of } C_{gd} \text{ dominates the overall cap.} \right)$$


(2) high freq. approx

$$C_m \approx C_{gs} + C_{gd}$$

$$= \underline{433.3 \text{ fF}}$$



[prob. 9]

- low frequency  $C_m = 1.8 \text{ pF}$

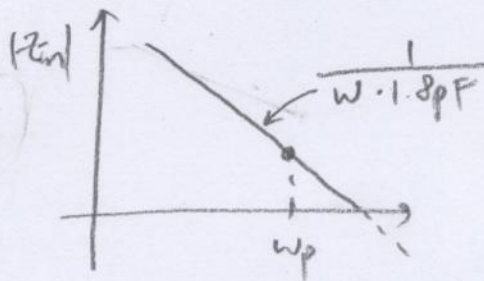

- high freq.  $C_m \approx 430 \text{ fF}$ .  $\times 4$  lower C


so,  $\times 4$  higher  $|Z|$

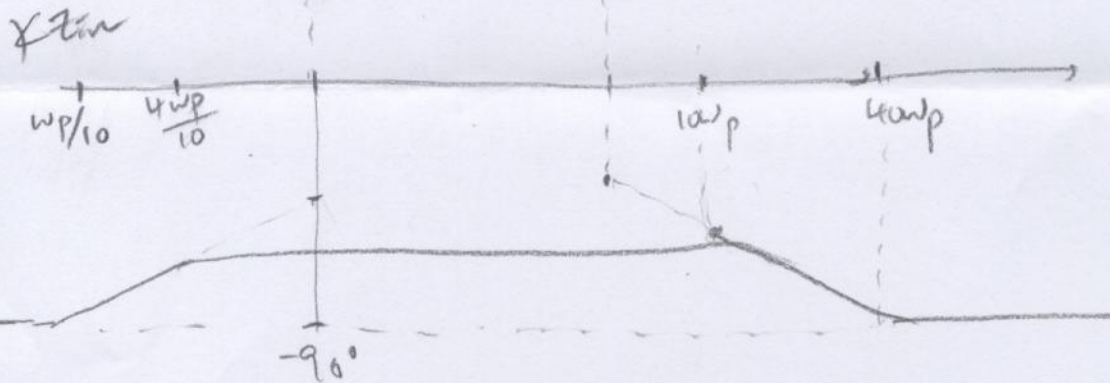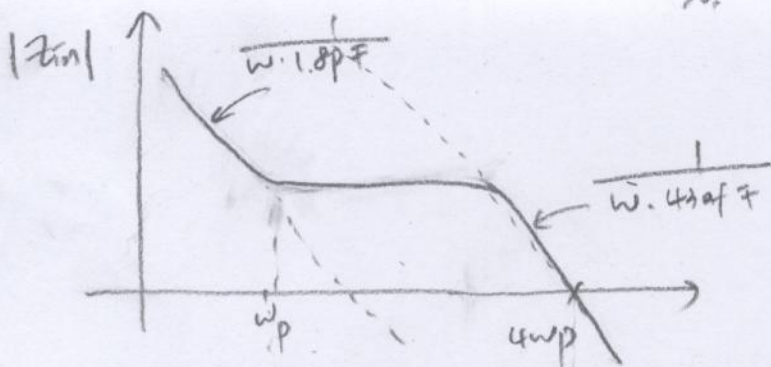

# Appendix

← probb. Node B gain derivation →

(1) B → 03

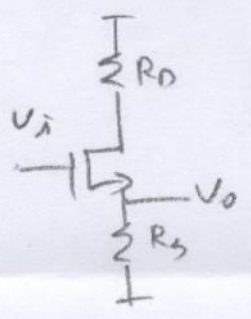

$$G_m = \frac{g_m}{1 + \frac{R_D}{r_o}} = \frac{g_m r_o}{r_o + R_D}$$

$$R_o = \frac{r_o + R_D}{1 + g_m r_o} \parallel R_S = \frac{R_S (r_o + R_D)}{R_S (1 + g_m r_o) + r_o + R_D}$$


$$A_v = \frac{g_m R_S}{1 + g_m R_S + \frac{R_S + R_D}{r_o}}$$

\* If,  $\frac{R_S + R_D}{r_o} \ll 1$ ,  $A_v \approx \frac{g_m R_S}{1 + g_m R_S}$

\* In probb,  $R_S = r_{on}$ ,  $R_D = r_{op}$ ,  $g_m = g_{m1}$ ,  $r_o = r_{o1}$

$$\therefore A_v = \frac{g_{m1} r_{on}}{2 + g_{m1} r_{on} + \frac{r_{op}}{r_{on}}}$$

(2) B → 02

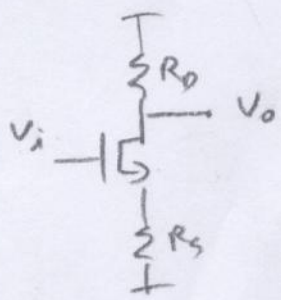

$$G_m = \frac{-g_m}{1 + g_m R_S + \frac{R_S}{r_o}}$$

$$R_o = (r_o + R_S + g_m r_o R_S) \parallel R_D \approx R_D$$

$$A_v = \frac{-g_m R_D}{1 + g_m R_S + \frac{R_S}{r_o}}$$

\* If,  $\frac{R_S}{r_o} \ll 1$ ,  $A_v = \frac{g_m R_D}{1 + g_m R_S}$

\* In probb,  $R_S = r_{on}$ ,  $R_D = r_{op}$ ,  $g_m = g_{m1}$ ,  $r_o = r_{o1}$

$$\therefore A_v = \frac{-g_{m1} r_{op}}{2 + g_{m1} r_{on}}$$