

Lecture 10: Supply & Temperature Indep. Biasing

• **Announcements:**

- ↪ HW#4 due tomorrow at 8 a.m.
- ↪ HW#5 online soon
- ↪ Lab#1 reports are due on Oct. 5
 - Submit them in your lab section
- ↪ Lab#2 is online
 - This is a hardware lab
 - You must show up to lab for Lab#2
- ↪ Videos online in the lecture chart


• **Lecture Topics:**

- ↪ Supply & Temperature Independent Biasing
- ↪ Output Swing
- ↪ Dynamic Range

• **Last Time:** Started supply independent biasing

over

Widlar Current Source (Any better?)

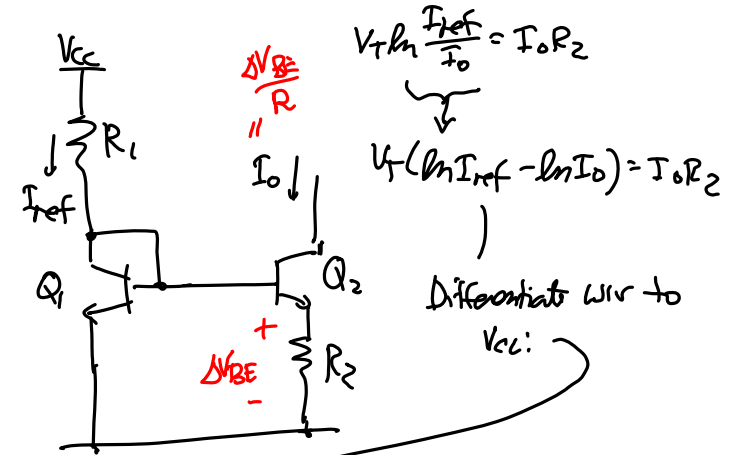

$$\rightarrow V_T \left(\frac{1}{I_{ref}} \frac{\partial I_{ref}}{\partial V_{cc}} - \frac{1}{I_o} \frac{\partial I_o}{\partial V_{cc}} \right) = R_2 \frac{\partial I_o}{\partial V_{cc}}$$

↓ rearrange

$$\frac{\partial I_o}{\partial V_{cc}} = \frac{V_T}{I_{ref}} \frac{\partial I_{ref}}{\partial V_{cc}}$$

$$\left(R_2 + \frac{V_T}{I_o} \right)$$

$$\therefore S_{V_{cc}}^{I_o} = \frac{V_{cc}}{I_o} \frac{\partial I_o}{\partial V_{cc}} = \frac{V_T \left(\frac{V_{cc}}{I_{ref}} \frac{\partial I_{ref}}{\partial V_{cc}} \right)}{I_o R_2 + V_T}$$

$$\Rightarrow S_{V_{cc}}^{I_o} = \left(\frac{1}{1 + \frac{I_o R_2}{V_T}} \right) S_{V_{cc}}^{I_{ref}}$$

Since $I_{ref} = \frac{V_{CC} - V_{BE(m)}}{R_1} \approx \frac{V_{CC}}{R_1} \Rightarrow S_{V_{CC}}^{I_{ref}} \approx 1$

$$\therefore S_{V_{CC}}^{I_0} = \frac{1}{1 + \frac{I_0 R_2}{V_T}}$$

For $I_{ref} = 1\text{mA}$, $I_0 = 10\mu\text{A}$, $R_2 = 11.9\text{k}\Omega$, then

10% Δ in $V_{CC} \rightarrow 1.3\%$ Δ in I_0

(better than a simple current source)

How can we do better? \rightarrow use another voltage reference!

- ✓ ① $V_{BE(m)}$ \rightarrow bcp emth junction voltage
- ✓ ② $V_Z \rightarrow$ Zener diode
- ✓ ③ $V_t \rightarrow$ threshold voltage (MOS)
- ✓ ④ $V_T = \frac{kT}{q} \rightarrow$ thermal voltage
- ✓ ⑤ $E_g \rightarrow$ bandgap



V_{BE}-Referenced Biasing

$I_{ref} = \frac{V_{CC} - 2V_{BE(m)}}{R_1} \Rightarrow S_{V_{CC}}^{I_{ref}} = 1$

$I_0 = \frac{V_{BE1}}{R_2} = \frac{V_T}{R_2} \ln \frac{I_{ref}}{I_{S1}}$

$\frac{\partial I_0}{\partial V_{CC}} = \frac{V_T}{R_2} \left(\frac{1}{I_{ref}} \frac{\partial I_{ref}}{\partial V_{CC}} - \frac{1}{I_{S1}} \frac{\partial I_{S1}}{\partial V_{CC}} \right)$

$S_{V_{CC}}^{I_0} = \frac{V_{CC}}{I_0} \frac{\partial I_0}{\partial V_{CC}} = \frac{V_{CC}}{\ln(I_{ref}/I_{S1})} \left(\frac{1}{I_{ref}} \frac{\partial I_{ref}}{\partial V_{CC}} - \frac{1}{I_{S1}} \frac{\partial I_{S1}}{\partial V_{CC}} \right) = \frac{1}{V_{CC}}$

Problem: I_{ref} still depends on V_{CC}

$S_{V_{CC}}^{I_{ref}} = 1 = \frac{V_{CC}}{I_{ref}} \frac{\partial I_{ref}}{\partial V_{CC}}$

$S_{V_{CC}}^{I_0} = \frac{1}{\ln(I_{ref}/I_{S1})} \left[1 - \frac{V_{CC}}{I_0} \frac{\partial I_{S1}}{\partial V_{CC}} \right] = \frac{1}{\ln(I_{ref}/I_{S1})}$

0

If we can eliminate this '1', then $S_{V_{CC}}^{I_0} = 0$

Need to eliminate the dependence of I_{ref} on V_{CC} !

Solution: Derive I_{ref} independently of V_{CC}
 ↳ use self-biasing!

Graphically: Use startup ckt. to drive operation to here

$I_0 = \frac{V_T}{R_2} \ln \frac{I_{ref}}{I_S}$

$I_0 = I_{ref}$ gets shift in bias pt.

depends on V_{CC}
 ↳ because $V_{CE3} \neq V_{CE4}$

$V_{CE3} = V_{CC} - 2V_{BE(m)} + \Delta V_{CC} \rightarrow \Delta V_{CE3} = \Delta V_{CC}$

$I_{ref} = I_S \exp\left(\frac{V_{BE3}}{V_T}\right) \left(1 + \frac{V_{CE3}}{V_A}\right)$

$\therefore I_{ref} = f(V_{CC}) \neq I_0$
 $\therefore S_{V_{CC}}^{I_0} \neq 0$, but it's close

$V_{CE3} = V_{CC} - 2V_{BE(m)} + \Delta V_{CC}$
 $|V_{CE4}| = |V_{BE4}|$
 $I_0 \neq I_{ref}$ (but it's close)

$I_{ref} \downarrow$ mirror $2V_{BE(m)}$
 $I_0 = I_{ref}$

V_{BE1}
 V_{BE1}
 V_{BE1}

$I_{ref} \rightarrow I_0$
 $S_{V_{CC}}^{I_{ref}} \rightarrow S_{V_{CC}}^{I_0} \approx 0$

Pretty Damn Good!

$V_{CC} + \Delta V_{CC}$

$|V_{CE4}| = |V_{BE4(m)}| \leftarrow$ stays still

$I_0 = I_S \exp\left(\frac{V_{BE4}}{V_T}\right) \left(1 + \frac{V_{CE4}}{V_A}\right)$
 $\Delta V_{CE4} = 0$

$V_{CE3} = V_{CC} - 2V_{BE(m)} + \Delta V_{CC} \rightarrow \Delta V_{CE3} = \Delta V_{CC}$

$I_{ref} = I_S \exp\left(\frac{V_{BE3}}{V_T}\right) \left(1 + \frac{V_{CE3}}{V_A}\right)$

$\therefore I_{ref} = f(V_{CC}) \neq I_0$
 $\therefore S_{V_{CC}}^{I_0} \neq 0$, but it's close

↳ Can we do better?

Want $|V_{CE3}| = V_{CC}$ clamped $\neq f(V_{CC})$ holds V_{CC} just like

$V_{BE(m)}$
 $V_{BE(m)}$
 $V_{BE(m)}$

These not current

$V_{CC} - V_{BE(m)}$
 $V_{CC} - 2V_{BE(m)}$
 $I_0 = I_{ref}$

\therefore w/ $|V_{CE3}|$ & $|V_{CE4}|$ clamped $\rightarrow S_{V_{CC}}^{I_0} = 0$

Determine Temperature Dependence of the V_{BE-REF}

Define: Fractional Temperature Coefficient
 $TC_f = \frac{1}{I_0} \frac{\partial I_0}{\partial T}$ [ppm/K]
 temperature parts per million (same as 10^{-6})

For $I_0 = \frac{V_{BE}}{R}$:

$$TC_f = \frac{1}{I_0} \frac{\partial I_0}{\partial T} = \frac{R}{V_{BE}} \left(\frac{1}{R} \frac{\partial V_{BE}}{\partial T} - \frac{V_{BE}}{R^2} \frac{\partial R}{\partial T} \right)$$


$$\therefore TC_f = \underbrace{\frac{1}{V_{BE}} \frac{\partial V_{BE}}{\partial T}}_{TC_f/V_{BE}} - \underbrace{\frac{1}{R} \frac{\partial R}{\partial T}}_{TC_f/R}$$

Some Typical TC_f 's:

- Diffused R's $\sim 1000 - 1500$ ppm/ $^{\circ}C$
- poly Si R's ~ 500 ppm/ $^{\circ}C$
- $V_{BE} \sim -3300$ ppm/ $^{\circ}C$
- $TC_f \sim -3300 - 1000$
 $= -4300$ ppm/ $^{\circ}C \sim 0.43\%$ / $^{\circ}C$
- $0 \rightarrow 70^{\circ}C$: $\sim 25\%$ I_0 variation
- $-55 \rightarrow 125^{\circ}C$: $\sim 60-70\%$ I_0 variation
- \Downarrow
Not so good!


$\frac{I}{2}$ -Referenced Bias Clk.

Based on the Widlar current source:

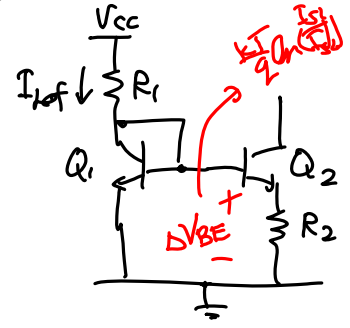

Here, $I_{ref} \neq I_0$.
 \downarrow
 so sensitive to V_{CC} variations
 \downarrow
 But can fix this by setting $I_{ref} = I_0$.

Use self-biasing:

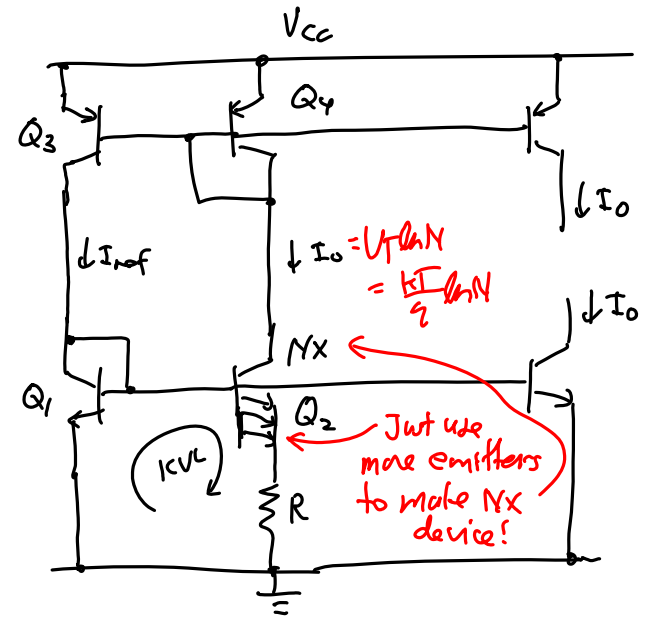

Assuming $I_{R2} = NI_{R1}$:

KVL: $I_0 R = V_{BE1} - V_{BE2} = V_T \ln N$
 ← at least wrt to V_{CC}

$I_0 = \frac{V_T}{R} \ln N = \frac{kT}{q} (\text{const.})$



Two possible operating ptr.
 ⇒ we startup ckt to guarantee this one
 (where we have very small $S_{I_0}^{V_{CC}}$)

$\frac{kT}{q}$ - Reference Temperature Dependence

$$TC_f = \frac{1}{I_0} \frac{\partial I_0}{\partial T} = \ln N \left(\frac{1}{R} \frac{\partial V_T}{\partial T} - \frac{V_T}{R^2} \frac{\partial R}{\partial T} \right) \frac{R}{V_T \ln N}$$


$$\therefore TC_f = \frac{1}{V_T} \frac{\partial V_T}{\partial T} - \frac{1}{R} \frac{\partial R}{\partial T}$$

$$= \underbrace{TC_f|_{V_T}}_{3300 \text{ ppm}/^\circ\text{C}} - \underbrace{TC_f|R}_{1800 \text{ ppm}/^\circ\text{C}} \sim 1500 \text{ ppm}/^\circ\text{C}$$


↪ Better than V_{BE} -Ref, but still not zero...
 How can get ↗?

Bandgap Reference

Basic Idea:

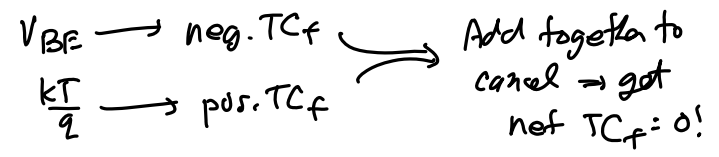


0th Order Picture:

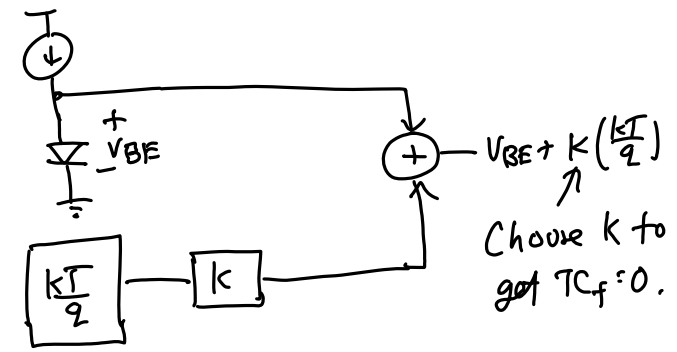

What should k be? (0th order Picture)

⇒ get ballpark estimate

↪ over

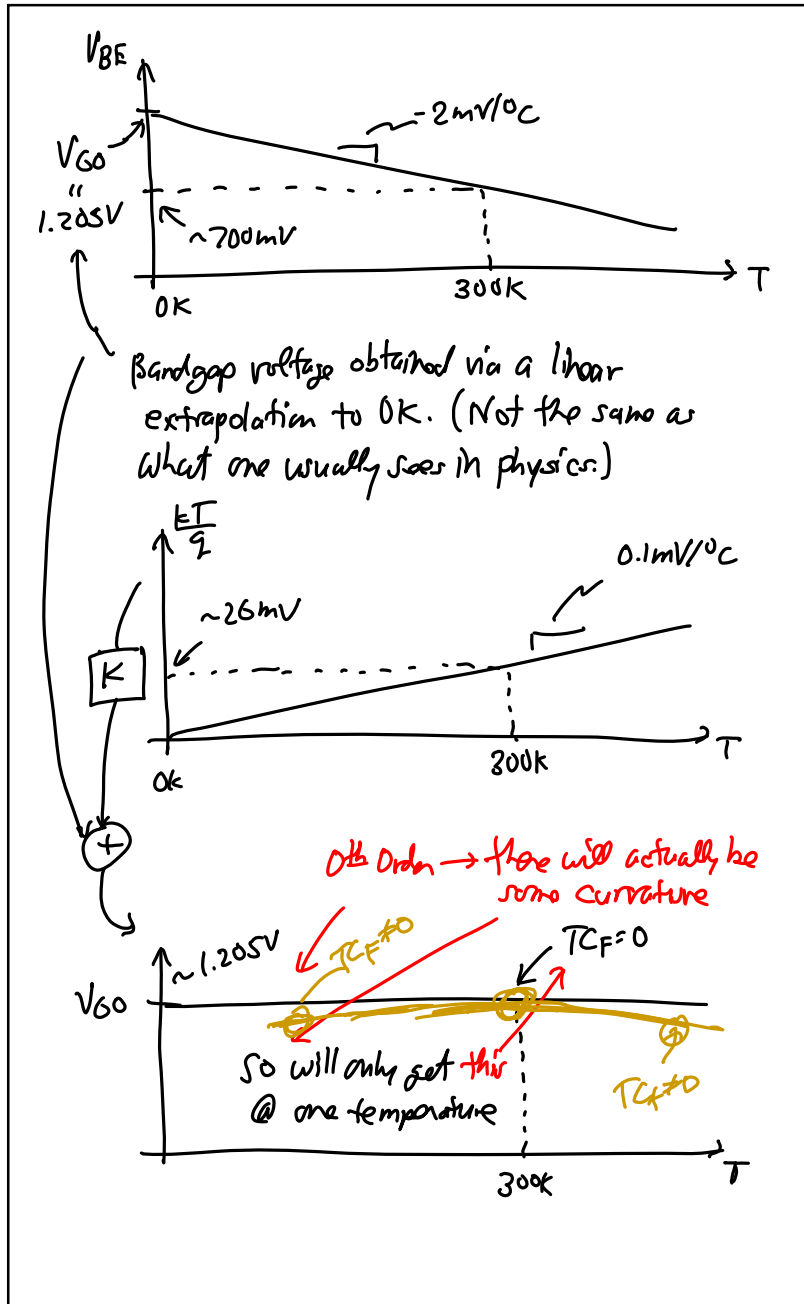

- 240A folks: read Gray & Meyer
 - ↪ Sections 4.4.2 through 4.4.3
 - ↪ These cover supply and temperature independent biasing, including bandgap references
 - ↪ Can also read Razavi, Chpt. 11, on bandgap references