

Lecture 12: Current Source Matching


Announcements:

- ↪ HW#5 due tomorrow
- ↪ HW#6 online soon
- ↪ 240A HW#1A online soon

Lecture Topics:

- ↪ High Swing Current Sources (cont.)
- ↪ Current Source Matching Considerations
- ↪ Op Amp Review

Last Time:

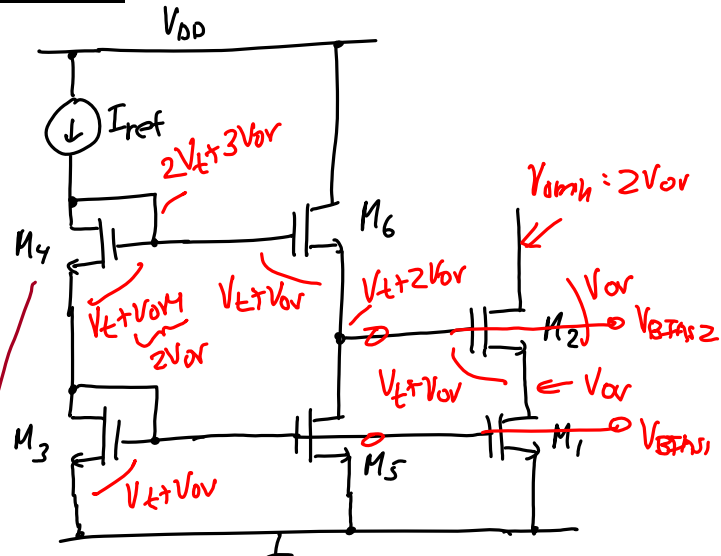

Need to design M_4 so that $V_{ov4} = 2V_{ov} = 2V_{ov3}$

$$I_{D3} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_3 (V_{ov3})^2$$


$$I_{D4} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_4 (V_{ov4})^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_4 (2V_{ov3})^2$$

↓
 $I_{D3} = I_{D4} = I_{ref}$
 $\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_3 (V_{ov3})^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_4 (2V_{ov3})^2$
 $\left(\frac{W}{L}\right)_4 = \frac{1}{4} \left(\frac{W}{L}\right)_3 \dots$ and $\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_5 = \left(\frac{W}{L}\right)_6$

Problem: Body effect in M_4, M_6, M_2 .

$$V_t = V_{t0} + \gamma (\sqrt{2|\phi_{f1}} + |V_{SB1}|} - \sqrt{2|\phi_{f1}})$$

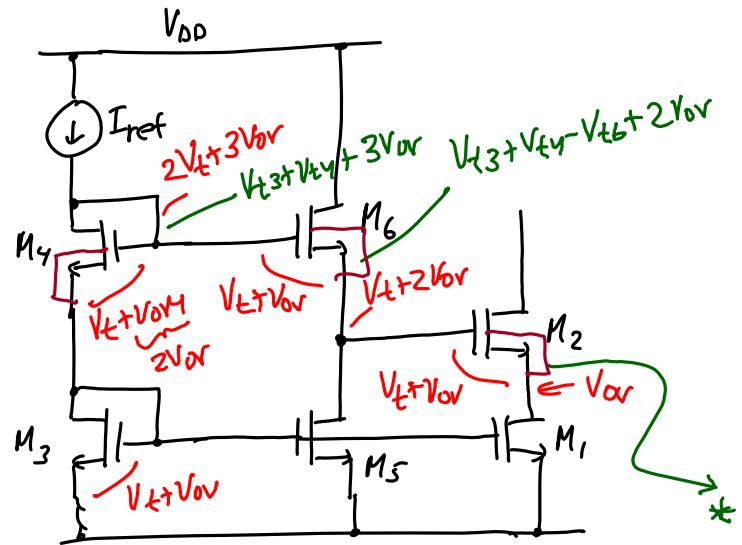if $V_{SB} \neq 0 \rightarrow V_t > V_{t0}$
 $\therefore V_t$'s of M_4, M_6, M_2 increase.



$V_{t4} = V_{t6} \rightarrow V_{S4} = V_t + V_{ov}$
 $V_{S6} = V_t + 2V_{ov}$ } $V_{S6} > V_{S4} + V_{t6} > V_{t4}$

→ Could make $V_{DS1} < V_{ov}$ (trick) ← problem!

* What exactly is this voltage?

$V_{D1} = V_{t3} + V_{t4} - V_{t6} - V_{t2} + V_{ov}$
 $= \underbrace{(V_{t4} - V_{t6})}_{(-)} + \underbrace{(V_{t3} - V_{t2})}_{(-)} + V_{ov} \rightarrow V_{D1} < V_{ov}$
 ($M_1 \rightarrow$ triode)
 M_1 not saturated!
 Big Problem! → R_{oL}

Solutions:

① Tie the wells of $M_4, M_6,$ & M_2 to their sources.
 $V_t = V_{to} \rightarrow \delta(\sqrt{2I_{ref}} \rightarrow V_{DS} - \sqrt{2I_{ref}}) \rightarrow V_{t6}$
 ↓
 Problem: too much die area consumed when giving these devices their own wells
 → cost ↑

Aside:

$I_0 = I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_t)^2 (1 + \lambda V_{DS1})$
 high $R_o \rightarrow$ because M_2 shields M_1 from ΔV_x

② Bias M_4 so that $V_{GS4} \geq V_t + 2V_{ov}$
 e.g., $V_{GS4} = V_t + 3V_{ov}$

$\left(\frac{W}{L}\right)_4 = \frac{1}{9} \left(\frac{W}{L}\right)_3$ ← safety margin!



← $V_{omh} = 3V_{ov}$ if all V_t 's = V_{to}
 ↓
 w V_t 's $\neq V_{to}$:
 $2V_{ov} < V_{omh} < 3V_{ov}$
 \Rightarrow keeps M_1 saturated ✓

Issue: $I_0 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{DS} - V_t)^2 (1 + \lambda V_{DS})$
 ↗ channel length $\rightarrow \lambda \uparrow$

If $V_{DS1} \neq V_{DS3}$

$I_0 = \frac{(1 + \lambda V_{DS1})}{(1 + \lambda V_{DS3})} I_{ref} \rightarrow I_0 \neq I_{ref}$

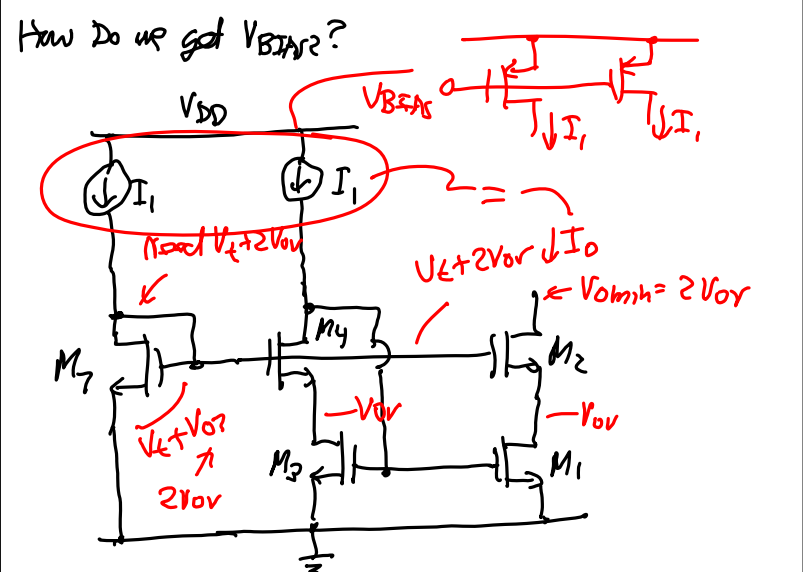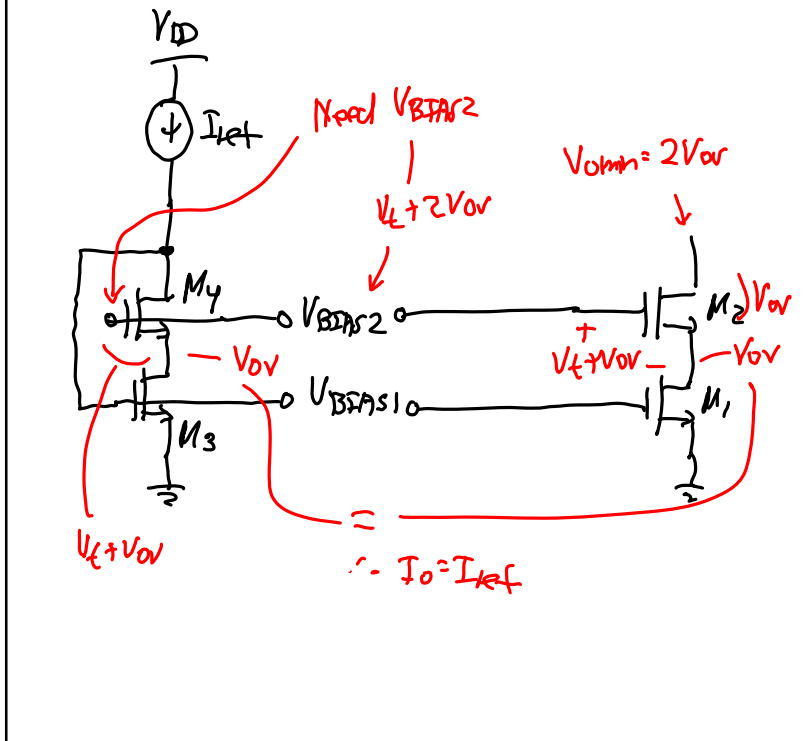Solution: Alternate Biasing Scheme for Cascode



$I_{D1} = I_{D3}$

$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (2V_{ov})^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_3 (V_{ov})^2$

$\left(\frac{W}{L}\right)_2 = \frac{1}{4} \left(\frac{W}{L}\right)_3, \left(\frac{W}{L}\right)_{rest} = \left(\frac{W}{L}\right)_3$


Note: Still murr worry about Body effect!

↳ design defensively

↳ make $V_{DS1} = V_t + 2V_{ov}$


↳ $3V_{ov}$?

Current Source Matching Considerations

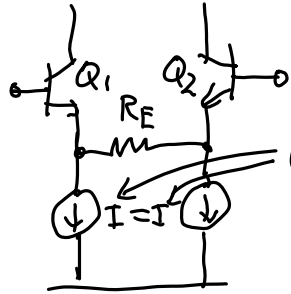

Need equal currents in this differential amplifier stage.
 won't ~~be~~ perfectly matched current sources!

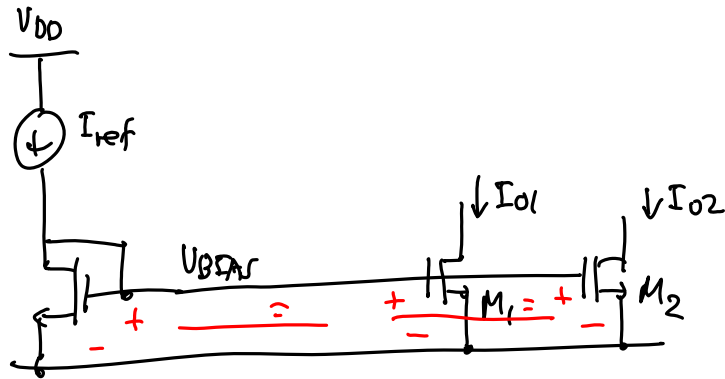Consider matching of Simple Current Source:



In MOS

$$I_{01} = I_{02} \rightarrow I_{D1} = I_{D2}$$

$$I_{01} = I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{t1})^2$$

$$I_{02} = I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{GS2} - V_{t2})^2$$

Same

I_{01} & I_{02} will ~~not~~ be perfectly matched if

$$\left\{ \left(\frac{W}{L}\right)_1 \neq \left(\frac{W}{L}\right)_2 \quad \& \quad V_{t1} \neq V_{t2} \right\}$$

will always have this due to finite fabrication tolerances!

Need to quantify their impact \rightarrow How much mismatch caused by

Define average & mismatch quantities:

Average:

Mismatch:

$$I_D = \frac{1}{2} [I_{D1} + I_{D2}]$$

$$\Delta I_D = I_{D1} - I_{D2}$$

$$\left(\frac{W}{L} = \frac{1}{2} \left[\left(\frac{W}{L}\right)_1 + \left(\frac{W}{L}\right)_2 \right] \right.$$

$$\Delta \left(\frac{W}{L}\right) = \left(\frac{W}{L}\right)_1 - \left(\frac{W}{L}\right)_2$$

$$V_t = \frac{1}{2} [V_{t1} + V_{t2}]$$

$$\Delta V_t = V_{t1} - V_{t2}$$

$$\frac{\Delta I_D}{I_D} \triangleq \text{fractional current mismatch}$$

$$\frac{\Delta(W/L)}{(W/L)} \triangleq \text{''} \quad \left(\frac{W}{L}\right) \text{ ''}$$

$$\frac{\Delta V_t}{V_t} \triangleq \text{''} \quad V_t \text{ ''}$$

$$\Rightarrow \text{want } \frac{\Delta I_D}{I_D} = f\left(\frac{\Delta(W/L)}{(W/L)}, \frac{\Delta V_t}{V_t}\right)$$

Reorganizing:

$$I_{D1} = I_D + \frac{\Delta I_D}{2}$$

$$I_{D2} = I_D - \frac{\Delta I_D}{2}$$

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right) + \frac{\Delta(W/L)}{2}$$

$$\left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right) - \frac{\Delta(W/L)}{2}$$

$$V_{t1} = V_t + \frac{\Delta V_t}{2}$$

$$V_{t2} = V_t - \frac{\Delta V_t}{2}$$

Plug these into the current equation:

$$I_{D1} = I_D + \frac{\Delta I_D}{2}$$

$$= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{t1})^2$$

$$= \frac{1}{2} \mu_n C_{ox} \left[\left(\frac{W}{L}\right) + \frac{\Delta(W/L)}{2}\right] (V_{GS} - V_t - \frac{\Delta V_t}{2})^2$$

$$= \frac{1}{2} \mu_n C_{ox} \left[\left(\frac{W}{L}\right) + \frac{\Delta(W/L)}{2}\right] (V_{OV} - 2V_{OV} \frac{\Delta V_t}{2} + \frac{(\Delta V_t)^2}{4})$$

$$= \frac{1}{2} \mu_n C_{ox} \left[\left(\frac{W}{L}\right) V_{OV}^2 + \frac{\Delta(W/L)}{2} V_{OV}^2 - \left(\frac{W}{L}\right) V_{OV} \Delta V_t - \frac{\Delta(W/L)}{2} V_{OV} \Delta V_t \right]$$

neg!

$$= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) V_{OV}^2 + \frac{1}{2} \mu_n C_{ox} V_{OV}^2 \left[\frac{\Delta(W/L)}{2} - \frac{(W/L)}{V_{OV}} \Delta V_t \right]$$

$$\frac{\Delta I_D}{2} = \frac{I_D}{2} \left[\frac{\Delta(W/L)}{2} - \frac{\Delta V_t}{V_{OV}} \right]$$

$$\therefore \frac{\Delta I_D}{I_D} = \frac{\Delta(W/L)}{(W/L)} - \frac{\Delta V_t}{(V_{OV}/2)}$$

$$\frac{\Delta I_D}{I_D} = \frac{\Delta(W/L)}{(W/L)} + \frac{\Delta V_t}{(V_{OV}/2)}$$

(-) means nothing
always take worst case, so can replace (-) w (+)

Fractional Current Mismatch
Geometry Bias Component
Indep of Bias
V_{OV} → to minimize this component

Today Ckts: Driven by power saving for digital.
V_{DD} → V_{OV} → $\frac{\Delta I_D}{I_D} \uparrow$ X **Bad!**
To combat this: $\left(\frac{W}{L}\right) \uparrow \rightarrow \frac{\Delta(W/L)}{(W/L)} \downarrow \rightarrow \frac{\Delta I_D}{I_D} \downarrow$ ✓
@ the expense of die area = cost!

Chip Size With Time:

1990's Digital → 2015 Digital Ckt.
chip area shrinks

1990's Analog → 2015 Analog Ckt.
L smaller, but must ramp (w/L) to reduce mismatch to allow small V_{OV}