

EE 140

Ideal Op Amps

$$\text{Gain} = \frac{V_o}{V_s} = \frac{R_i}{R_i + R_s} A_v \frac{R_L}{R_L + R_o}$$

CTN

1

Ideal Voltage Amplifier

→ ideal when  $\frac{V_o}{V_s} = A_v$ ; i.e., when source and load  $R$ 's do not influence the gain of the amplifier.

For this to occur, the voltage division at the input & output must be eliminated. This happens when:

$$\left. \begin{matrix} R_i = \infty \\ R_o = 0 \end{matrix} \right\} \text{These resistance values define an ideal voltage amplifier.}$$


We'll look at other amplifier types later.

→ This, then, actually leads us to:

Ideal Operational Amplifier (Op Amps)


The work horse of analog electronics → combination of op amps w/ feedback components allow the implementation of analog computers, sampled-data systems, analog filters, A/D converters, DAC's, instrumentation amplifiers

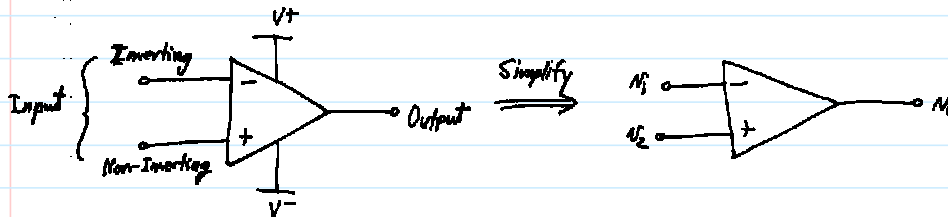In general, have a minimum of 5 terminals:



Perhaps the best way to define an op amp is thru its equivalent ckt.

Equivalent Ckt. of an Ideal Op Amp:

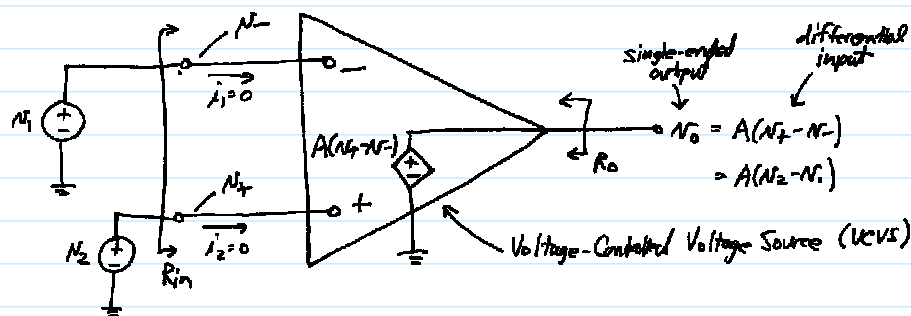


EE 140 Ideal Op Amps CTN 2

Properties of Ideal Op Amps:

- ①  $R_{in} = \infty$  leads to ④  $i_+ = i_- = 0$
- ②  $R_o = 0$
- ③  $A = \infty$  leads to ⑤  $V_+ = V_-$ , assuming  $A\beta = \text{finite}$   
 Why? Because for  $\infty (V_+ - V_-) = V_o = \text{finite}$   
 $\therefore V_+ - V_- = 0 \rightarrow V_+ = V_-$   
 $\frac{V_o}{V_o} \Rightarrow$  virtual short ckt. (virtual ground)

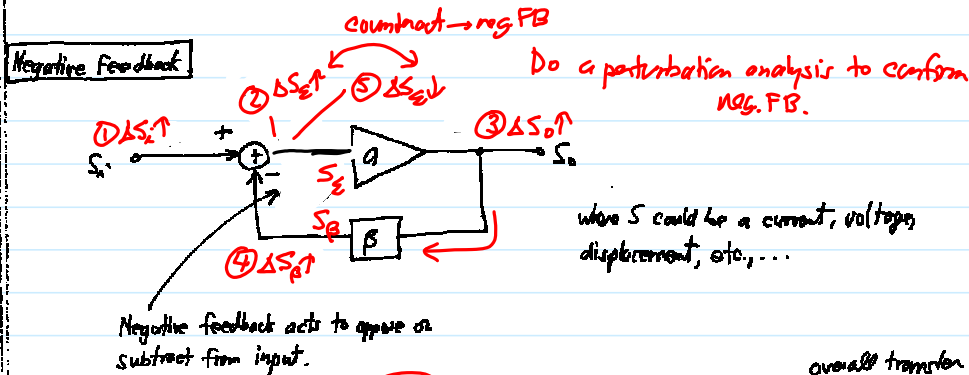Big assumption! ( $A\beta = \text{finite}$ )  
How can we assume this?  $\Rightarrow$  only when there is an appropriate negative feedback path!



Negative feedback acts to oppose or subtract from input.

$$\left. \begin{aligned} S_o &= a \Delta S_i \\ S_o &= S_i - \beta S_o \end{aligned} \right\} \Rightarrow S_o = a(S_i - \beta S_o)$$

$$S_o(1 + a\beta) = a S_i \rightarrow \frac{S_o}{S_i} = \frac{a}{1 + a\beta}$$

[ $a \rightarrow \infty$ ]  $\Rightarrow \frac{S_o}{S_i} \approx \frac{a}{a\beta} = \frac{1}{\beta} = \text{finite!}$

$\therefore S_o = \frac{1}{\beta} S_i = \text{finite}$  ✓  
(when there is neg. FB around the amplifier)

In Summary:

- ① Neg. FB can insure  $S_o = \text{finite}$  even with  $a = \infty$ .
- ② Gain dependent (or overall T.F.) dependent only on external components. (e.g.,  $\beta$ )
- ③ Overall (closed-loop) gain  $\frac{S_o}{S_i}$  is independent of amplifier gain  $a$ .

very important!  $\Rightarrow$  as you'll see, when designing amplifiers using transistors, it's easy to get large gain, but it's hard to get an exact gain.  
i.e., if you're shooting for  $a = 50,000$ , you might get 47,000 or 60,000 instead.


EE 140

Op Amp Circuits

CTN

3


Contrast with **Positive Feedback**

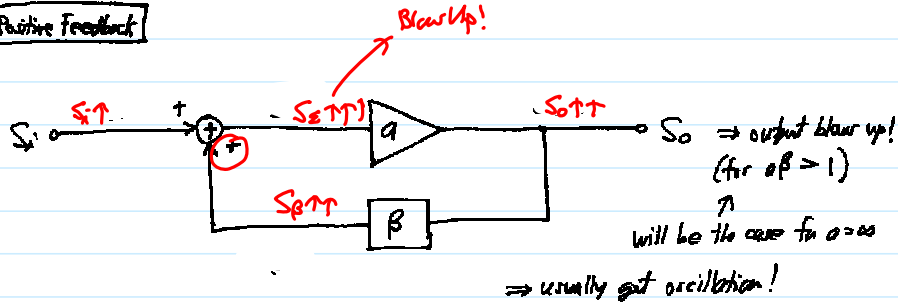

Thus, for a bounded, controllable function, need negative FB around an op amp.

**Op Amp Ckts.**

Example. Inverting Amplifier

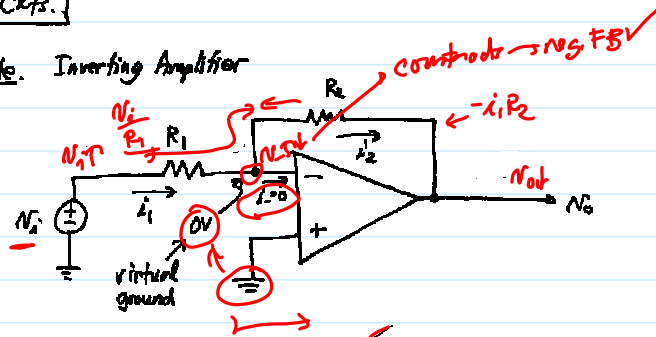


- ① Verify that there is negative FB. ✓
- ②  $\therefore N_o \neq \text{finite} \rightarrow N_o = N_- \rightarrow$  node attached to (-) terminal is virtual ground
- ③  $i_- = 0 \therefore i_1 = i_2$

$$\left. \begin{aligned} i_1 &= \frac{N_i - 0}{R_1} = \frac{N_i}{R_1} = i_2 \\ N_o &= 0 - i_2 R_2 = -i_2 R_2 \end{aligned} \right\} \Rightarrow N_o = -\left(\frac{R_2}{R_1}\right) N_i = -\frac{R_2}{R_1} N_i \therefore \frac{N_o}{N_i} = -\frac{R_2}{R_1}$$

Note: Gain dependent only on  $R_1$  &  $R_2$  (external components), not on the op amp gain.

Example.

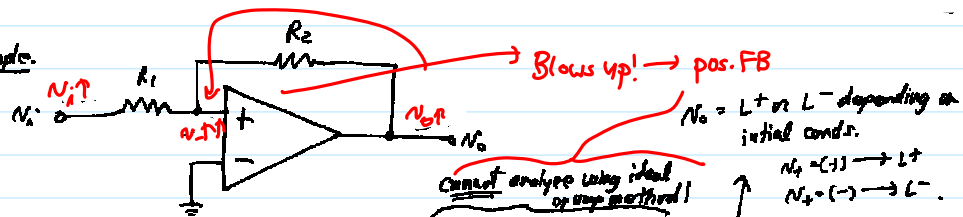

- ① Verify that there is neg. FB X

$\therefore N_o \neq \text{finite}, N_i \neq N_- \Rightarrow$  this ckt. will "rail out"

EE 140

Basic Op Amp Design


CTN

4

How does one make an op amp? (It turns out, you already know!)


⇒ Basic Needed Attributes:

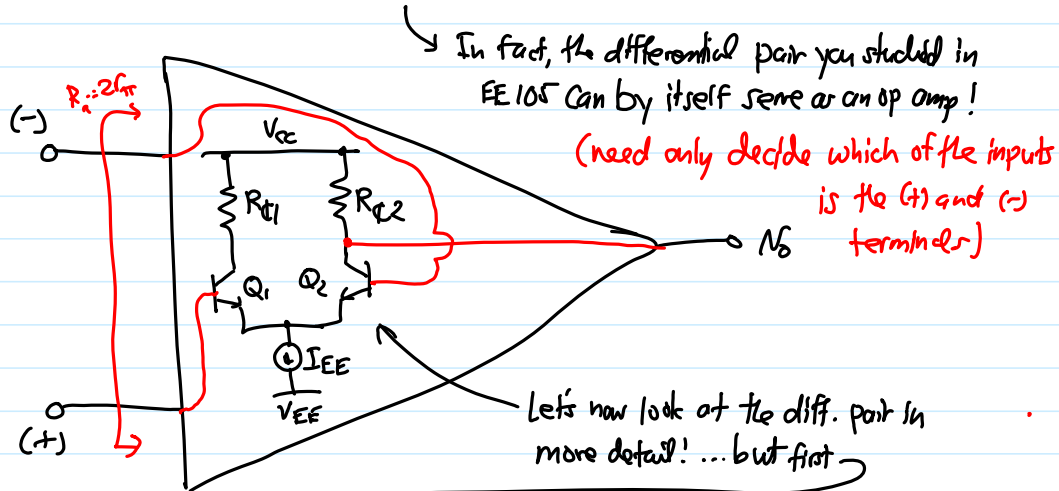- ① Gain (voltage gain).
- ② Two inputs, (+) and (-).
- ③ One output equal to the difference of the inputs multiplied by some gain.




Why have 2 inputs?

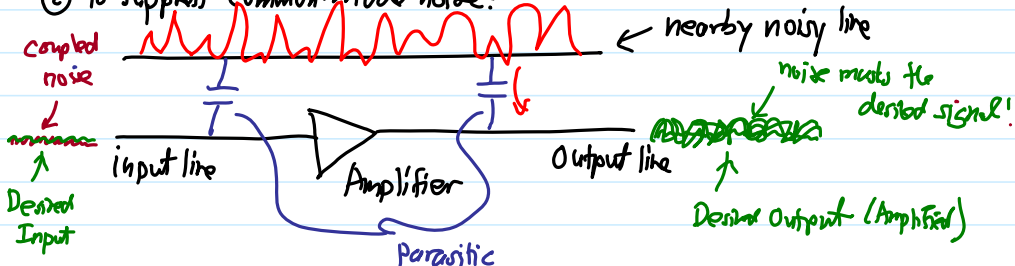- ① To get a virtual short for op amp dets.
- ② To suppress common-mode noise:



Can avoid this w/ a differential input:

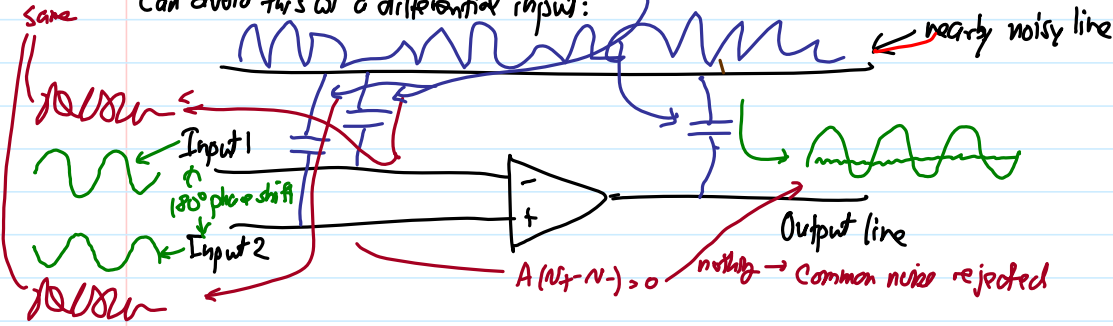


EE 140

Differential Pair (Bipolar)

CTN

5

Differential Pair (Emitter-Coupled Pair)

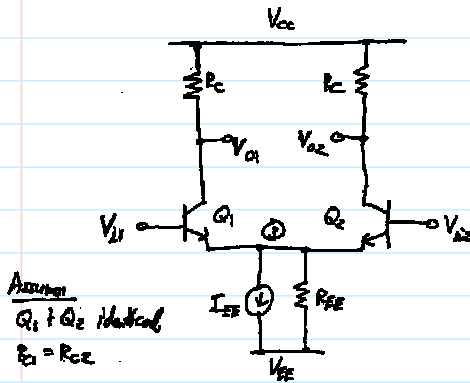


Requires: Amplify the difference between two signals regardless of their common-mode DC values (or their common-mode values in general)

Definition:

$$V_{id} = V_{i1} - V_{i2} \quad (\text{differential input})$$

$$V_{icm} = \frac{V_{i1} + V_{i2}}{2} \quad (\text{common-mode input})$$
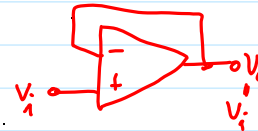
$$\Rightarrow \begin{cases} V_{i1} = V_{icm} + \frac{V_{id}}{2} \\ V_{i2} = V_{icm} - \frac{V_{id}}{2} \end{cases}$$



Differential Gain =  $A_d = \frac{V_{o1} - V_{o2}}{V_{id}} = \frac{V_{od}}{V_{id}}$  (Want this to be large for this differential amplifier)

Common-Mode Gain =  $A_{cm} = \frac{V_{o1}}{V_{icm}} \approx \frac{V_{o2}}{V_{icm}}$  (Want this to be small so that the amp rejects common-mode signals)

Common-Mode Rejection Ratio =  $CMRR = \frac{A_{dm}}{A_{cm}}$  (Should be very high to favor the differential mode and reject the common-mode)

⇒ we also want a high Common-Mode Input Range to reject DC input offsets

⇒ Note No need for bypass capacitors (large) to the inputs or outputs → can just use direct coupling!

Biases of Large Signal Common-Mode Behavior

Case:  $R_{EE} = \infty$  → ideal current source biasing →  $I_{E1} = I_{E2} = \frac{I_{EE}}{2} \rightarrow V_{o1} = V_{o2} \Rightarrow V_{od} = 0$


If  $V_{icm} \uparrow \rightarrow V_{cb} \uparrow$ , but current drawn from  $I_{EE}$  stays constant ∴  $I_{C1}$  &  $I_{C2}$  stay constant → bias pt. doesn't change

$g_m = \frac{1}{2} \frac{I_{EE}}{V_T}$

Case:  $R_{EE} = \text{finite}$  →  $V_{cb} = V_{i1} - V_{BE(on)}$


If  $V_{icm} \uparrow \rightarrow V_{cb} \uparrow \rightarrow I_{E1} = I_{E2} \uparrow$  (current draw =  $I_{EE} + \frac{V_{cb}}{R_{EE}}$ )

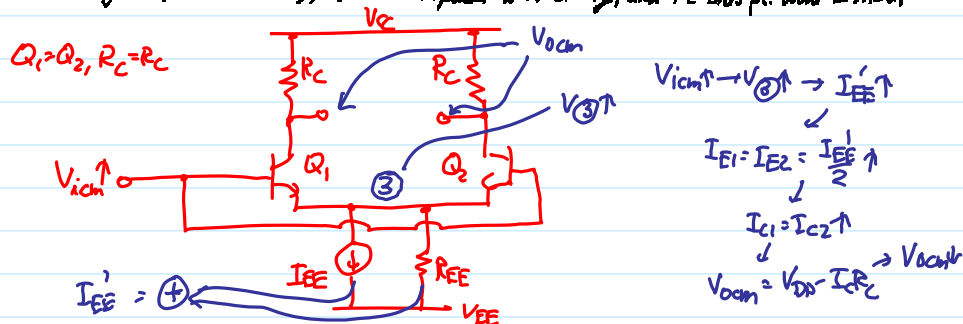⇒ In general,  $R_{EE}$  will be large, so this component won't be large, and the bias pt. won't Δ much




EE 140 Differential Mode Analysis CTN 6

Small-Signal Analysis of Diff. Pair

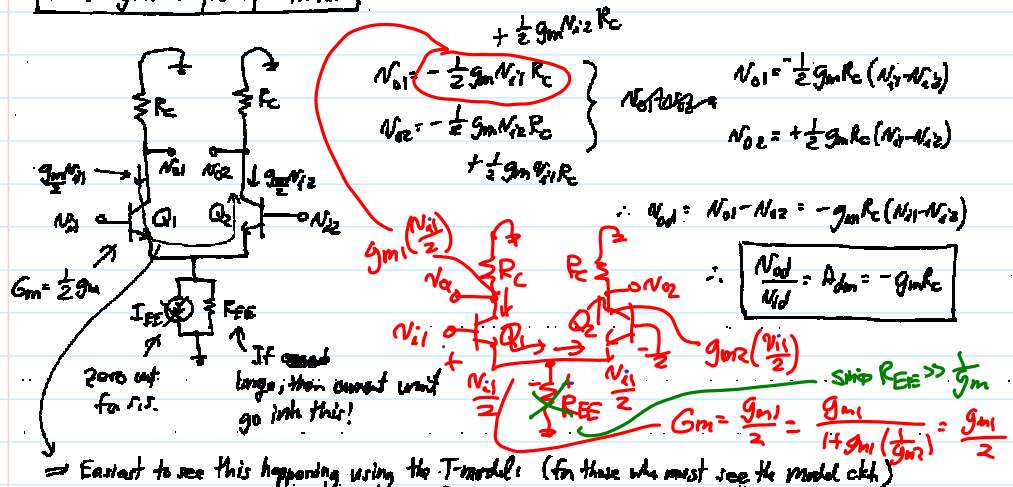

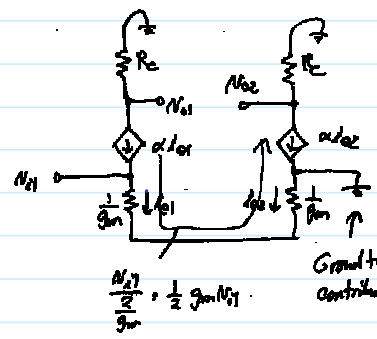Easiest to see this happening using the T-model: (for those who must see the model ckt)  
 Take time also get the  $\frac{v_{o1} - v_{o2}}{v_{i1}}$  gain!



$$v_{o1} = -\frac{1}{2} g_m R_C v_{i1}$$

$$v_{o2} = +\frac{1}{2} g_m R_C v_{i1}$$


$$v_{o1} - v_{o2} = -g_m R_C v_{i1}$$

$$\frac{v_{o1}}{v_{i1}} = -\frac{1}{2} g_m R_C$$

$$\frac{v_{o2}}{v_{i1}} = +\frac{1}{2} g_m R_C$$

Diff. Mode Analysis

Assume a ckt. w/ only diff. input:

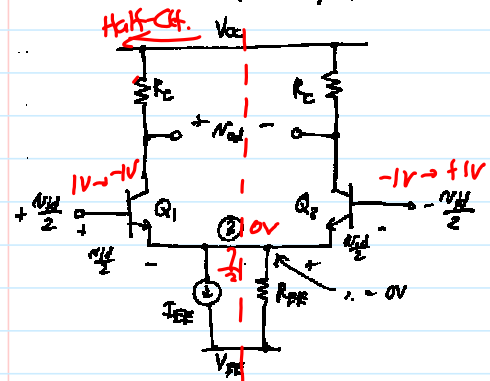


Total current thru  $I_{EE} = \text{const.}$   
 $\rightarrow V_E = \text{const. as input changes}$   
 $\rightarrow Q_2$  acts as an incremental ground!  $\rightarrow v_g = 0V$  (always!)  
 1. we can ground  $Q_2$ , and then have a **Differential Half Ckt.**

Note: Can really only make this for a purely symmetrical ckt!

EE 140 Common-Mode Analysis CTN 7

Differential Half Ckt.

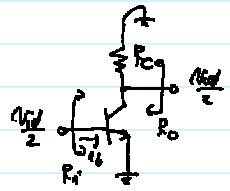

By inspection:  $\frac{v_{out}/2}{v_{in}/2} = \frac{v_{out}}{v_{in}} = A_{dm} = -g_m R_C$



$\frac{v_{out}/2}{i_b} = R_{id} \rightarrow R_{id} = \frac{v_{out}/2}{i_b} = 2r_{\pi} = R_{id}$

$\frac{v_{out}/2}{i_o} = r_o || R_C \rightarrow R_{od} = \frac{v_{out}}{i_o} = 2(r_o || R_C) = 2R_C = R_{od}$

S.S. params. determined w/  $I_C = \frac{I_{EE}}{2}$

Common-Mode Analysis

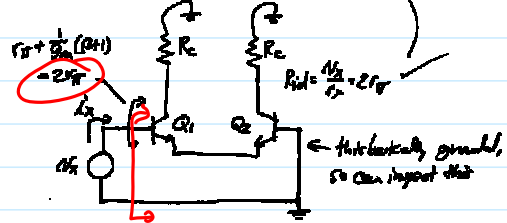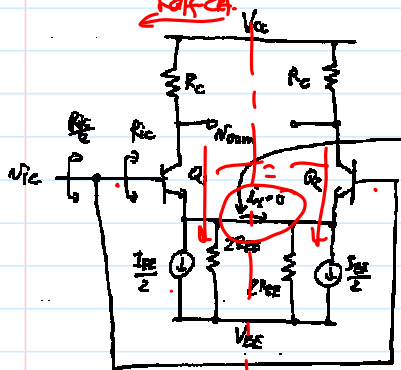
Assume a pure CM input  $\rightarrow$  tie inputs together



By symmetry,  $i_x = 0$ .  $\Rightarrow$  then, locally have the equivalent of an open ckt. here

$\therefore \Rightarrow$  can split the ckt. into CM half-ckt.!

S.S. CM Half-Ckt.

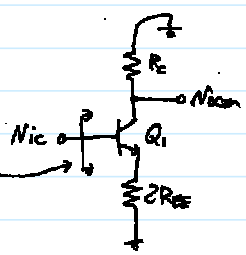

$R_{ic} = r_{\pi} + (\beta + 1)(2R_{EE})$  @ each input

$A_{cm} = \frac{v_{out,cm}}{v_{in,cm}} = -\frac{g_m R_C}{1 + g_m(2R_{EE})} \approx -\frac{R_C}{2R_{EE}}$

Want small  $\beta$  for large CMRR  $\therefore$  want  $\beta_{eff} = \log \beta!$

Common-Mode Rejection Ratio = CMRR =  $\frac{A_{dm}}{A_{cm}} = \frac{-g_m R_C}{-\frac{g_m R_C}{1 + g_m(2R_{EE})}} \Rightarrow \text{CMRR} = 1 + 2g_m R_{EE}$

Having looked at S.S. parameters, we now turn to large signal performance. Here, we'll be particularly interested in the linear range of the ECP.